

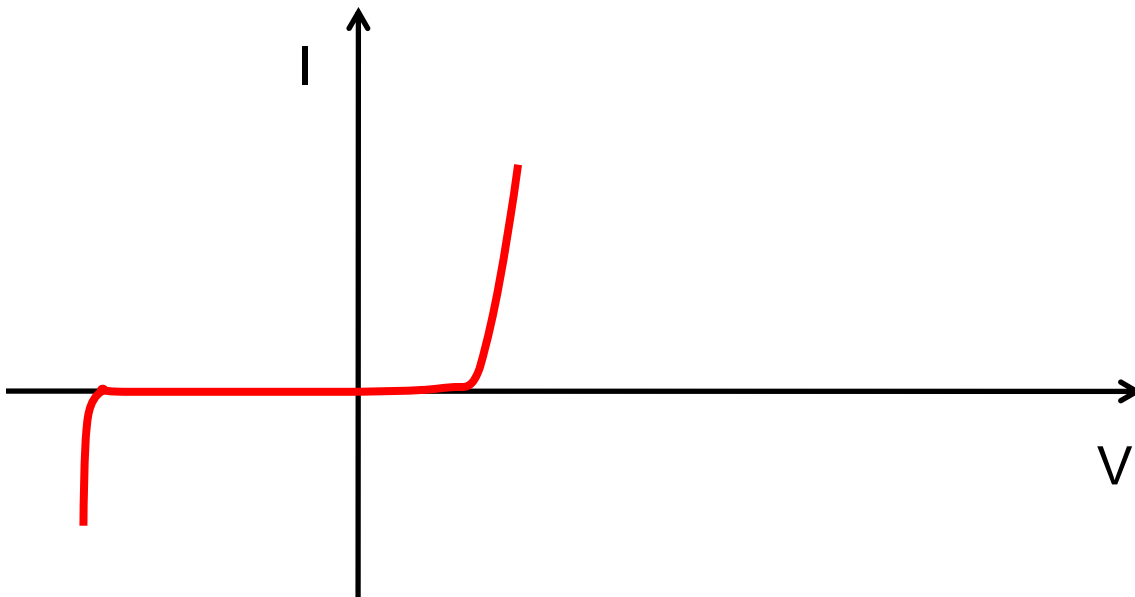


Peak Inverse Voltage

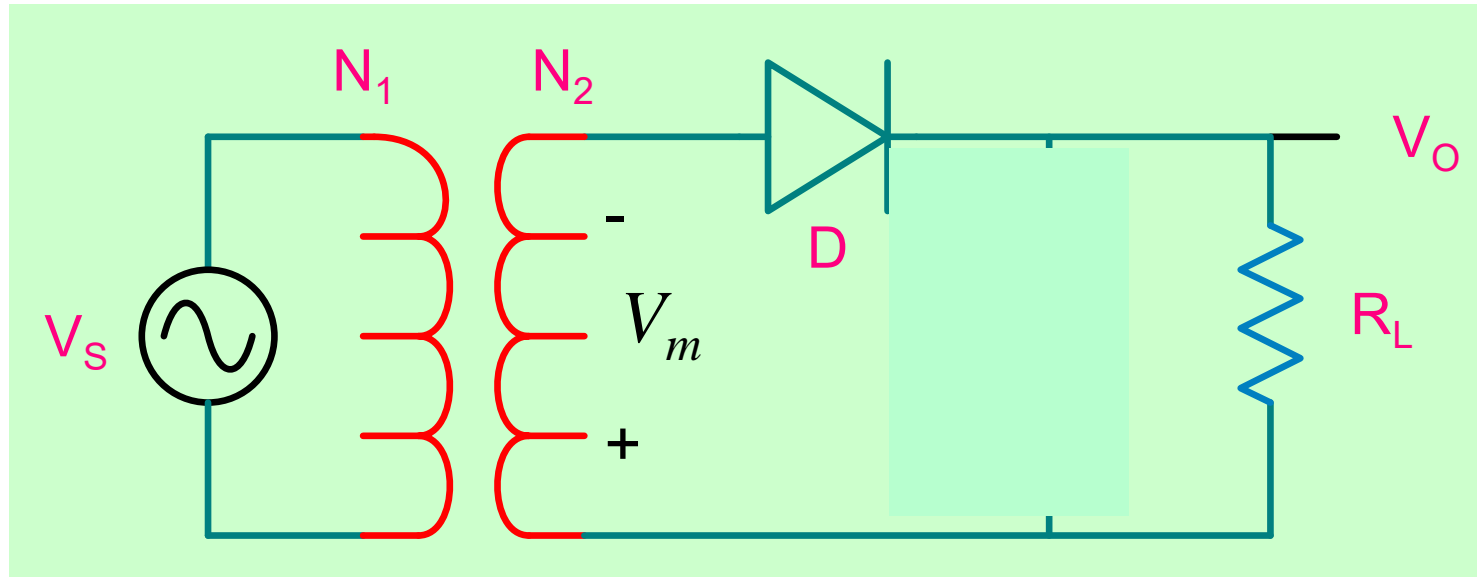

$$PIV = V_m$$

Peak Inverse Voltage

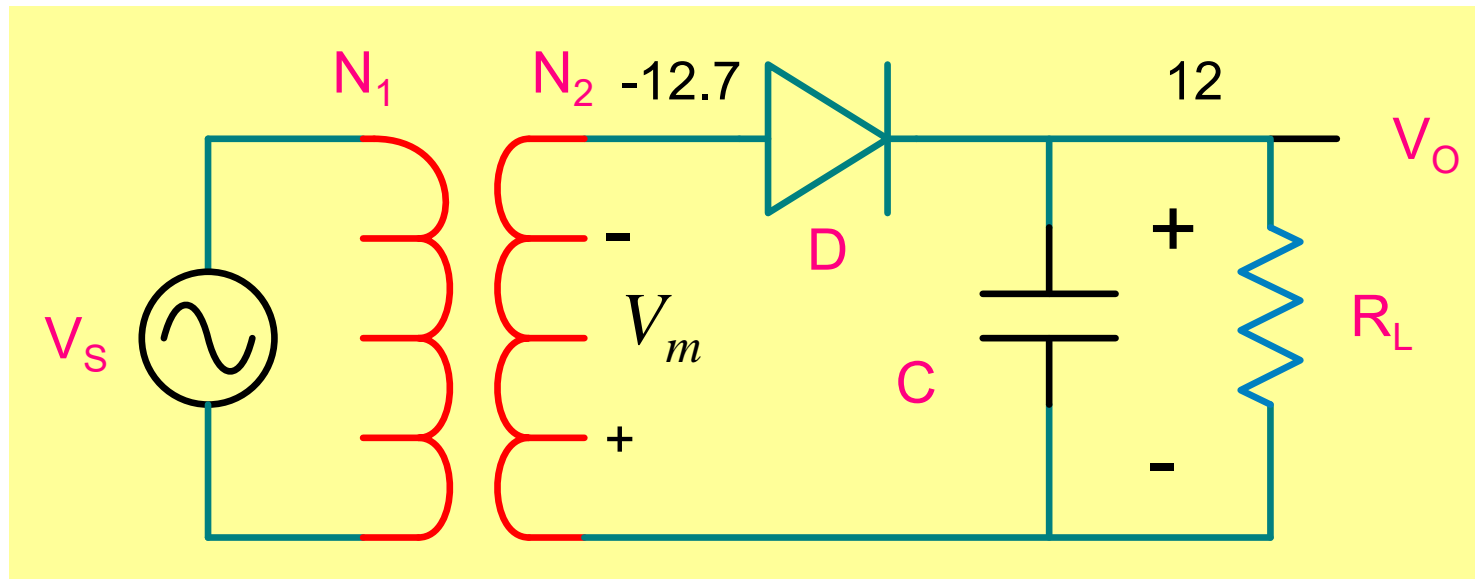


$$V_m = 12.7$$

$$12 + 12.7 = 24.7V$$



$$PIV \cong 2v_o + 0.7$$



$$PIV = 2V_M + V_\gamma$$

Full wave Rectifier

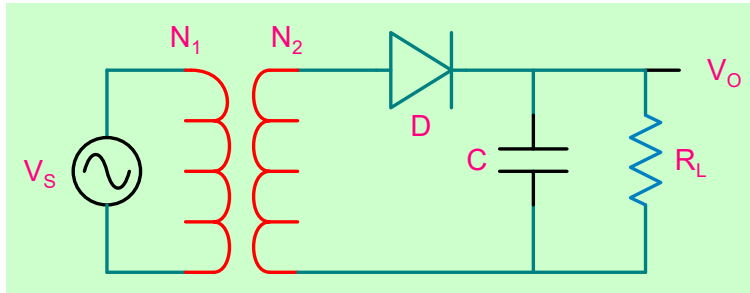

$$V_r \cong \frac{V_M}{fR_L C}$$

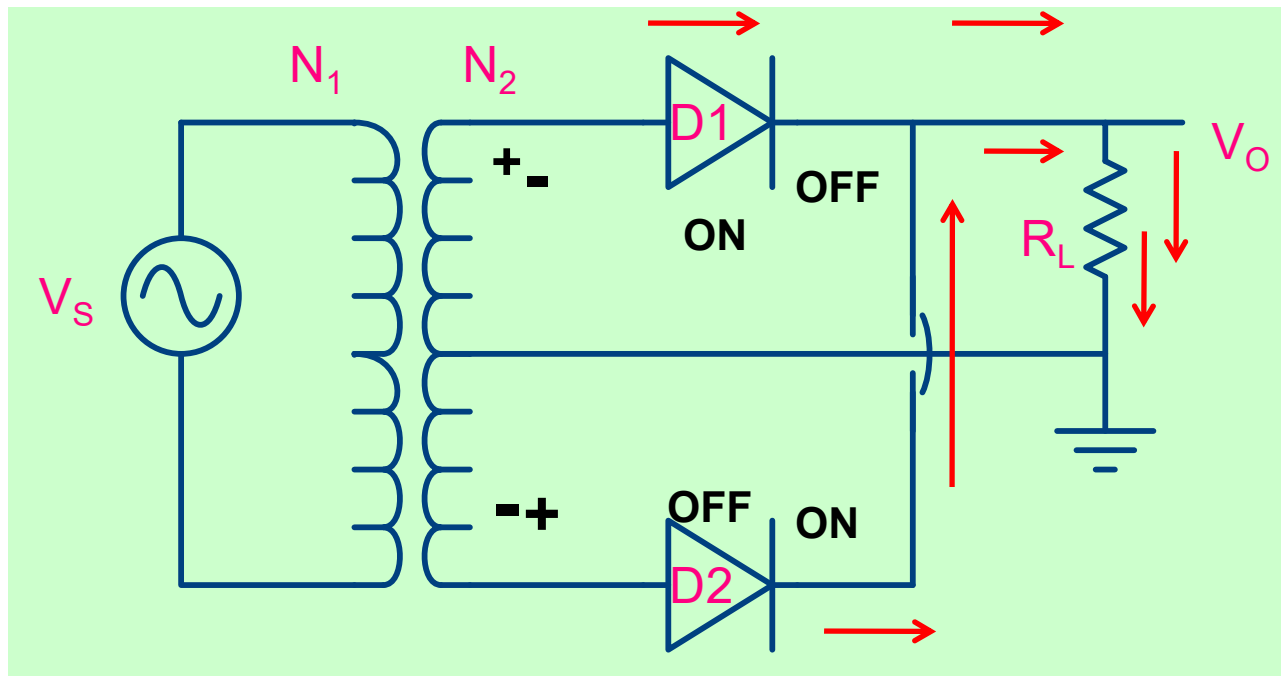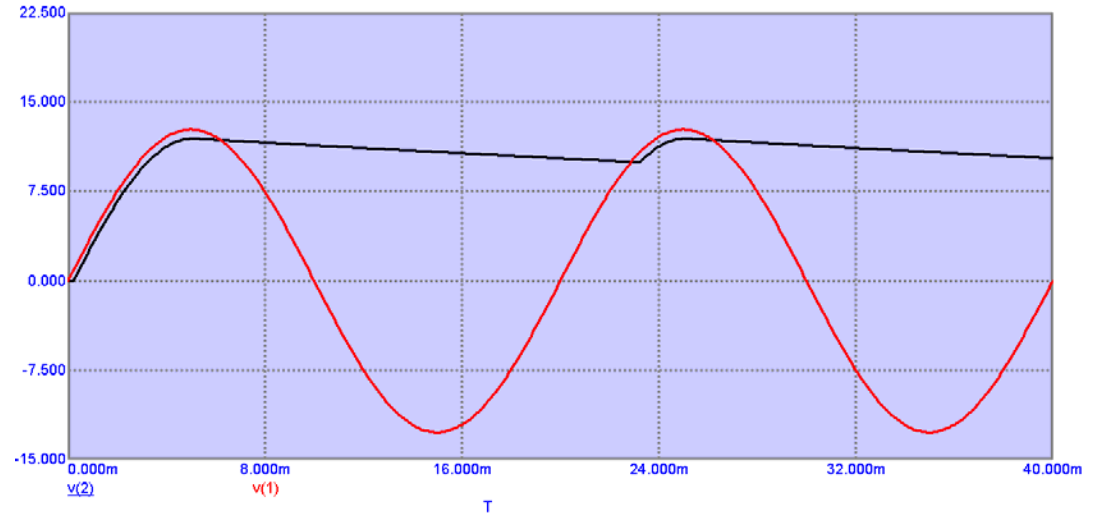


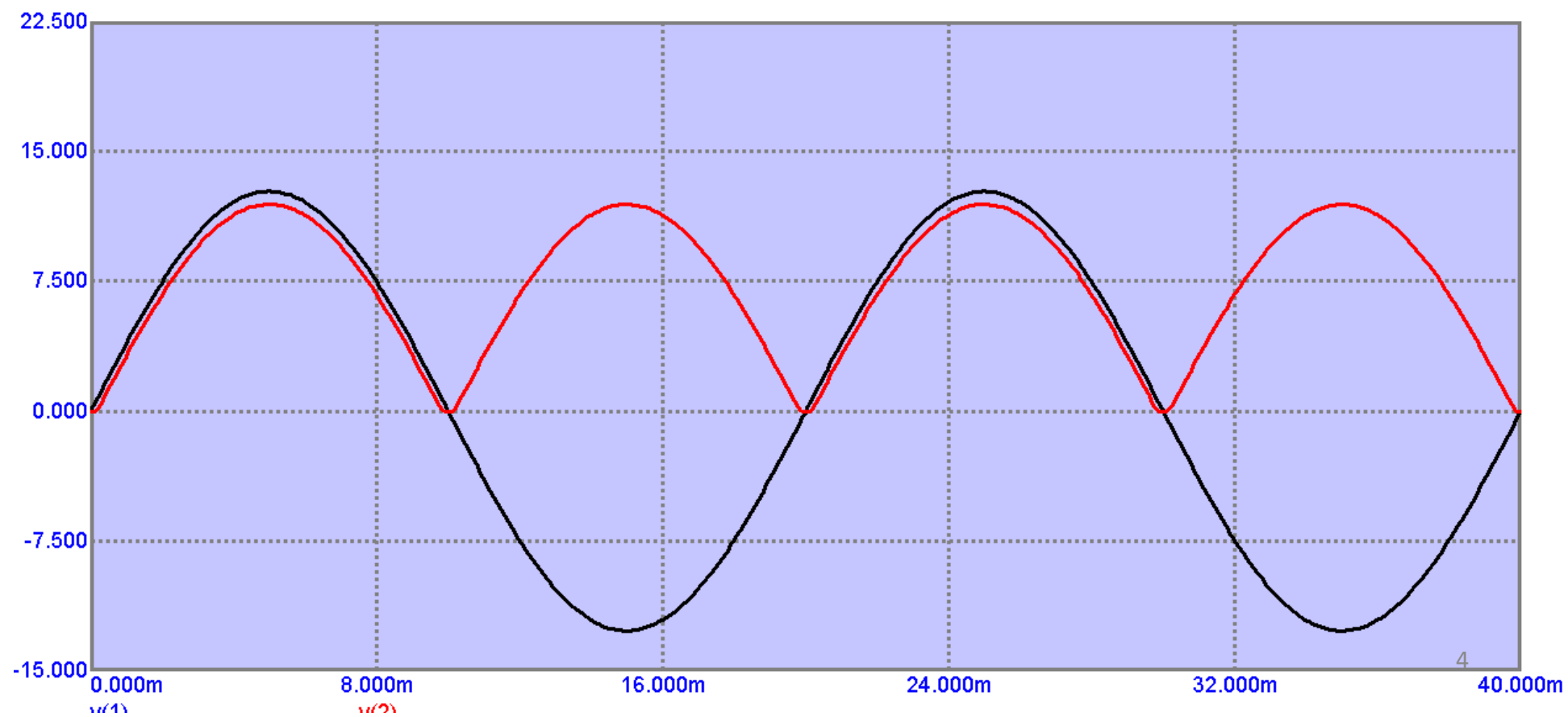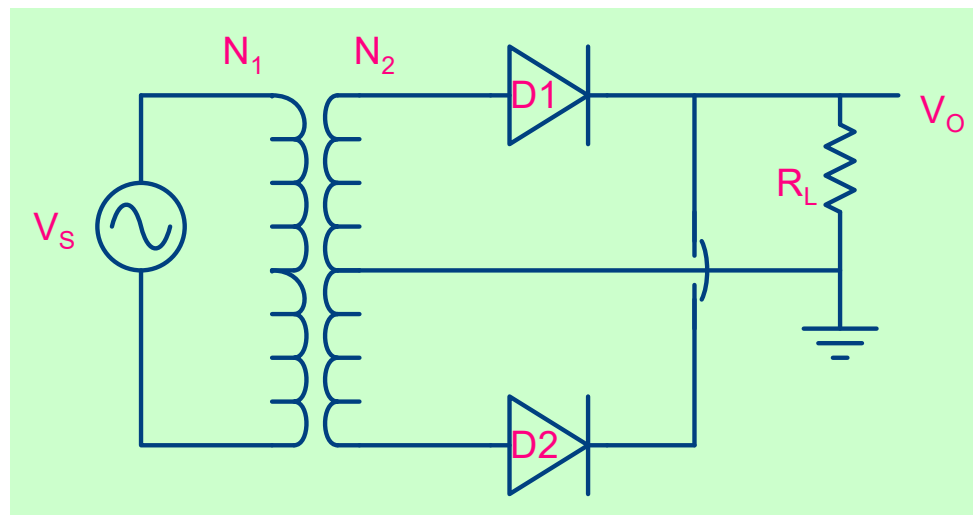




$$V_r = V_M - V_L = V_M \times (1 - e^{-\frac{t_1}{R_L C}})$$
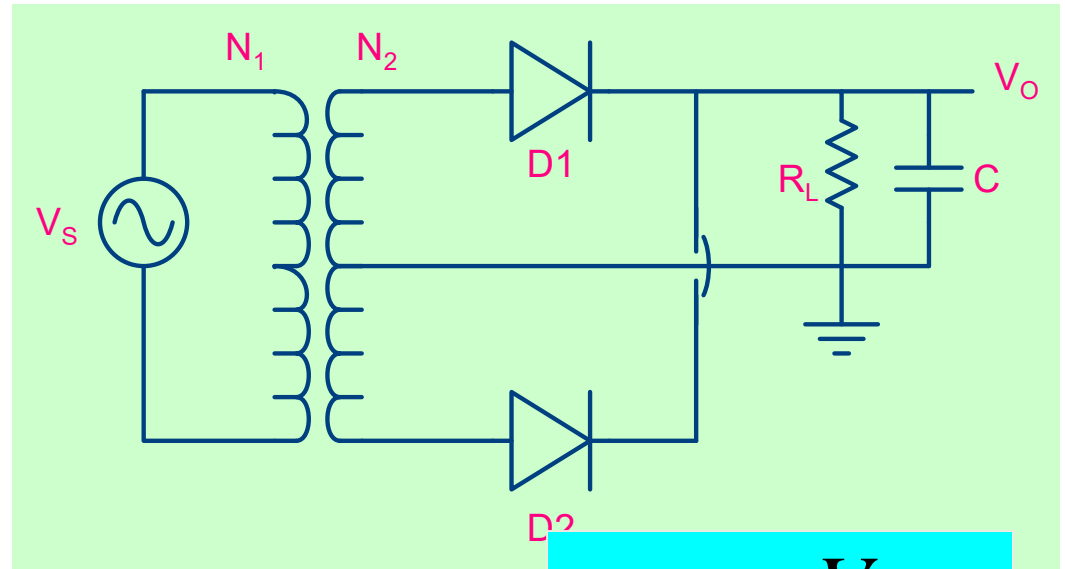
$$V_r \cong V_M \times \left\{ 1 - \left(1 - \frac{t_1}{R_L C} \right) \right\} = \frac{V_M t_1}{R_L C}$$





$$V_r = \frac{V_M t_1}{R_L C} \cong \frac{V_M T}{2 R_L C}$$

$$V_r \cong \frac{V_M}{2 f R_L C}$$

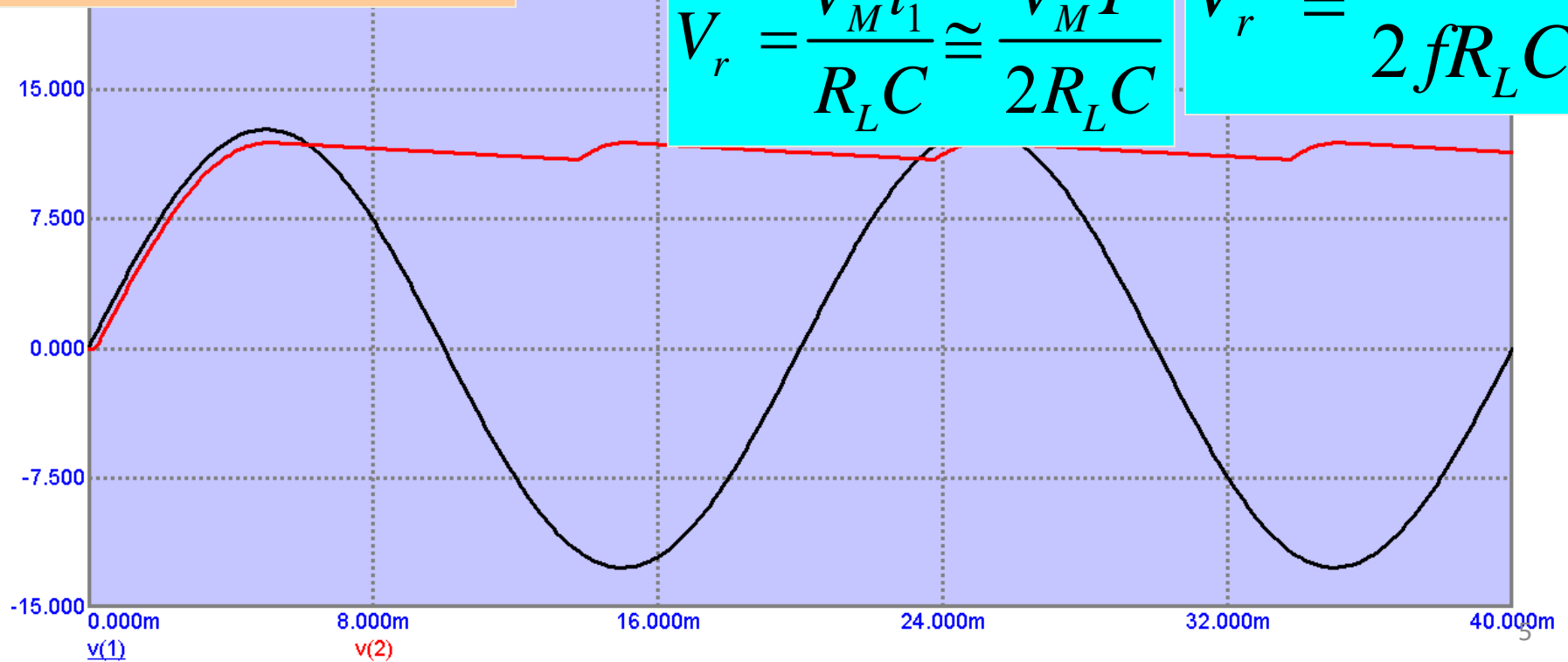


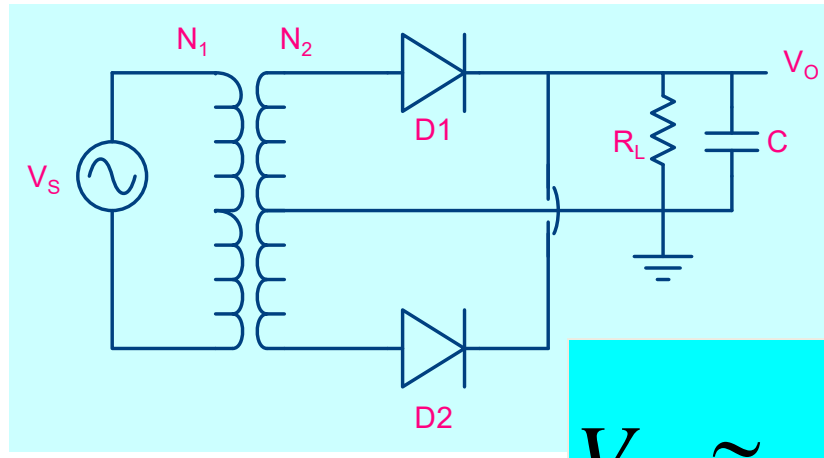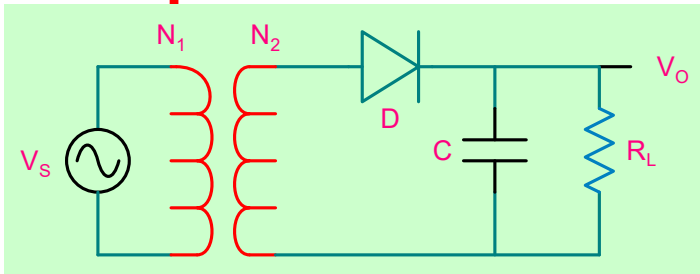Comparison of Full and Half Wave Rectifier




$$V_r \cong \frac{V_M}{fR_L C}$$

$$V_r \cong \frac{V_M}{2fR_L C}$$


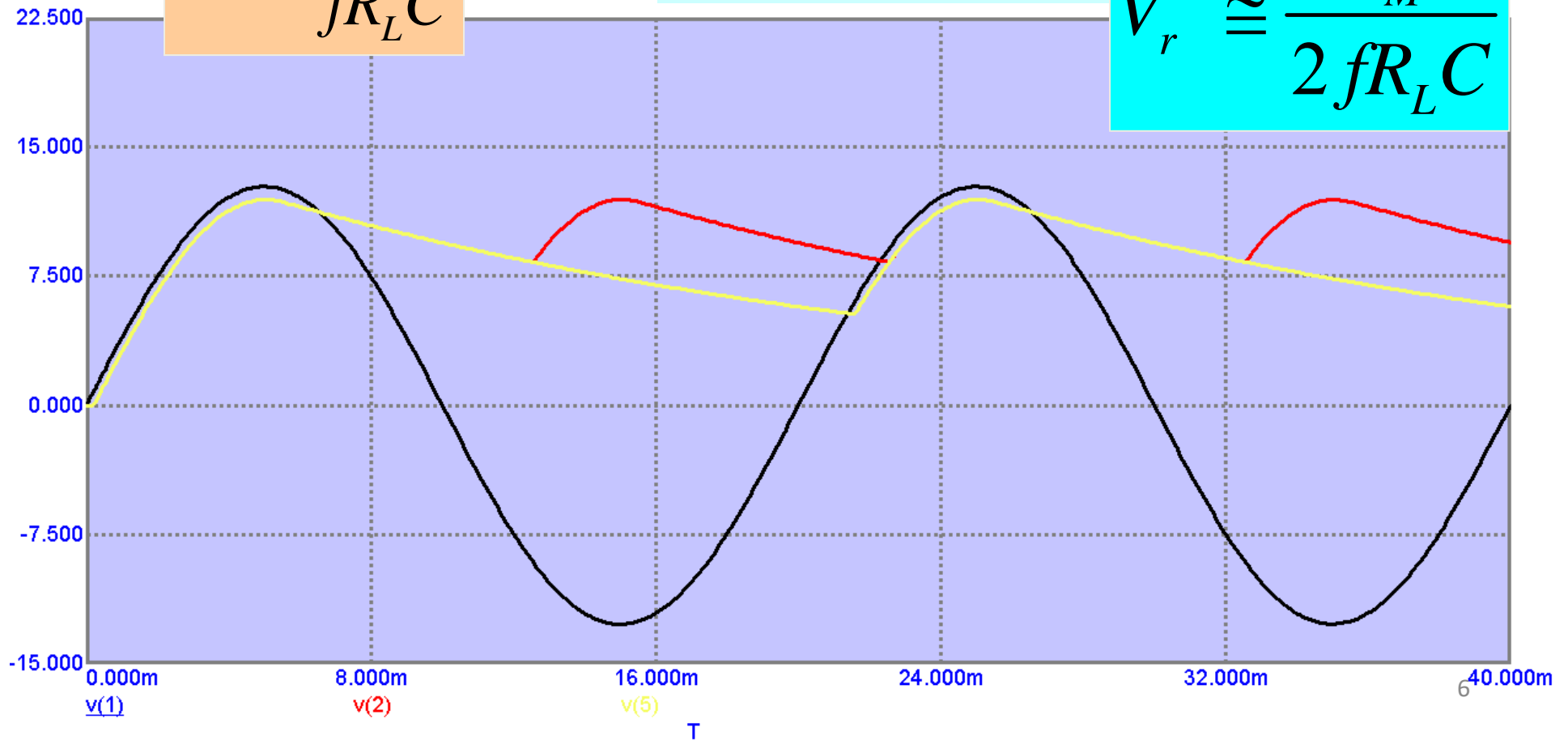


Diode Currents in Full wave Rectifier

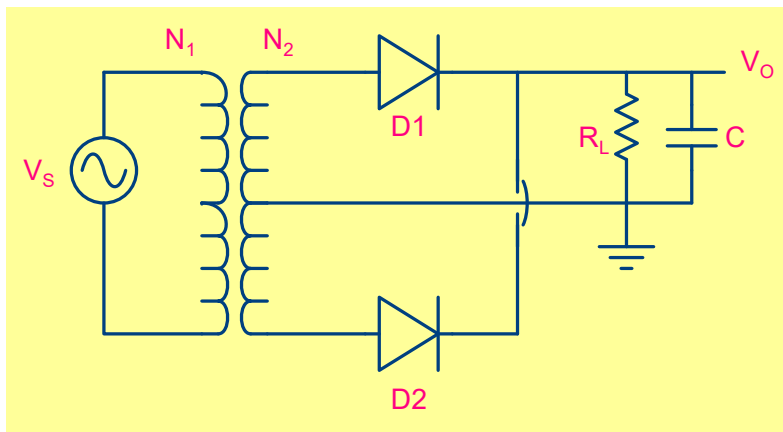



$$i_{D_{\max}} \cong \omega C \times \sqrt{2V_r V_M} + \frac{V_M}{R_L}$$
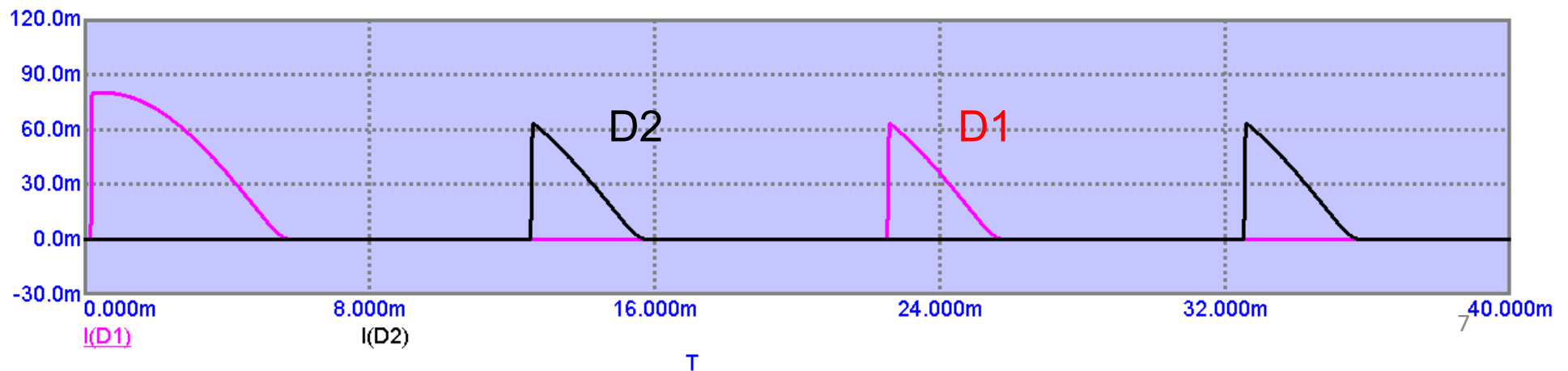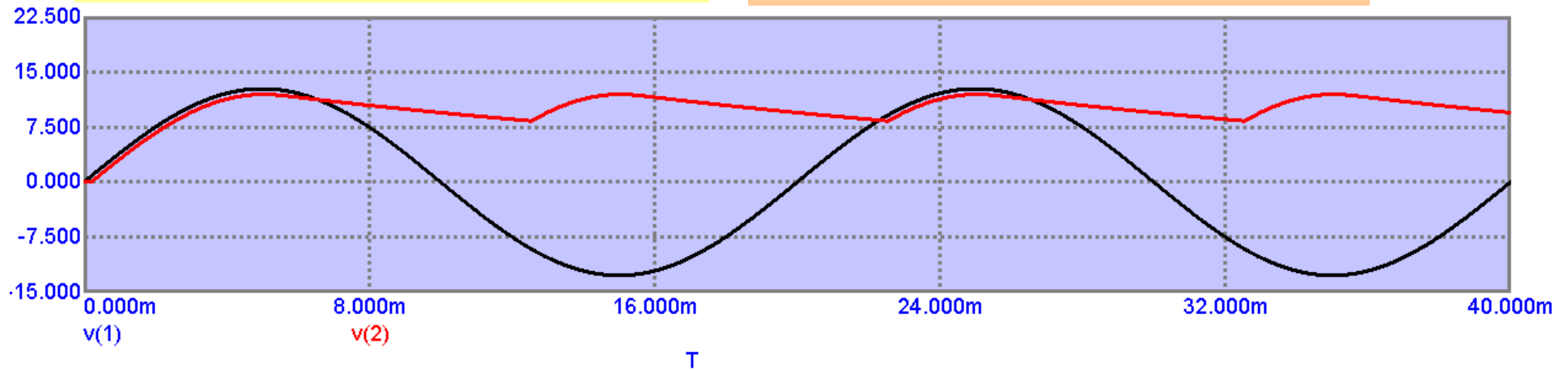
$$i_{D_{\max}} = \frac{V_M}{R_L} \left[1 + \pi \sqrt{\frac{2V_M}{V_r}} \right]$$







Bridge Rectifier

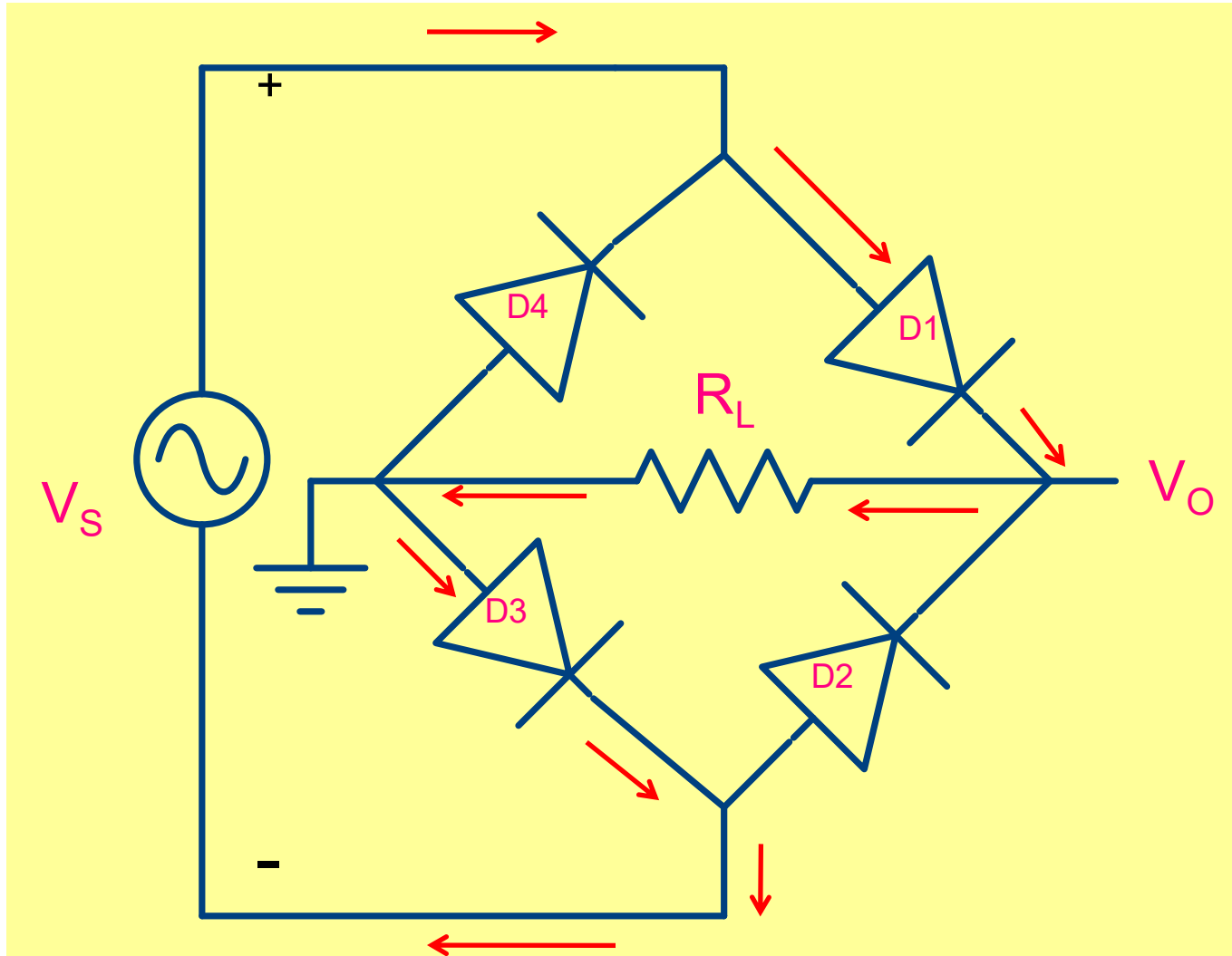

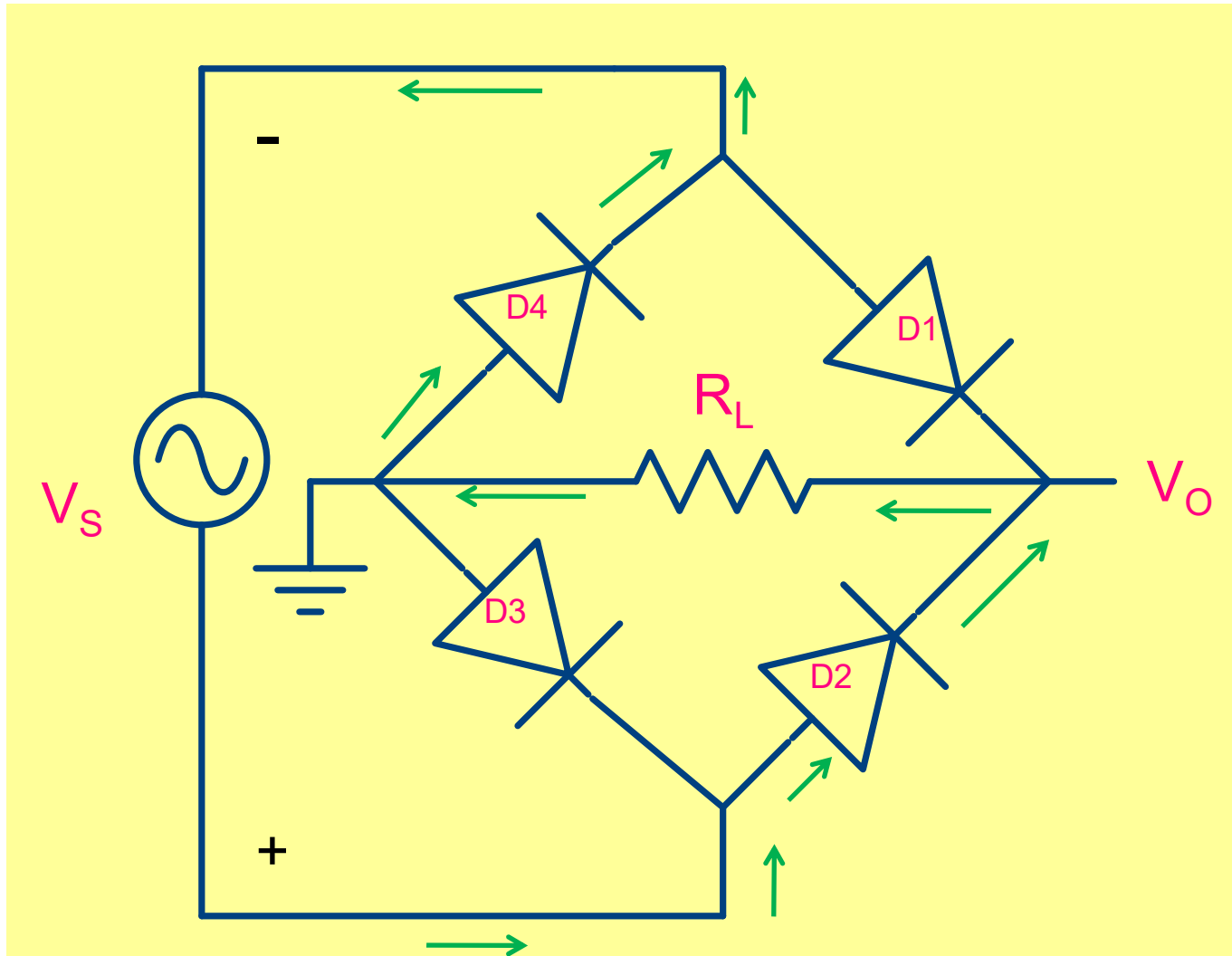

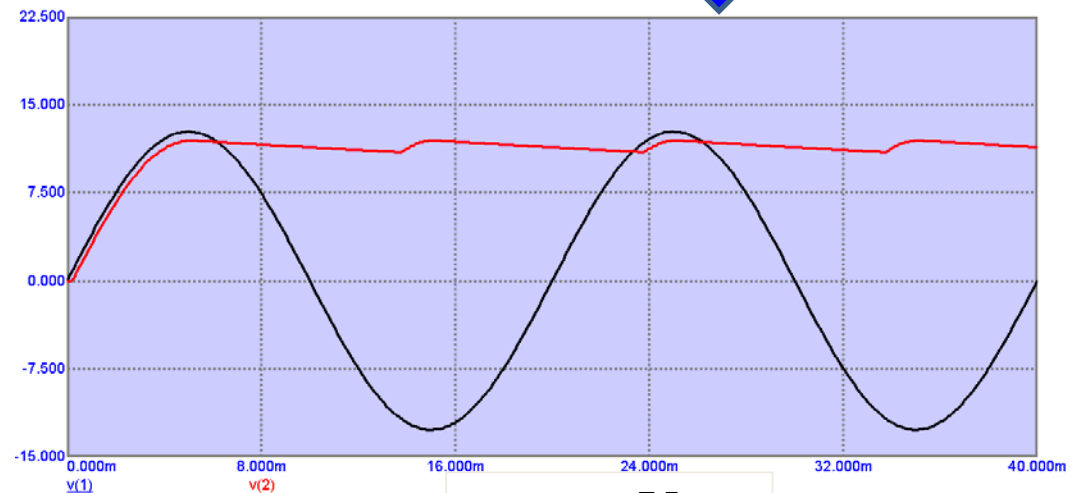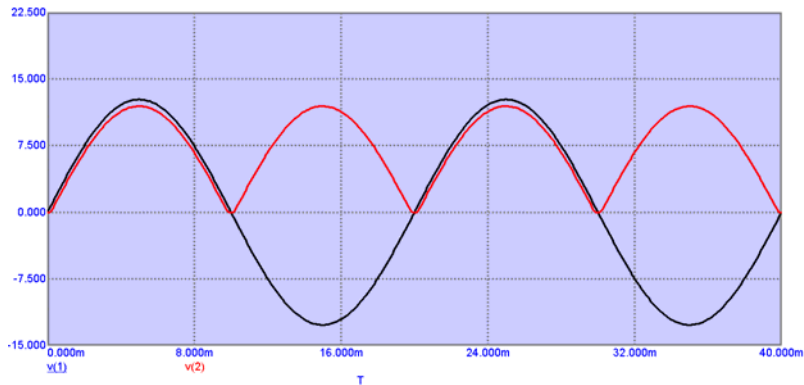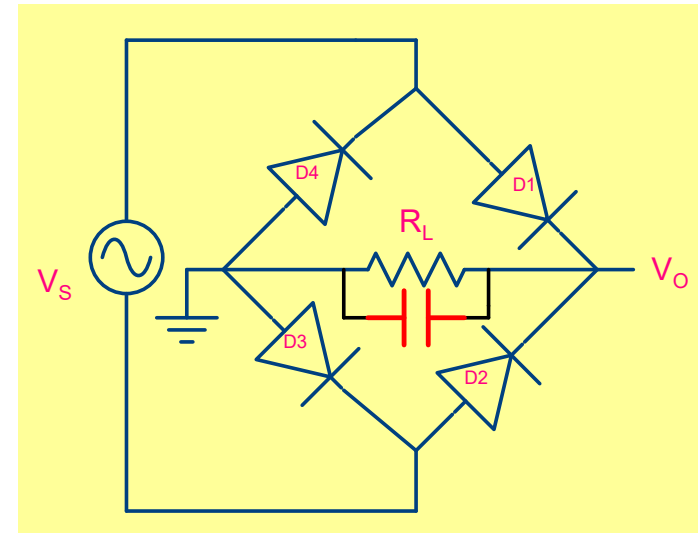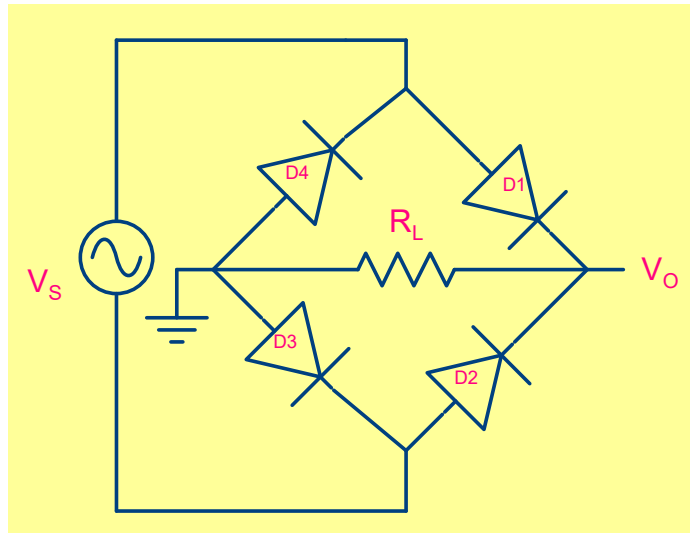
Power supply using full wave Bridge Rectifier



Ripple is smaller in full wave rectifier based power supply

$$V_r \cong \frac{V_M}{2fR_L C}$$

Peak Inverse Voltage

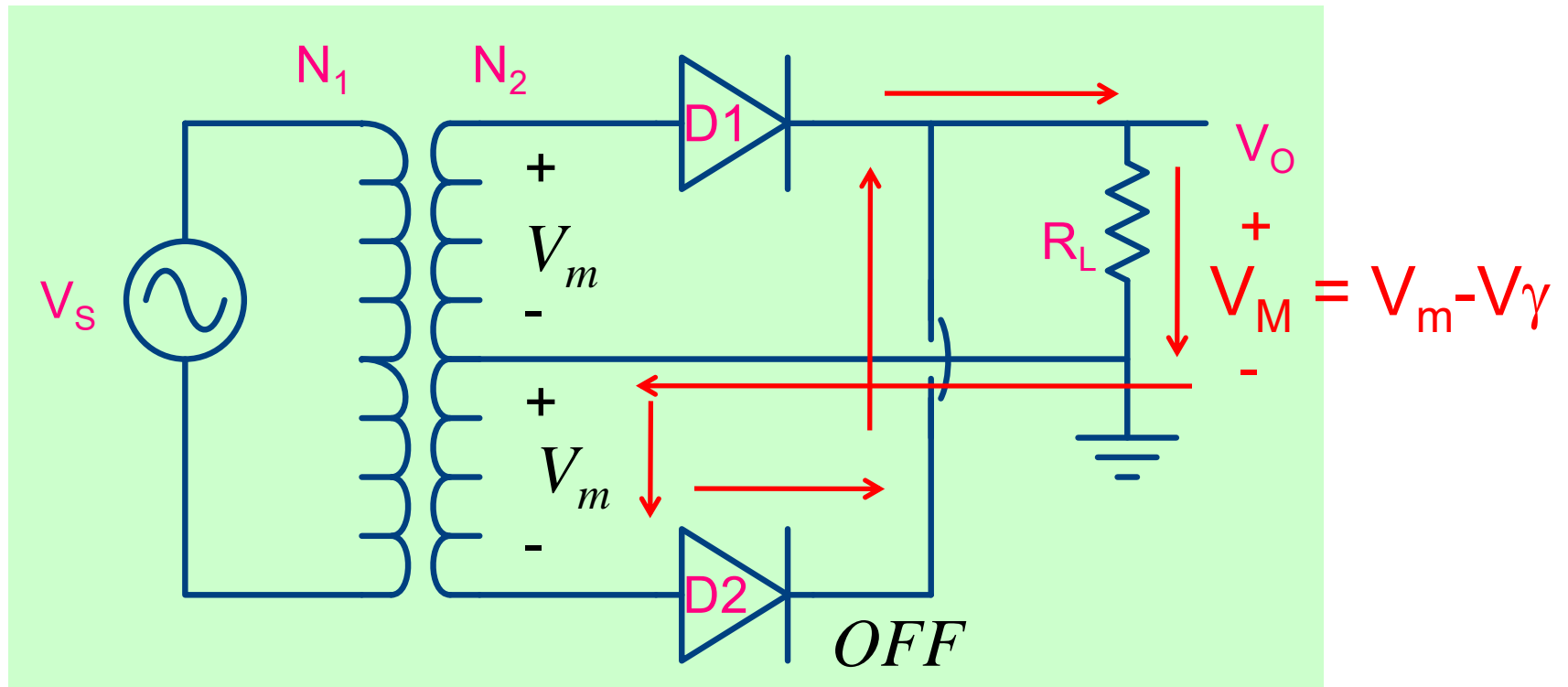


$$V_m + V_D + V_m - V_\gamma = 0$$

$$V_D = -(2V_m - V_\gamma)$$

$$PIV = 2V_m - V_\gamma$$

Peak Inverse Voltage

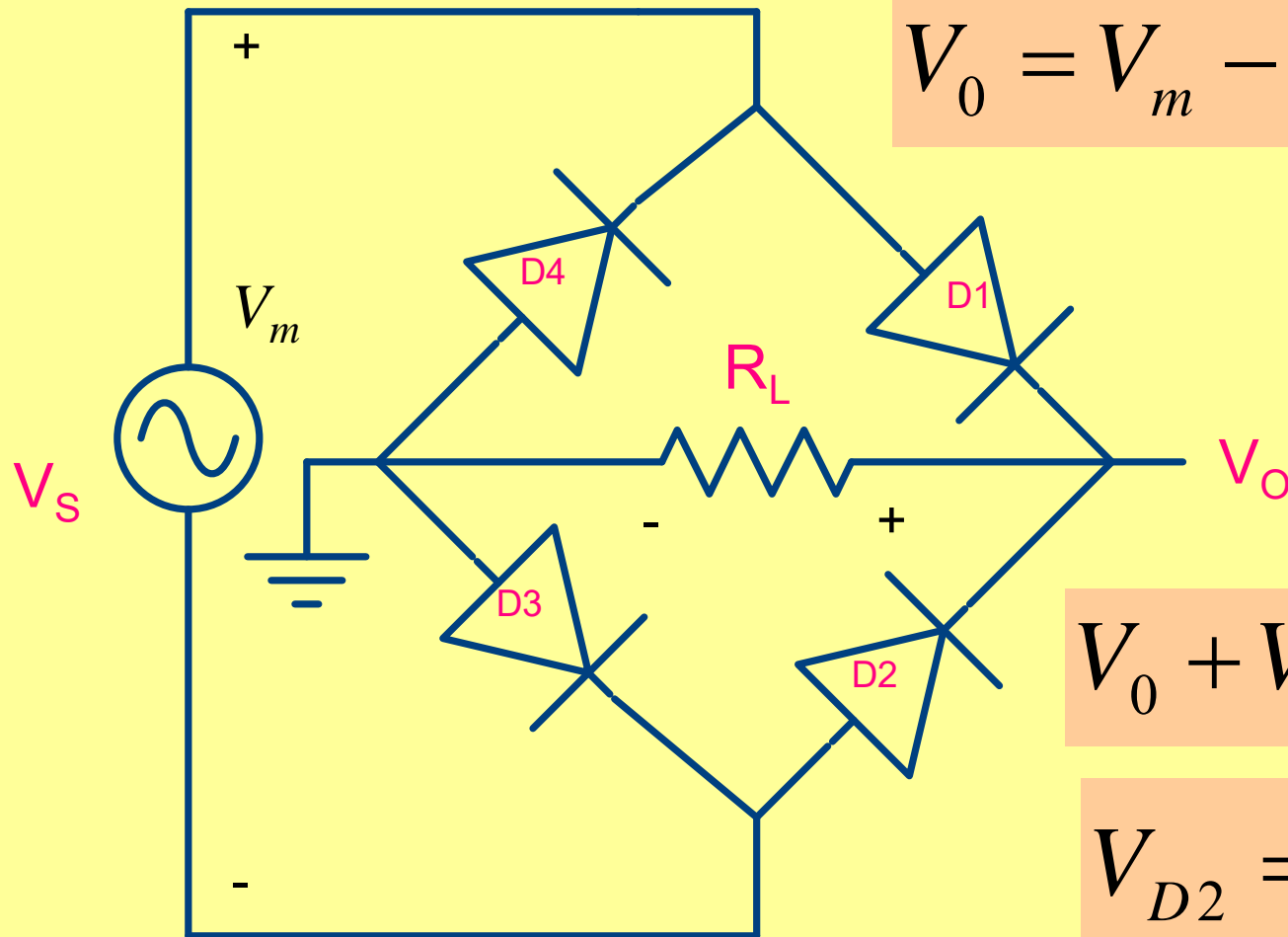

$$-V_m + V_{\gamma 1} + V_o + V_{\gamma 3} = 0$$


$$V_o = V_m - 2V_{\gamma}$$

$$V_o + V_{\gamma 3} + V_{D2} = 0$$

$$V_{D2} = -(V_o + V_{\gamma})$$


$$PIV = V_o + V_{\gamma} = V_m - V_{\gamma}$$

Full wave Rectifier

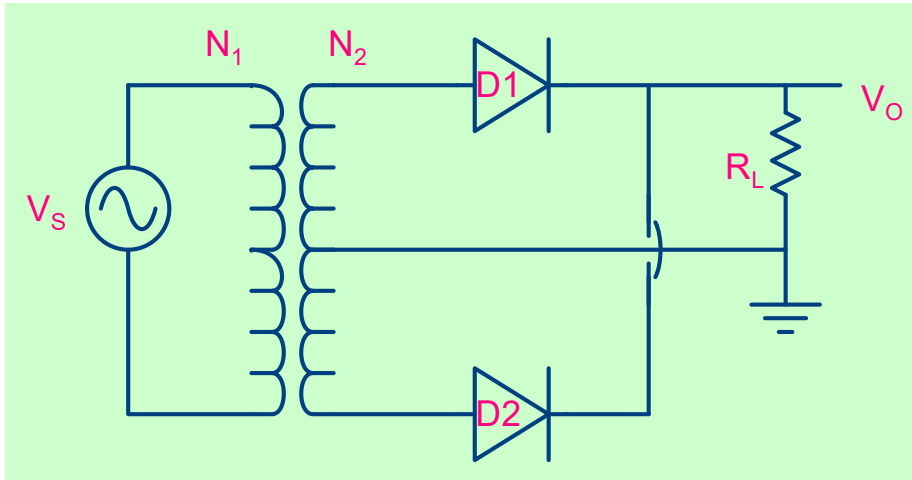

$$PIV = 2V_m - V_\gamma$$




Bridge Rectifier

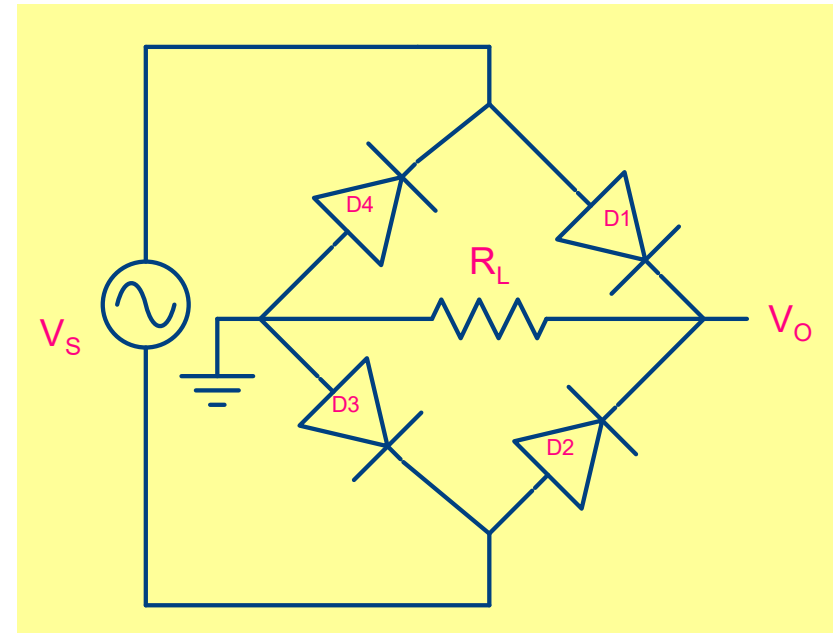



$$PIV = V_m - V_\gamma$$

Zener Diode

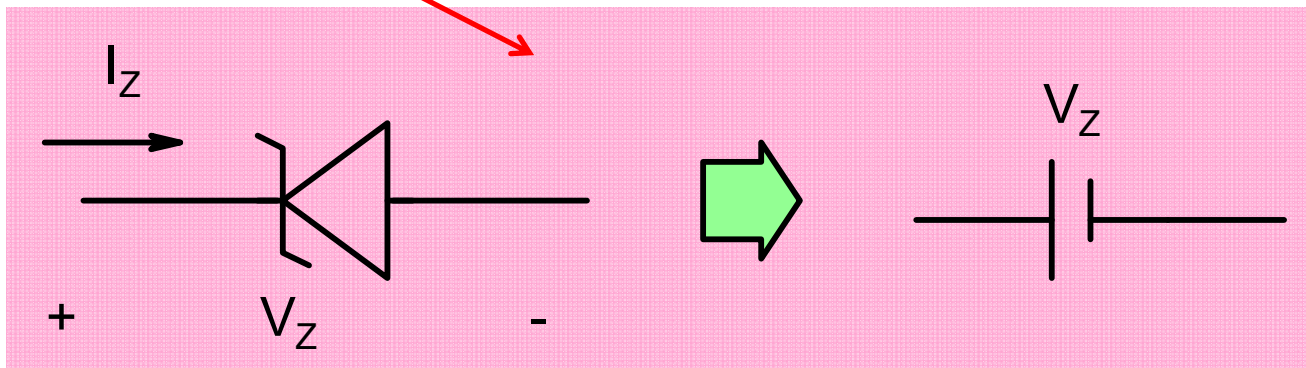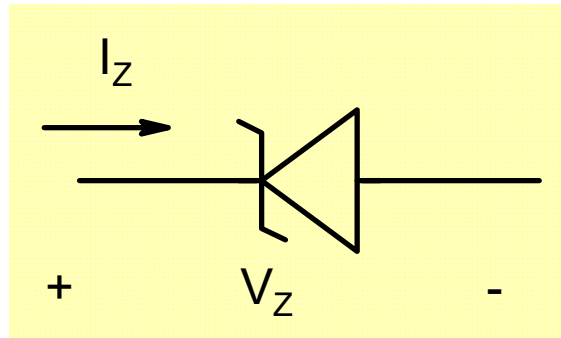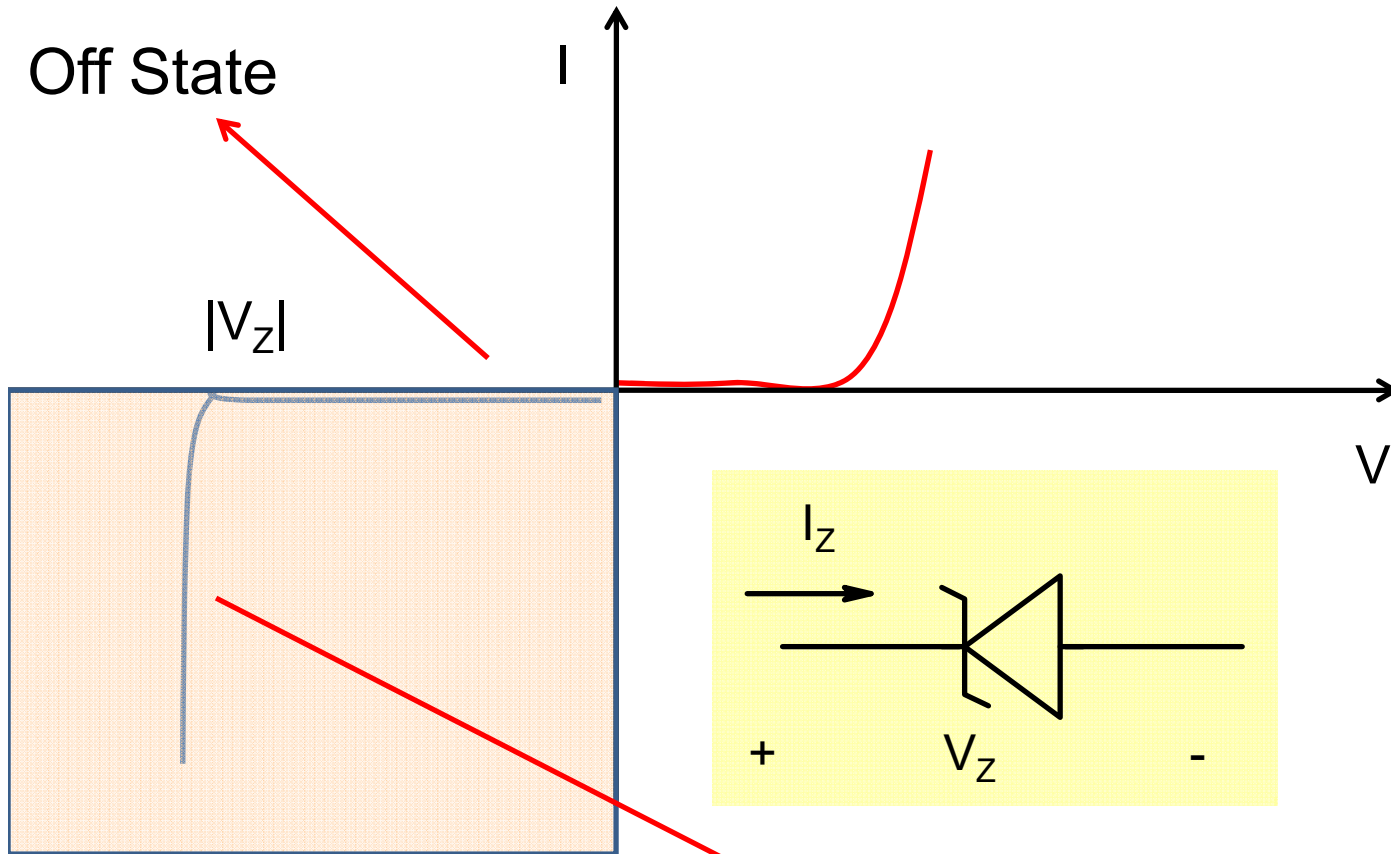A diode specially designed to operate in reverse bias and in 'breakdown' region



Model

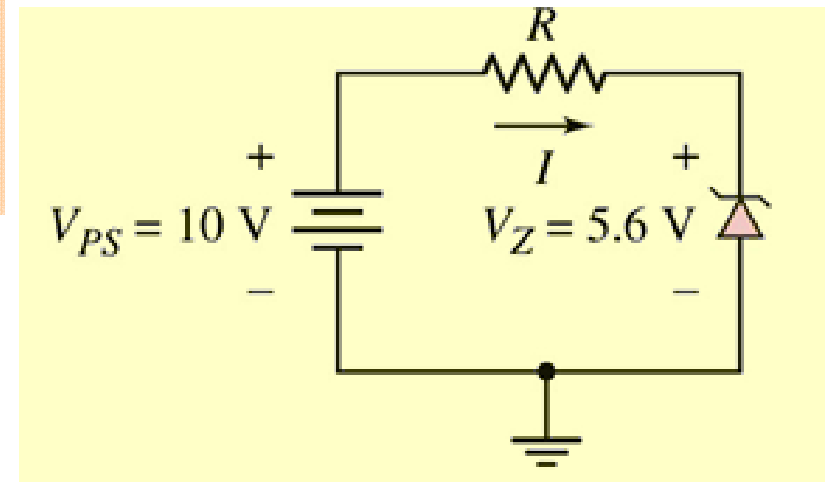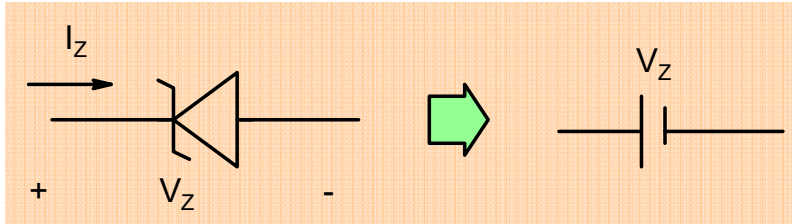

Example


Given $V_Z = 5.6\text{ V}$

$$r_Z = 0\Omega$$


Find a value for R such that the current through the diode is limited to 3 mA

$$I = \frac{V_{PS} - V_Z}{R}$$



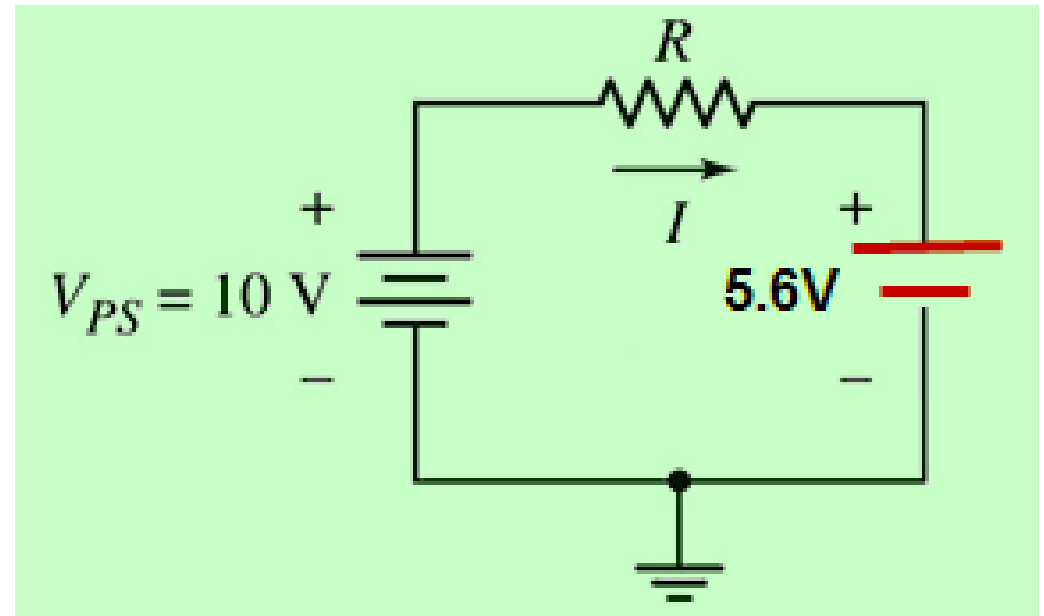
$$R = \frac{V_{PS} - V_Z}{I} = \frac{10\text{ V} - 5.6\text{ V}}{3\text{ mA}} = 1.47\text{ k}\Omega$$







Zener diode: Important Characteristics


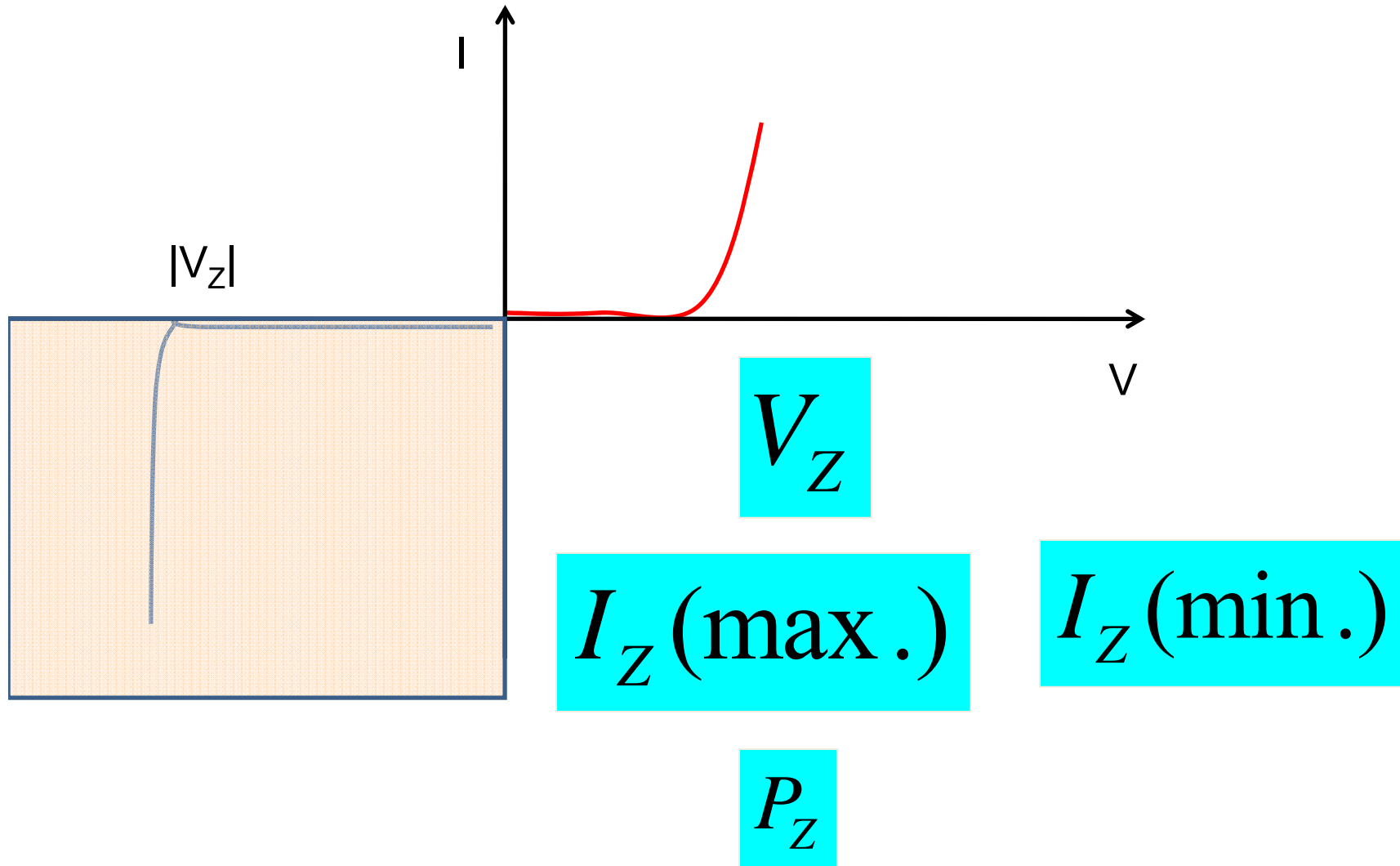


Voltage Reference Circuit

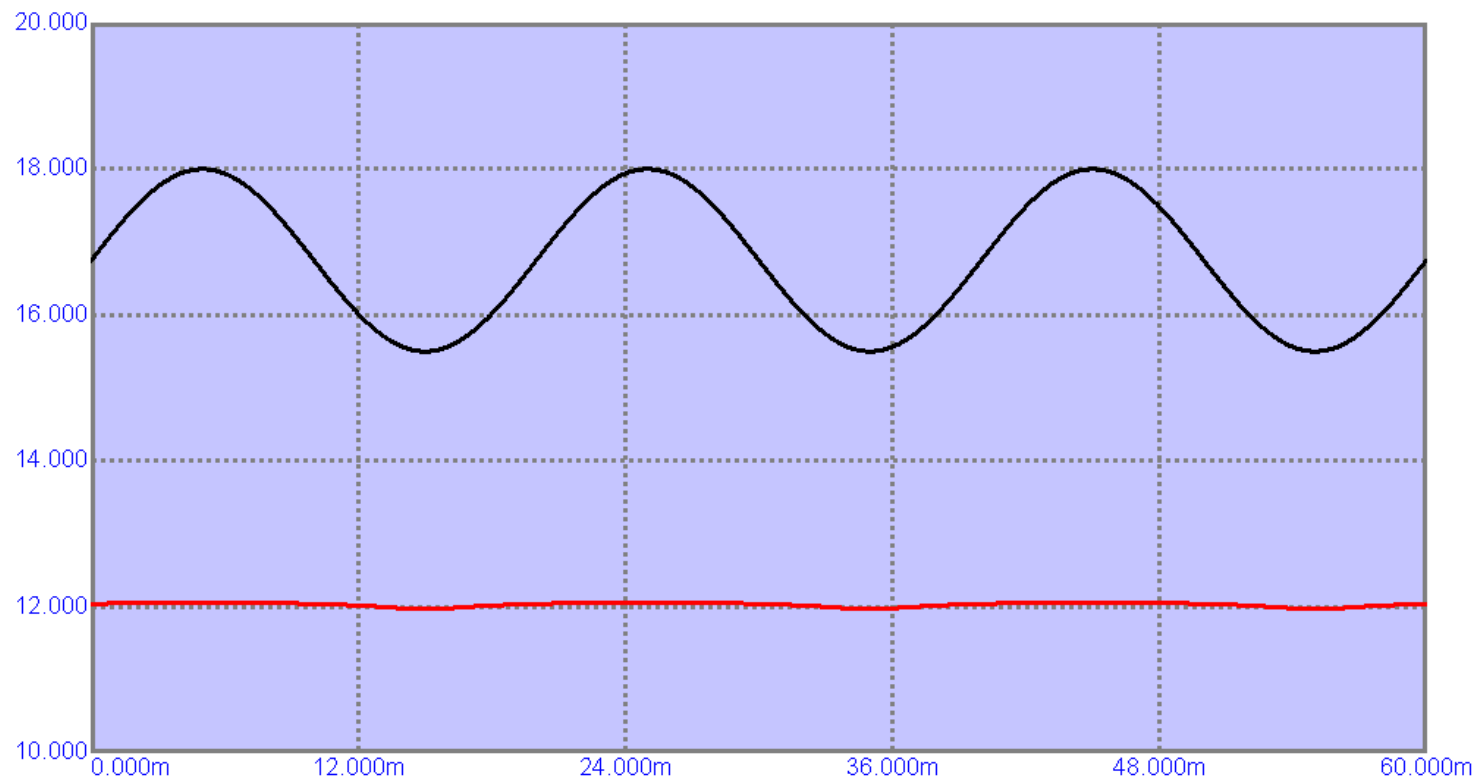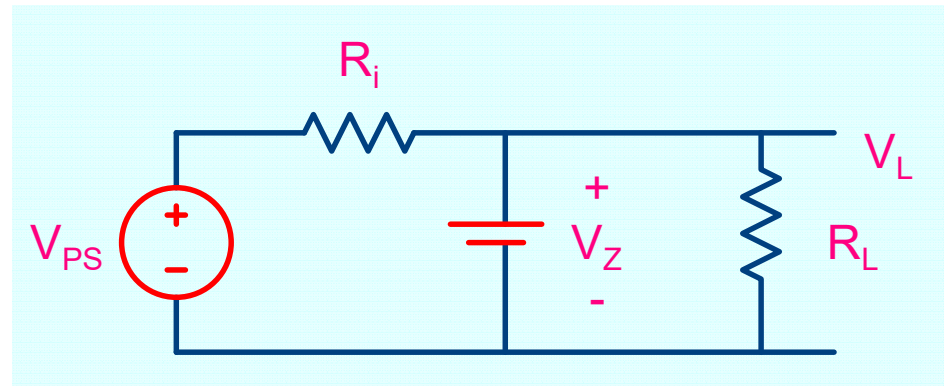
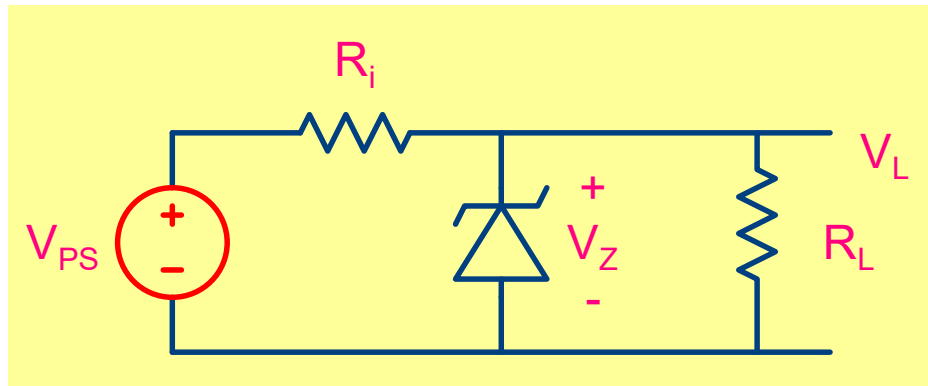


Power supply with regulator

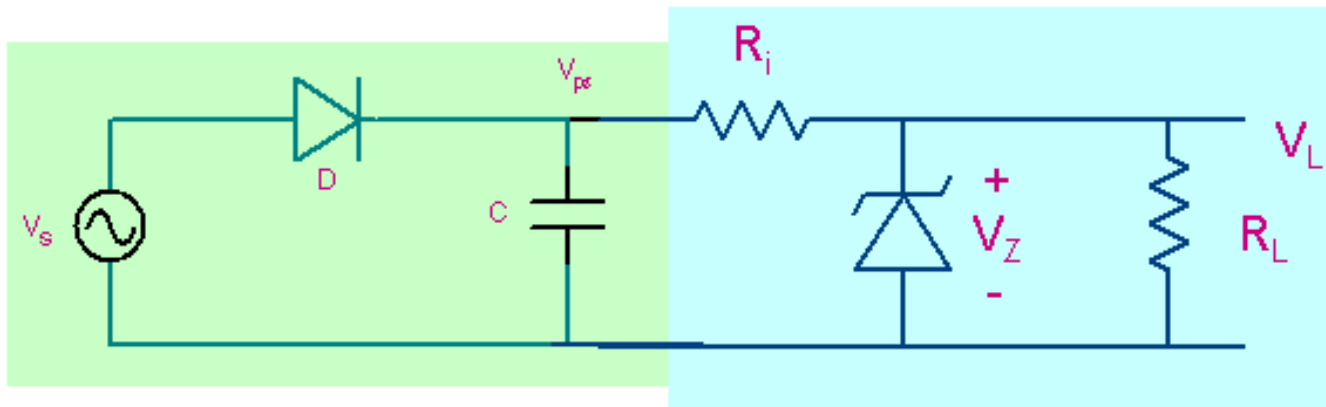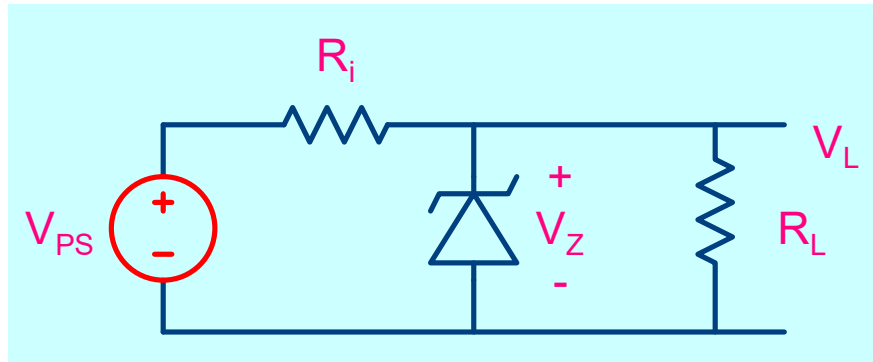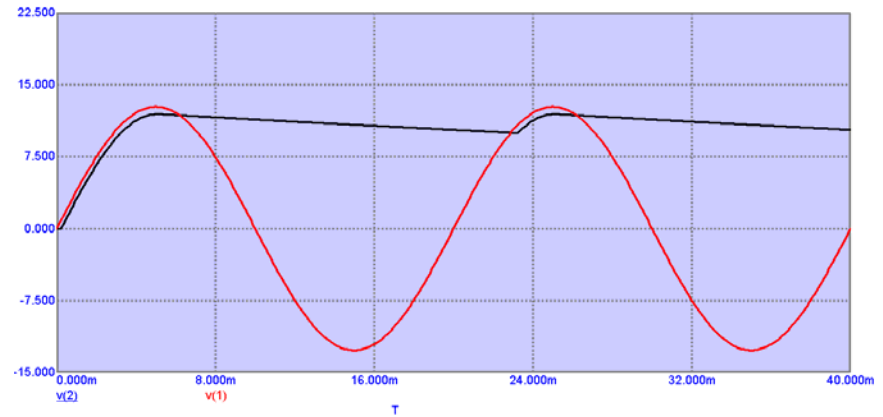
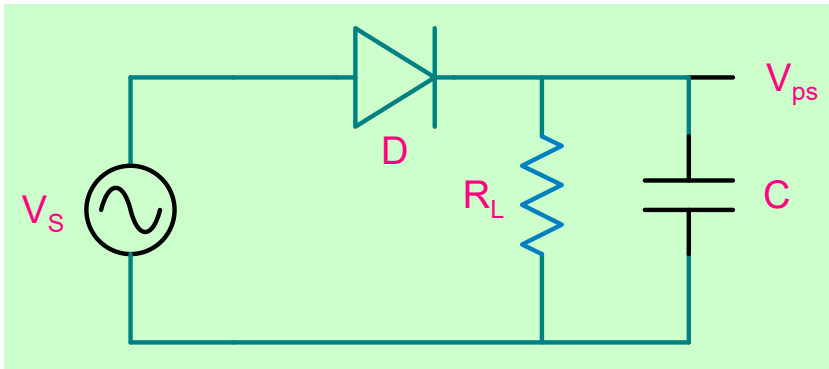


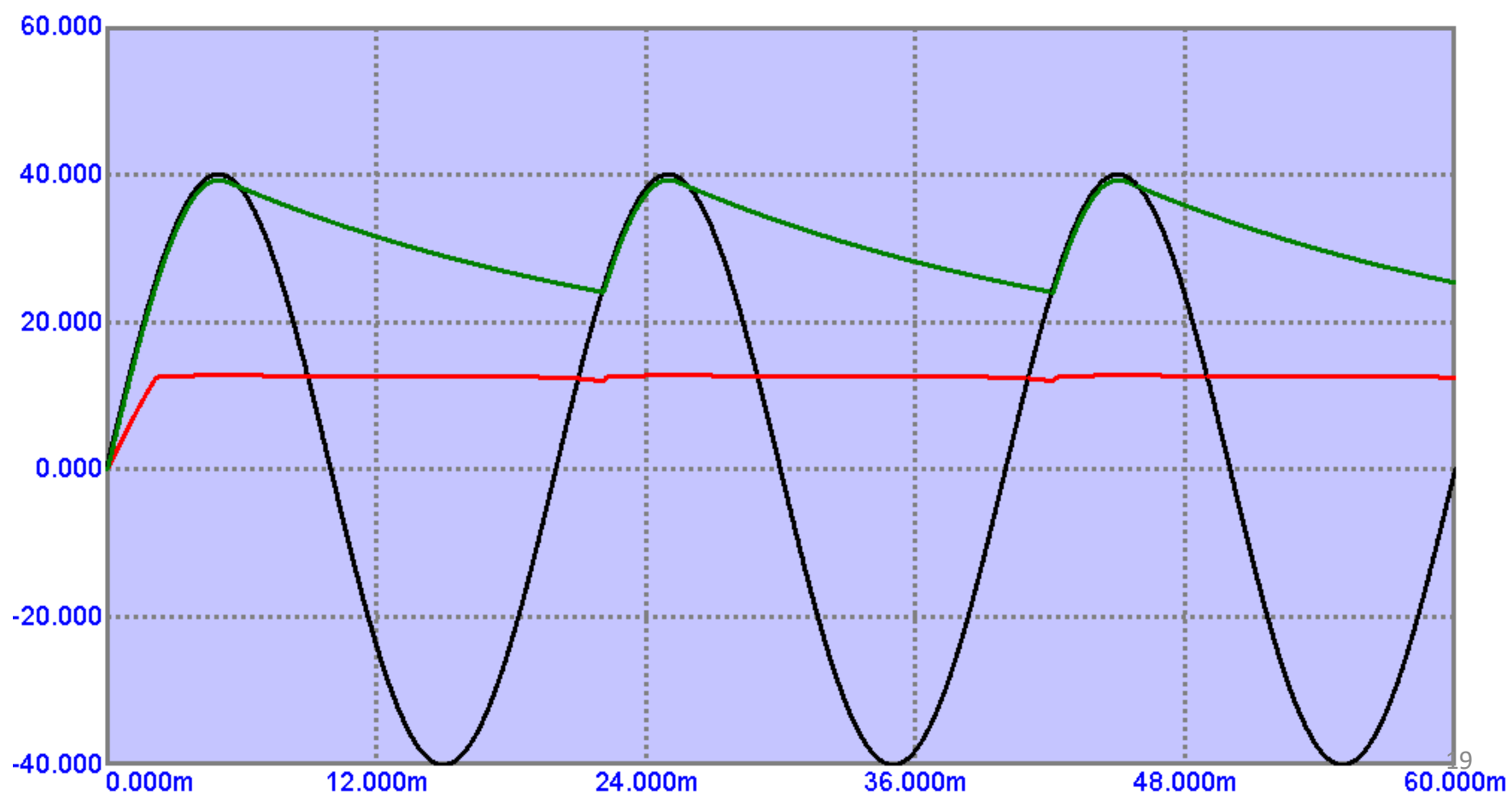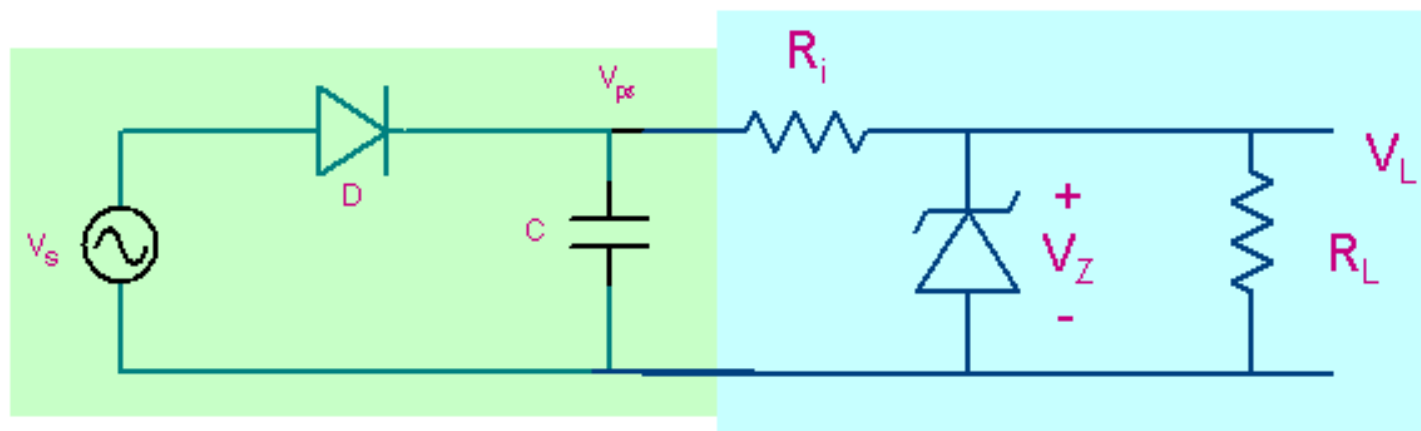

Zener diode as Voltage Regulator

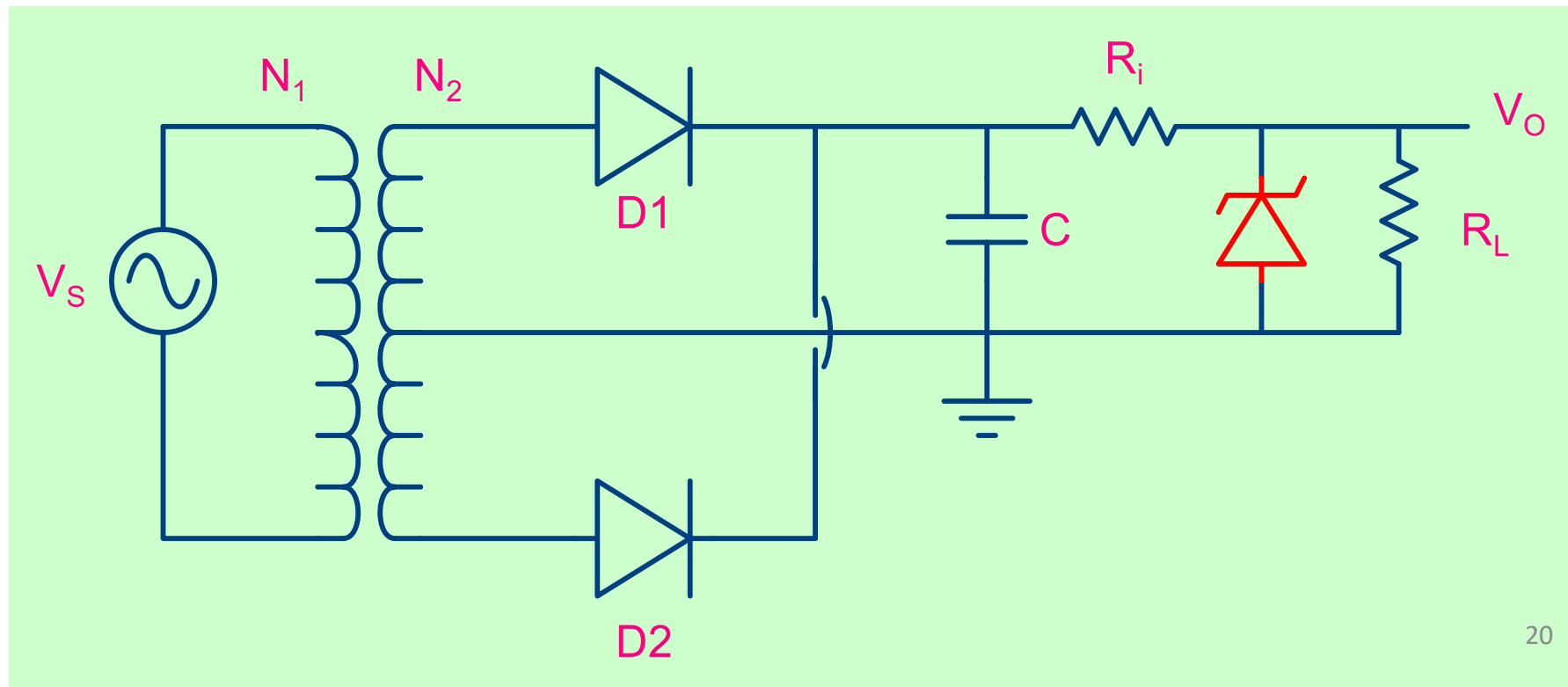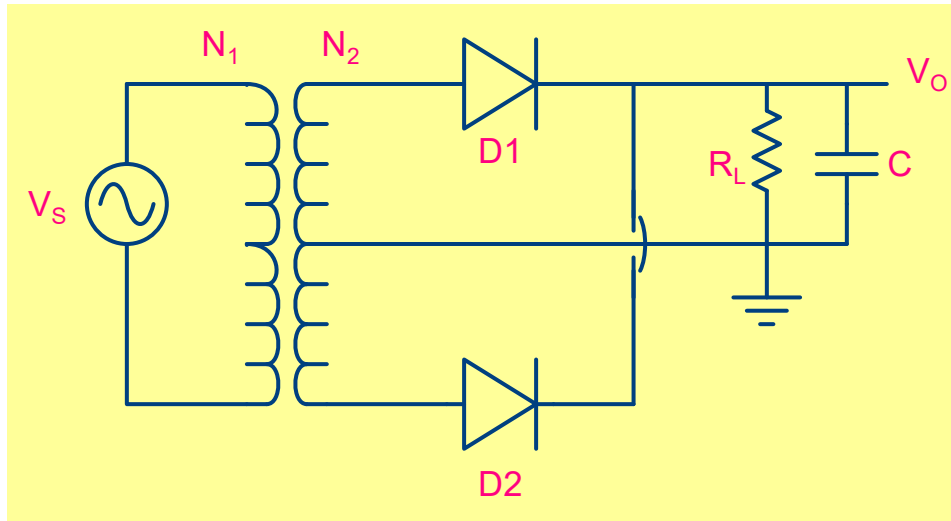


Voltage Reference Circuit

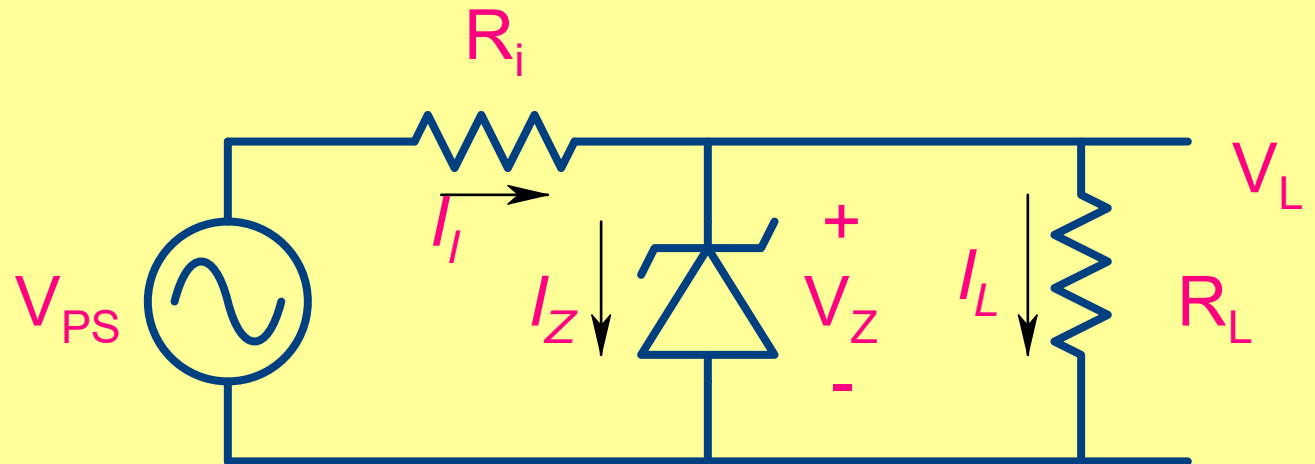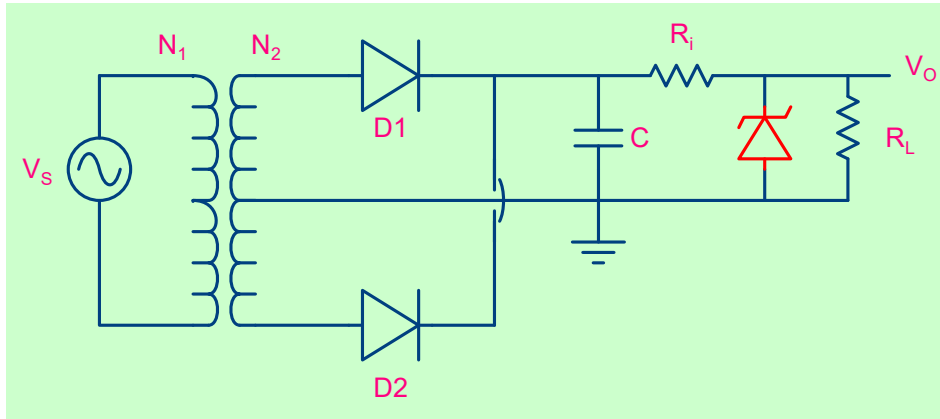

Design Problem: Determine R_i and zener diode specifications such that output voltage is +12 V and ratio of maximum to minimum zener current is 10. The input voltage may vary between 18 to 15.5V. $R_L = 108 \Omega$.

Design Equations

$$P_{Z \max} = V_Z I_{Z \max}$$

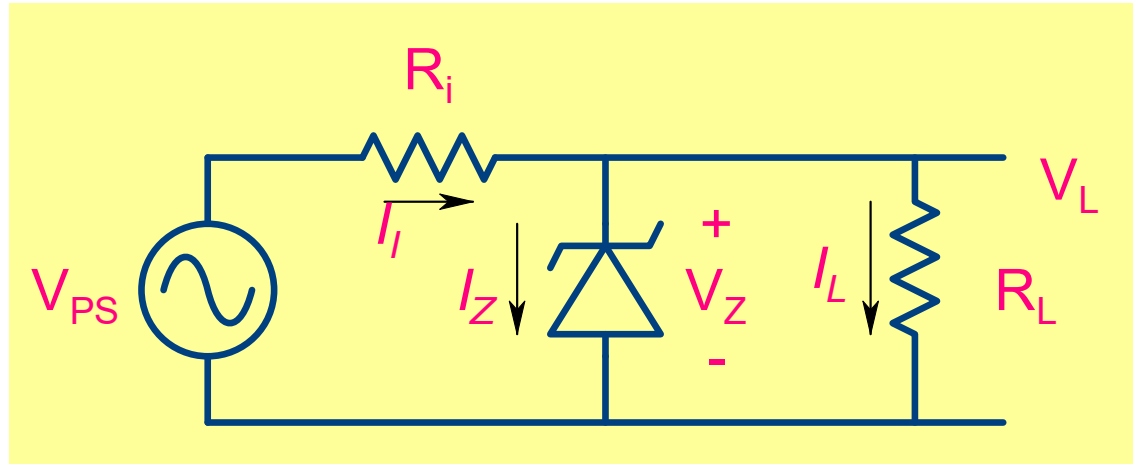

$$I_i = \frac{V_{PS} - V_Z}{R_i} = I_Z + I_L$$

$$I_Z = \frac{V_{PS} - V_Z}{R_i} - I_L$$

$$I_{Z \max} = \frac{V_{PS \max} - V_Z}{R_i} - I_L$$

$$I_{Z \min} = \frac{V_{PS \min} - V_Z}{R_i} - I_L$$

$$\frac{I_{Z \max}}{I_{Z \min}} \cong 10$$

$$R_i = \frac{V_{PS \min} - 0.1V_{PS \max} - 0.9V_Z}{0.9I_L}$$

$$I_{Z \max} = \frac{V_{PS \max} - V_Z}{R_i} - I_L$$

$$I_{Z \min} = \frac{V_{PS \min} - V_Z}{R_i} - I_L$$

$$\frac{I_{Z \max}}{I_{Z \min}} \cong 10$$

$$10 = \frac{V_{PS \max} - V_Z - R_i I_L}{V_{PS \min} - V_Z - R_i I_L}$$

$$V_{PS \min} - V_Z - R_i I_L = 0.1(V_{PS \max} - V_Z - R_i I_L)$$

$$V_{PS \min} - 0.1V_{PS \max} - 0.9V_Z = 0.9R_i I_L$$

$$R_i = \frac{V_{PS \min} - 0.1V_{PS \max} - 0.9V_Z}{0.9I_L}$$

Design Problem: Determine R_i and zener diode specifications such that output voltage is +12V and ratio of maximum to minimum zener current is 10. The input voltage may vary between 18 to 15.5V. $R_L = 108 \Omega$.

$$I_L = \frac{V_L}{R_L} = \frac{12}{108} = \frac{1}{9}$$

$$\begin{aligned} R_i &= \frac{V_{PS \min} - 0.1V_{PS \max} - 0.9V_Z}{0.9I_L} \\ &= \frac{15.5 - 0.1 \cdot 18 - 0.9 \cdot 12}{0.9(1/9)} \\ &= \frac{15.5 - 1.8 - 10.8}{0.1} = \frac{2.9}{0.1} = 29 \Omega \end{aligned}$$

$$\begin{aligned} I_{Z \max} &= \frac{V_{PS \max} - V_Z}{R_i} - I_L \\ &= \frac{18 - 12}{29} - \frac{1}{9} = \frac{6}{29} - \frac{1}{9} = 0.096 \text{ A} \end{aligned}$$

$$\begin{aligned} I_{Z \min} &= \frac{V_{PS \min} - V_Z}{R_i} - I_L \\ &= \frac{15.5 - 12}{29} - \frac{1}{9} = \frac{3.5}{29} - \frac{1}{9} \\ &= 0.0096 \text{ A} \end{aligned}$$

$$\begin{aligned} P_{Z \max} &= V_Z I_{Z \max} \\ &= 12 \cdot 0.096 = 1.152 \text{ W} \end{aligned}$$

