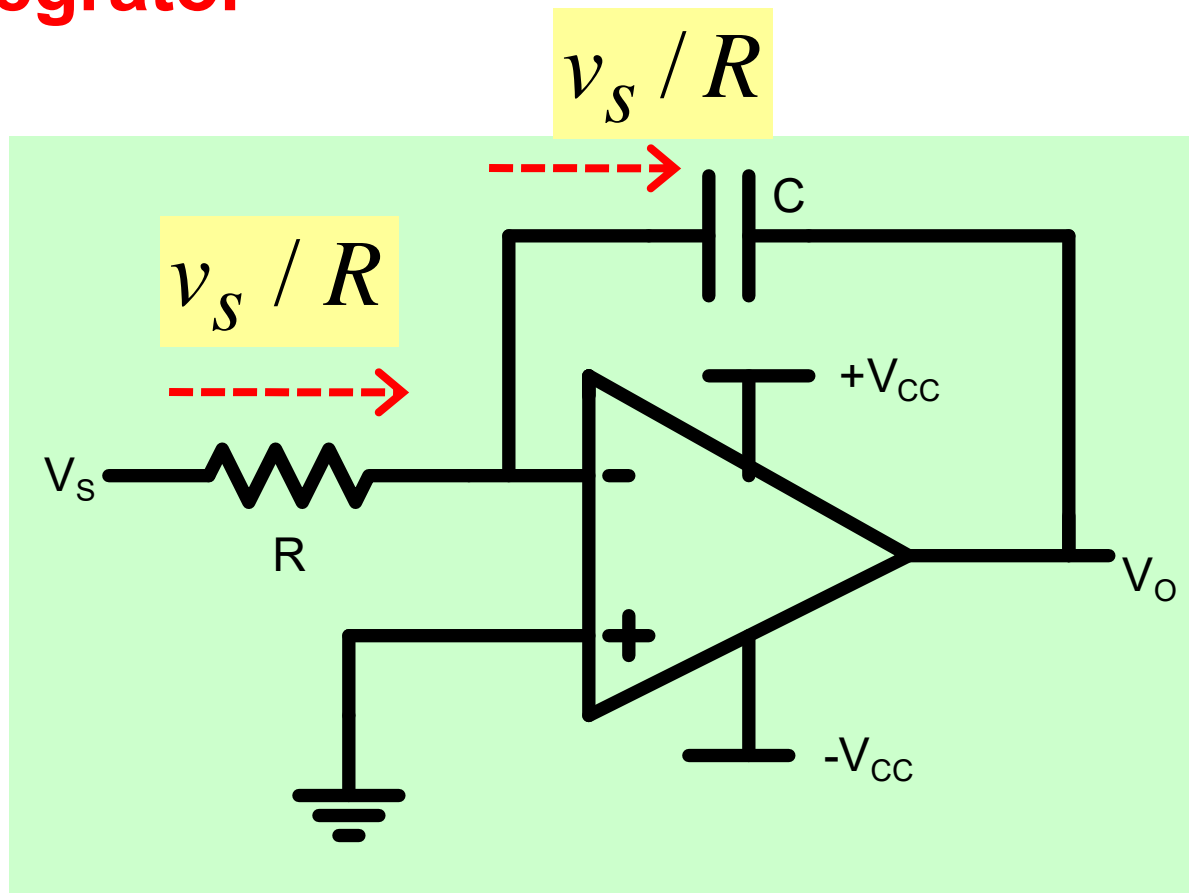


# **ESc201 : Introduction to Electronics**

## **Operational Amplifier Part-2**


Dr. Y. S. Chauhan  
Dept. of Electrical Engineering  
IIT Kanpur

# Integrator




$$\frac{v_s}{R} = -C \frac{dV_o}{dt} \Rightarrow V_o(t) = -\frac{1}{RC} \int v_s dt$$

# Differentiator

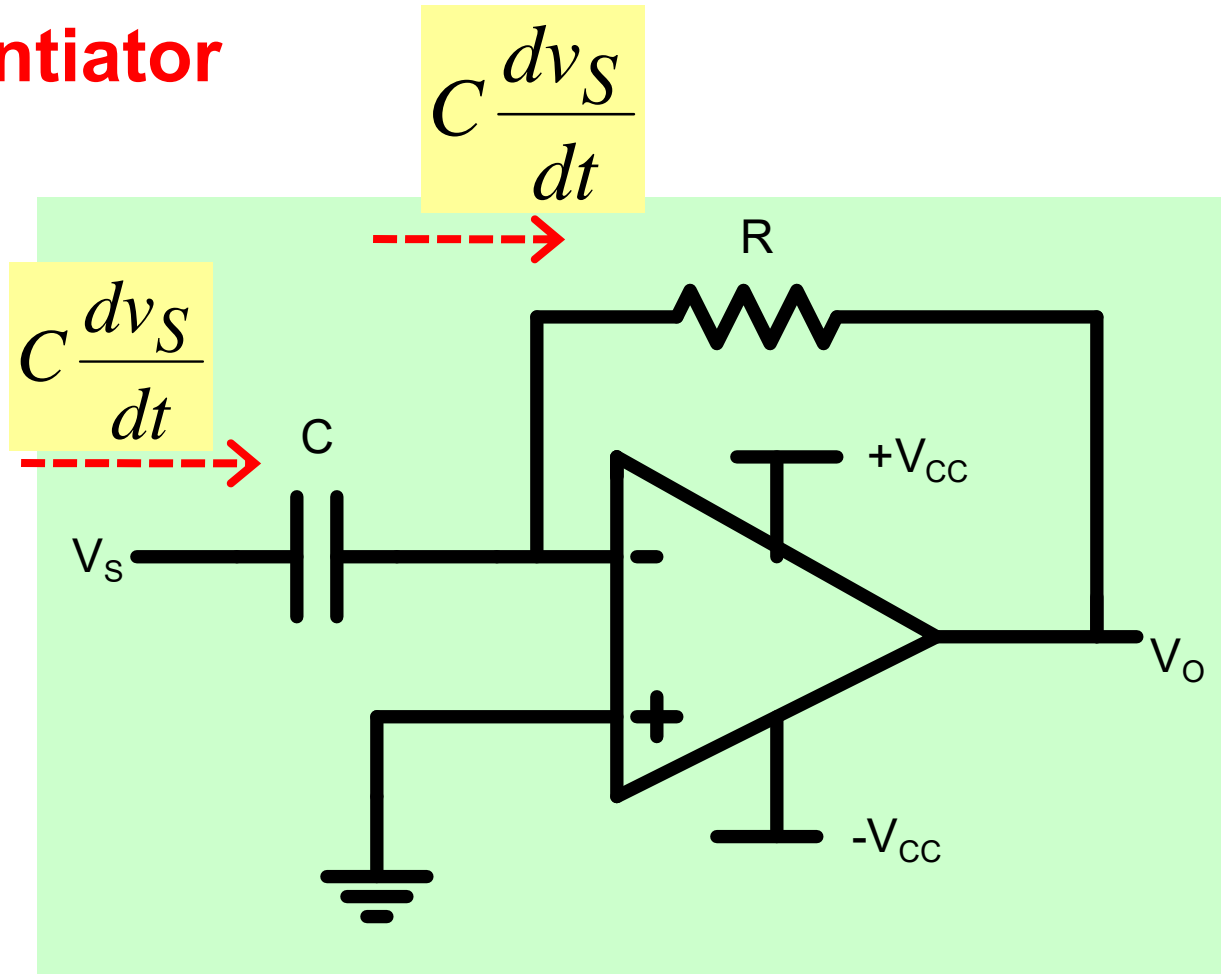

$$-\frac{V_o}{R} = C \frac{dv_s}{dt} \Rightarrow V_o(t) = -RC \frac{dv_s}{dt}$$

# Log Amplifier

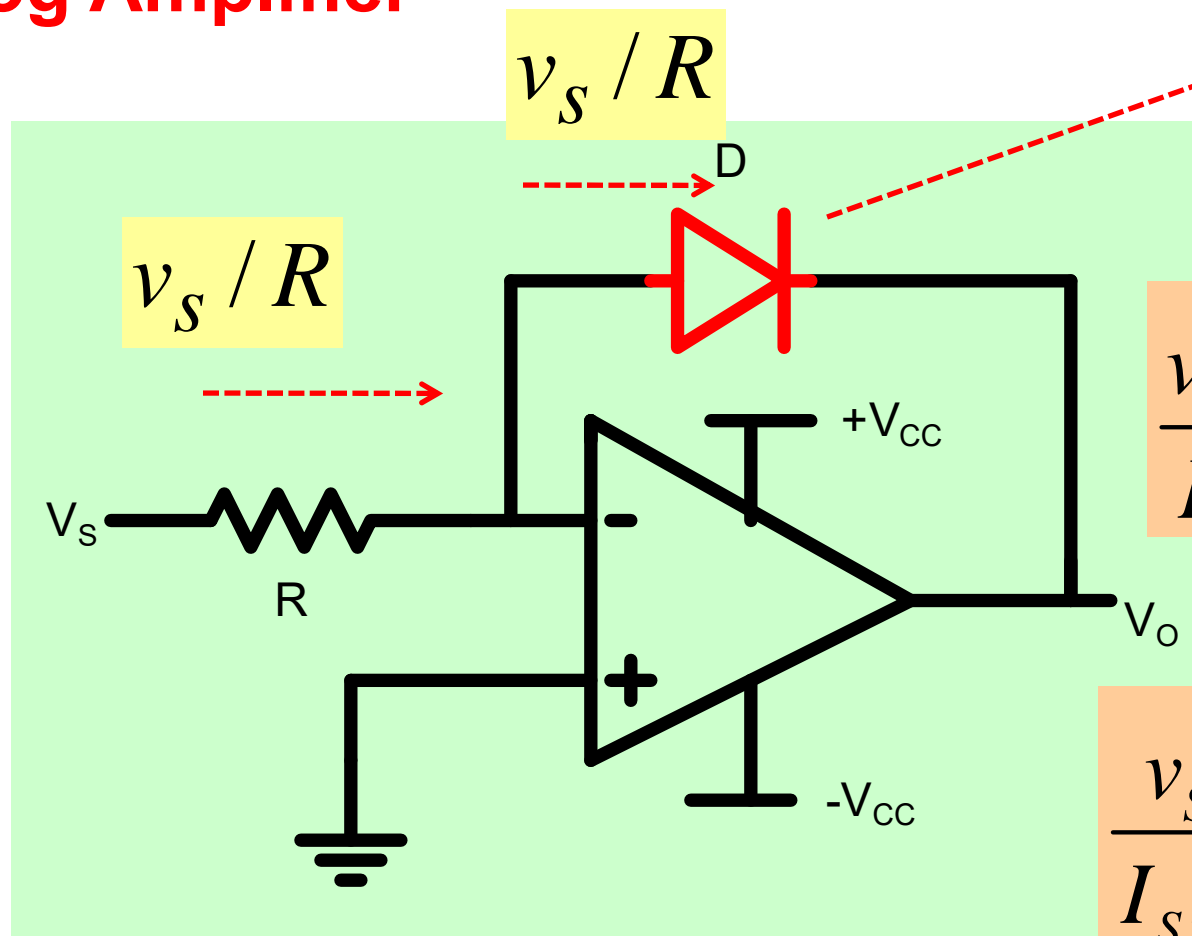


$$I = I_s (e^{\frac{V}{V_T}} - 1)$$

$$\frac{v_s}{R} = I_s (e^{-\frac{V_o}{V_T}} - 1)$$

$$\frac{v_s}{I_s R} + 1 = e^{-\frac{V_o}{V_T}}$$


$$\Rightarrow -V_o = V_T \times \ln\left(1 + \frac{v_s}{RI_s}\right) \cong V_T \times \ln\left(\frac{v_s}{RI_s}\right)$$

# Temperature Sensor ?

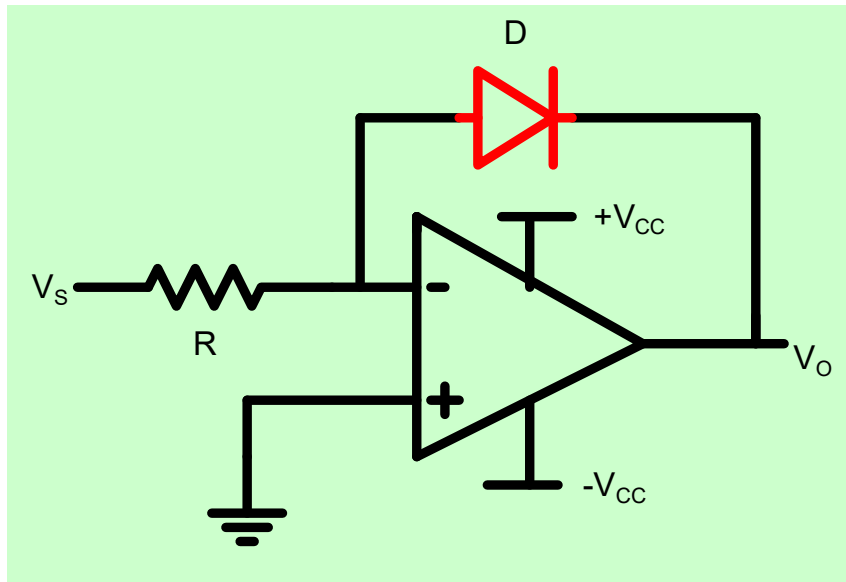


$$V_O = -V_T \times \ln\left(\frac{V_S}{RI_S}\right); V_T = \frac{k_B T}{q}$$

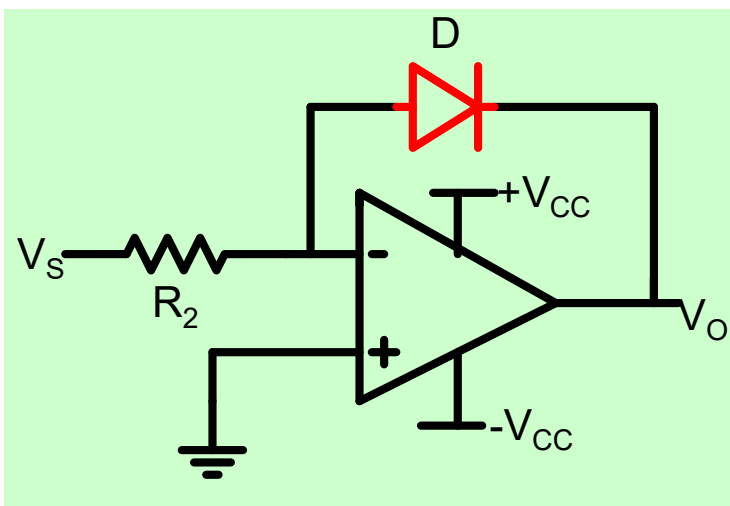
But  $I_S$  is a function of temperature as well.



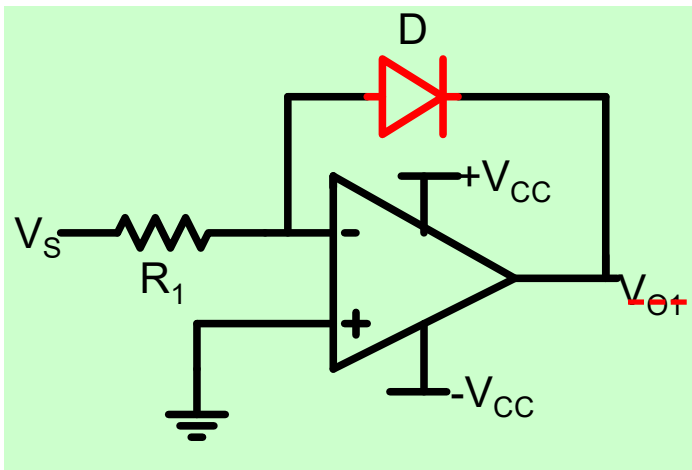
$$V_O = -V_T \times \ln\left(\frac{V_S}{R_2 I_S}\right)$$


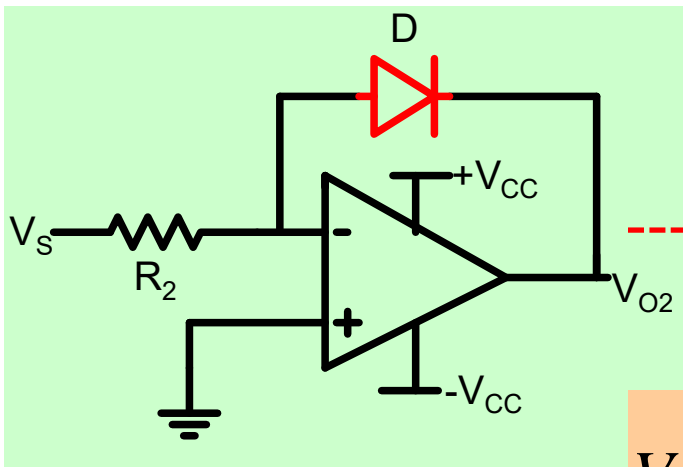
$$V_{O1} = -V_T \times \ln\left(\frac{V_S}{R_1 I_S}\right)$$



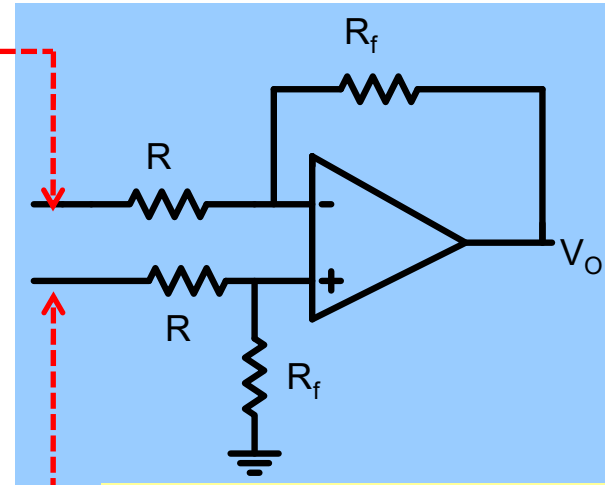
$$V_{O2} = -V_T \times \ln\left(\frac{V_S}{R_2 I_S}\right)$$




$$V_O = -\frac{R_f}{R} V_{O1} + \left(1 + \frac{R_f}{R}\right) \times \frac{R_f}{R_f + R} V_{O2}$$

$$V_O = \frac{R_f}{R} (V_{O2} - V_{O1})$$

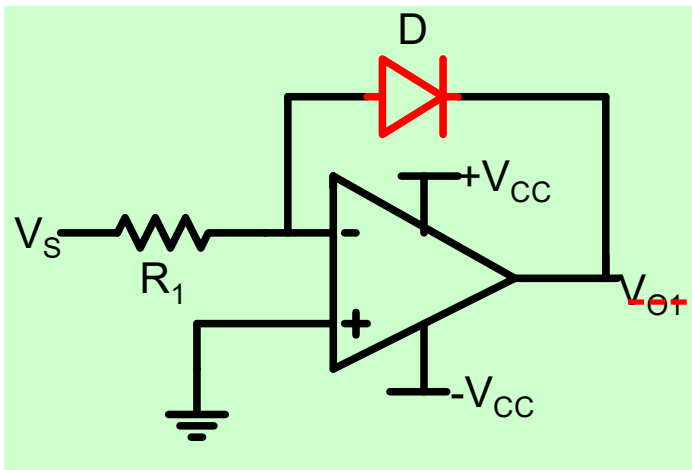
$$V_O = \frac{R_f}{R} V_T \left( -\ln\left(\frac{V_S}{R_2 I_S}\right) + \ln\left(\frac{V_S}{R_1 I_S}\right) \right)$$


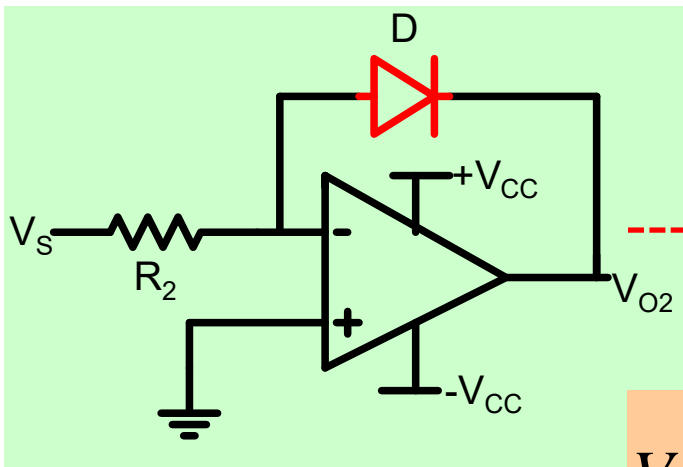
$$V_{O1} = -V_T \times \ln\left(\frac{V_S}{R_1 I_S}\right)$$


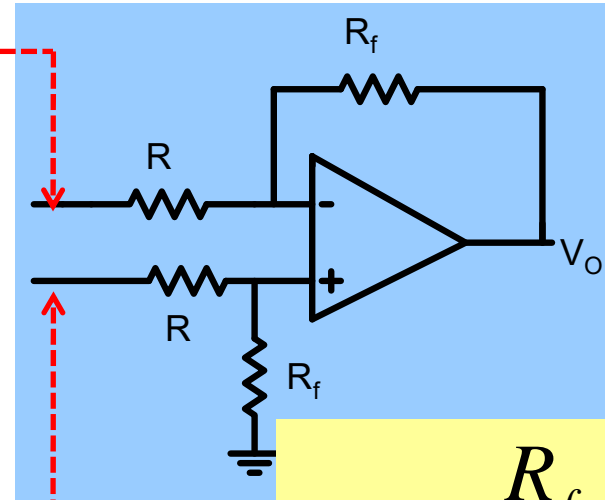
$$V_{O2} = -V_T \times \ln\left(\frac{V_S}{R_2 I_S}\right)$$




$$V_O = \frac{R_f}{R} V_T \times \ln\left(\frac{R_2}{R_1}\right)$$

Output voltage is directly proportional to temperature
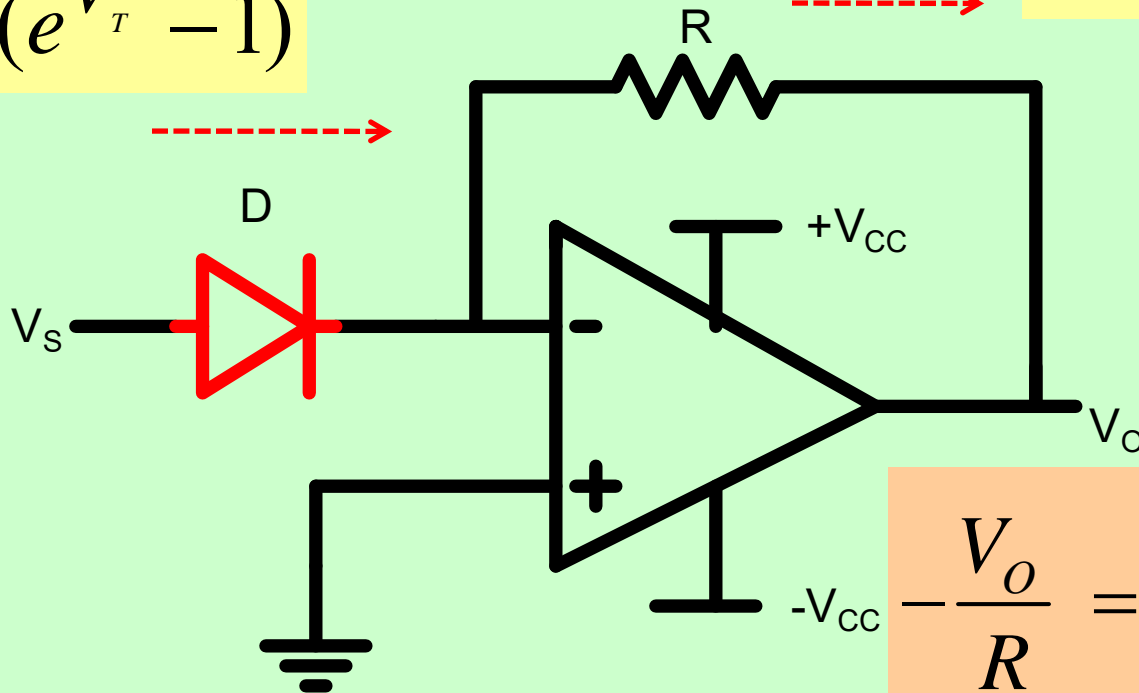
# AntiLog Amplifier

$$I = I_s \left( e^{\frac{V_s}{V_T}} - 1 \right)$$

$$I = I_s \left( e^{\frac{V_s}{V_T}} - 1 \right)$$




$$-\frac{V_o}{R} = I_s \left( e^{\frac{V_s}{V_T}} - 1 \right)$$

$$\Rightarrow V_o = -RI_s \left( e^{\frac{V_s}{V_T}} - 1 \right) \cong -RI_s \times e^{\frac{V_s}{V_T}}$$



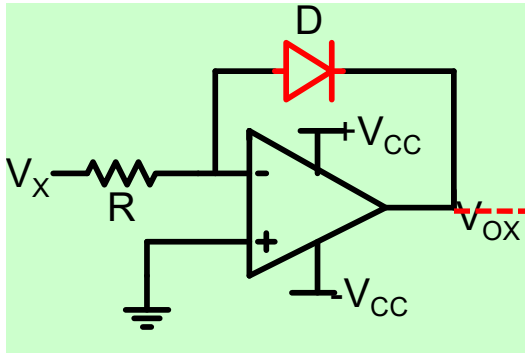
# Multiplier


$$V_{O1} = V_T \times \left( \ln\left(\frac{V_X}{RI_S}\right) + \ln\left(\frac{V_Y}{RI_S}\right) \right)$$



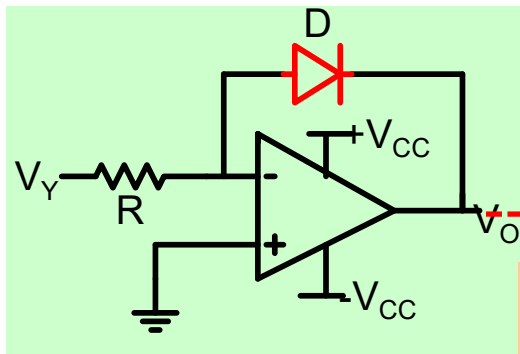
$$V_{OX} = -V_T \times \ln\left(\frac{V_X}{RI_S}\right)$$


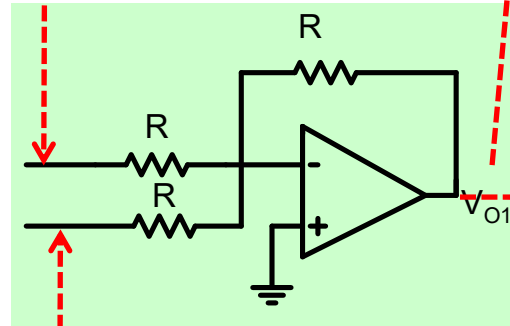
$$V_{OY} = -V_T \times \ln\left(\frac{V_Y}{RI_S}\right)$$



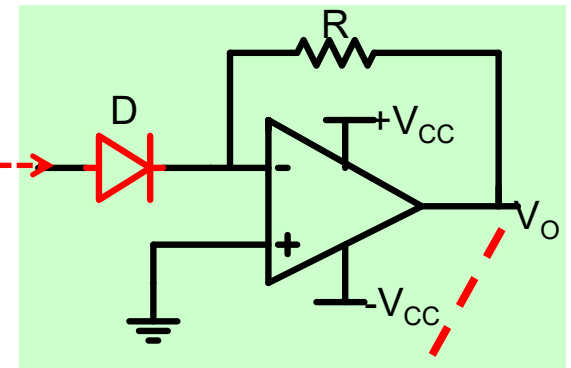
$$V_{O1} = V_T \times \ln\left(\frac{V_X V_Y}{R^2 I_S^2}\right)$$



$$V_O \cong -RI_S \times e^{\frac{V_{O1}}{V_T}} = -\frac{V_X V_Y}{RI_S}$$

# Difference Amplifier

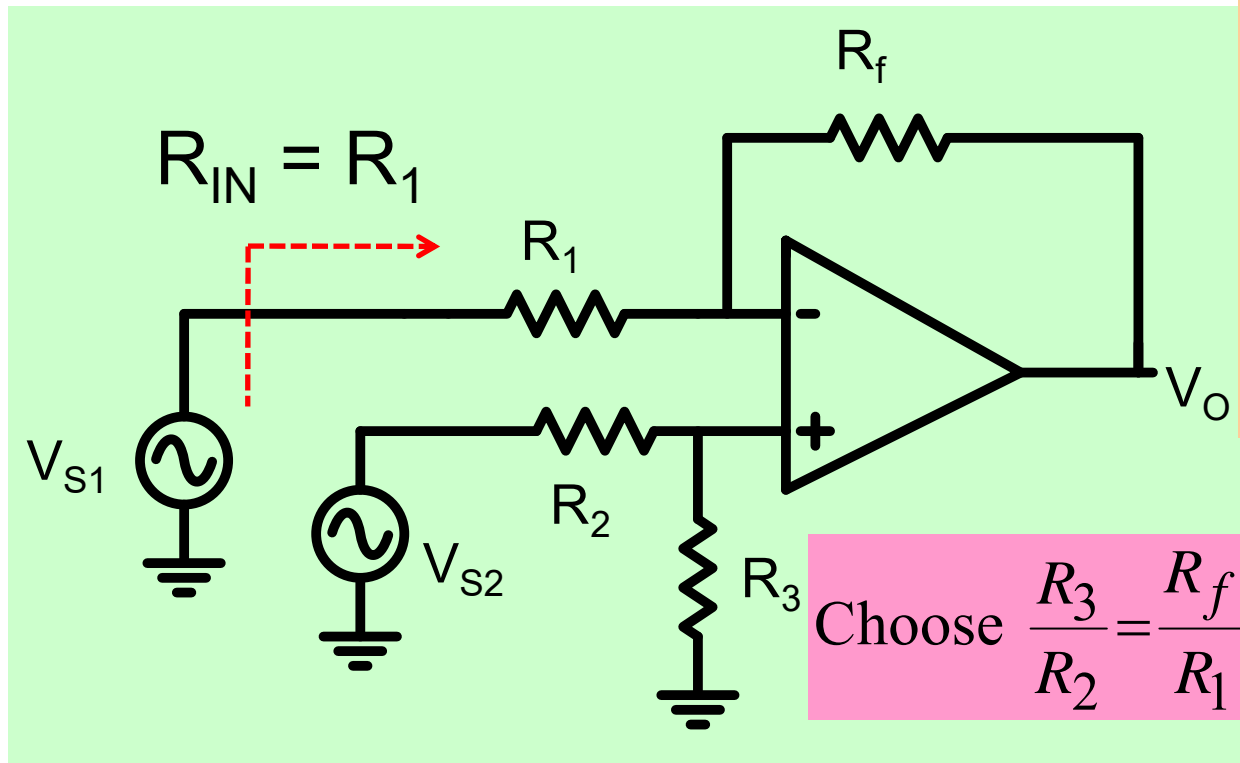

$$v_o = v_{s2} \frac{\frac{R_3}{R_2}}{(1 + \frac{R_3}{R_2})} (1 + \frac{R_f}{R_1}) - (\frac{R_f}{R_1}) v_{s1}$$

Choose  $\frac{R_3}{R_2} = \frac{R_f}{R_1}$


$$v_o = \frac{R_f}{R_1} (v_{s2} - v_{s1})$$

Need to be checked input resistance

A drawback is that input resistance is relatively Lower

To change gain, we have to change two resistors and a slight mismatch can drastically reduce common mode rejection ratio

# Instrumentation Amplifier

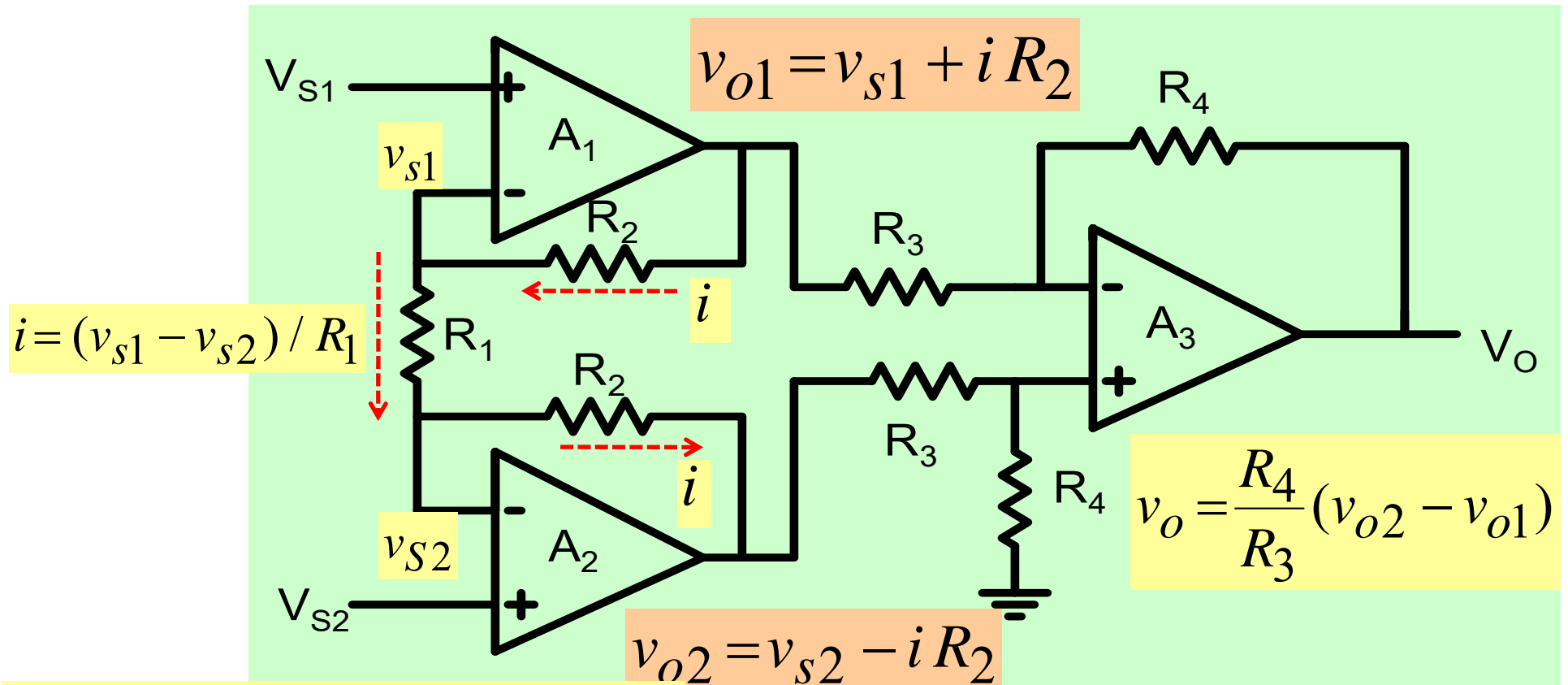


$$v_o = \frac{R_4}{R_3} (v_{s2} - i R_2 - v_{s1} - i R_2)$$

$$v_o = \frac{R_4}{R_3} (\{v_{s2} - v_{s1}\} - 2R_2 \{(v_{s1} - v_{s2}) / R_1\})$$

$$v_o = \frac{R_4}{R_3} (v_{s2} - v_{s1} - 2i R_2)$$

$$v_o = \frac{R_4}{R_3} (v_{s2} - v_{s1}) \left(1 + 2 \frac{R_2}{R_1}\right)$$

# Instrumentation Amplifier



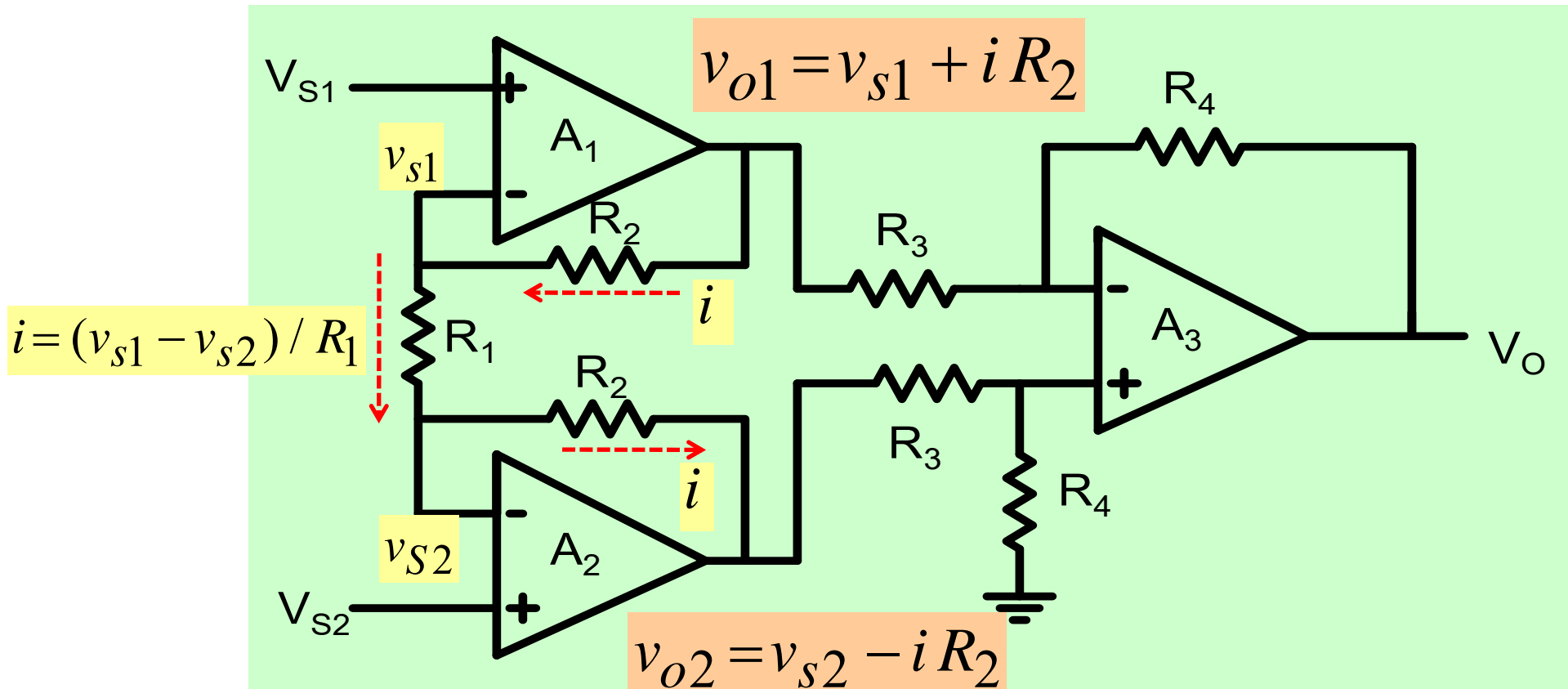



$$v_o = \frac{R_4}{R_3} \times \left(1 + \frac{2R_2}{R_1}\right) \times (v_{s2} - v_{s1})$$

Very high input Resistance


Can change one resistor  $R_1$  and change gain
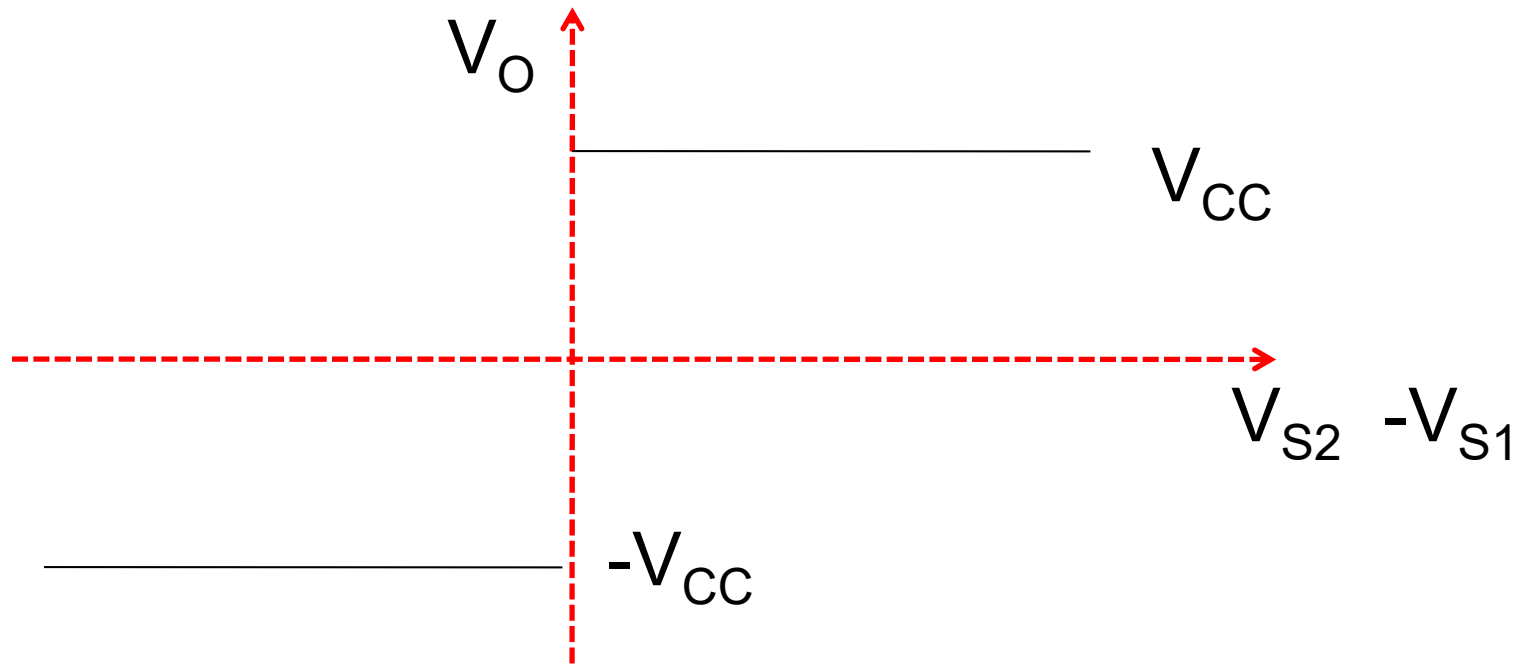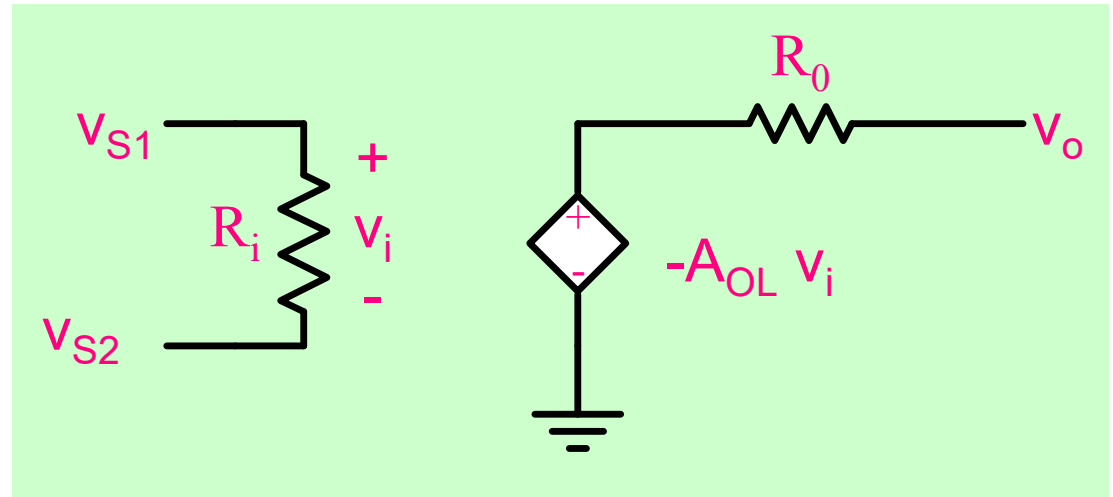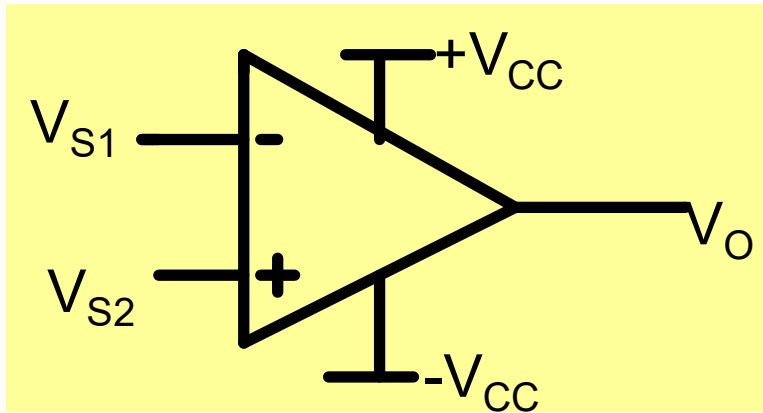
# Comparator: Opamp under open Loop condition



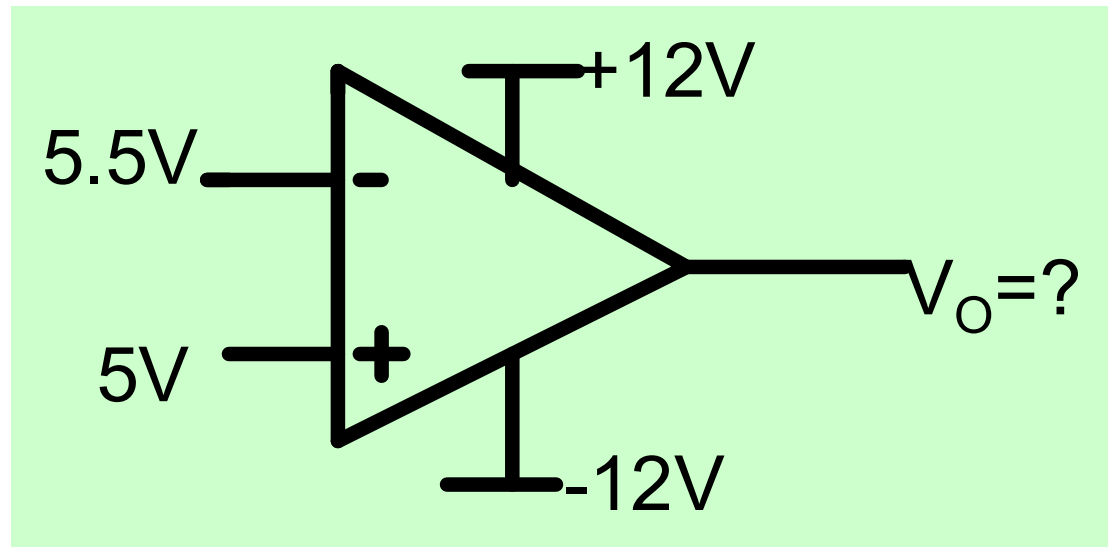

**$\sim -12V$**

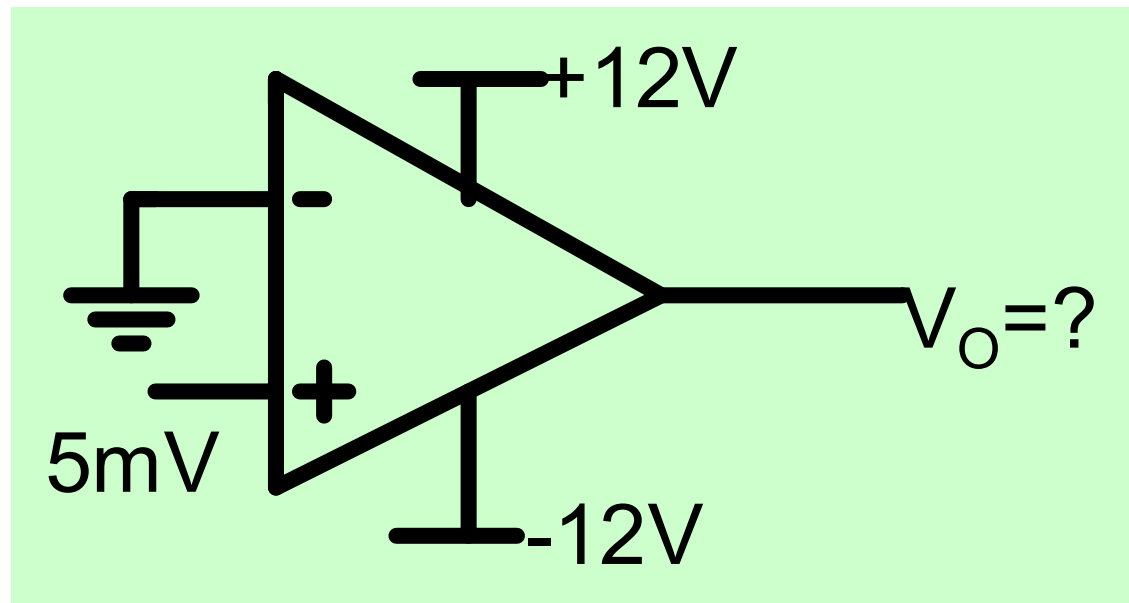




**$\sim +12V$**

## Example





$$v_{in} = 1V \sin(2\pi ft);$$

$$f = 1KHz$$
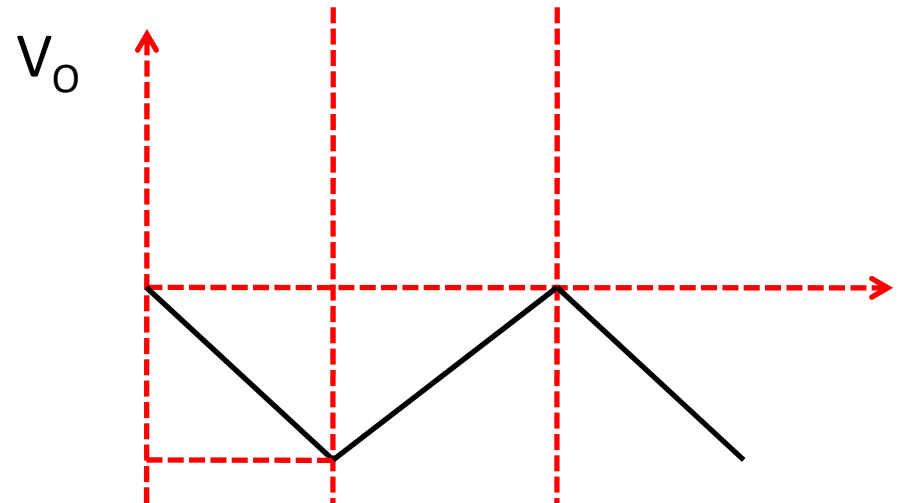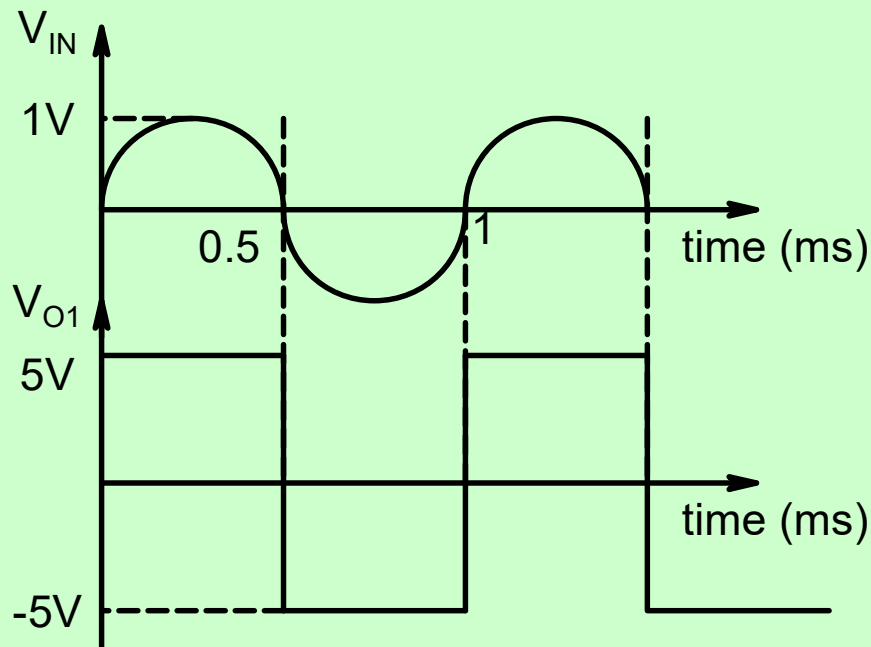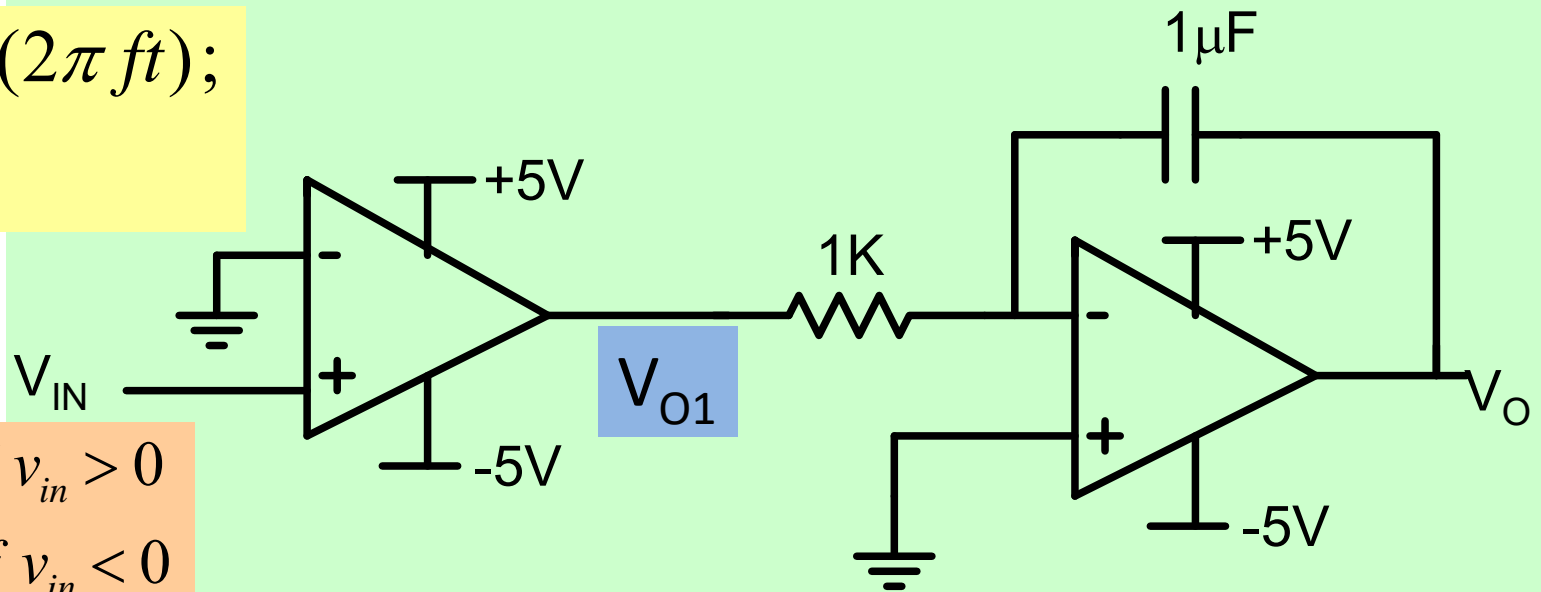
$$\begin{aligned} V_{O1} &= +5V \text{ if } v_{in} > 0 \\ &= -5V \text{ if } v_{in} < 0 \end{aligned}$$



# Example

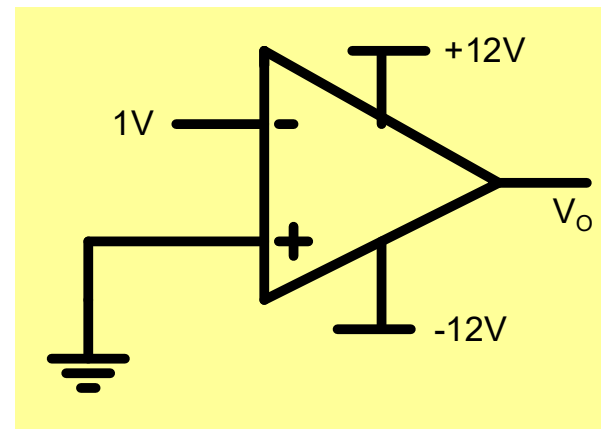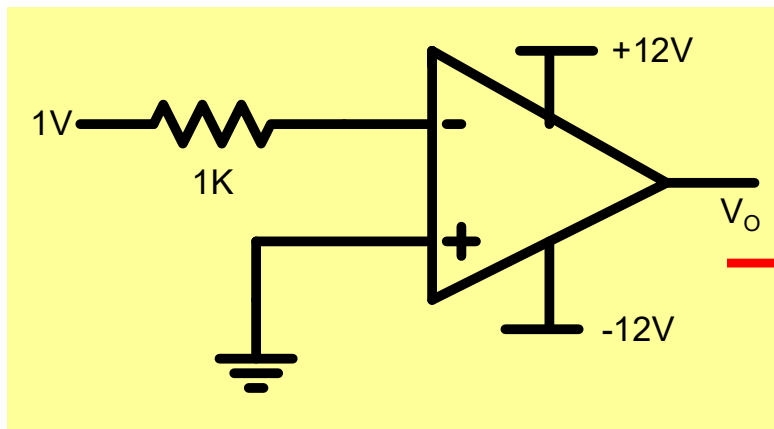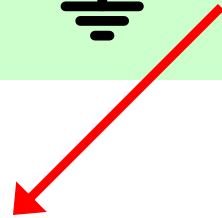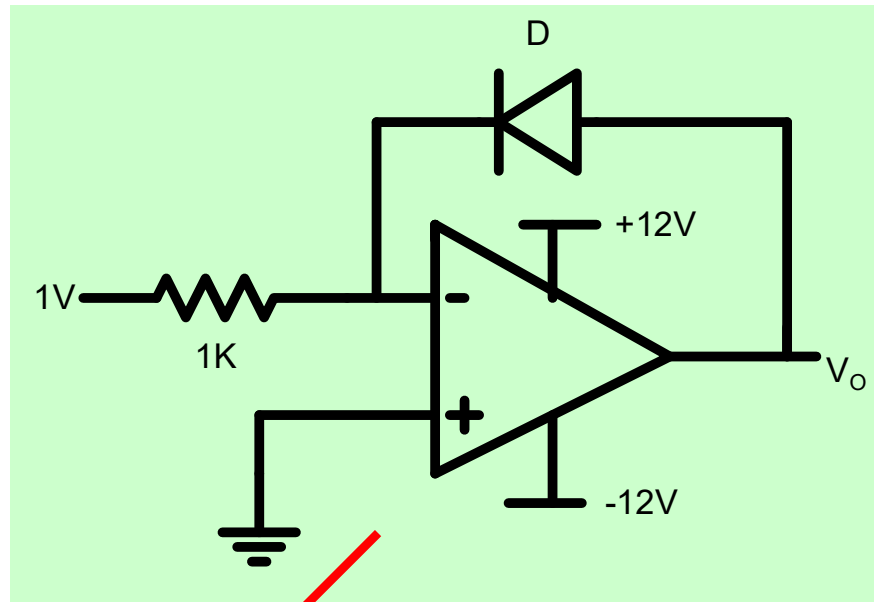

**$\sim -12V$**




# Comparator

$$V_2 > V_3 \Rightarrow V_0 = -V_{sat}$$

$$V_2 < V_3 \Rightarrow V_0 = +V_{sat}$$

$$V_0 = A_v (V_3 - V_2)$$

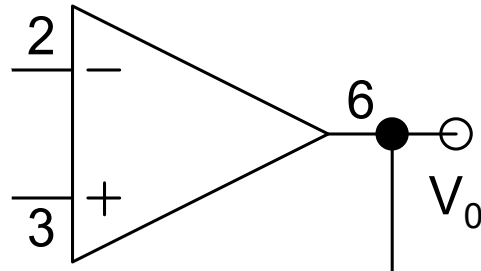

# Schmitt Trigger

$$V_2 > V_3 \Rightarrow V_0 = -V_{sat}$$


$$V_2 < V_3 \Rightarrow V_0 = +V_{sat}$$

$$V_3 = V_0 \frac{R_2}{R_1 + R_2}$$

$$R_2 = 10k$$

$$V_3 = \pm V_{sat} \frac{10}{10+15}$$
$$= \pm 12 \times \frac{2}{5} = \pm 4.8V$$

$$V_0 = A_v (V_3 - V_2)$$

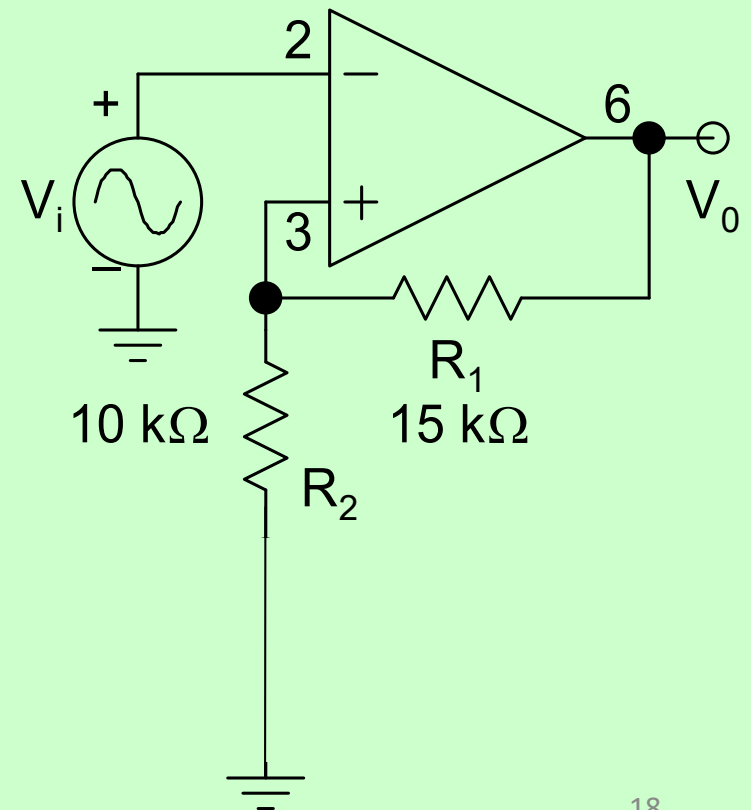

# Schmitt Trigger

$$V_2 > V_3 \Rightarrow V_0 = -V_{sat}$$



$$V_2 < V_3 \Rightarrow V_0 = +V_{sat}$$

$$V_0 = A_v (V_3 - V_2)$$


$$V_3 = \pm 4.8V$$

$$V_{IH} = +4.8V$$


$$V_{IL} = -4.8V$$

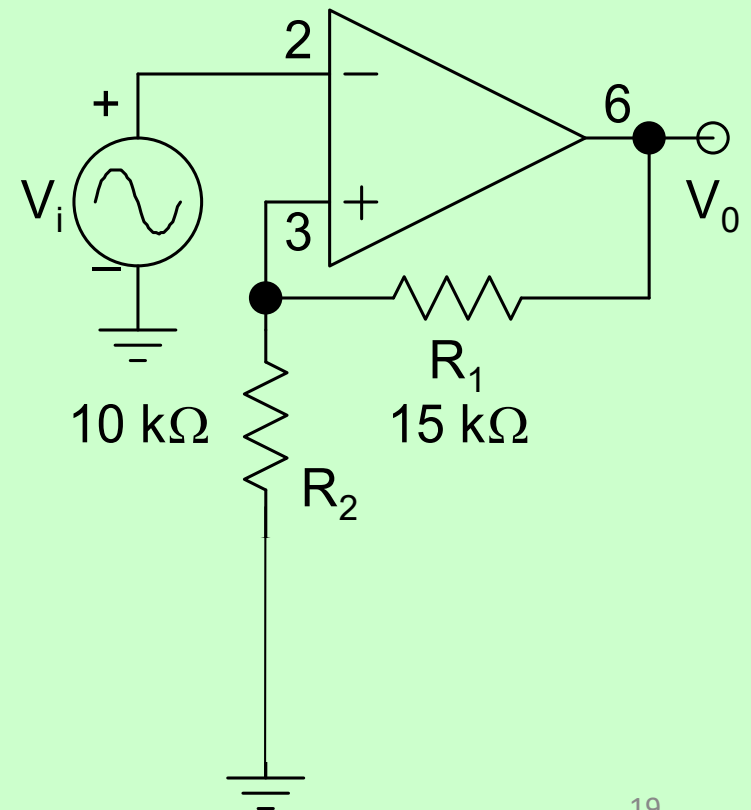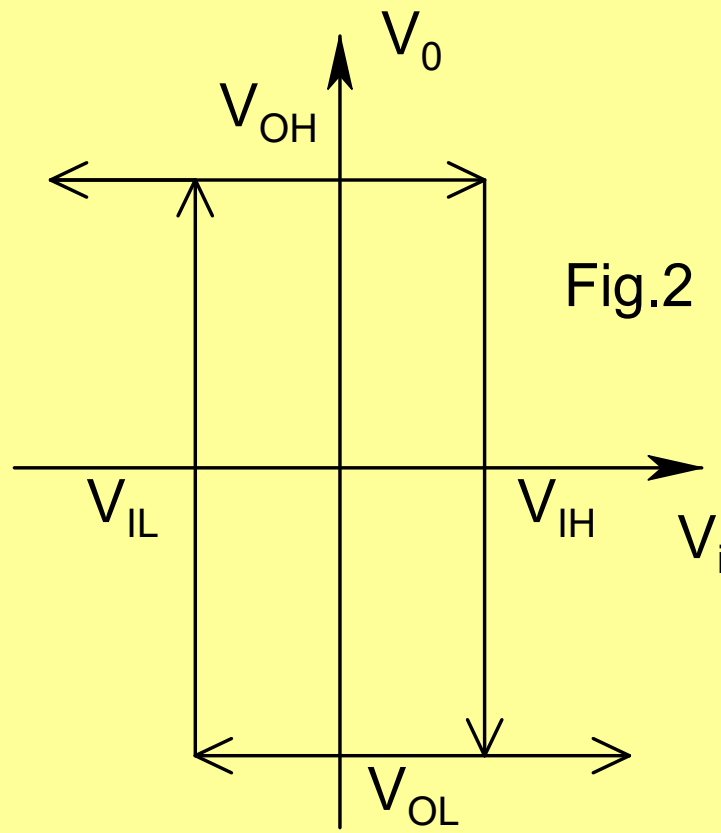

## Bring in a Capacitor

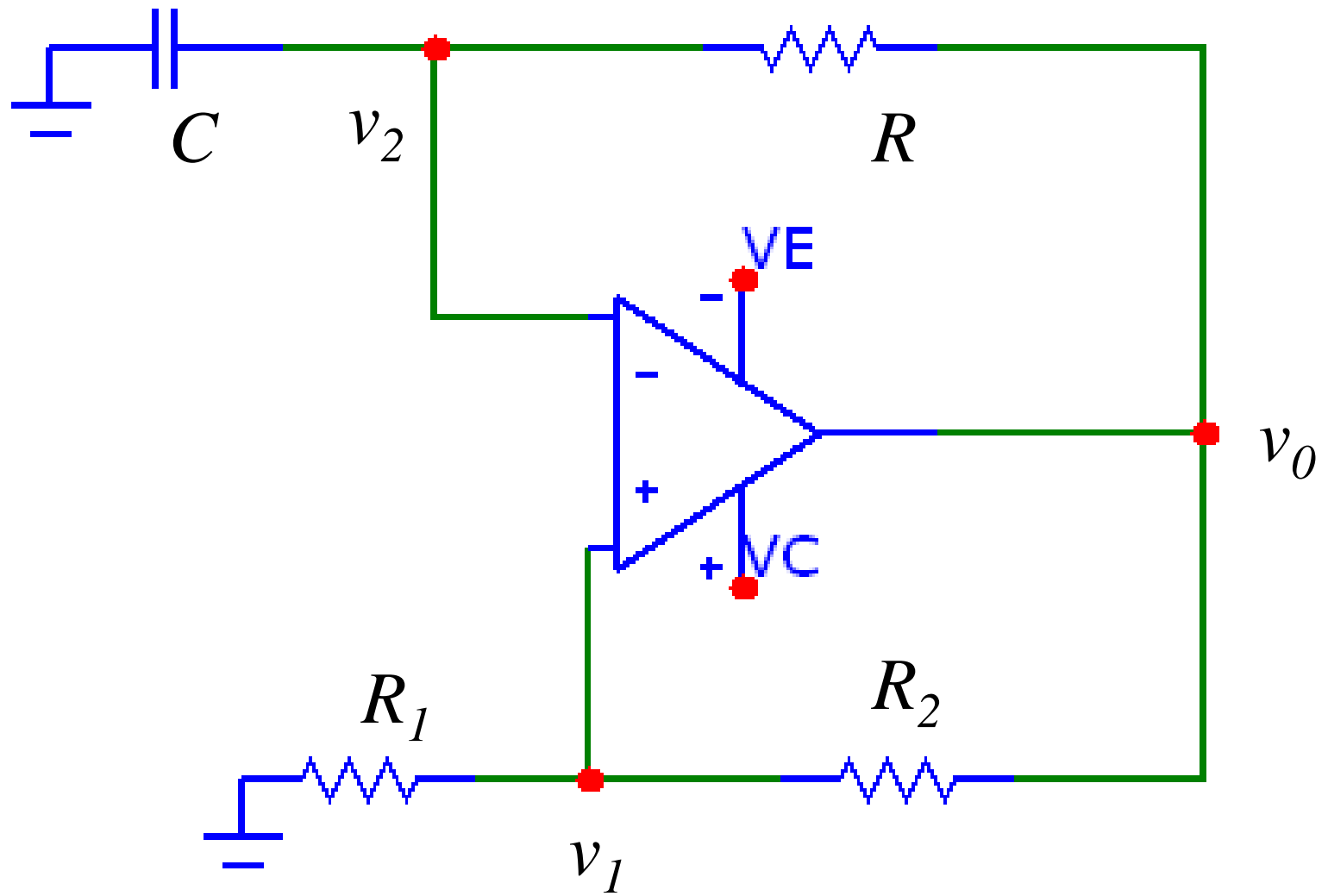


# Square Wave Generator

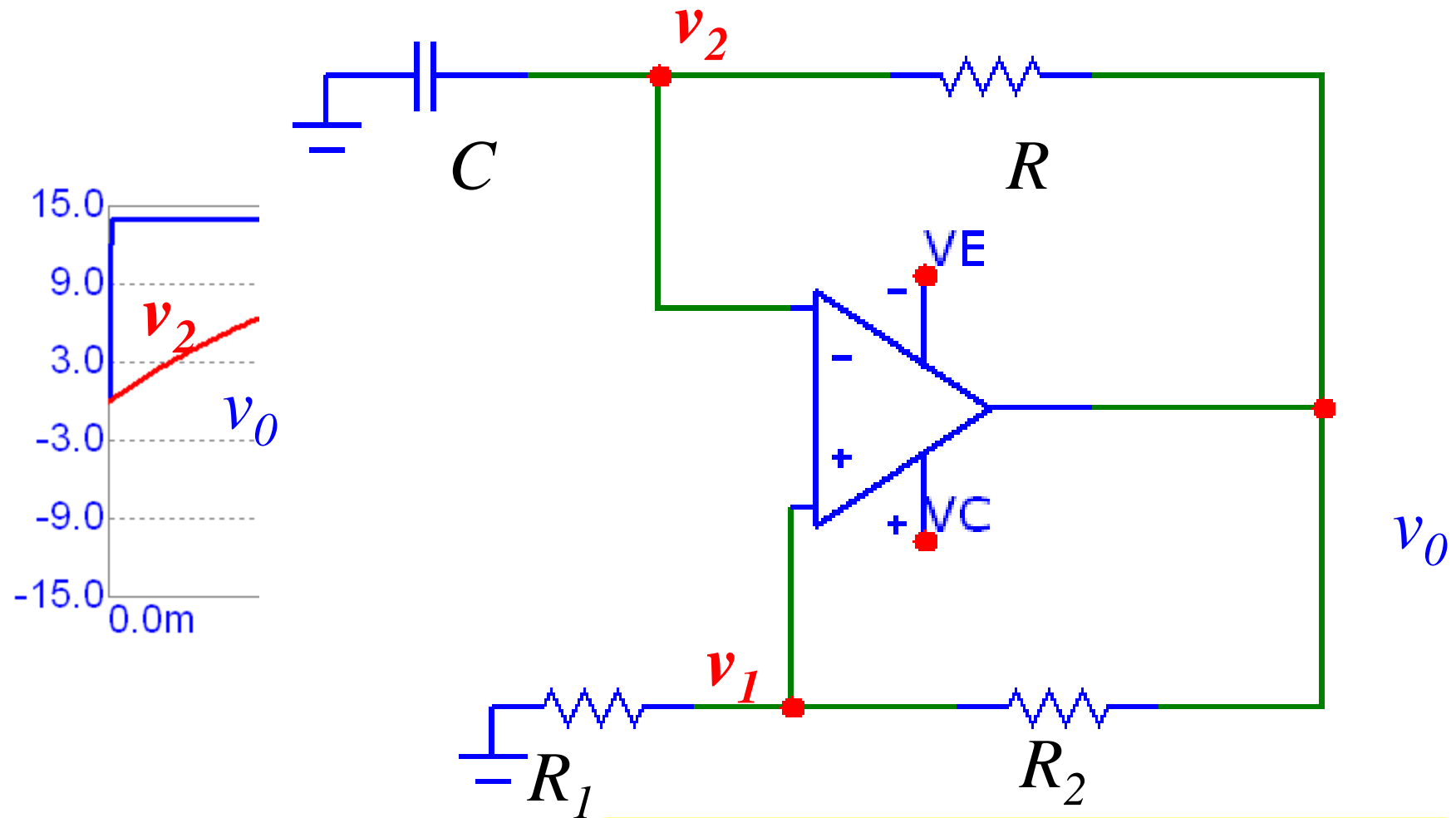


$$v_1 = v_0 \frac{R_1}{R_1 + R_2} = +V_{sat} \frac{R_1}{R_1 + R_2}$$

# Square Wave Generator

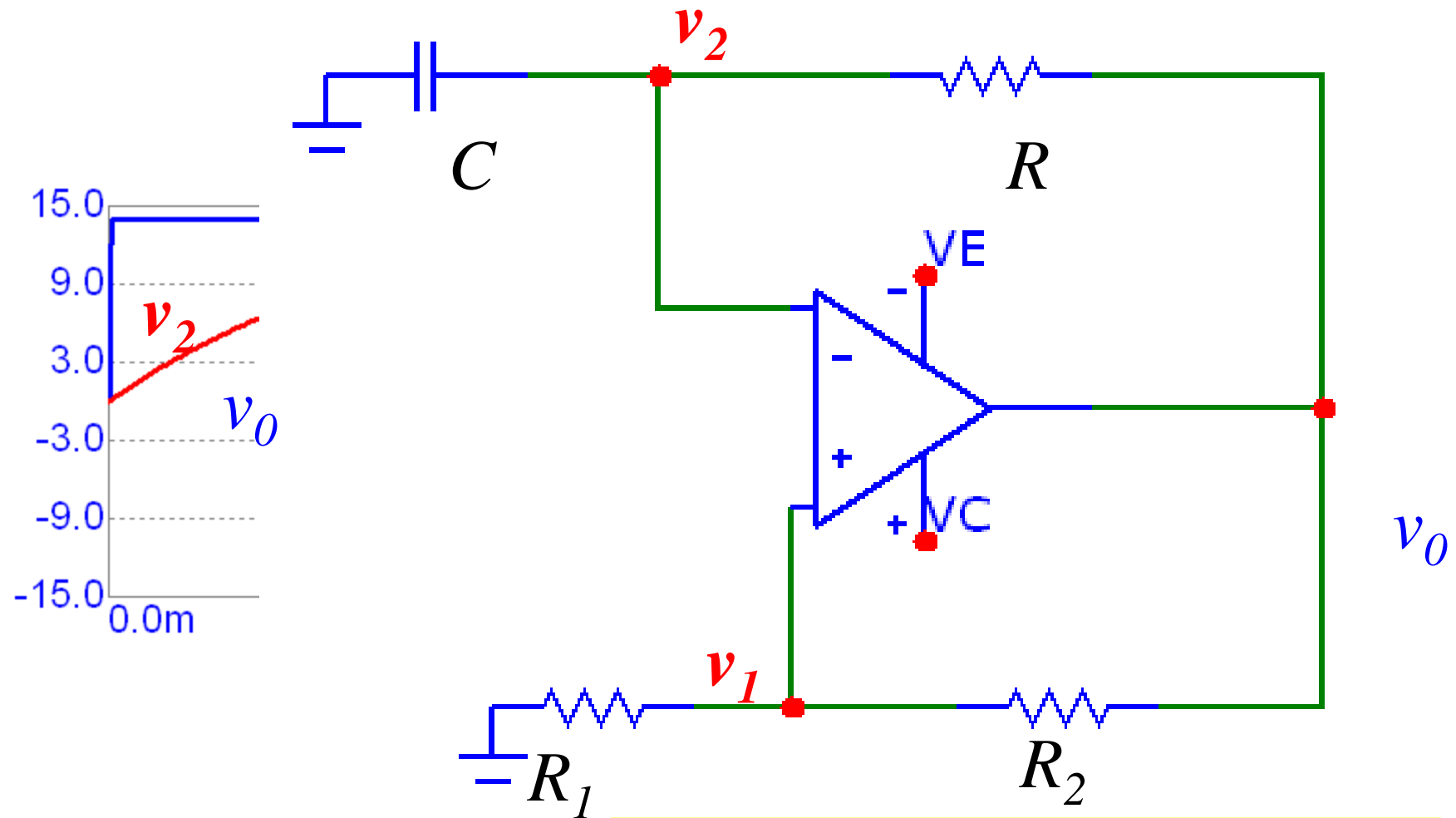

$$v_1 = v_0 \frac{R_1}{R_1 + R_2} = -V_{sat} \frac{R_1}{R_1 + R_2}$$


# Square Wave Generator

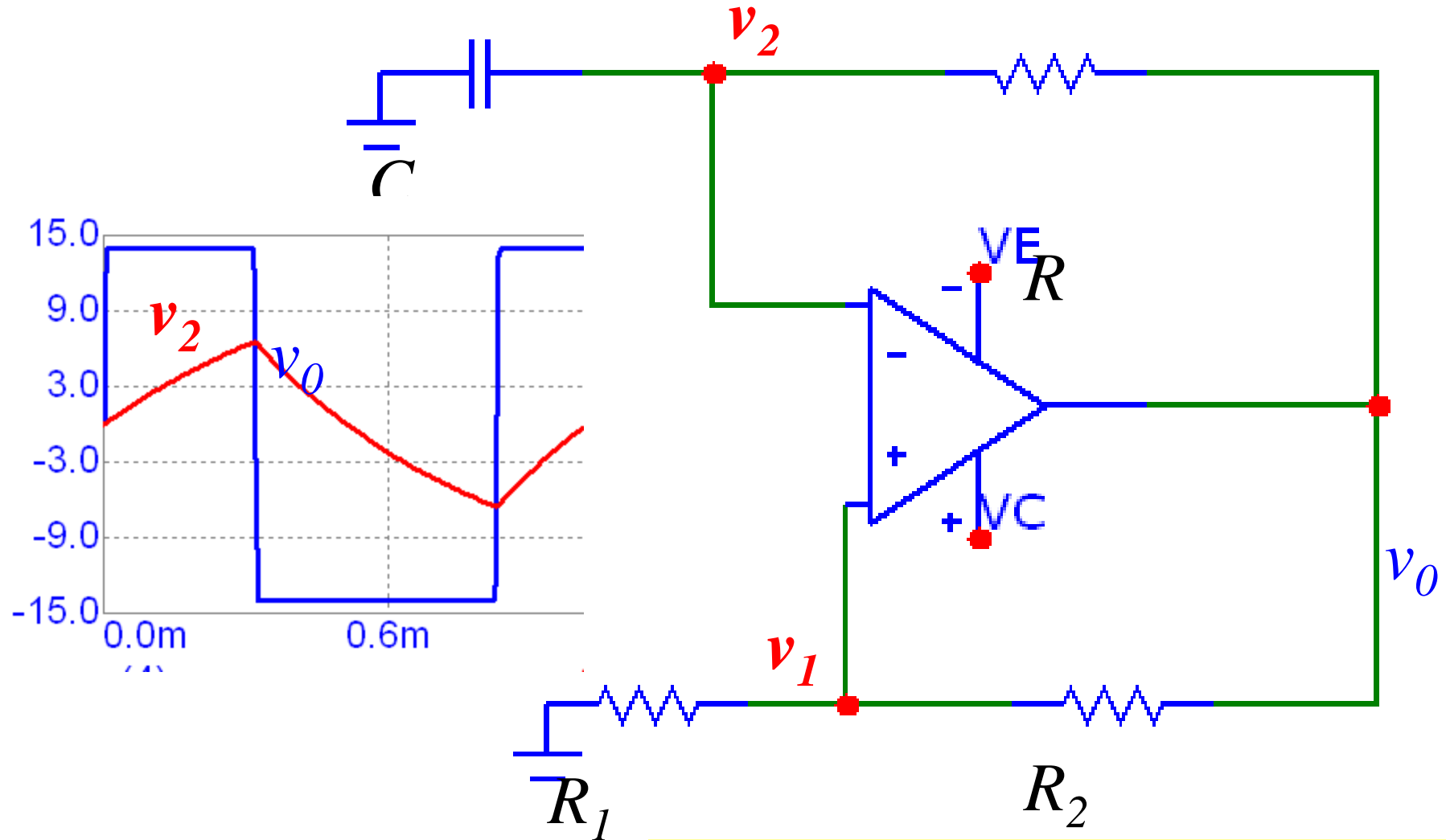

$$v_1 = v_0 \frac{R_1}{R_1 + R_2} = -V_{sat} \frac{R_1}{R_1 + R_2}$$

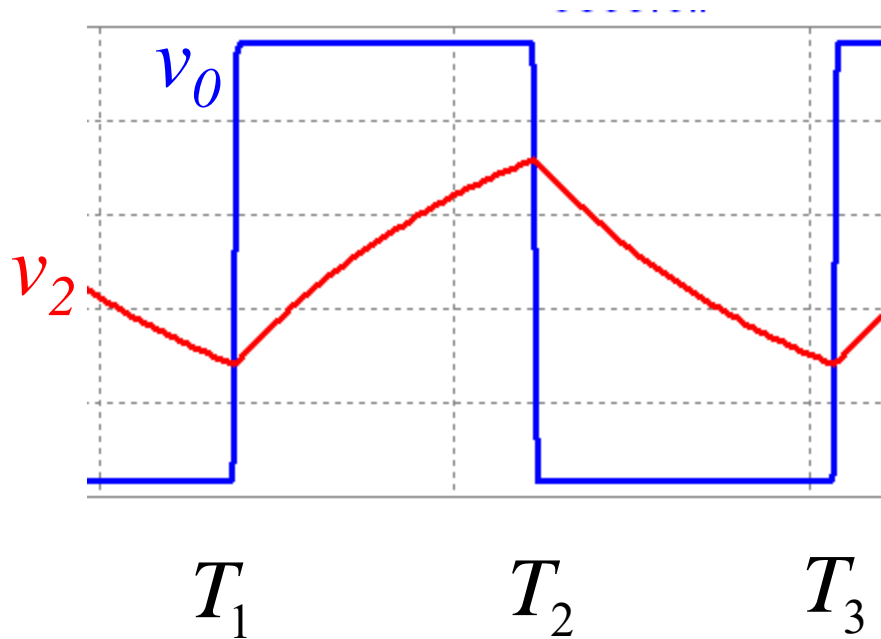
# Square Wave Generator

$$v_C(t) = v_C(\infty) + \{v_C(0^+) - v_C(\infty)\} e^{-\frac{t}{RC}}$$



$$v_2(t) = +V_{sat} - [V_{sat} - v_2(T_1)]e^{-\frac{(t-T_1)}{\tau}}$$

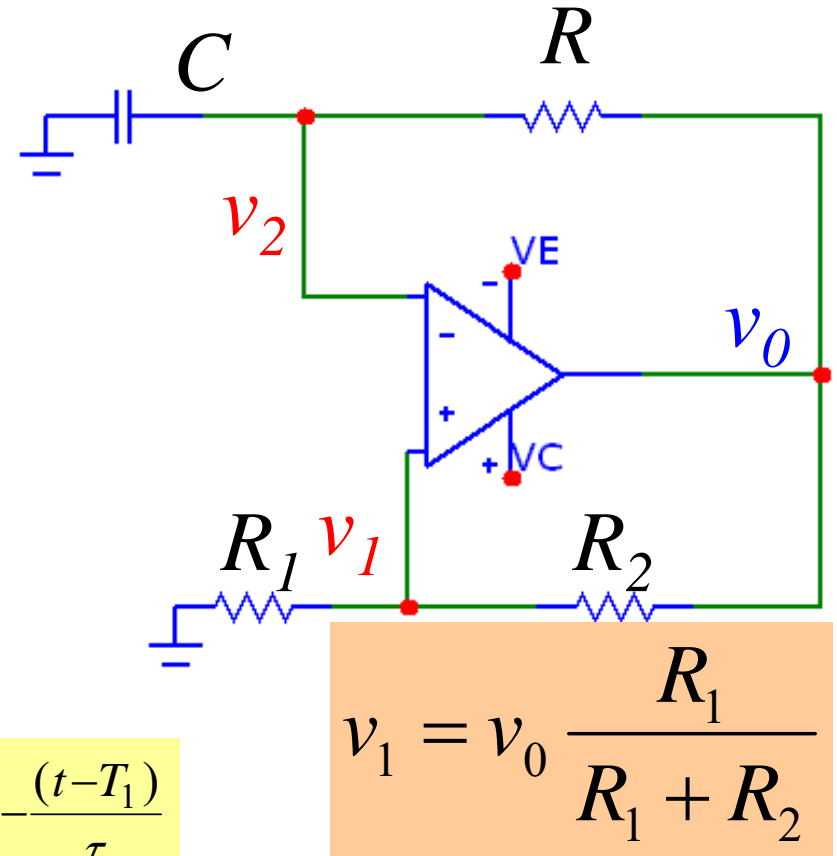
$$v_2(T_2) = +V_{sat} - [V_{sat} - v_2(T_1)]e^{-\frac{(T_2-T_1)}{\tau}}$$



$$v_1 = v_0 \frac{R_1}{R_1 + R_2}$$




# Square Wave Generator

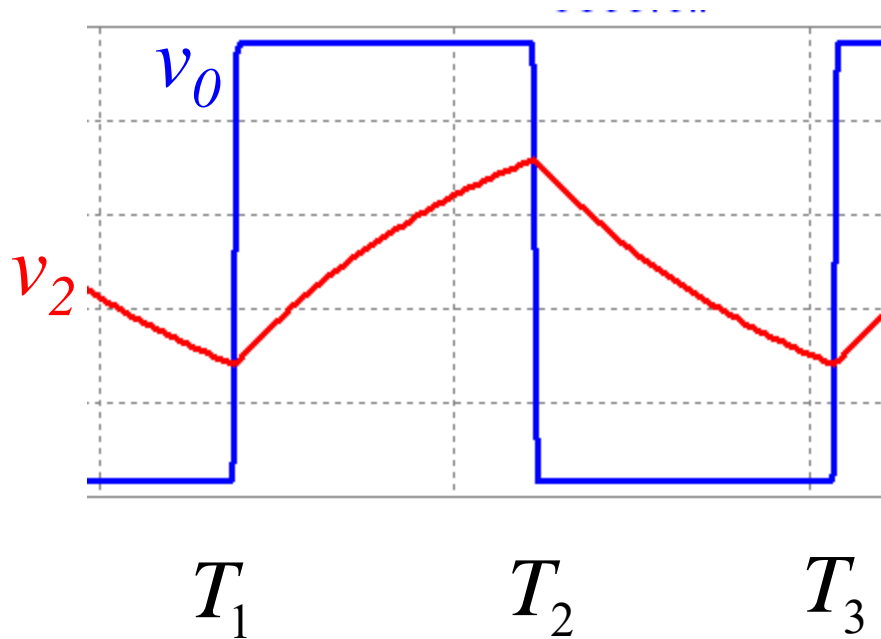

$$v_2(T_2) = +V_{sat} - [V_{sat} - v_2(T_1)]e^{-\frac{(T_2 - T_1)}{\tau}}$$

$$v_2(T_1) = -V_{sat} \frac{R_1}{R_1 + R_2}$$
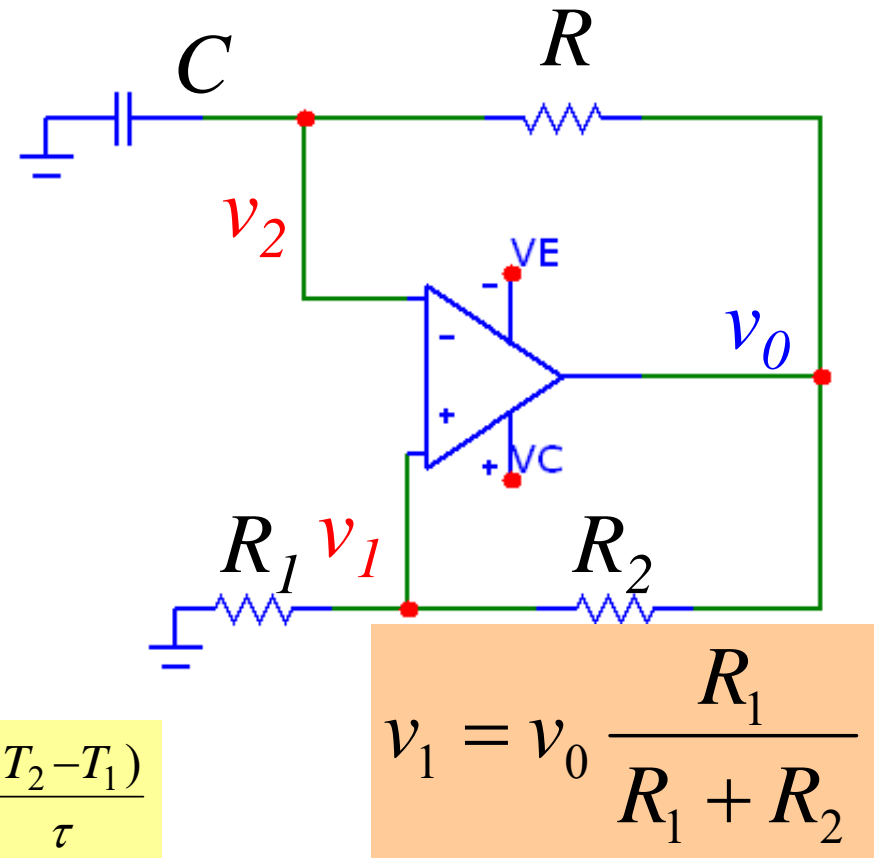
$$v_2(T_2) = +V_{sat} \frac{R_1}{R_1 + R_2}$$



$$v_1 = v_0 \frac{R_1}{R_1 + R_2}$$

# Square Wave Generator

$$T_2 - T_1 = \tau \ln \left[ 1 + 2 \frac{R_1}{R_2} \right]$$

Similarly,

$$T_3 - T_2 = \tau \ln \left[ 1 + 2 \frac{R_1}{R_2} \right]$$

$$T = T_3 - T_1 = 2\tau \ln \left[ 1 + 2 \frac{R_1}{R_2} \right]$$