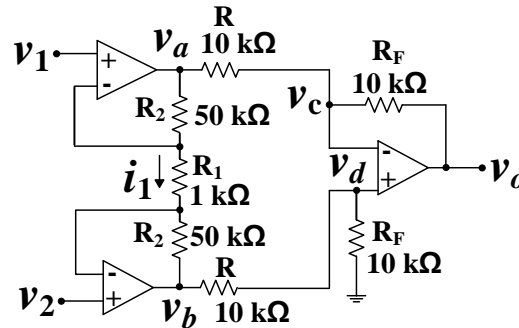
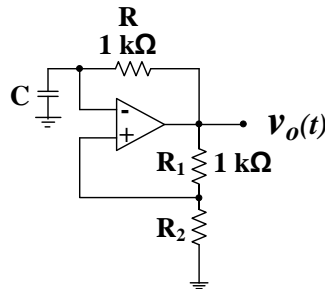


3rd October, 2016**Home Assignment –10**

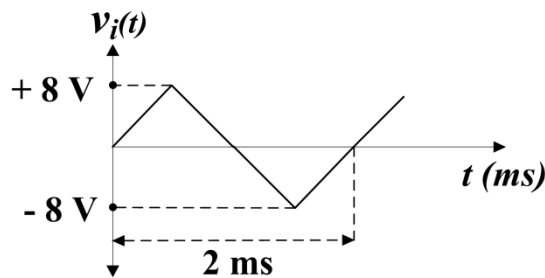
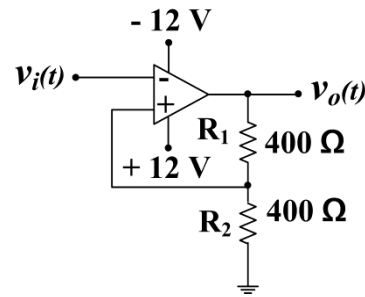
1. An **Instrumentation Amplifier** is shown in **Fig. 1**. If $v_1 = 3 + 0.04 \sin(\omega t)$ and $v_2 = 3 - 0.04 \sin(\omega t)$, find the voltages v_a , v_b , v_c and v_d . Also find the **voltage gain** of this circuit. Assume all op-amps are ideal.

**Fig. 1**

2. A **square wave generator** is shown in **Fig. 2**. If the period of the square wave is $400 \mu\text{s}$ and the capacitor voltage is $8 \text{ V}_{\text{p-p}}$, find 'C' and ' R_2 '. Assume $V_{\text{osat}} = \pm 10 \text{ V}$ and the op-amp is ideal.

**Fig. 2**

3. A triangular wave shown in **Fig. 3(a)** is fed to a **Schmitt trigger** circuit shown in **Fig. 3(b)**. Assuming $V_{\text{osat}} = \pm 12 \text{ V}$, sketch the output voltage $v_o(t)$ and v_o vs v_i with relevant information.

**Fig. 3(a)****Fig. 3(b)**

4. A **difference amplifier** is shown in **Fig. 4**. If $v_o = K (v_2 - v_1)$, determine ' K '. Assume all op-amps are ideal.

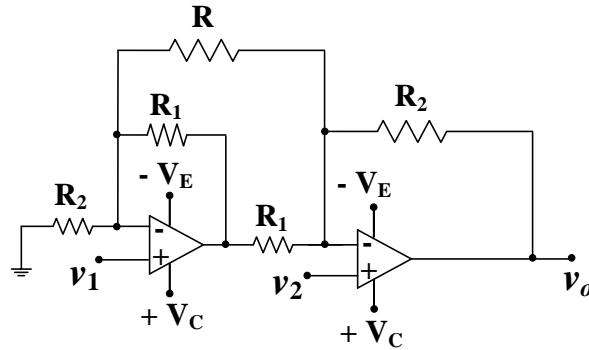


Fig. 4

5. For the ideal op-amp shown in **Fig. 5**, sketch v_o as a function of v_i . Assume that both diodes have cut-in voltages (V_γ) of 0.7 V and Zener voltages (V_Z) of 6 V.


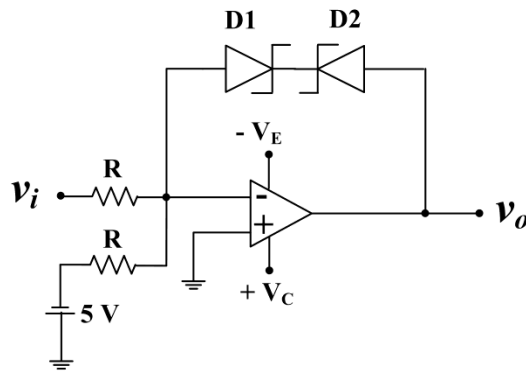


Fig.5

SOLN. ① P-1

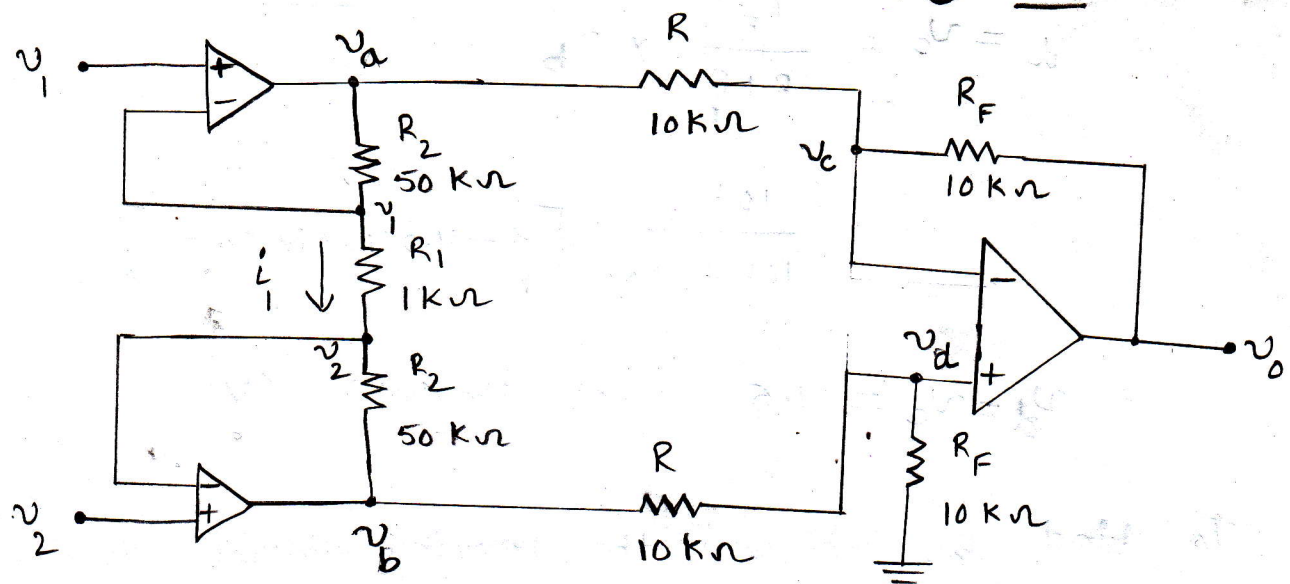

$$v_1 = 3 + 0.04 \sin(\omega t) \quad (\text{V})$$

$$v_2 = 3 - 0.04 \sin(\omega t) \quad (\text{V})$$

from the figure,

$$i_1 = \frac{v_1 - v_2}{R_1} = \frac{3 + 0.04 \sin(\omega t) - 3 + 0.04 \sin(\omega t)}{1\text{ k}} \\ = 0.08 \sin(\omega t) \text{ mA.}$$

Then,

$$v_a = v_1 + i_1 R_2 = 3 + 0.04 \sin(\omega t) + [0.08 \sin(\omega t) \times 10^{-3} \times 50 \times 10^3] \\ = 3 + 0.04 \sin(\omega t) + 4 \sin(\omega t) \\ = 3 + 4.04 \sin(\omega t) \quad (\text{V})$$


$$v_b = v_2 - i_1 R_2 = 3 - 0.04 \sin(\omega t) - [0.08 \times 10^{-3} \sin(\omega t) \times 50 \times 10^3] \\ = 3 - 0.04 \sin(\omega t) - 4 \sin(\omega t) \\ = 3 - 4.04 \sin(\omega t) \quad (\text{V})$$

$$v_d = v_c = \frac{R_F}{R + R_F} \times v_b$$

$$= \frac{10k}{10k + 10k} [3 - 4.04 \sin(\omega t)]$$

$$\Rightarrow v_d = v_c = 1.5 - 2.02 \sin(\omega t) \text{ (V)}$$

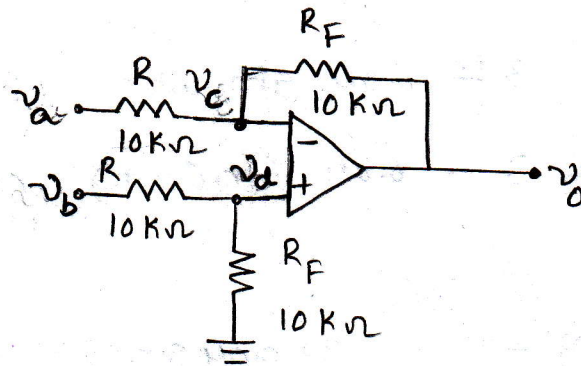To find v_o , we use the following deduced circuit.



$$v_o = v_a \left(-\frac{R_F}{R} \right) + v_b \times \frac{R_F}{R_F + R} \left(1 + \frac{R_F}{R} \right)$$

$$= \frac{R_F}{R} (v_b - v_a)$$

For $R_F = R = 10k\Omega$; $v_o = v_b - v_a$

$$= 3 - 4.04 \sin(\omega t) - 3 - 4.04 \sin(\omega t)$$

$$\Rightarrow v_o = -8.08 \sin(\omega t) \text{ (V)}$$

Now,

$$\text{Voltage gain, } A_{dm} = \frac{v_o}{v_2 - v_1} = \frac{-8.08 \sin(\omega t)}{3 - 4.04 \sin(\omega t) - 3 - 4.04 \sin(\omega t)}$$

$$= \frac{-8.08}{-8.08} = 101$$


$$\therefore v_a = 3 + 4.04 \sin(\omega t) \text{ (V)}$$

$$v_b = 3 - 4.04 \sin(\omega t) \text{ (V)}$$


$$v_c = v_d = 1.5 - 2.02 \sin(\omega t) \text{ (V)}$$

$$\text{Voltage gain, } A_{dm} = 101$$

→ Ans.

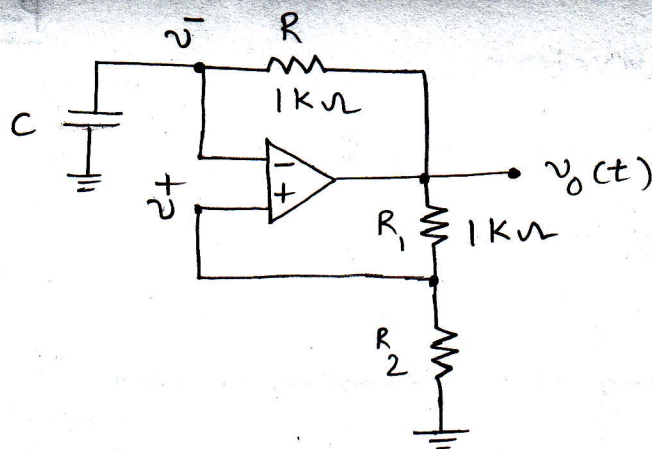

$$V_{o\text{sat}} = 10\text{V}$$

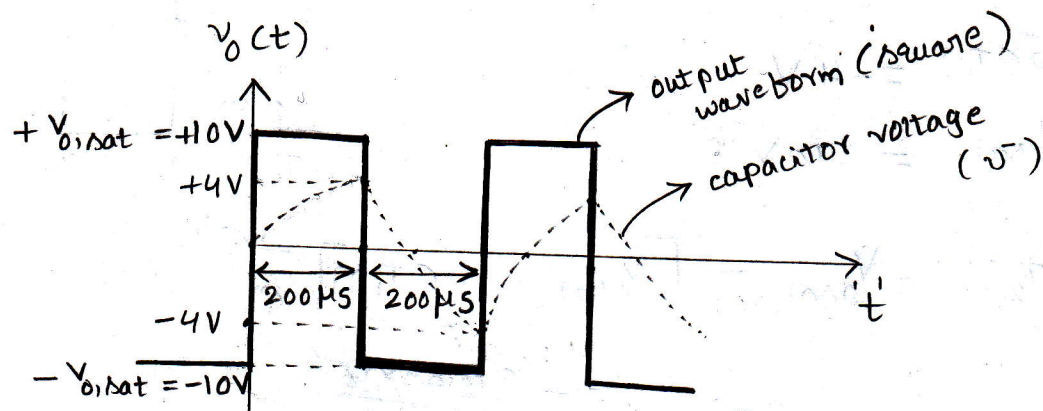

when $v_o = +10\text{V} = (V_{o\text{sat}})$

$$v^+ = \frac{R_2}{R_1 + R_2} \times v_o = \frac{10 R_2}{R_2 + 1000}$$

Capacitor will charge till v^- gets equal to v^+ .

From the waveform given above, we have

$$v^- = v^+ = 4\text{V} \quad \text{when } v_o = +V_{\text{sat}} = +10\text{V}$$

$$\Rightarrow 4 = \frac{10 R_2}{R_2 + 1000}$$

$$\Rightarrow 4 R_2 + 4000 = 10 R_2$$

$$\Rightarrow 6 R_2 = 4000$$

$$\Rightarrow R_2 = \frac{4000}{6} = \frac{2}{3} \text{ k}\Omega$$

And also from the waveform,

capacitor charges for the period of $200 \mu s$ and discharges for the period of $200 \mu s$

let's consider during the charging period

$$\bar{v}(T_1) = -4V$$

$$V_{osat} = 10V$$

then

$$\bar{v}(T_2) = +V_{osat} - [V_{osat} - \bar{v}(T_1)] e^{-\frac{(T_2 - T_1)}{RC}}$$

$$= 10 - [10 - (-4)] e^{-\frac{200 \times 10^{-6}}{RC}}$$

$$= 10 - 14 e^{-(200 \times 10^{-6})/RC}$$

from the above figure $\bar{v}(T_2) = +4V$

$$\Rightarrow 4 = 10 - 14 e^{-\frac{200 \times 10^{-6}}{RC}}$$


$$\Rightarrow 14 e^{-\frac{200 \times 10^{-6}}{1000 \times C}} = 10 - 4 = 6$$



$$\Rightarrow e^{-\frac{2 \times 10^{-7}}{C}} = \frac{6}{14} \Rightarrow -\frac{2 \times 10^{-7}}{C} = \ln \frac{6}{14} = -0.8473$$

$$\Rightarrow C = \frac{-2 \times 10^{-7}}{-0.8473} F = 0.236 \times 10^{-6} F = 0.236 \mu F$$

$$\therefore R_2 = \frac{2}{3} k\Omega$$

$$C = 0.236 \mu F$$

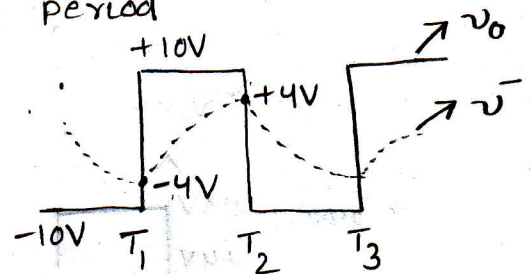

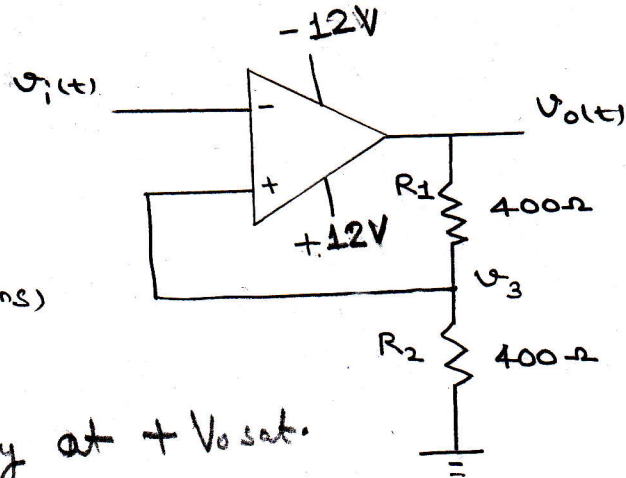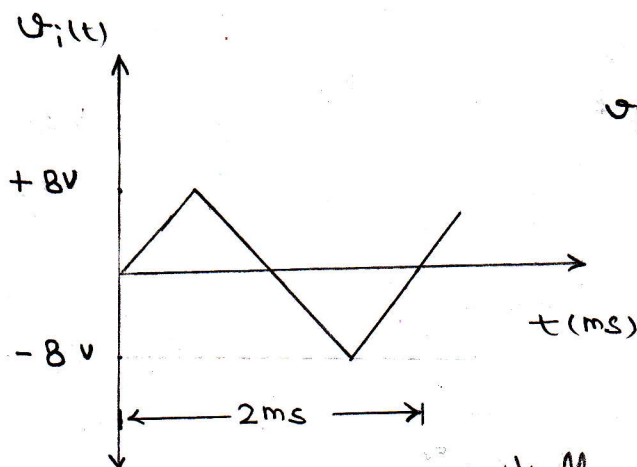



Considering op-amp is initially at $+V_{sat}$.
 $V_{osat} = +12V$


$$\text{So } V_3 = 12 \times \frac{400}{400+400} = 6V$$

Now if V_i goes more than $6V$, op-amp will switch to $-V_{sat} (= -12V)$

$$V_3 = -12 \times \frac{400}{400+400} = -6V$$

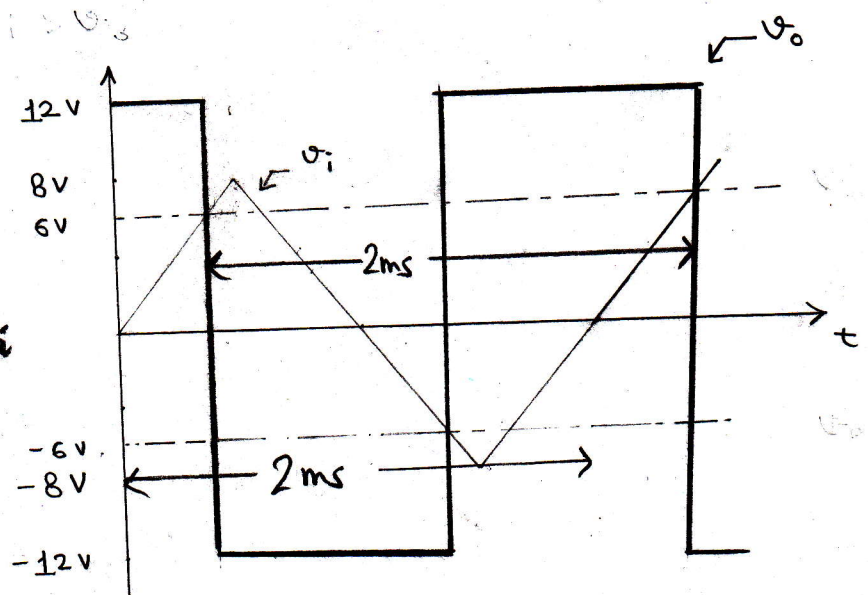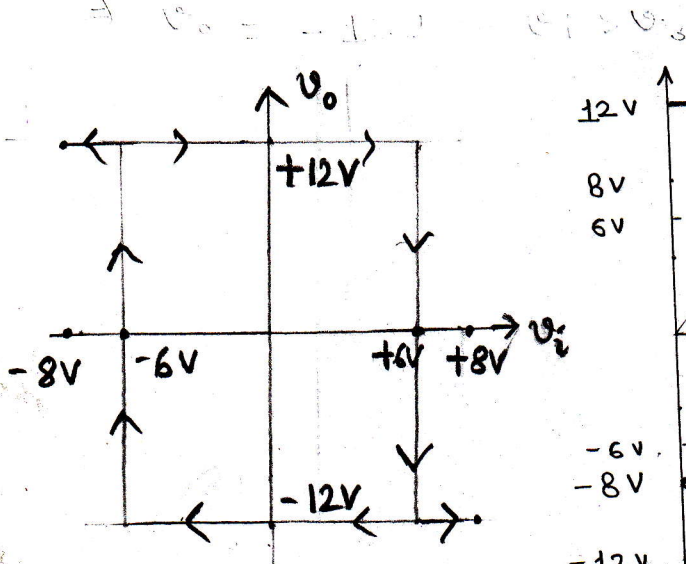Further, if V_i falls below $-6V$, op-amp will again switch to $+V_{sat} (= +12V)$



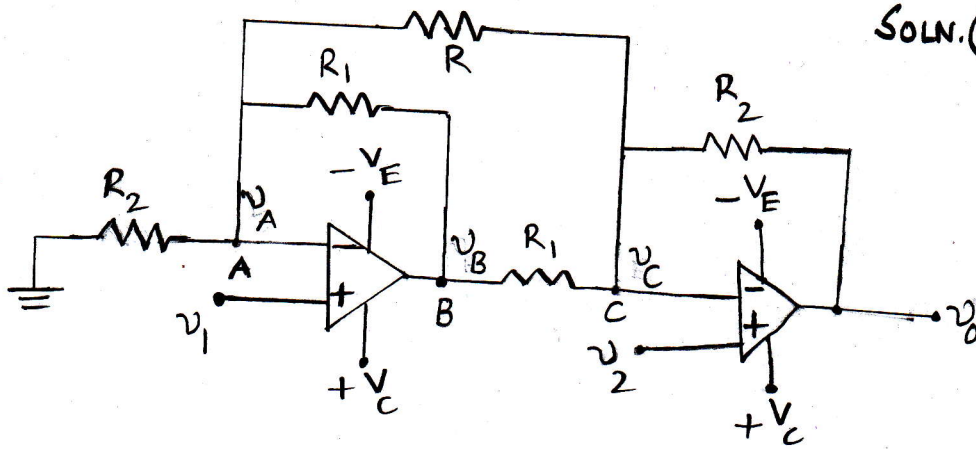

Given all the op-amps are ideal. So $v_A = v_1$ and $v_C = v_2$
 Apply 'KCL' at node 'A',

$$\frac{v_1}{R_2} + \frac{v_1 - v_B}{R_1} + \frac{v_1 - v_2}{R} = 0$$

$$\Rightarrow \frac{v_B}{R_1} = -\frac{v_2}{R} + v_1 \left(\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right) \quad \text{--- ①}$$

Apply 'KCL' at node 'C',

$$\frac{v_2 - v_B}{R_1} + \frac{v_2 - v_1}{R} + \frac{v_2 - v_0}{R_2} = 0$$

$$\Rightarrow \frac{v_0}{R_2} = v_2 \left(\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{v_1}{R} - \frac{v_B}{R_1}$$

$$= v_2 \left(\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{v_1}{R} + \frac{v_2}{R} - v_1 \left(\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$


[∵ From ①]

$$\Rightarrow \frac{v_0}{R_2} = v_2 \left(\frac{2}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right) - v_1 \left(\frac{2}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow v_0 = R_2 \left(\frac{2}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right) (v_2 - v_1)$$

$$= K (v_2 - v_1)$$
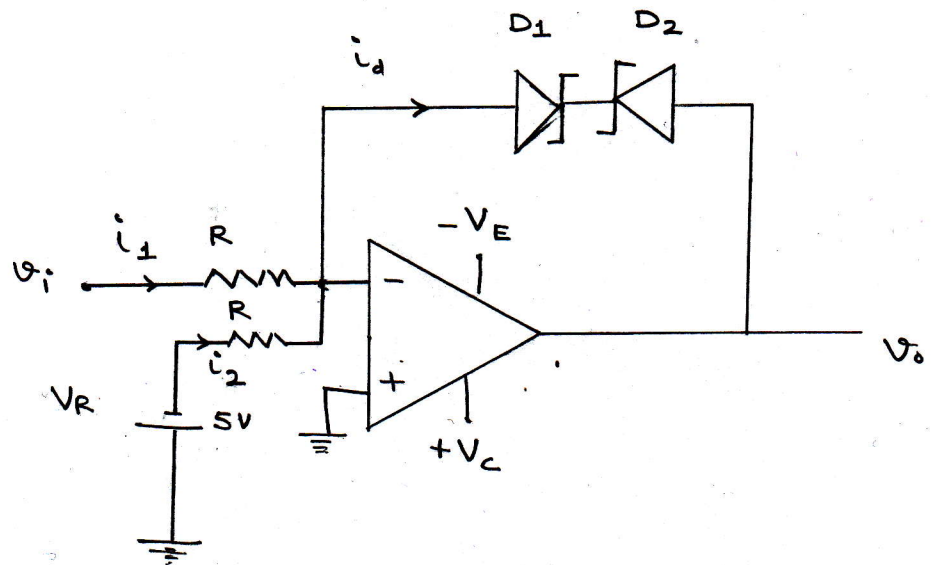
$$\therefore K = R_2 \left(\frac{2}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$



$$\Rightarrow \therefore i_d = i_1 + i_2$$

$$\Rightarrow i_d = \frac{V_i}{R} + \frac{V_R}{R} \quad \Rightarrow \quad i_d = \frac{(V_i - 5)}{R} \quad \left(\because i_1 = \frac{V_i}{R} \text{ and } V_R = -5V. \right.$$

$$\left. \therefore i_2 = -\frac{5}{R} \right)$$

$\Rightarrow i_d$ will be positive for $V_i > 5V$.

Otherwise i_d will remain negative.

$$\Rightarrow \text{if } V_i > 5V; \quad V_o = -(6 + 0.7) = -6.7V$$

(D_1 is forward biased & D_2 is reverse biased)

$$V_o = -(V_2 + V_2)$$

$$V_i < 5V; \quad V_o = 6 + 0.7 = 6.7V$$

(D_2 is forward biased & D_1 is reverse biased)

$$V_o = (V_2 + V_2)$$

