

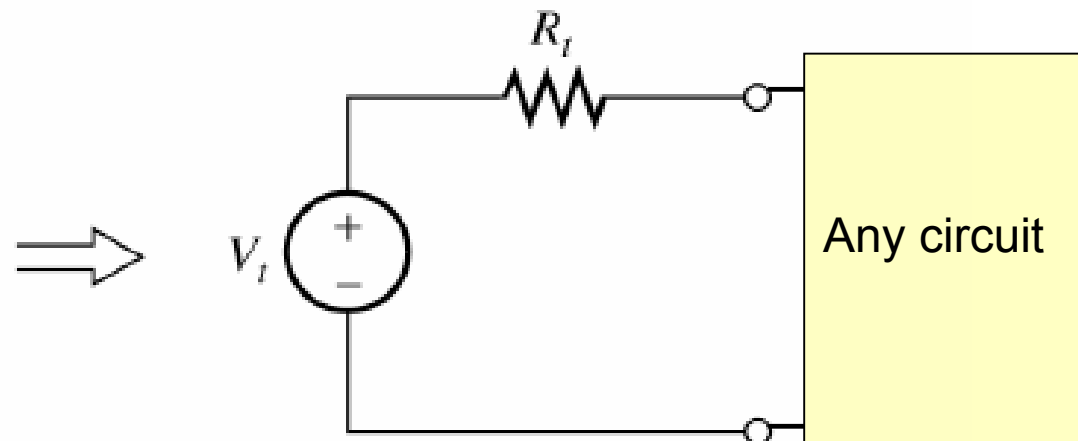
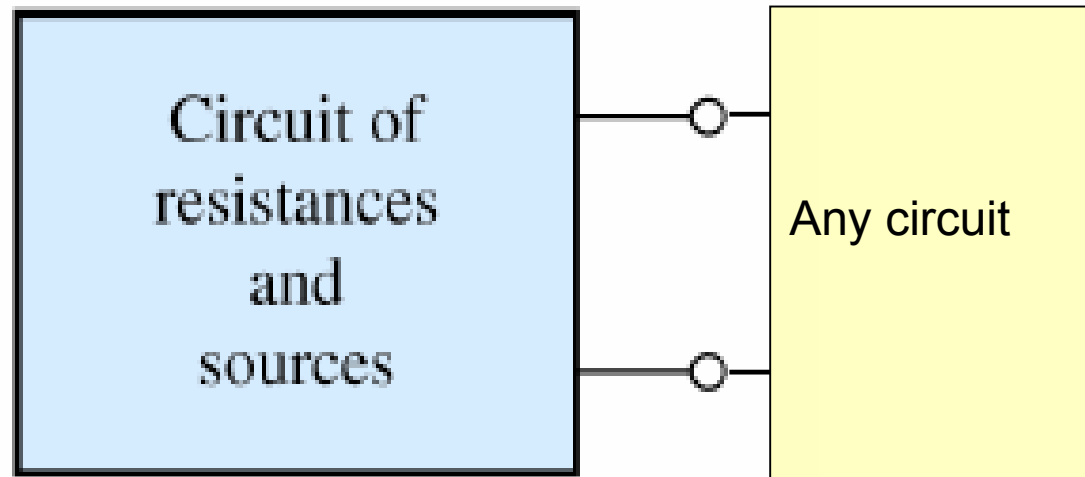


Thévenin Equivalent Circuits






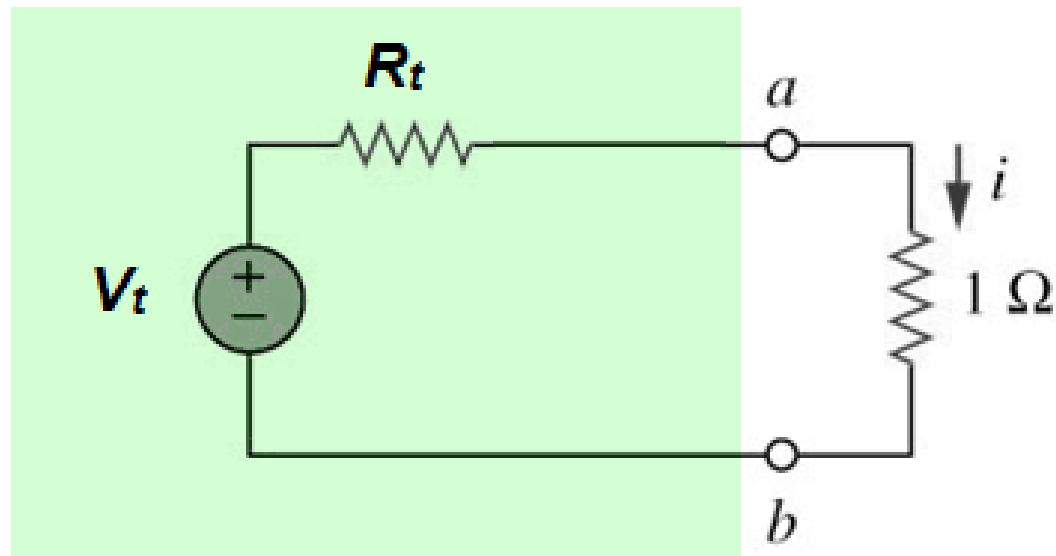


Thévenin equivalent
circuit


Thévenin Equivalent Circuits

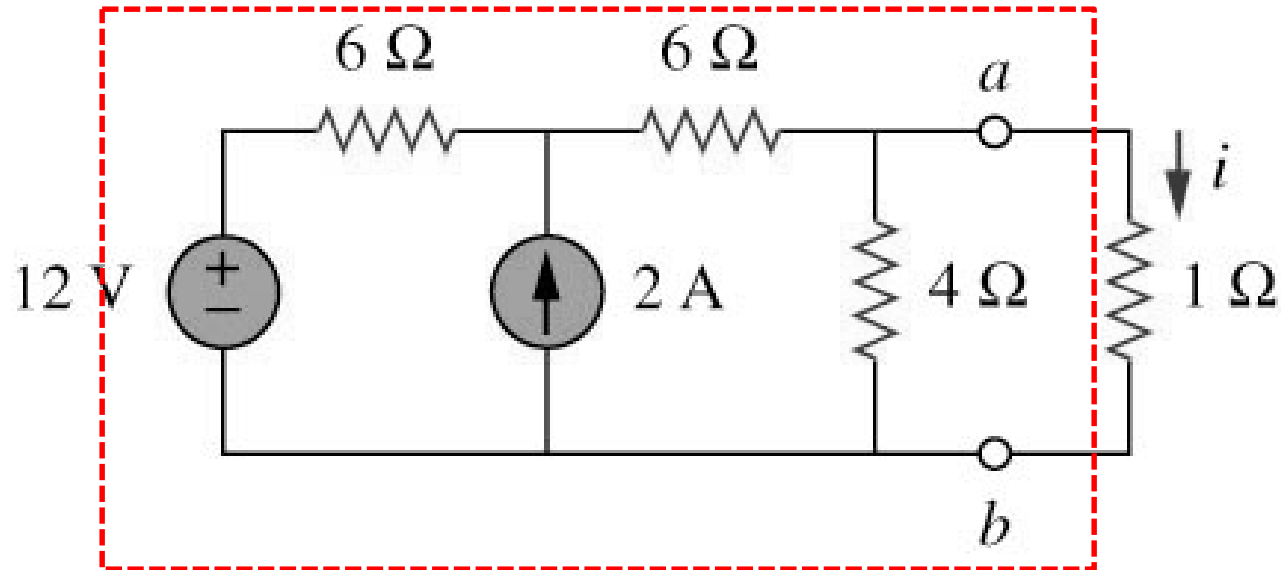

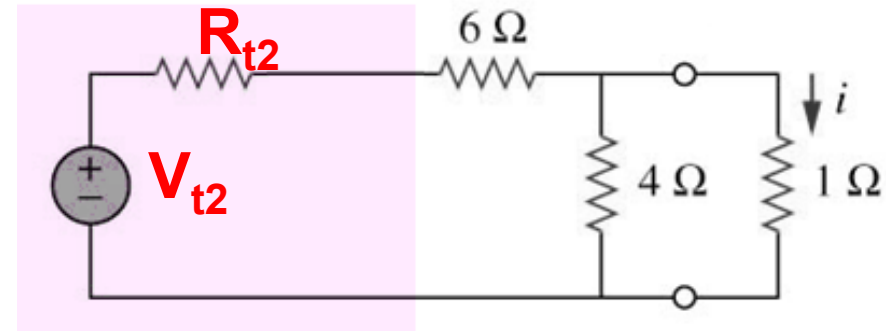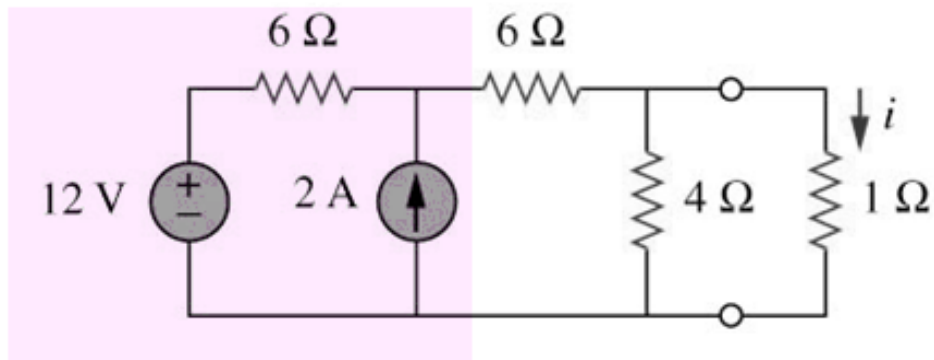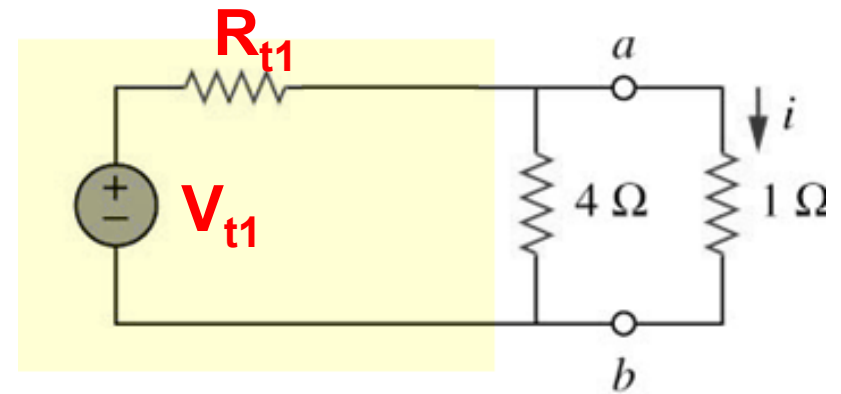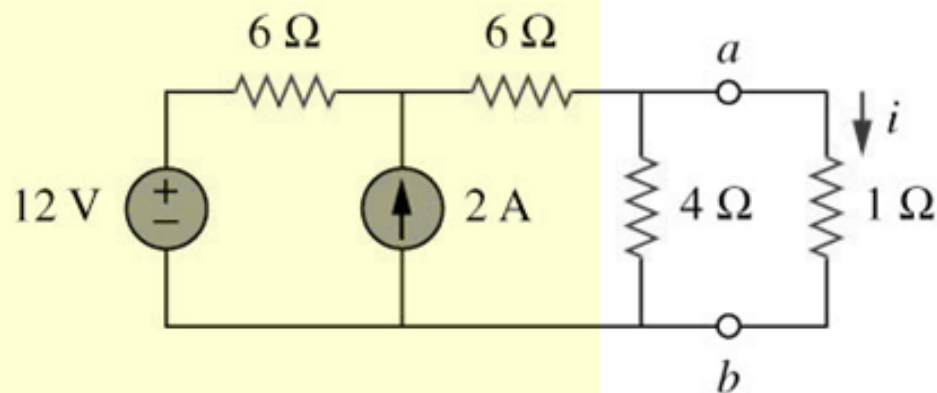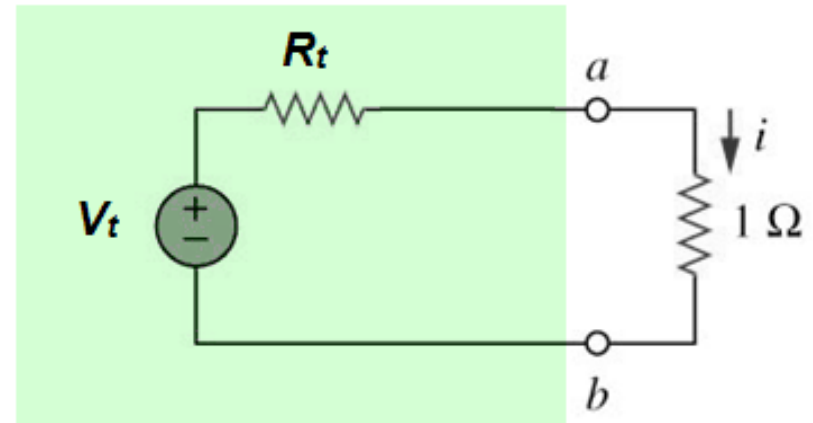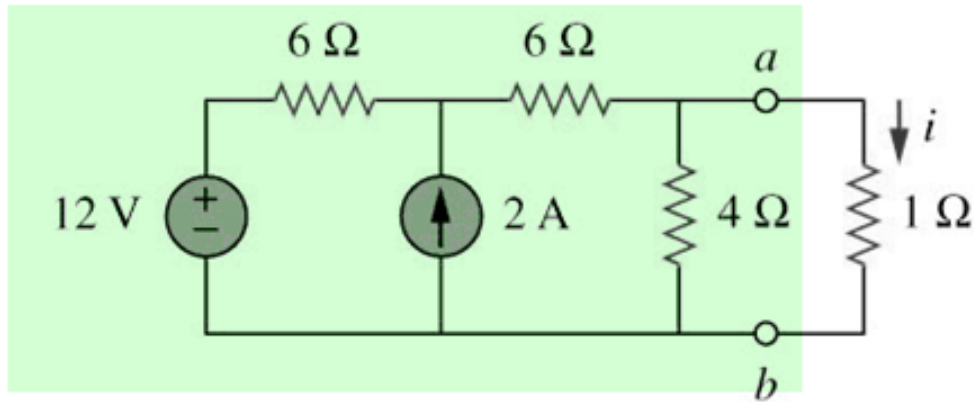
We can apply Thevenin's theorem to any part of the circuit




Thévenin Equivalent Circuits

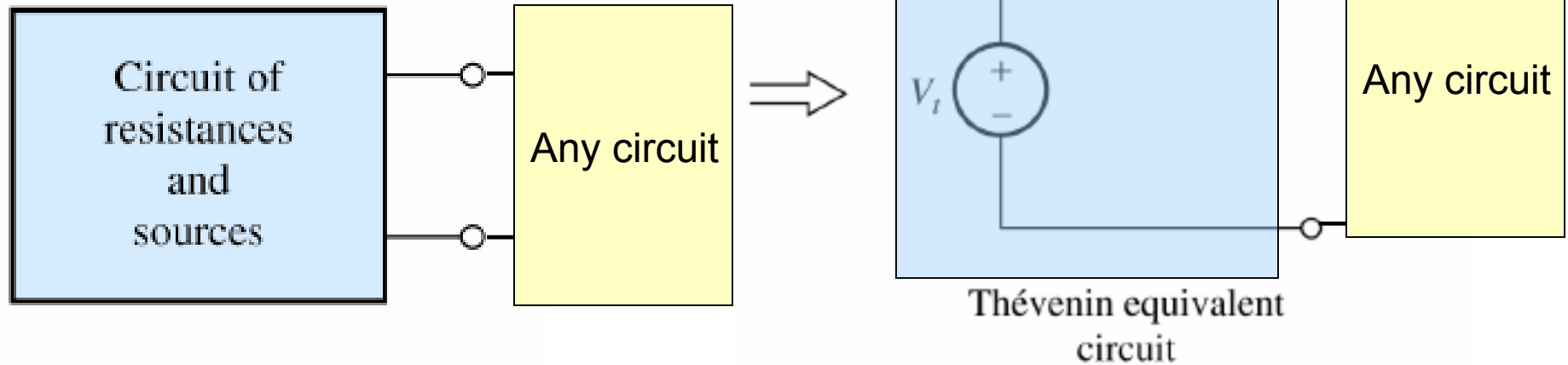


What is V_t ?

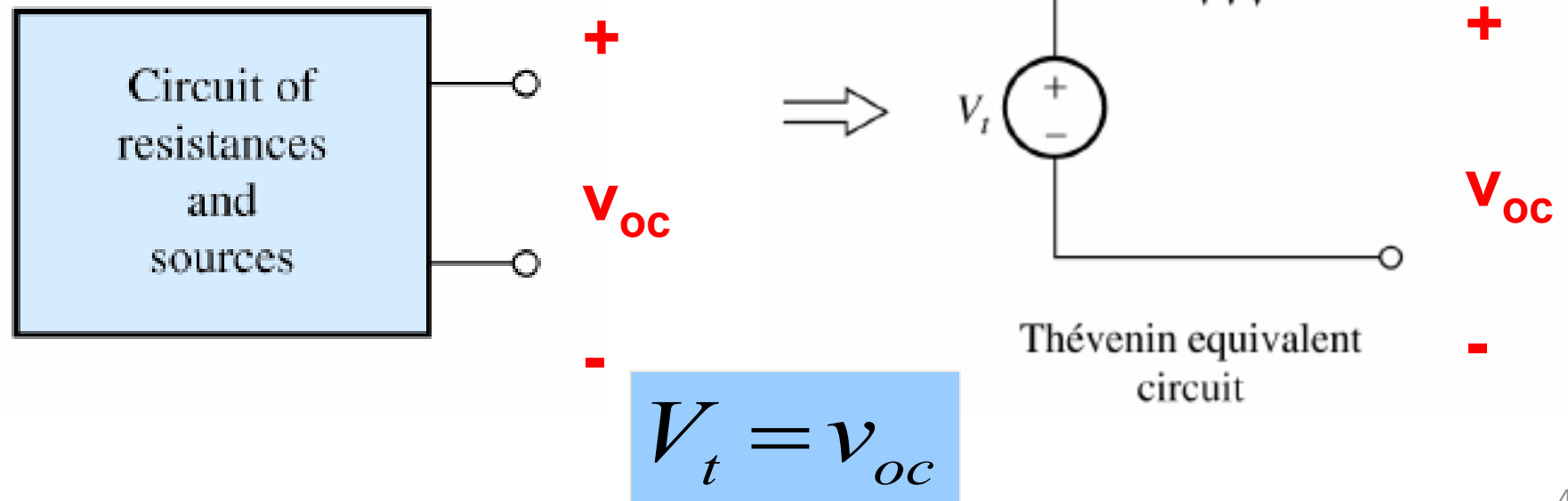


Thévenin Equivalent Circuits

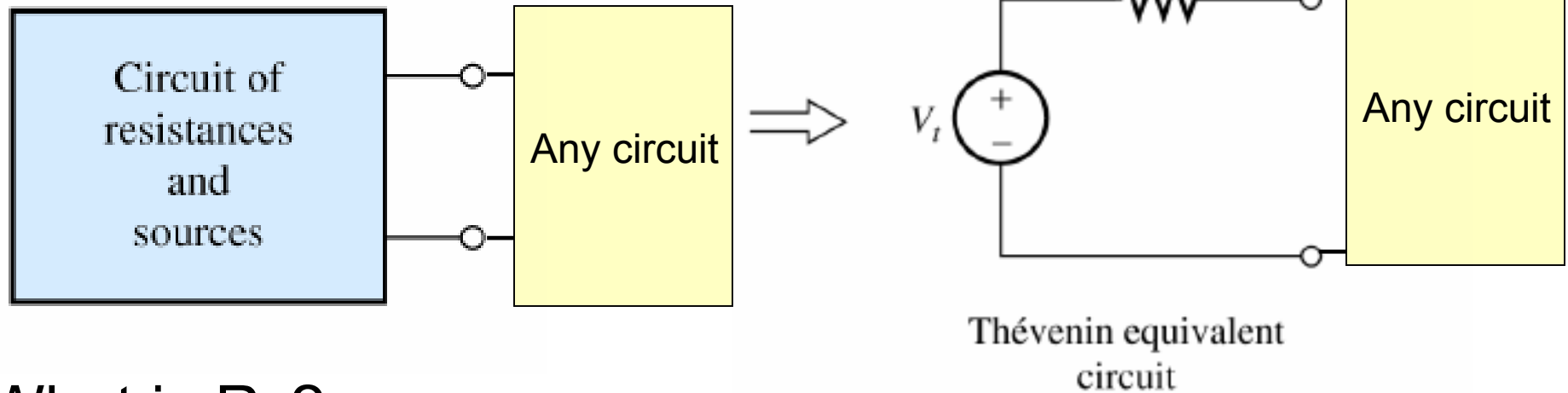

What is R_t ?

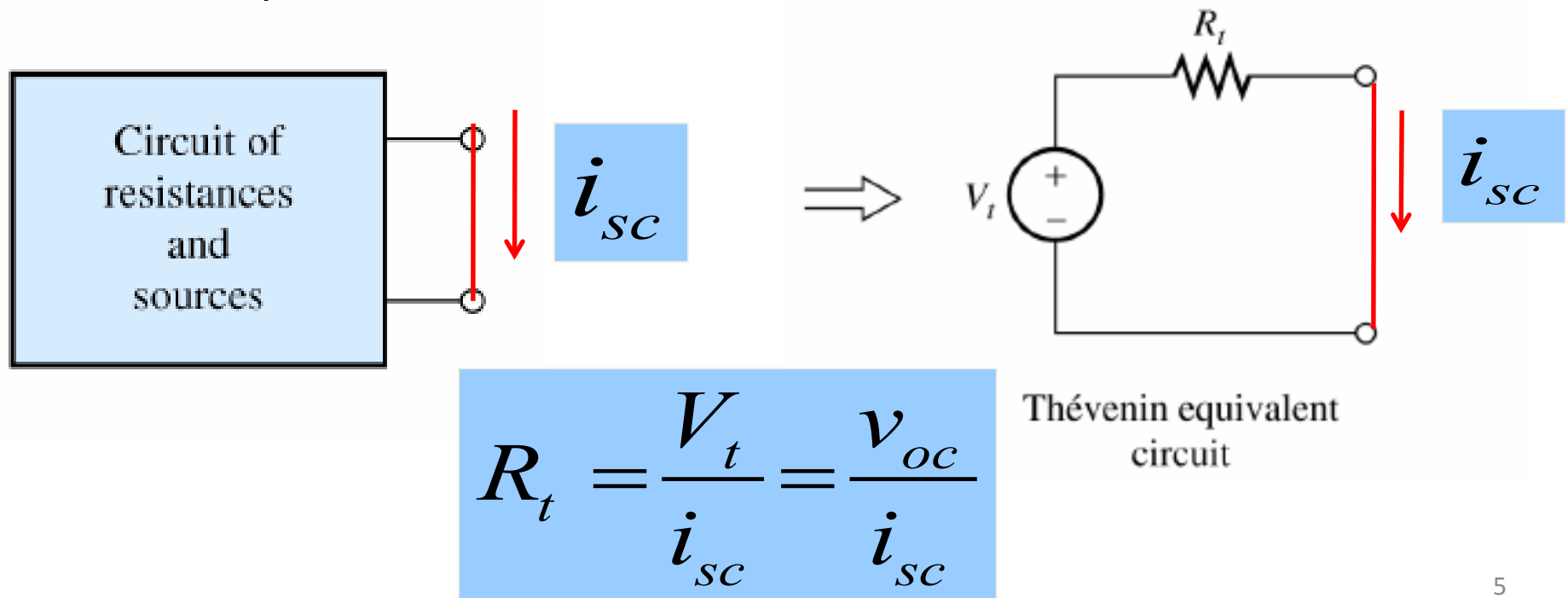


Examples

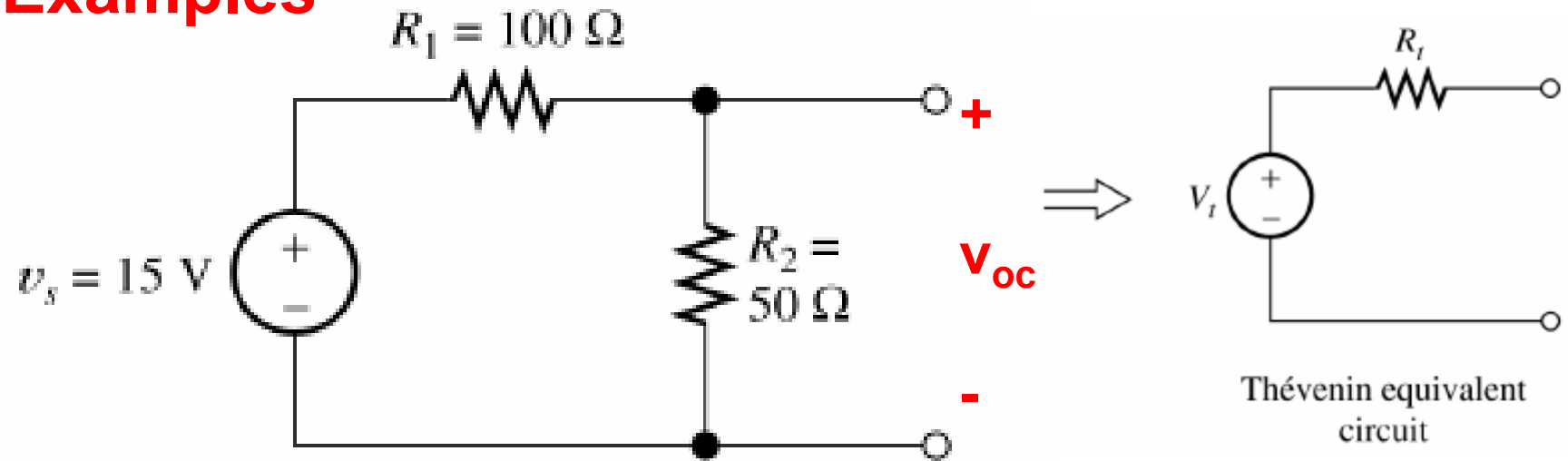


$$V_t = v_{oc}$$
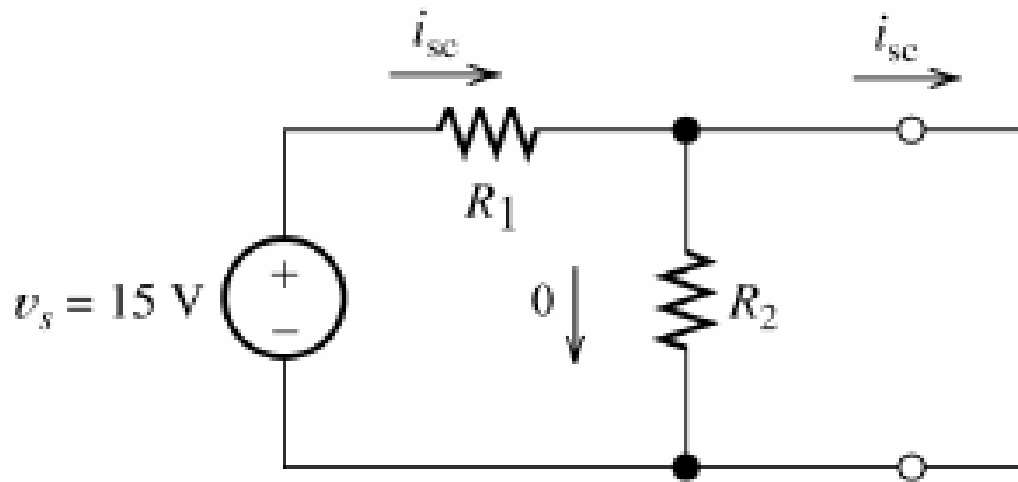
$$V_t = \frac{R_2}{R_2 + R_1} \times 15 = 5$$




$$i_{sc} = \frac{v_s}{R_1} = 0.15 \text{ A}$$
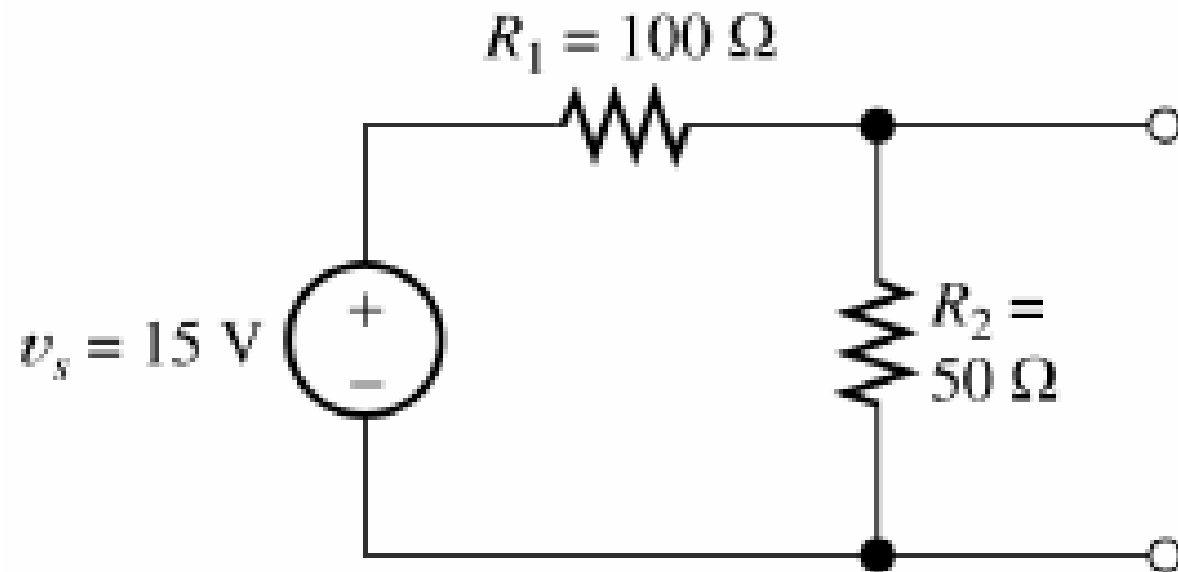
$$R_t = \frac{v_{oc}}{i_{sc}} = 33.3 \Omega$$




$$V_t = 5$$


$$R_t = 33.3\ \Omega$$

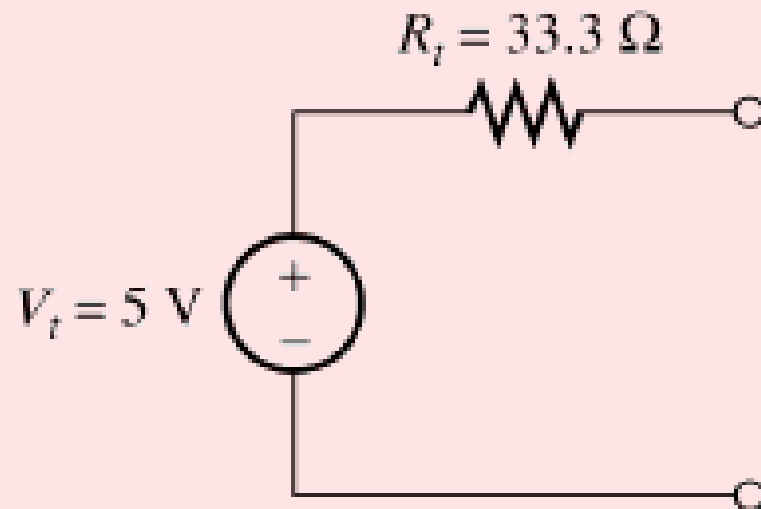

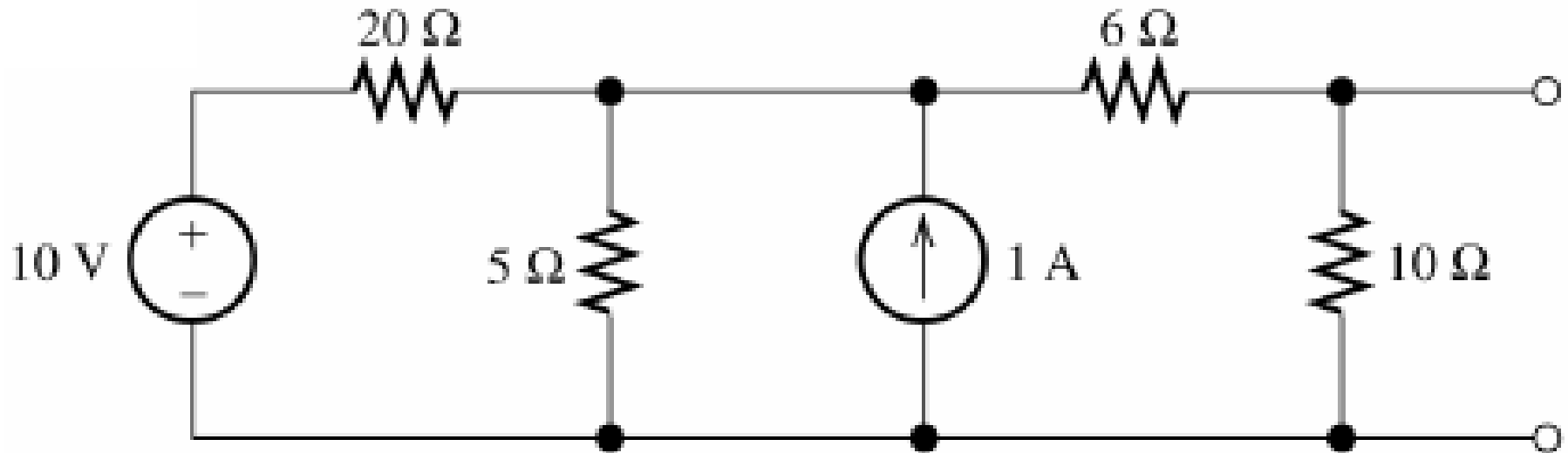
Currents and voltages in the circuit are only due to Independent Sources




Finding the Thévenin Resistance Directly

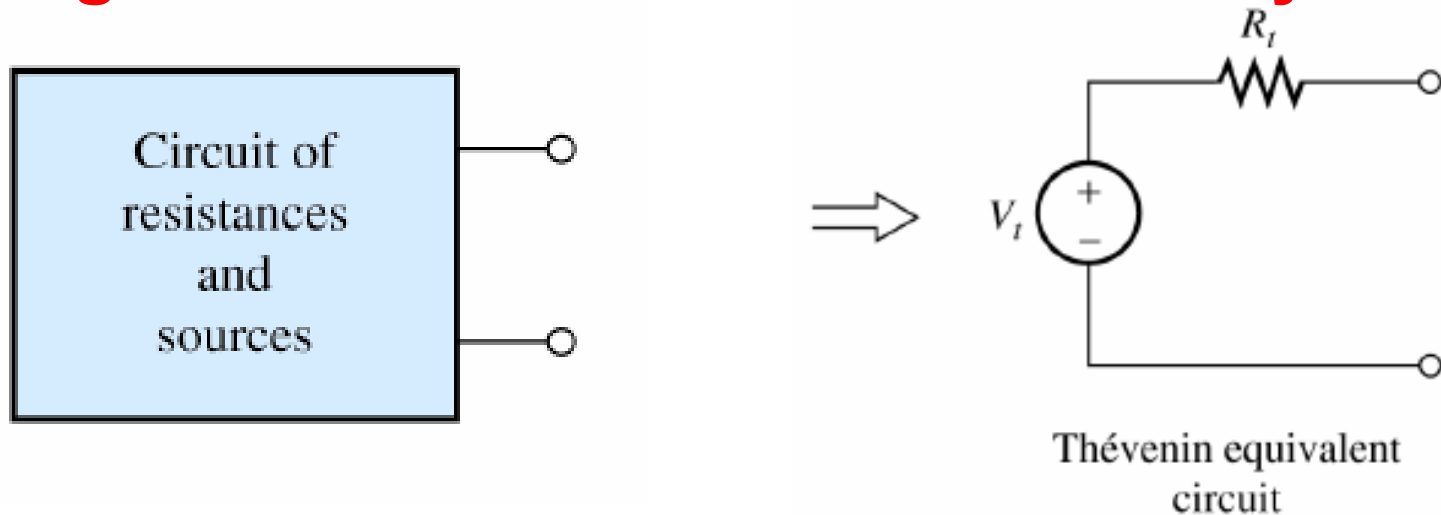

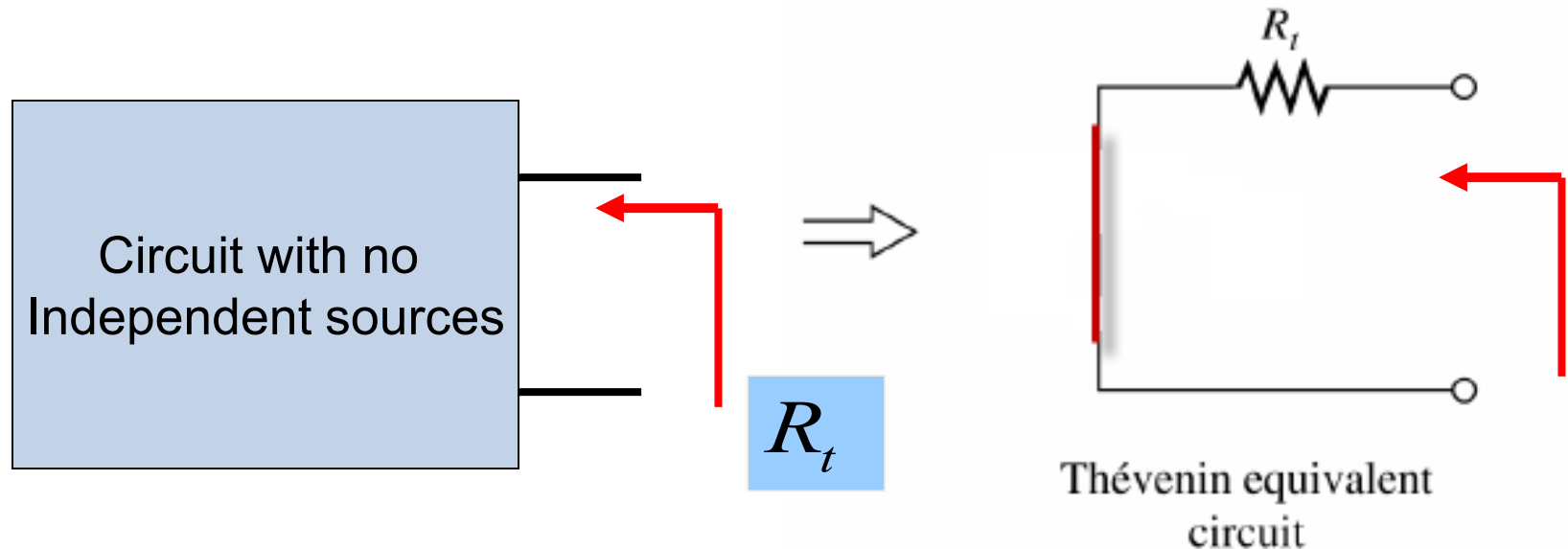Suppose we make all independent sources zero in the circuit







Finding the Thévenin Resistance Directly

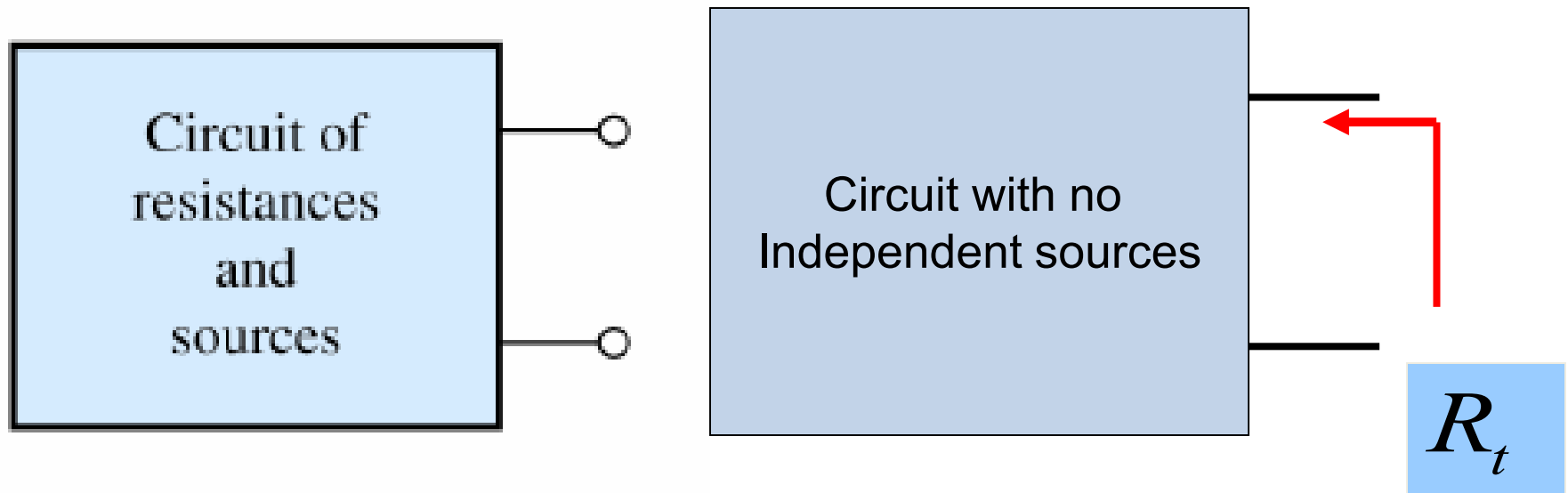


1. Turn off independent sources in the original network:


- A voltage source becomes a short circuit
- A current source becomes an open circuit

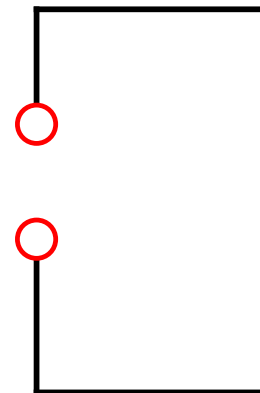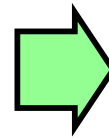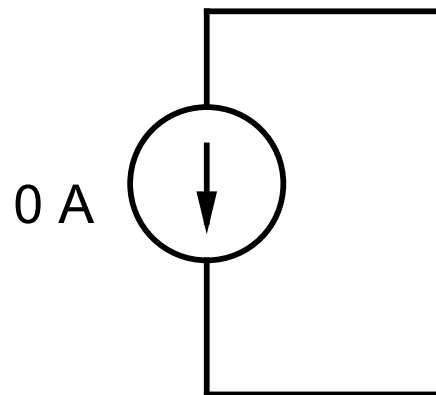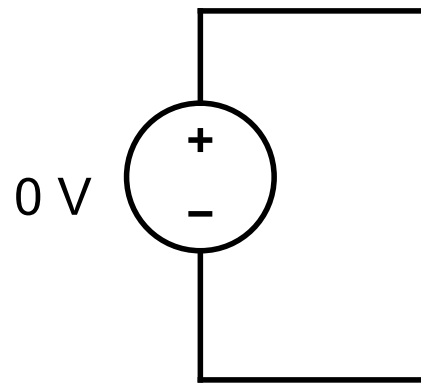2. Compute the resistance between the terminals



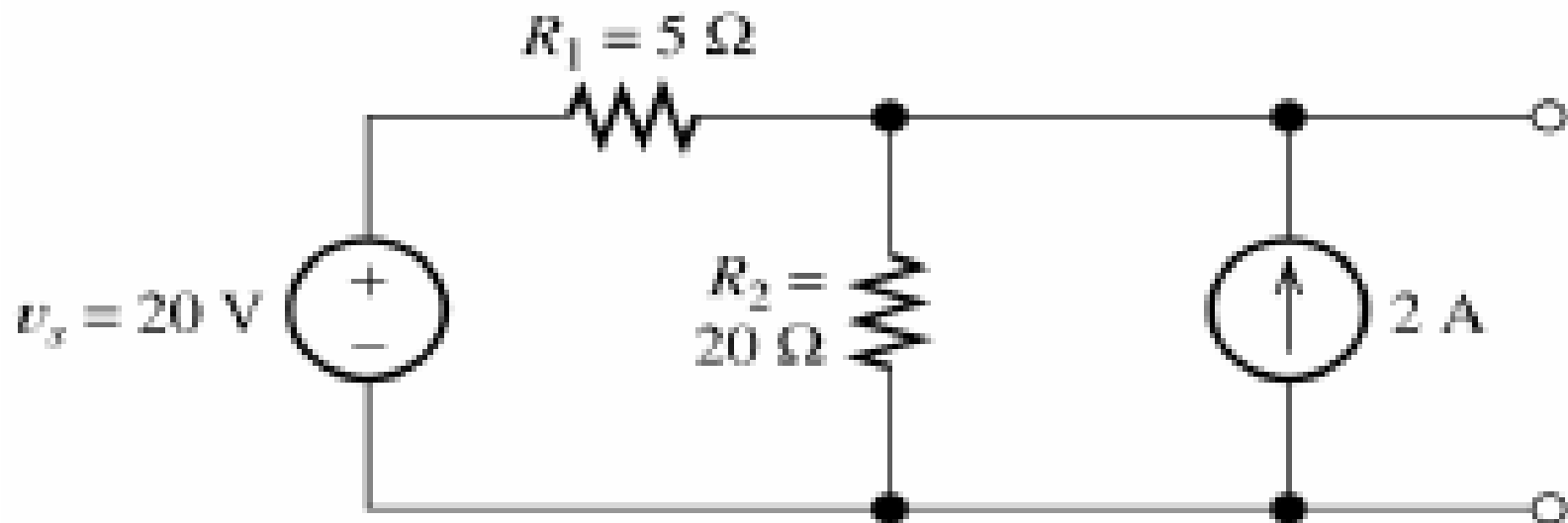

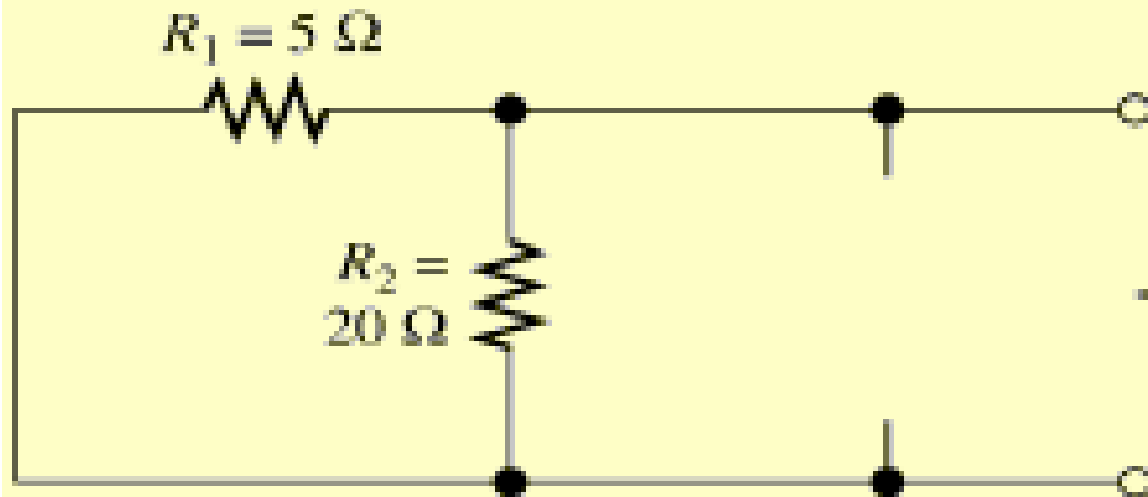
$$R_{eq} = \frac{5 \times 20}{5 + 20} = 4 \Omega$$



$$\leftarrow R_{eq} = R_i$$

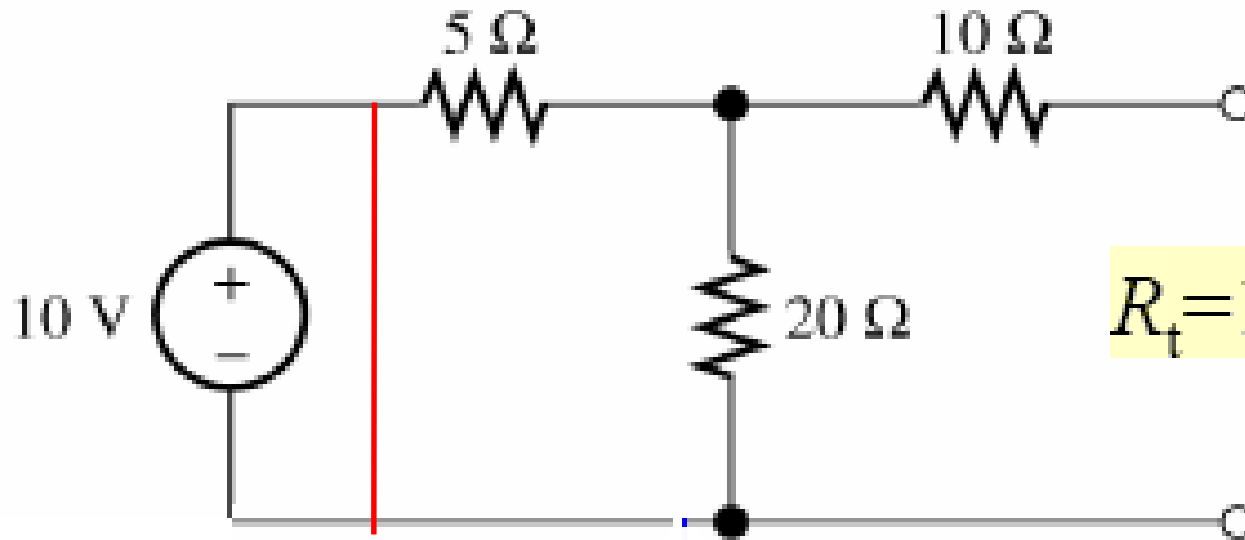
Find Thevenin resistance for each of the circuits shown below



$$R_t = 10 + (5 \parallel 20) = 14$$



$$V_{OC} = V_t = \frac{20}{20 + 5} \times 10 = 8$$
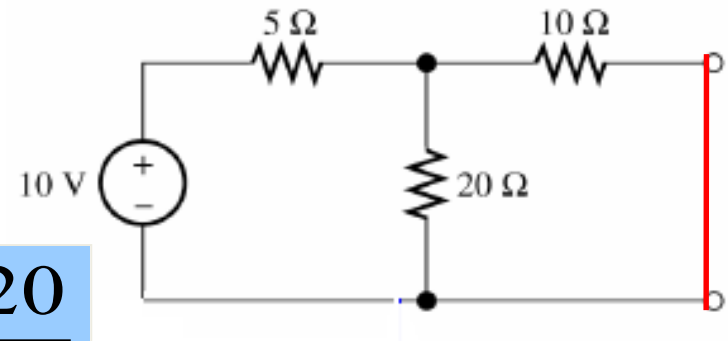
$$i_{sc} = \frac{10}{5 + (10 \parallel 20)} \cdot \frac{20}{20 + 10} = \frac{20}{35}$$




$$R_t = \frac{v_{oc}}{i_{sc}} = \frac{8 \times 35}{20} = 14$$

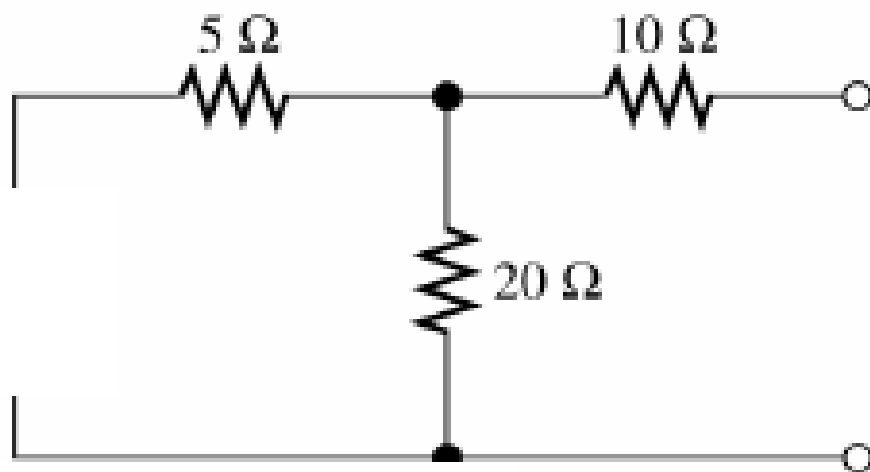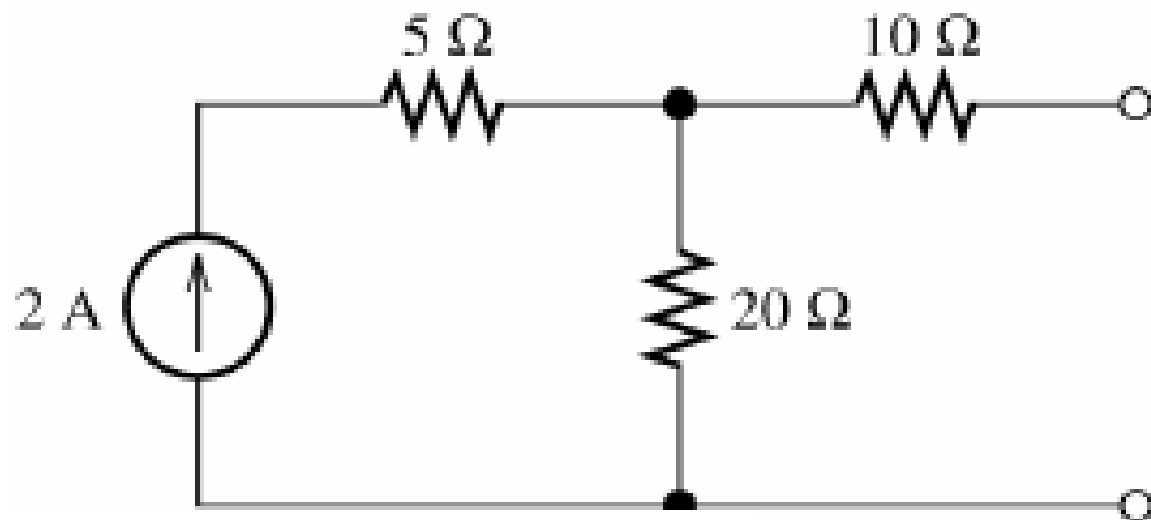Find Thevenin resistance for each of the circuits shown below





$$R_t = 10 + 20 = 30$$

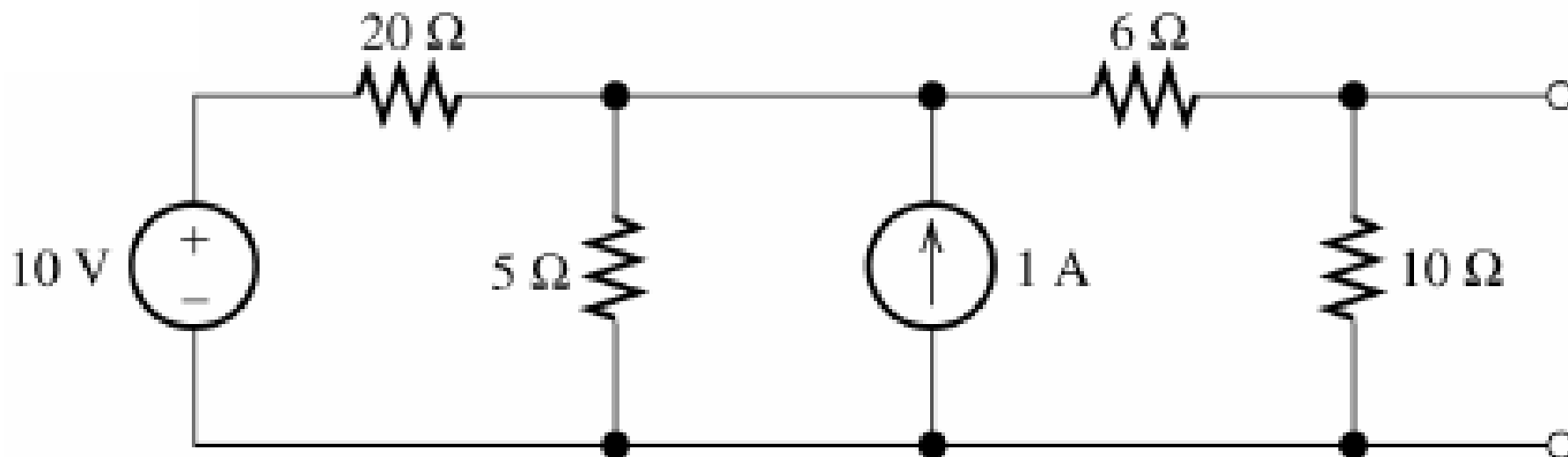Find Thevenin resistance for each of the circuits shown below




$$R_t = ((20 || 5) + 6) || 10 = 5$$

Circuit with dependent Sources

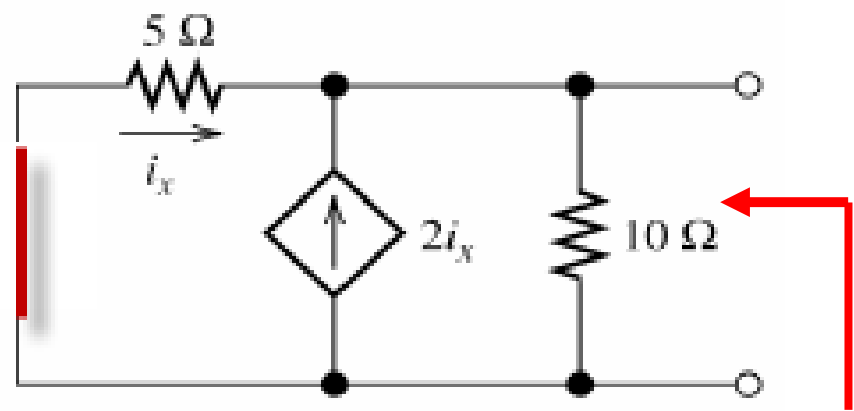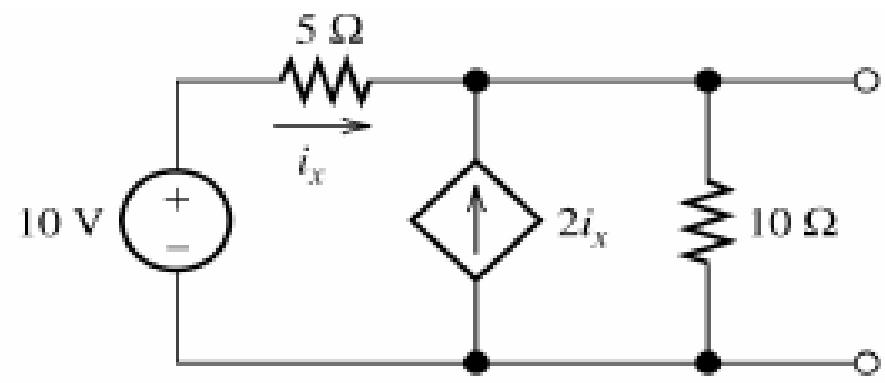



$R_t = ?$

I_Z

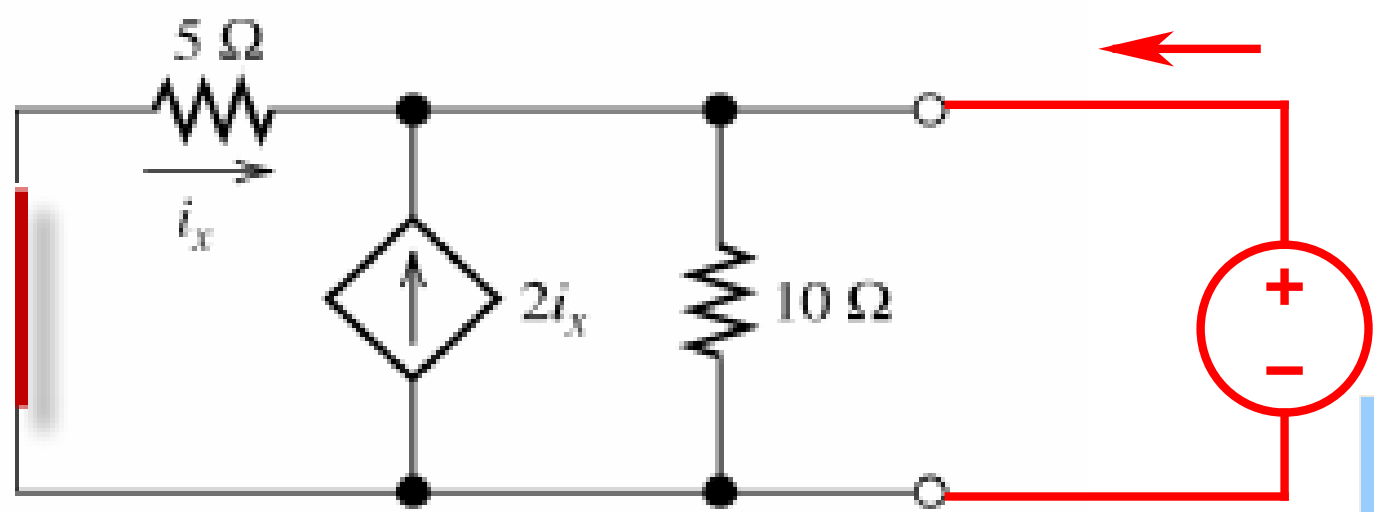


$R_t = \frac{V_Z}{I_Z}$


Norton's equivalent

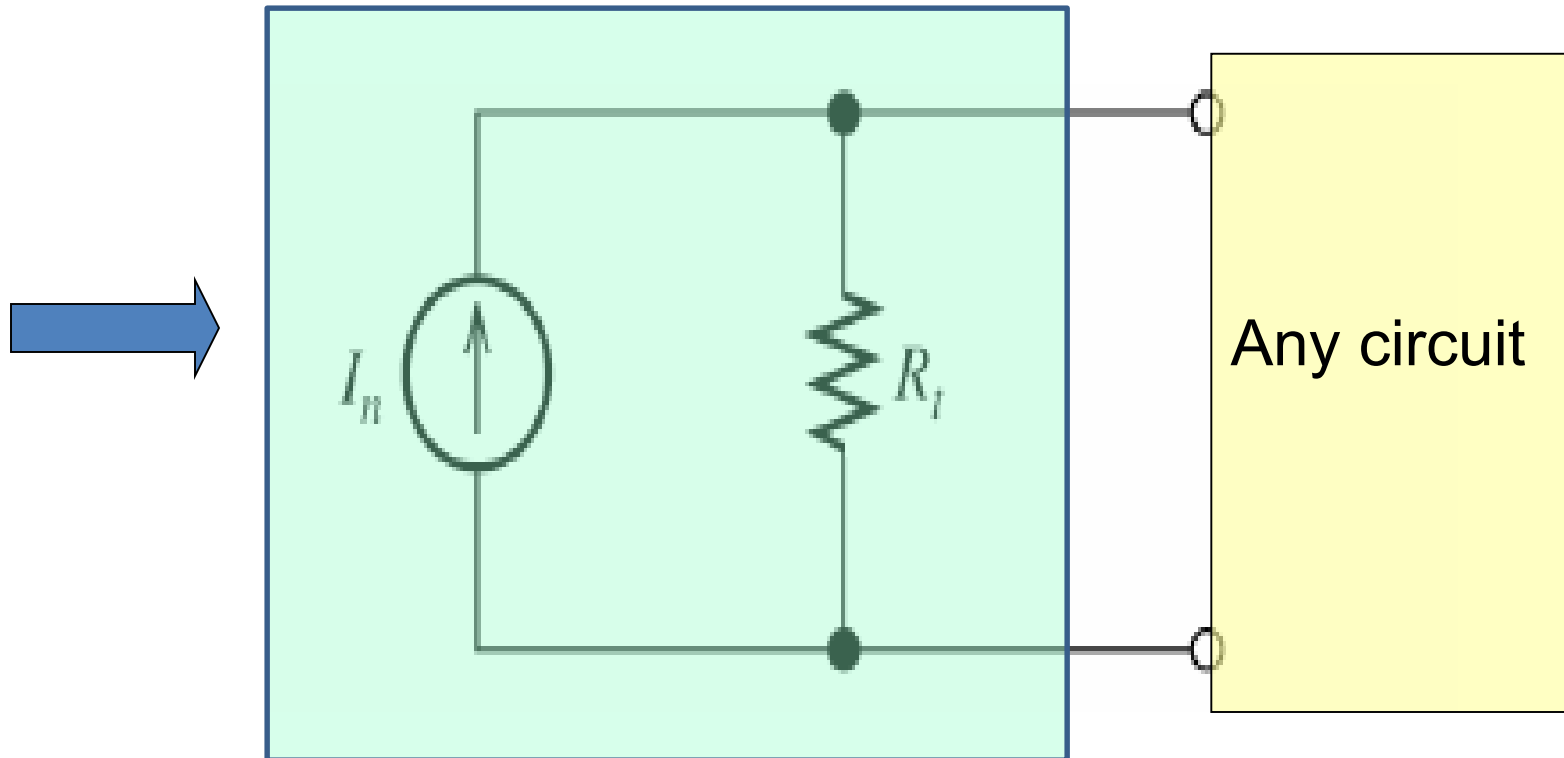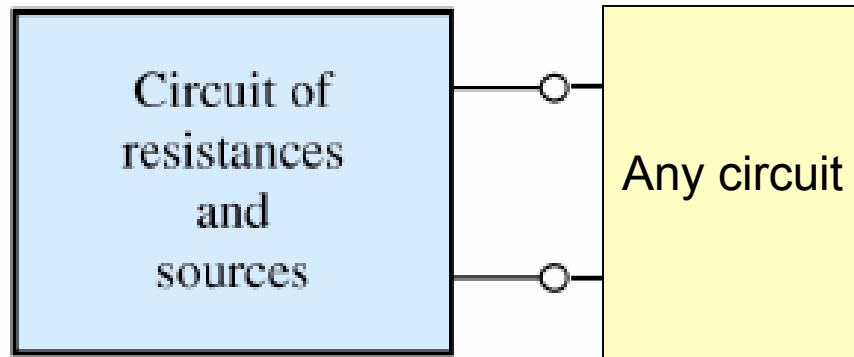


Norton's equivalent

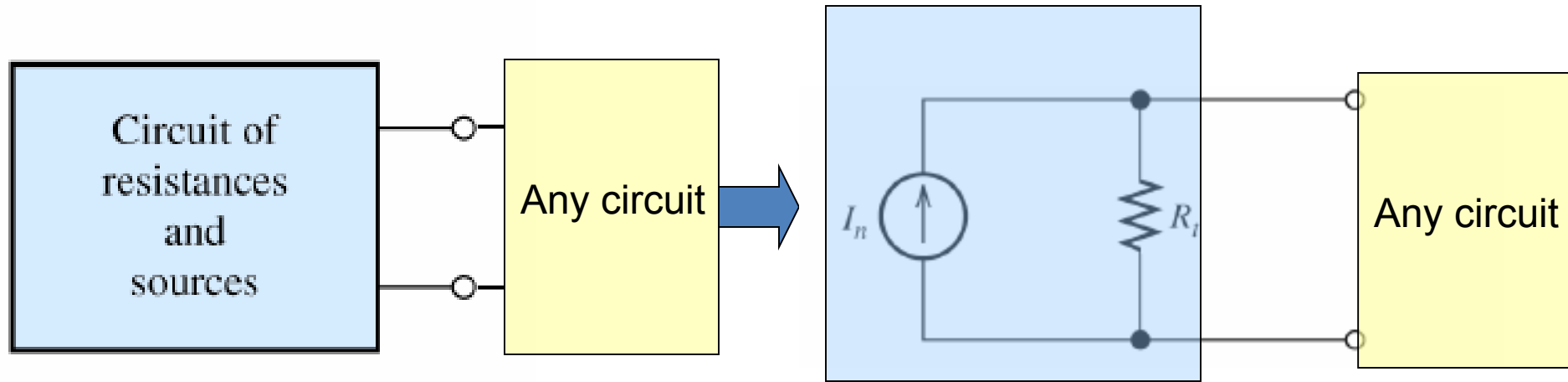


How do we find I_N ?

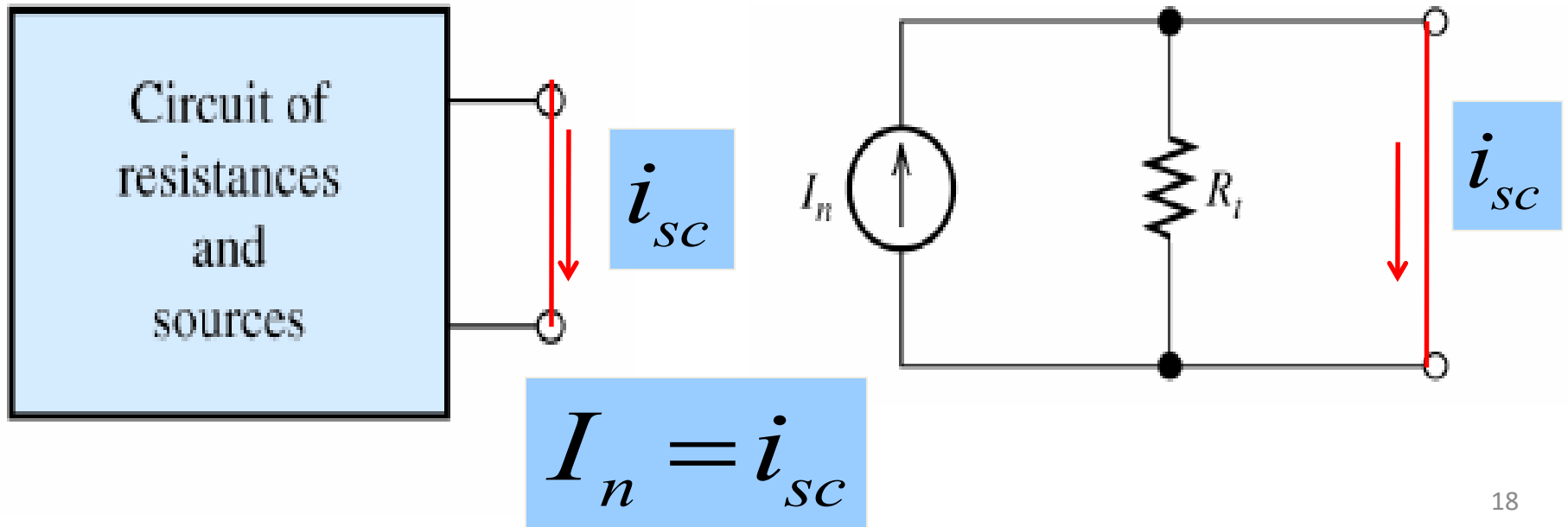

Norton's equivalent

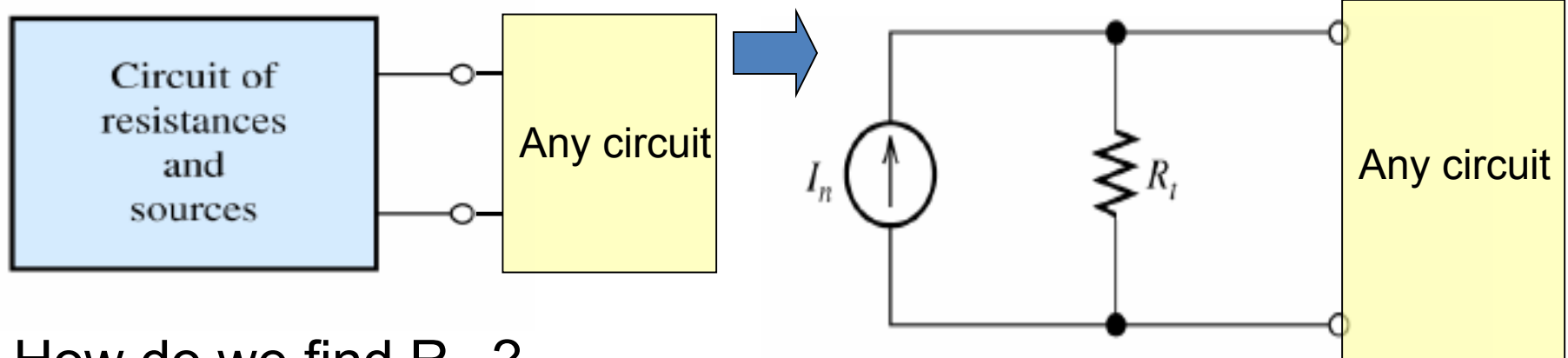


How do we find R_N ?

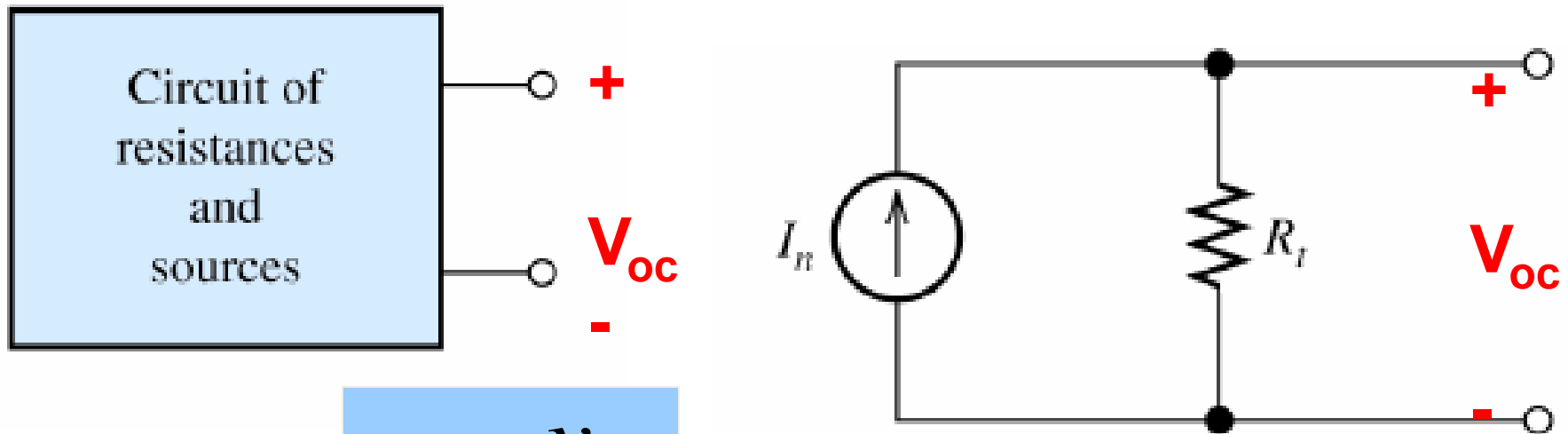


$$R_t = \frac{v_{oc}}{i_{sc}}$$

$$v_{oc} = I_n \times R_t$$

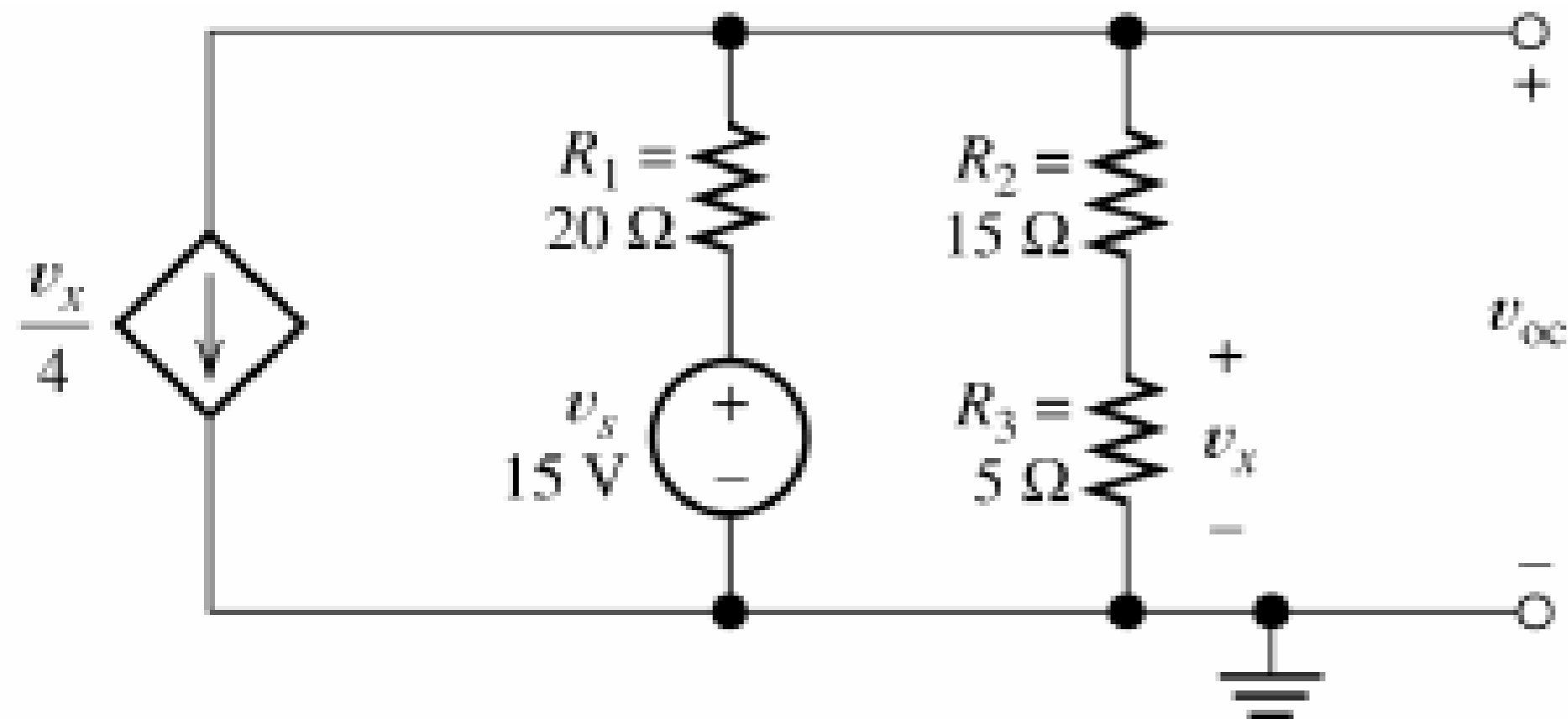Example: Find the Norton equivalent for the following circuit




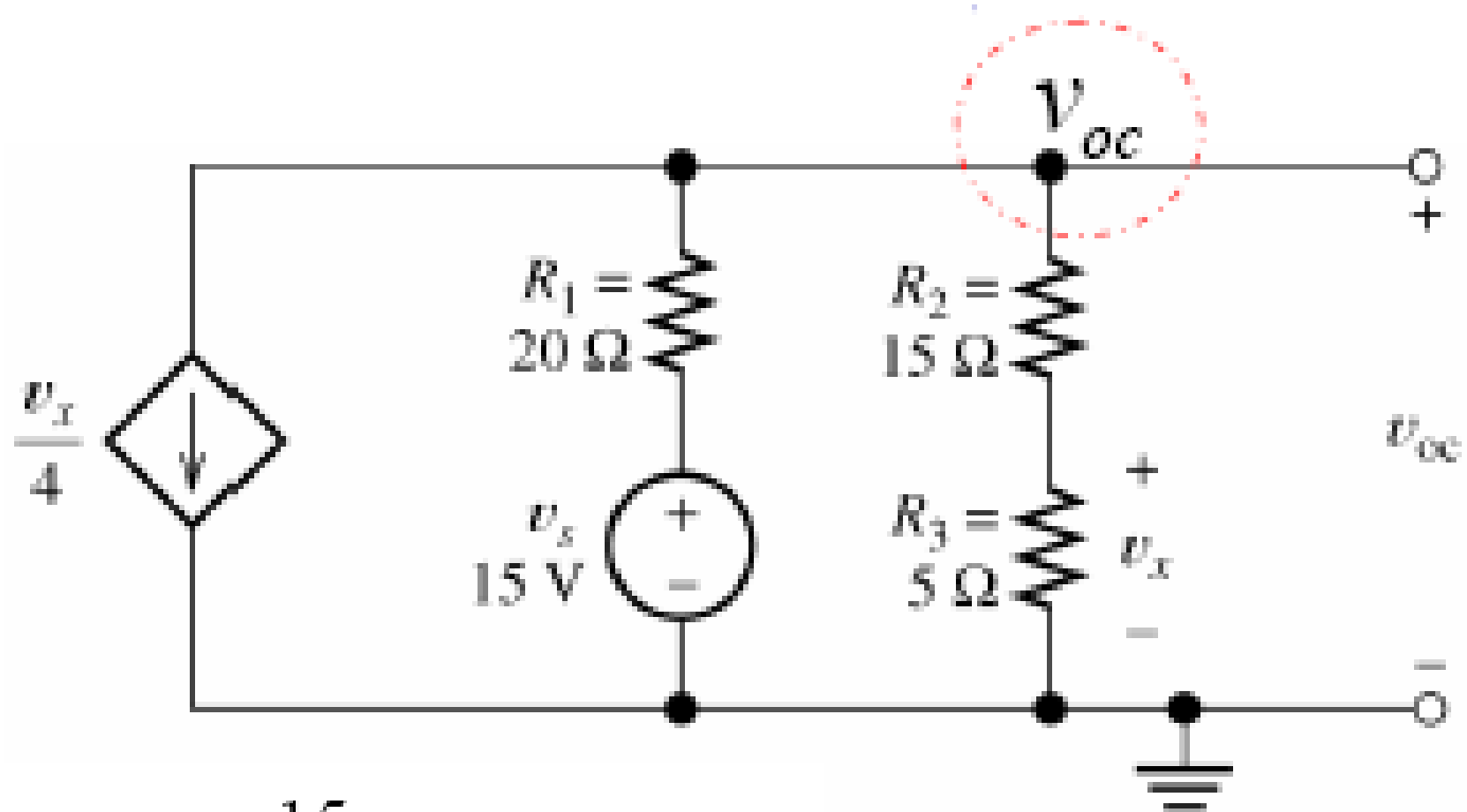

$$\frac{v_x}{4} + \frac{v_{oc} - 15}{R_1} + \frac{v_{oc}}{R_2 + R_3} = 0$$


$$v_x = \frac{R_3}{R_2 + R_3} v_{oc} = 0.25 v_{oc}$$

$$v_{oc} = 4.62 \text{ V}$$

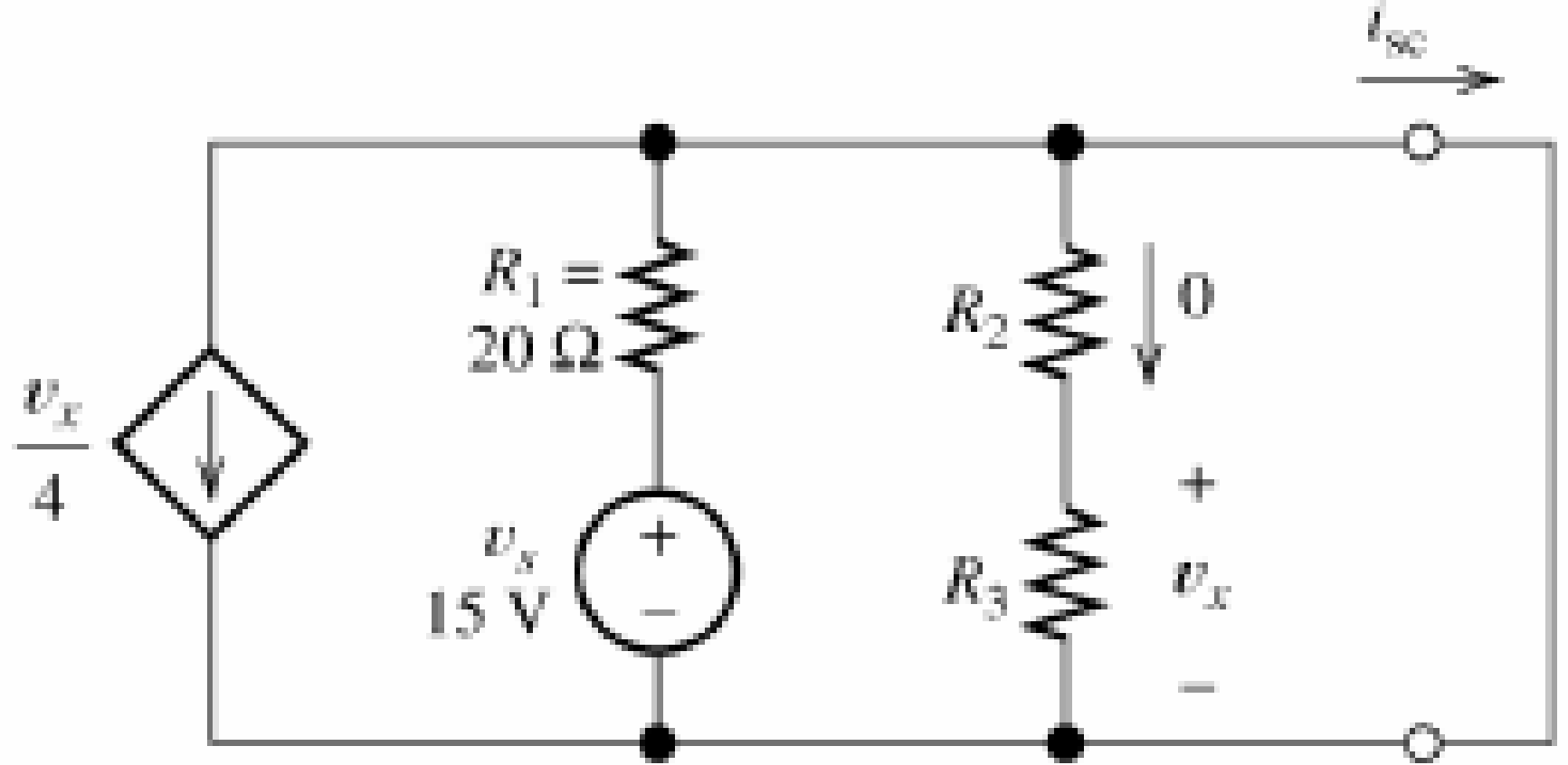

$$i_{sc} = \frac{v_s}{R_1} = \frac{15\text{ V}}{20\ \Omega} = 0.75\text{ A}$$

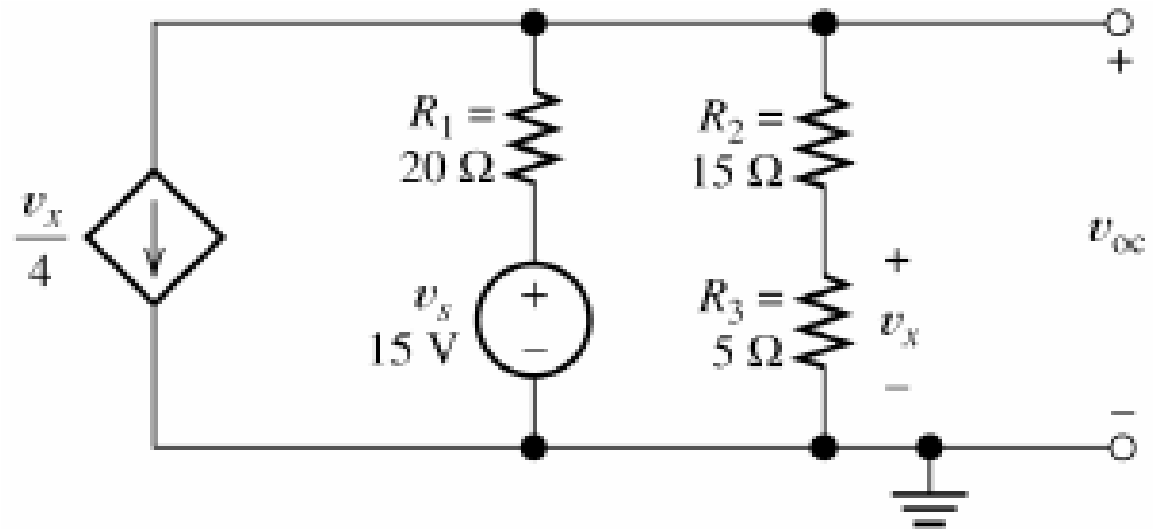
$$R_t = \frac{v_{oc}}{i_{sc}} = \frac{4.62\text{ V}}{0.75\text{ A}} = 6.15\ \Omega$$




Norton's equivalent

$$v_{oc} = 4.62V$$

$$R_t = 6.15 \Omega$$

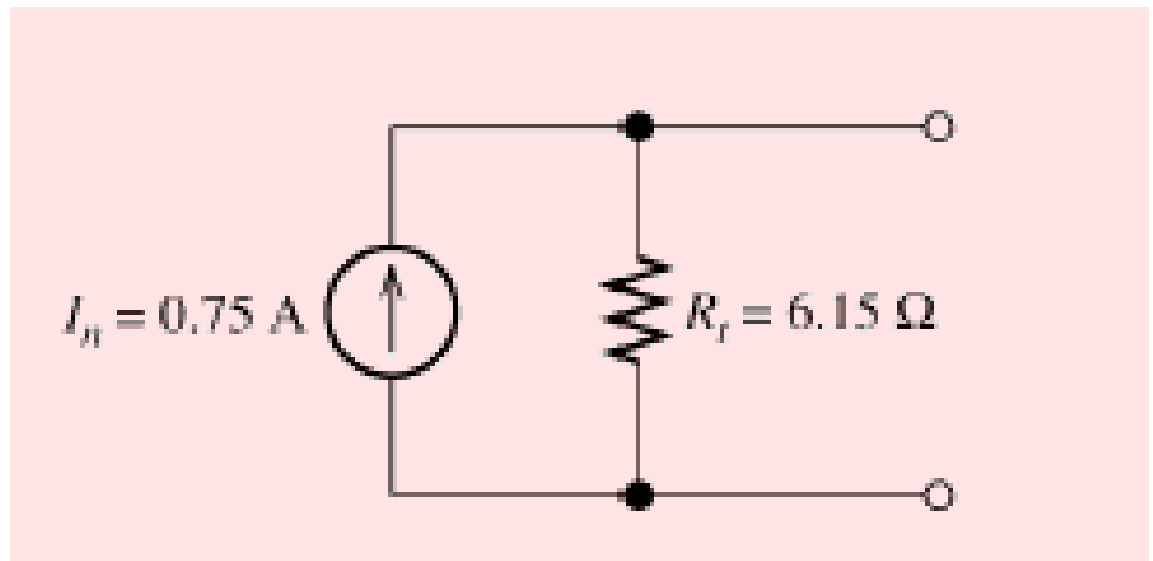


Examples

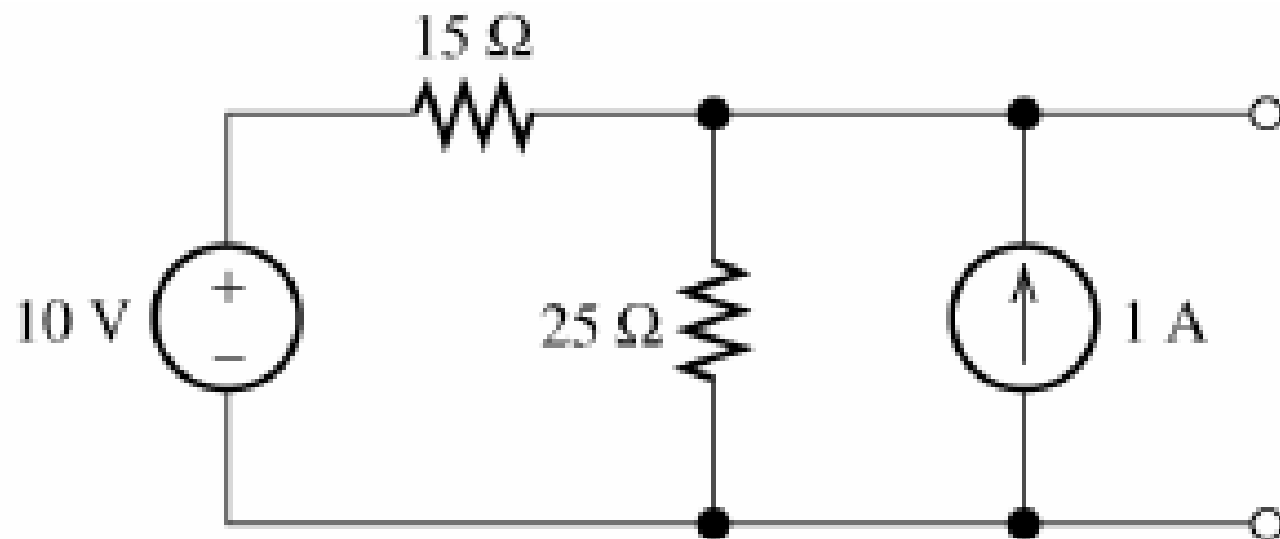



$$I_n = 1.67 \text{ A}, R_t = 9.375 \Omega$$

Solve for R_t

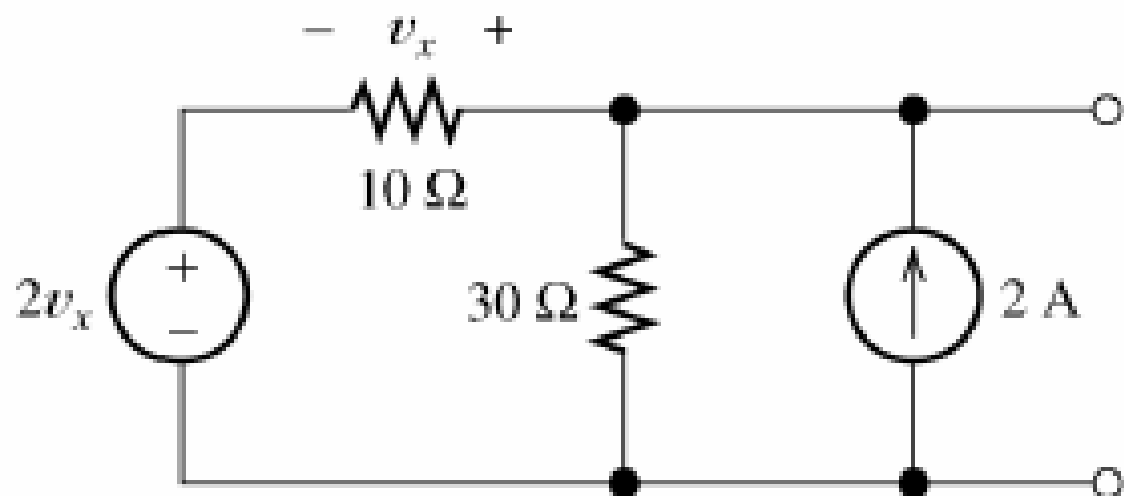


$$I_n = 2 \text{ A}, R_t = 15 \Omega$$

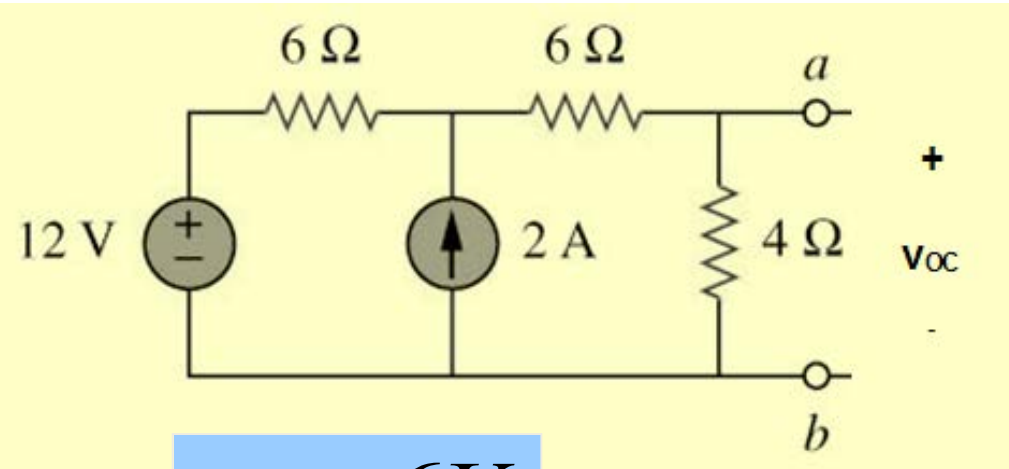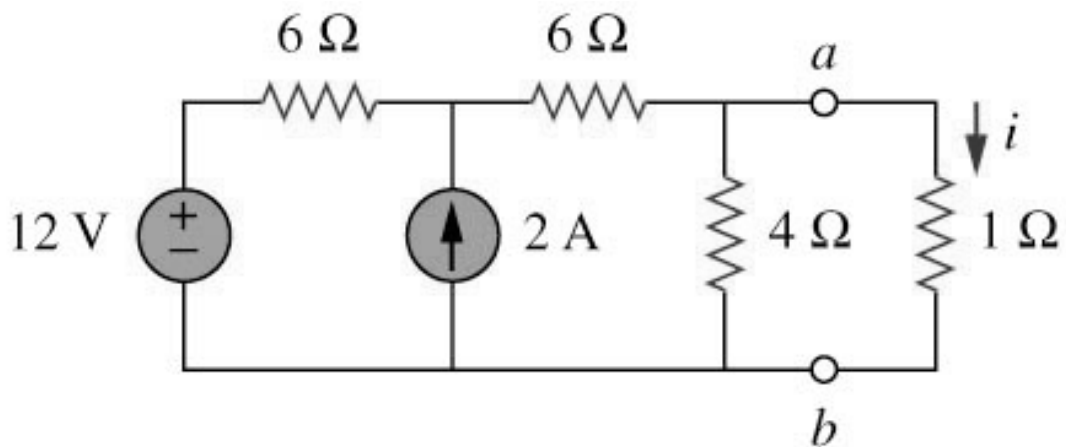
Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit shown below. Hence find i .



$$V_{oc} = 6V$$

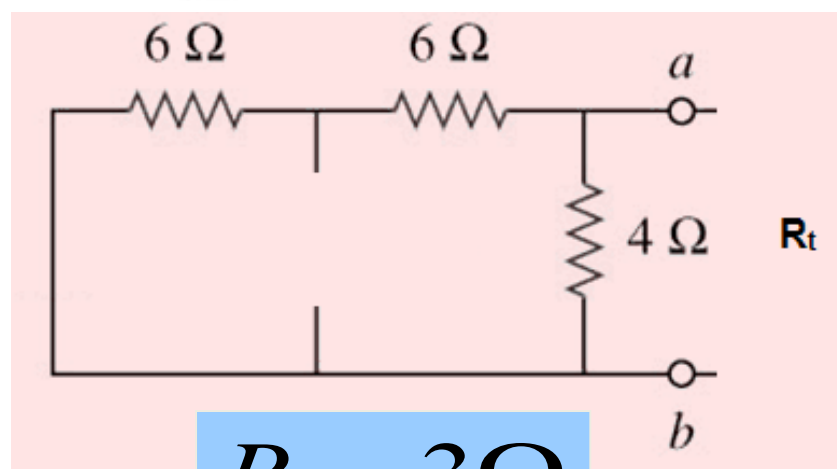


$$R_t = 3\Omega$$

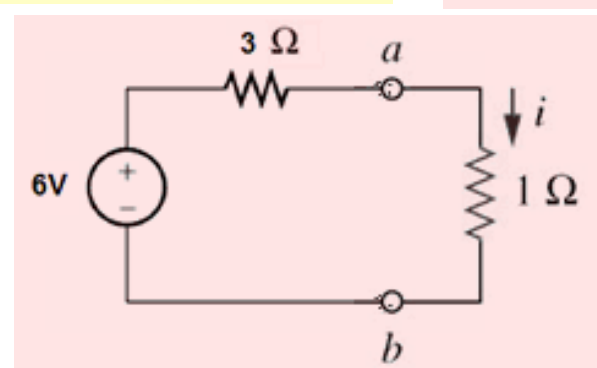


$$i = 1.5A$$

Use Superposition


$$v_{oc} = 6V$$

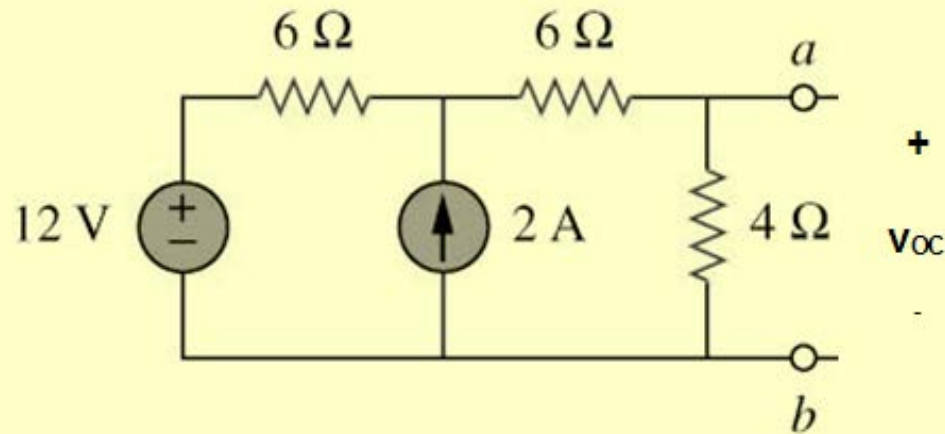

$$V_{oc} = V_{oc1} + V_{oc2} = 6$$

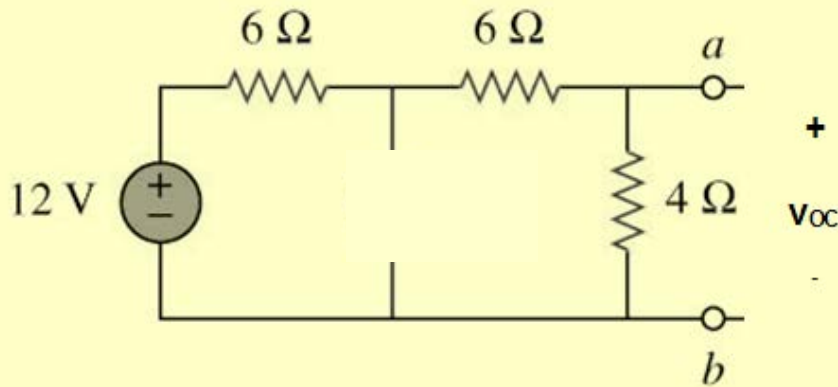

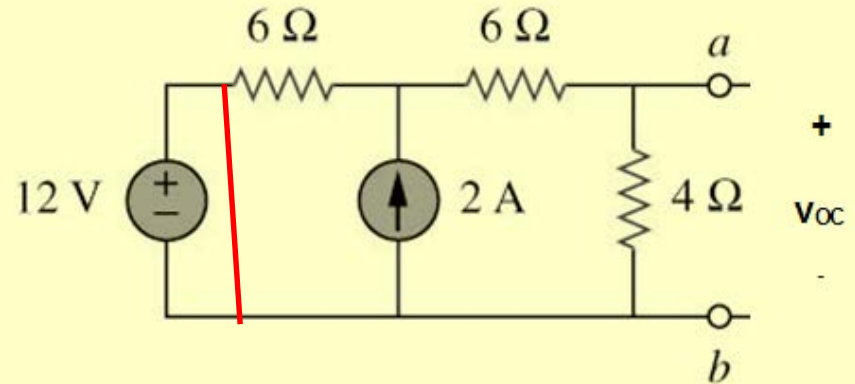
$$V_{oc1} = \frac{4}{4+12} \times 12 = 3$$




$$V_{oc2} = 4 \times \left(2 \times \frac{6}{6+10} \right) = 3$$

Source Transformation



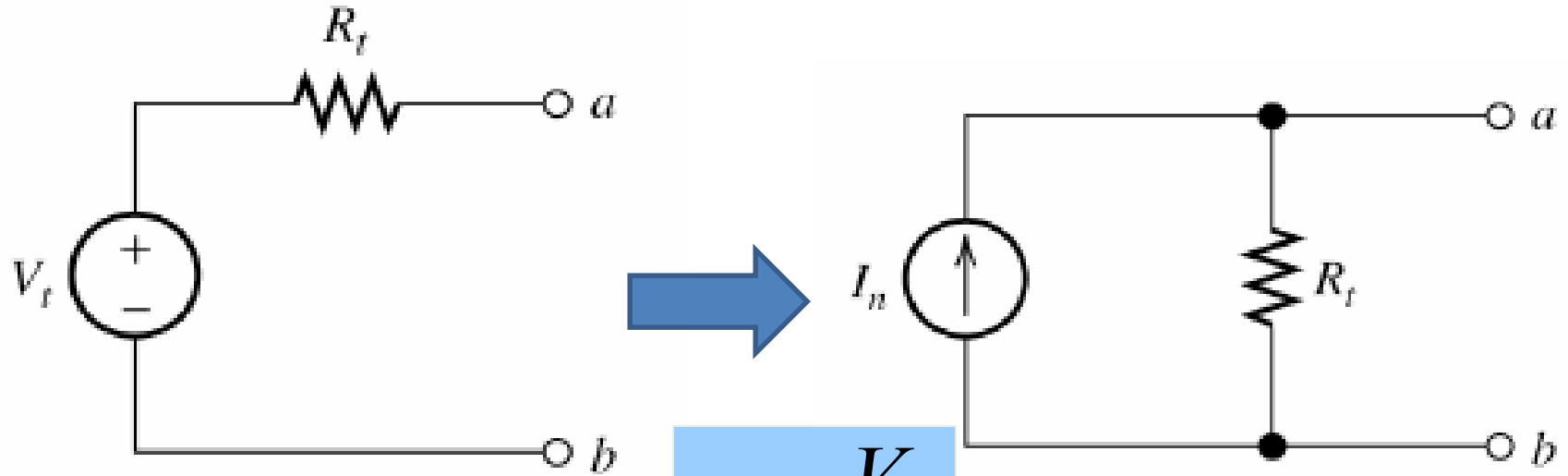


$$I_n = \frac{V_t}{R_t}$$

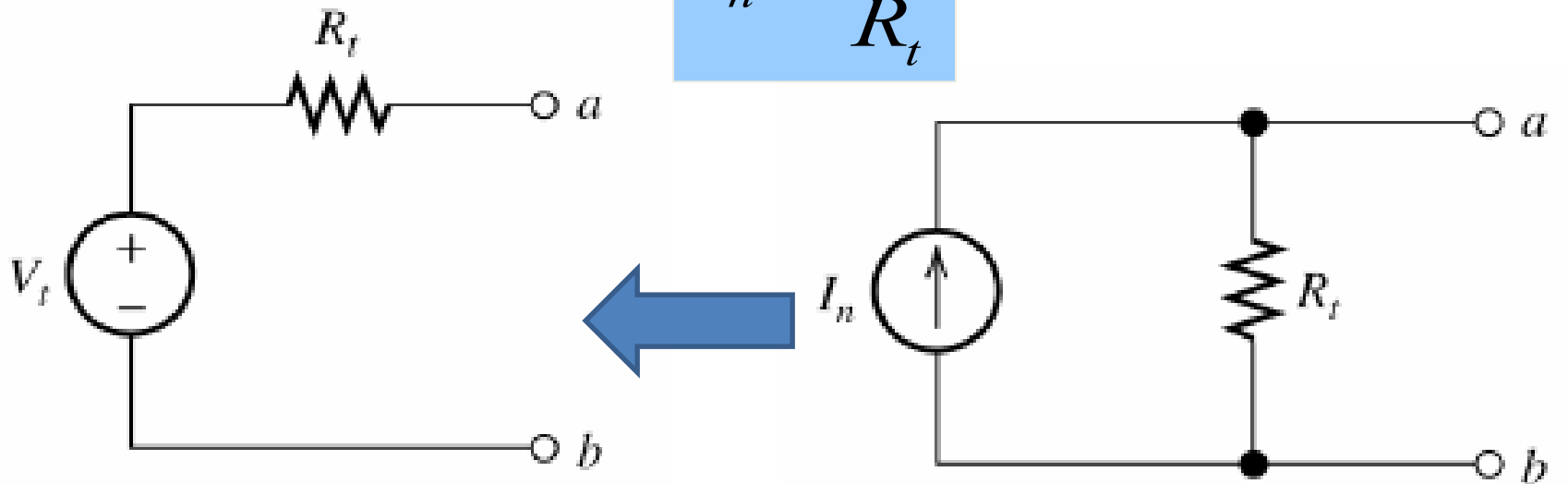


$$V_t = I_n \times R_t$$


Example

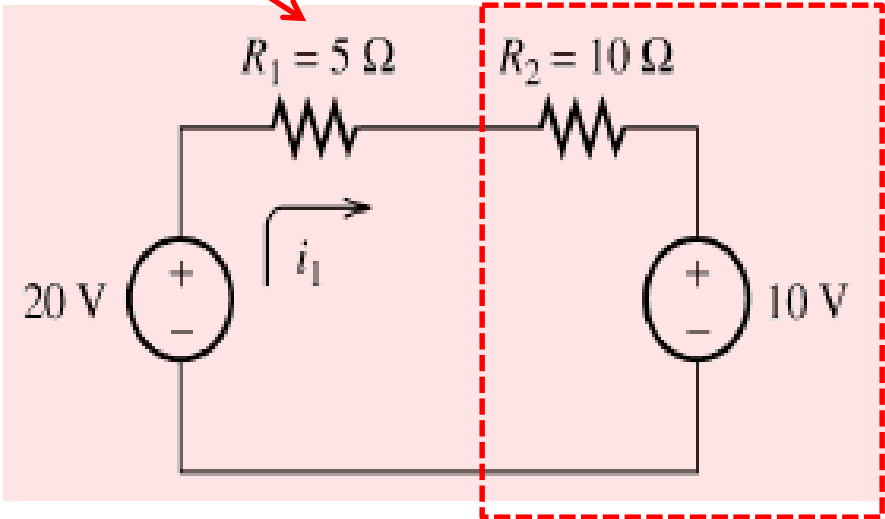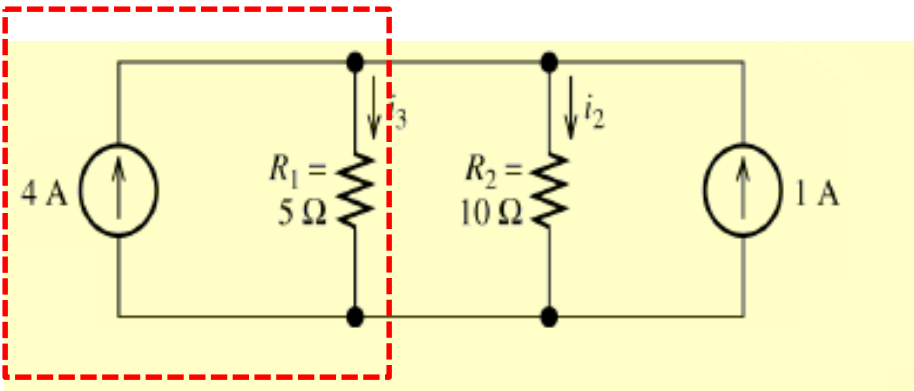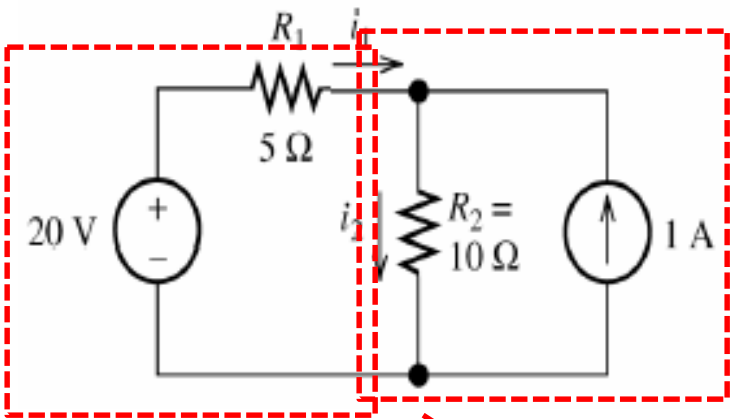

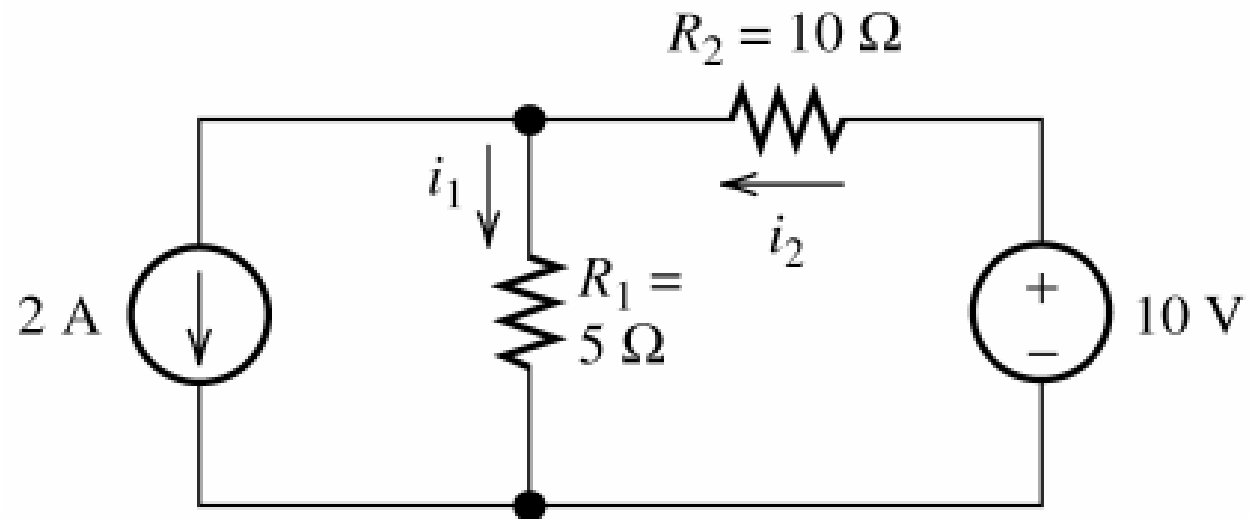Use source transformation to solve for the indicated currents



Maximum Power Transfer for dc circuits

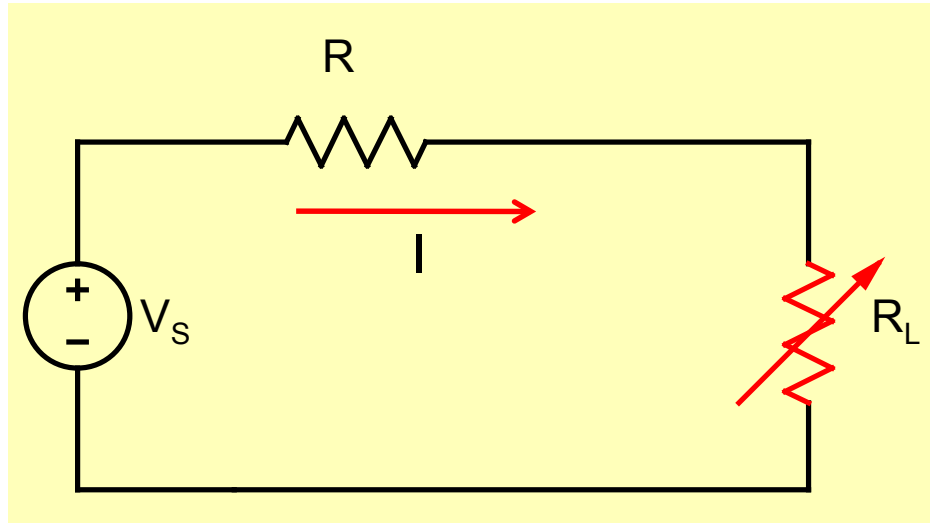

What value of R_L will give rise to maximum load power ?


$$I = \frac{V_s}{R + R_L}$$

$$P_L = I^2 R_L = V_s^2 \times \frac{R_L}{(R + R_L)^2}$$

$$\frac{\partial P_L}{\partial R_L} = 0$$

$$R_L = R$$

$$P_{L\max} = \frac{V_s^2}{4R_L}$$


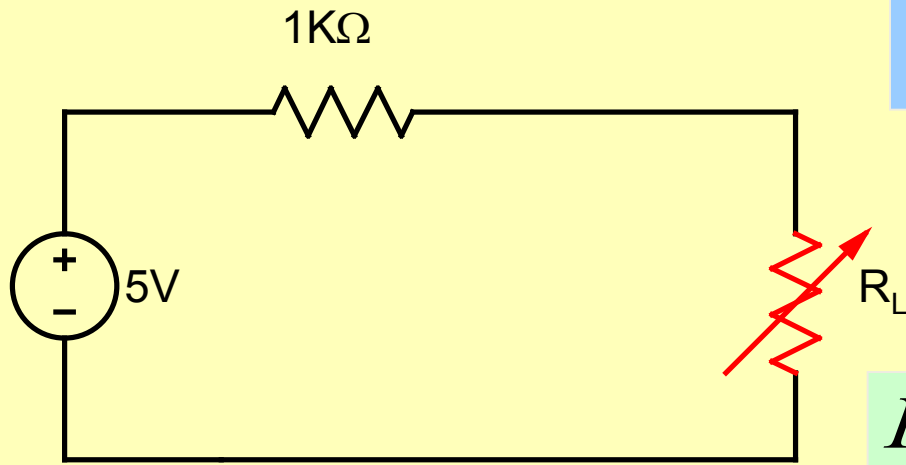


$$R_L = 1K \Rightarrow P_L = 6.25mW$$



$$R_L = 10K \Rightarrow P_L = 2mW$$

$$R_L = 0.2K \Rightarrow P_L = 3.47mW$$

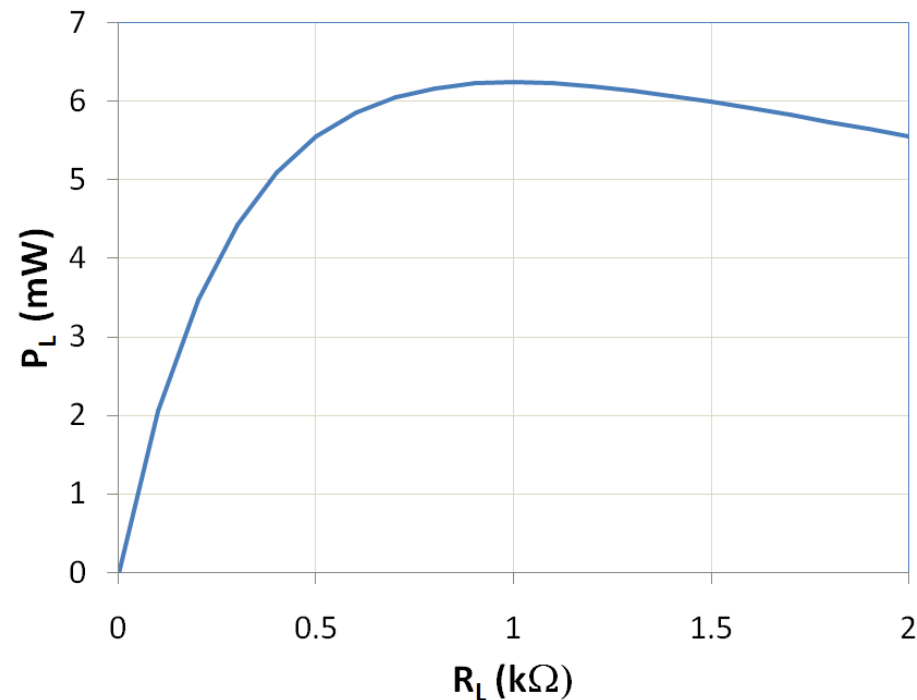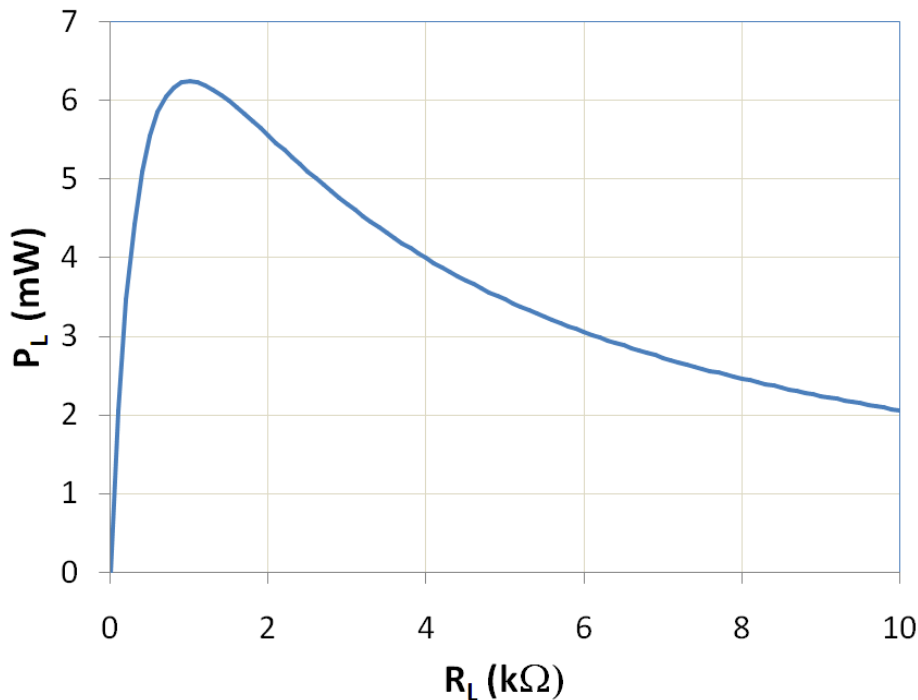Maximum power is delivered to the load when **$R_L = R$**





General Case

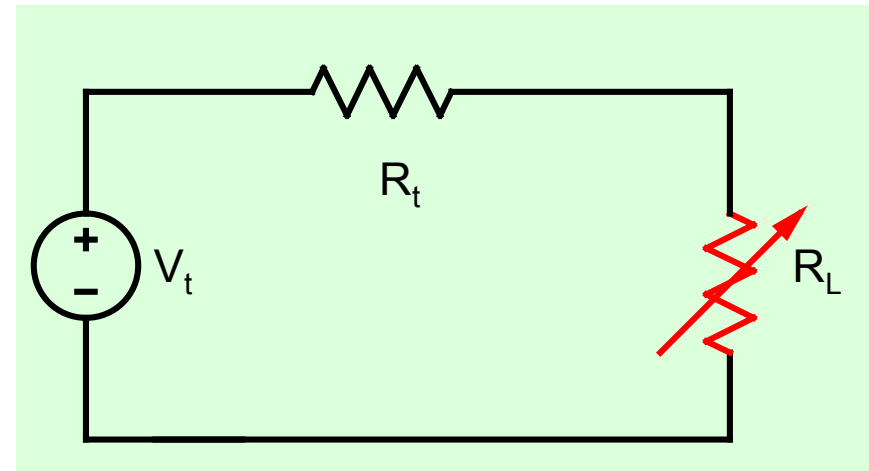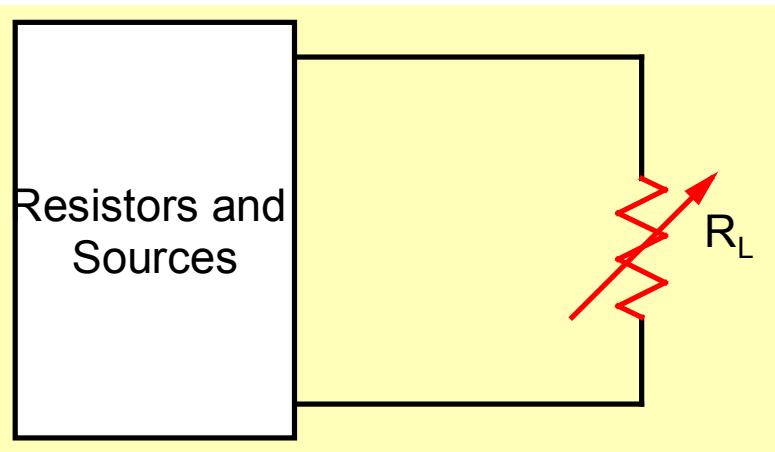


Maximum power is delivered to the load when **$R_L = R_t$**

Summary

Series/Parallel resistances

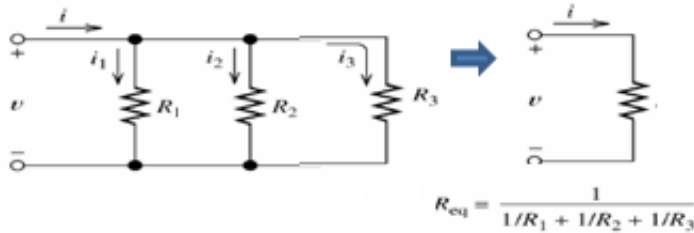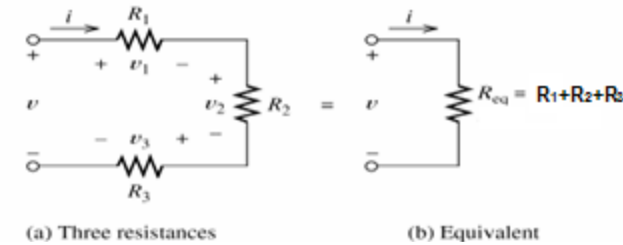


Voltage division

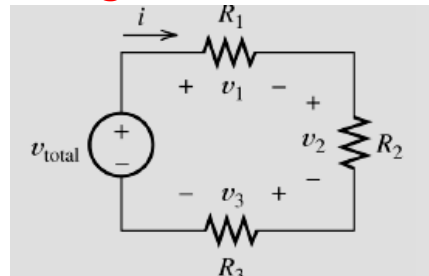

$$v_2 = R_2 i = \frac{R_2}{R_1 + R_2 + R_3} v_{total}$$

$$i_2 = \frac{v}{R_2} = \frac{R_1}{R_1 + R_2} i_{total}$$


Current division

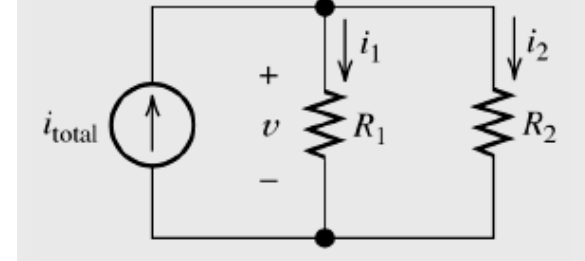

Mesh Analysis

1. Assign mesh currents i_1, i_2, \dots, i_n to the n meshes.
2. Apply KVL to each of the n meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the resulting n simultaneous equations to get the mesh currents.

Source Transformation

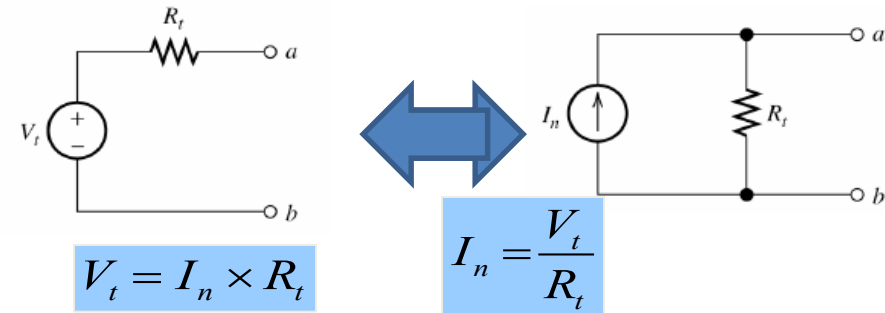



The **superposition principle** states that the total response is the sum of the responses to each of the independent sources acting individually.

Nodal Analysis:

1. Identify and number the nodes
2. Choose a reference node
3. Write KCL for each node such that

Sum of currents leaving a node is zero.

Super node

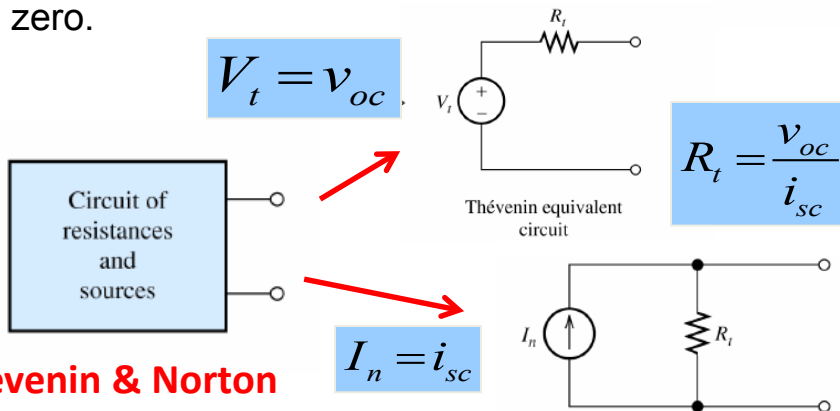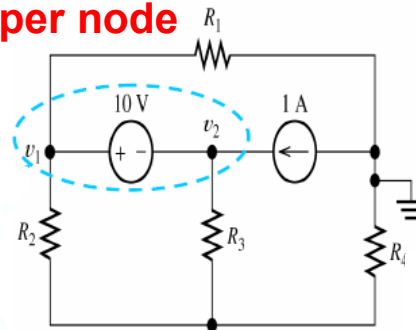

Thevenin & Norton