

# ESc201: Introduction to Electronics

## Circuit Fundamentals

A  *quick* Recap

Dr. Y. S. Chauhan

Dept. of Electrical Engineering

IIT Kanpur


# Concepts

- Charge, Current, Voltage, Power, and Energy
- Ohm's Law
- KCL
- KVL
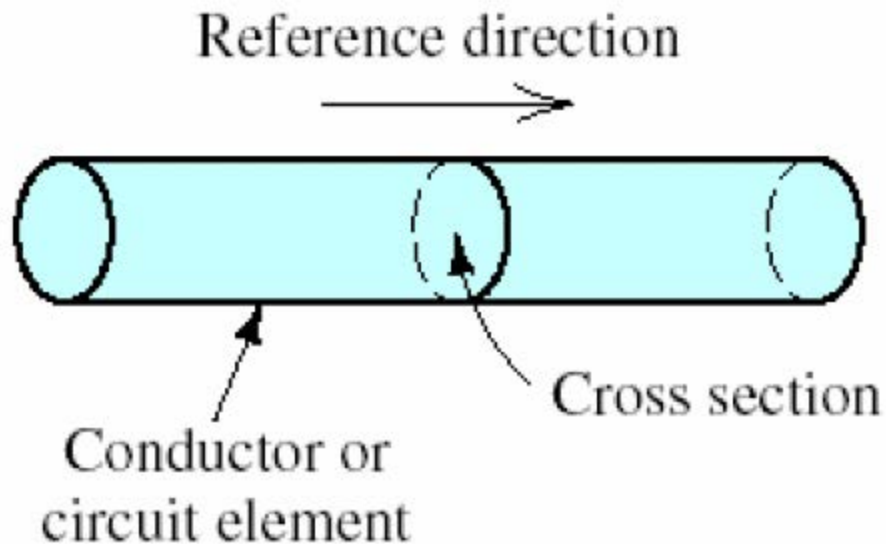
# Electrical Current

The time rate of flow of electrical charge

- The units are amperes (A), which are equivalent to coulombs per second (C/s)



$$i(t) = \frac{dq(t)}{dt}$$


André-Marie Ampère  
1775-1836



Flow of electrons through a wire or other electrical conductor gives rise to current

- Electrons are negatively charged particles

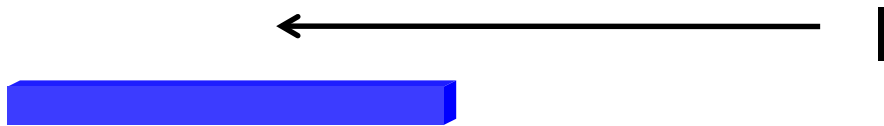The charge per electron is  **$-1.602 \times 10^{-19} \text{ C}$**




$10^{16}$  electrons flow per second

How much current flows?  $i(t) = \frac{dq(t)}{dt}$

$$I = \frac{Q}{t} = \frac{-1.6 \times 10^{-19} \times 10^{16}}{1} = -1.6 \times 10^{-3} \text{ A}$$

Current has a magnitude and a direction

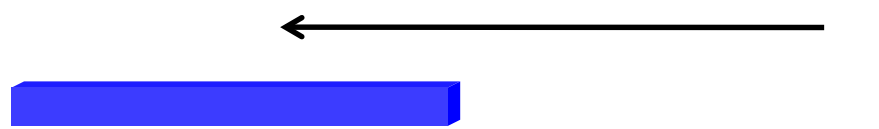

  
 $10^{16}$  electrons flow per second



Direction of current flow is opposite to direction of electron flow

Large number of electrons have to flow for appreciable current

Exercise 1: For  $q(t) = 2 - 2e^{-100t}$ ,  $t > 0$  and  $q(t) = 0$  for  $t < 0$ , find  $i(t)$
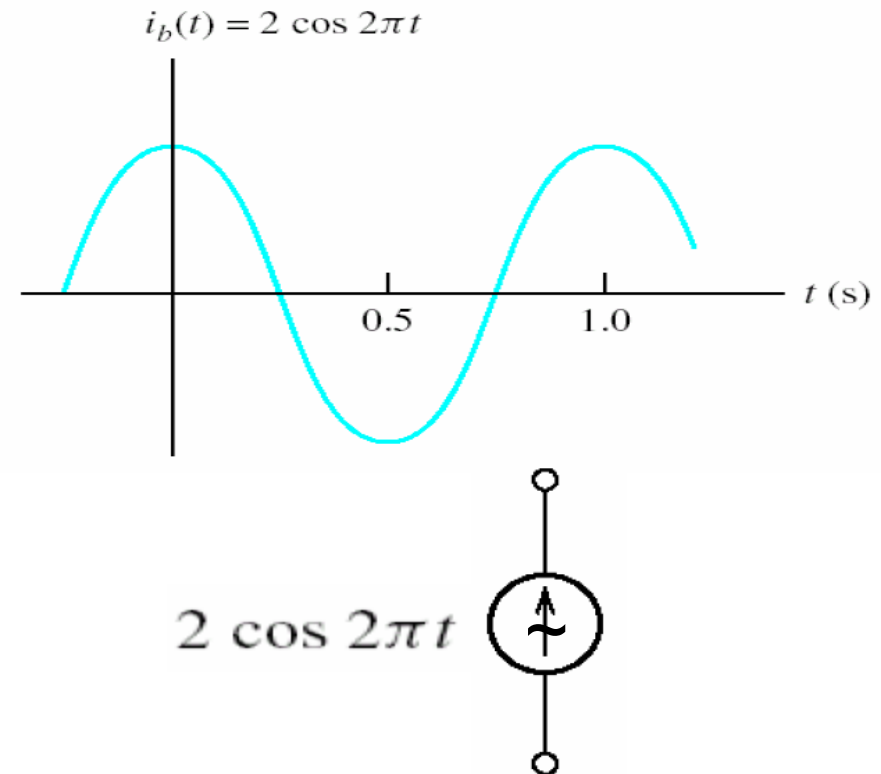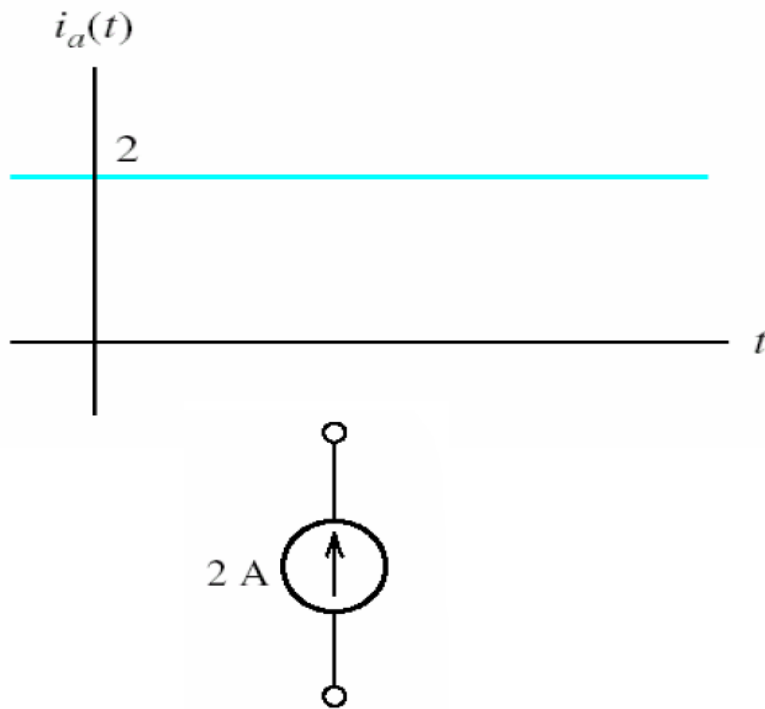
# Direct Current (DC) & Alternating Current (AC)

When current is constant with time, we say that we have direct current, abbreviated as DC.




On the other hand, a current that varies with time, reversing direction periodically, is called alternating current, abbreviated as **AC**

# Voltage

Voltage difference is a Source of current flow

Units of Voltage: Volts (V)

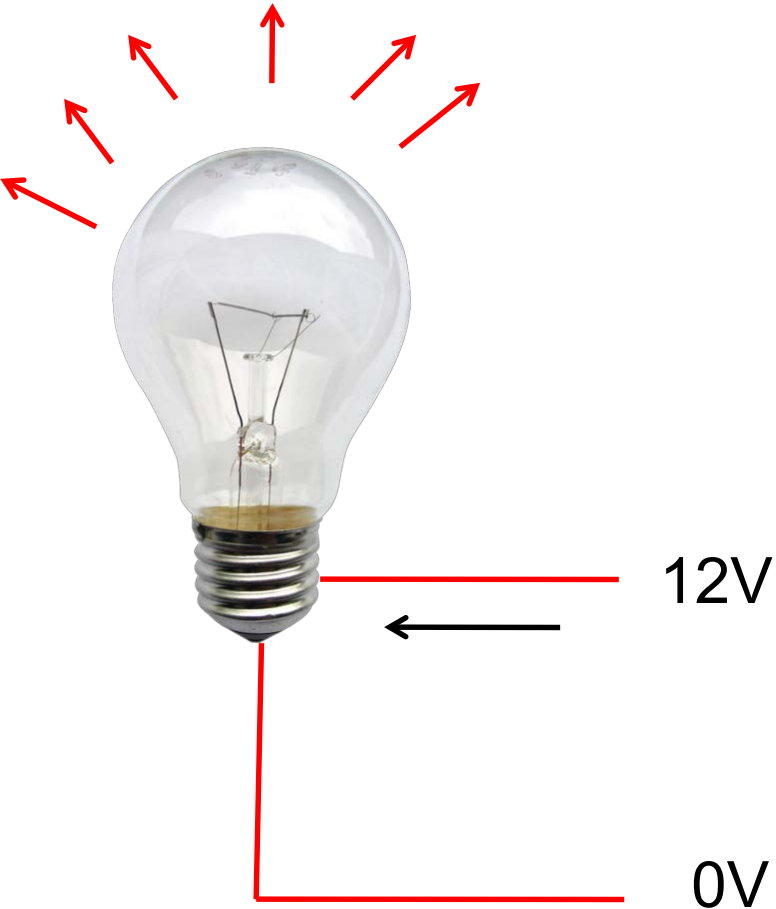

Alessandro Giuseppe Antonio  
Anastasio Volta 1745-1827

# Voltage Sources






# DC and AC voltages




$$V_+ - V_- = 12V$$

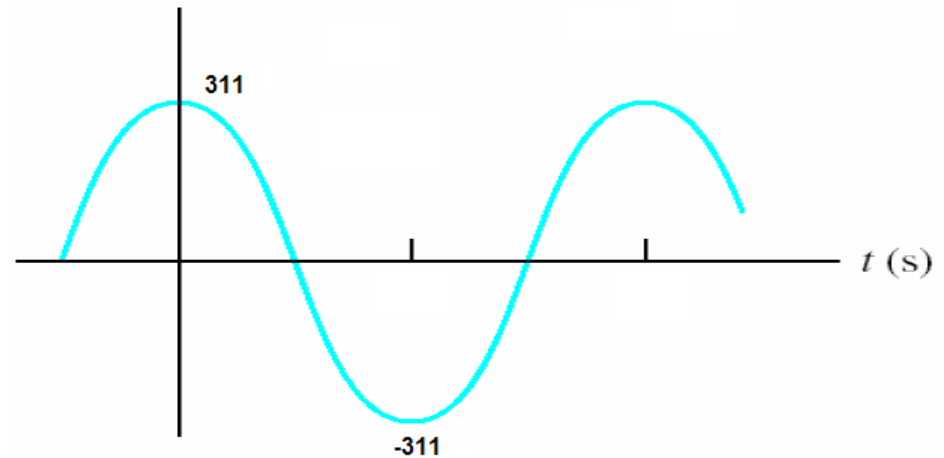

Electrical Systems are made of Voltage sources, wires and a variety of **electrical elements**




Resistor

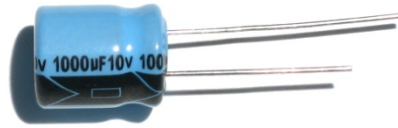

Capacitor




Inductor

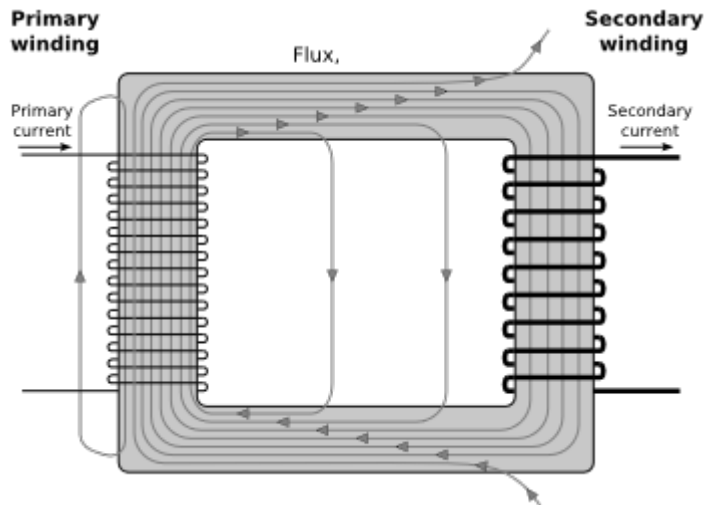

Transformer




Diode

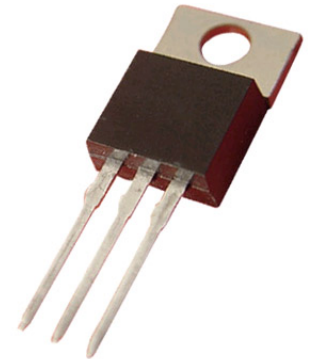

Transistor


# Current flows in a loop

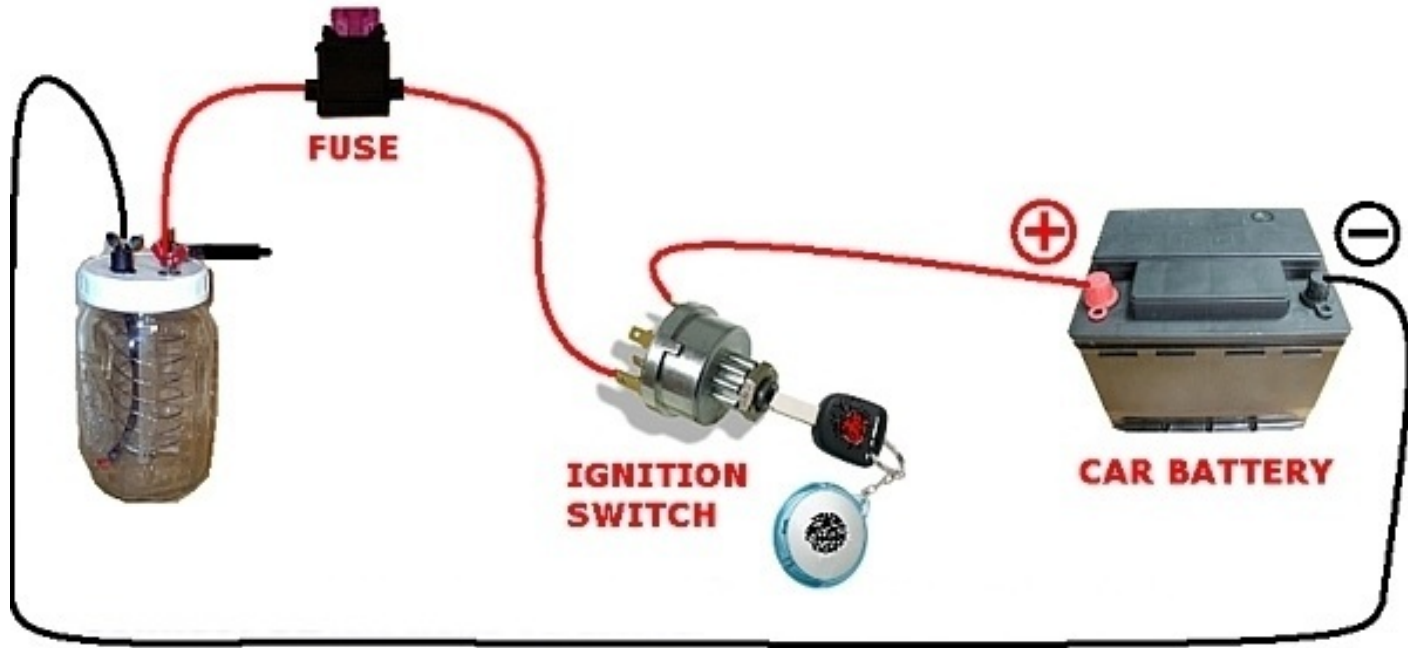

Electrical systems are called electrical circuits

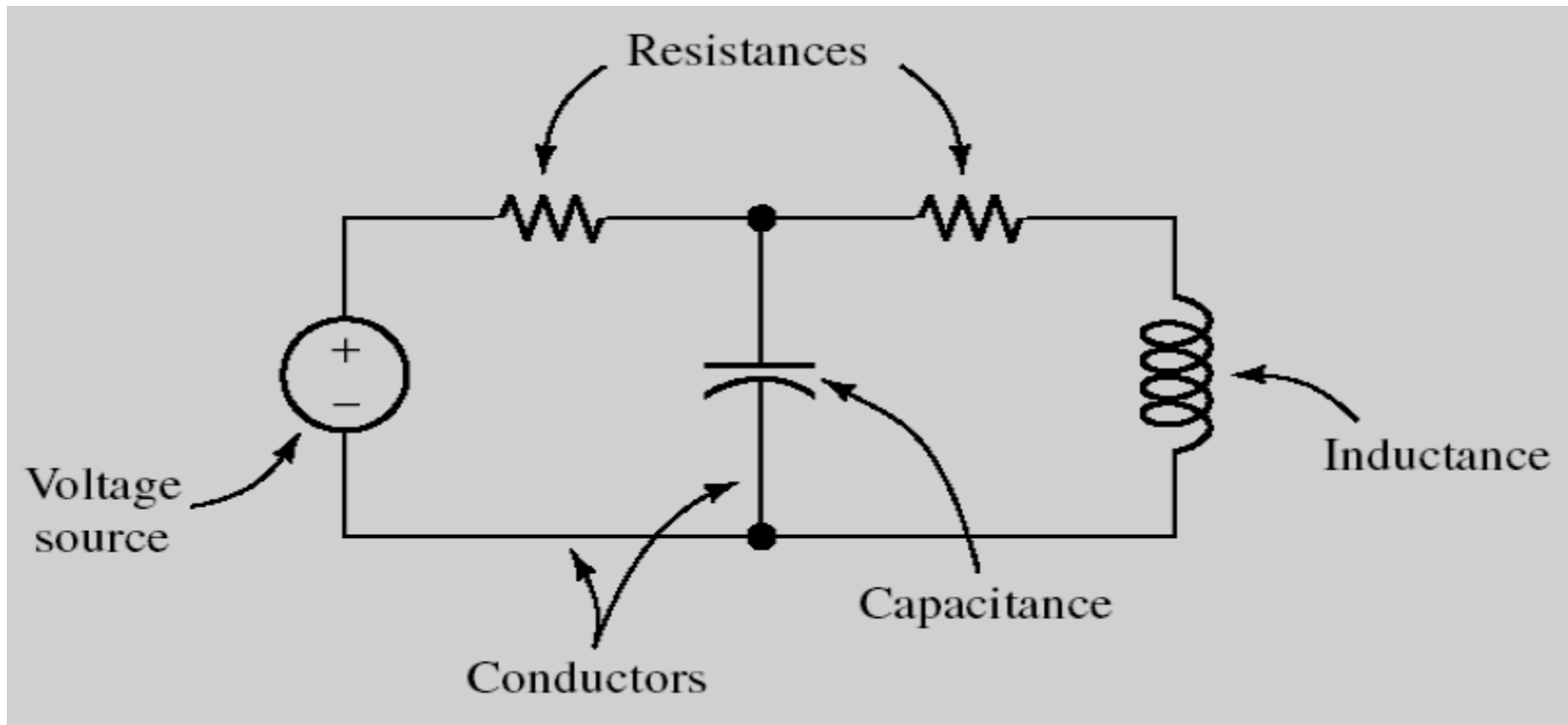
# Electrical Circuit

Connection of several circuit elements in closed paths by conductors



Before we learn how to analyze and design circuits, we must become familiar with some basic circuit elements.

# Resistance

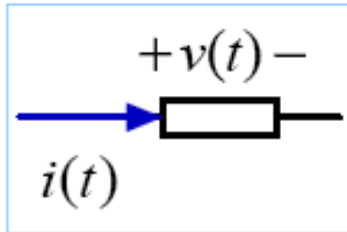

$$v(t) = R \times i(t)$$

Ohm's law

The constant,  $R$ , is called the resistance of the component and is measured in units of Ohm ( $\Omega$ )

Standard Multiples of Ohm

$M\Omega$  Mega Ohm ( $10^6 \Omega$ )


$k\Omega$  Kilo Ohm ( $10^3 \Omega$ )

Resistor Symbol:



Georg Simon Ohm  
1789-1854

# Conductance

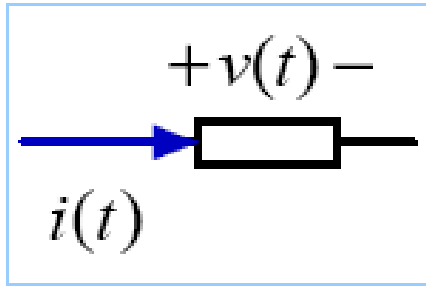

$$v(t) = R \times i(t)$$


$$i(t) = \frac{v(t)}{R} = G \times v(t)$$

$G = 1/R$  is called conductance and its unit is Siemens (S)




Ernst Werner von Siemens  
1816-1892

## Two special resistor values

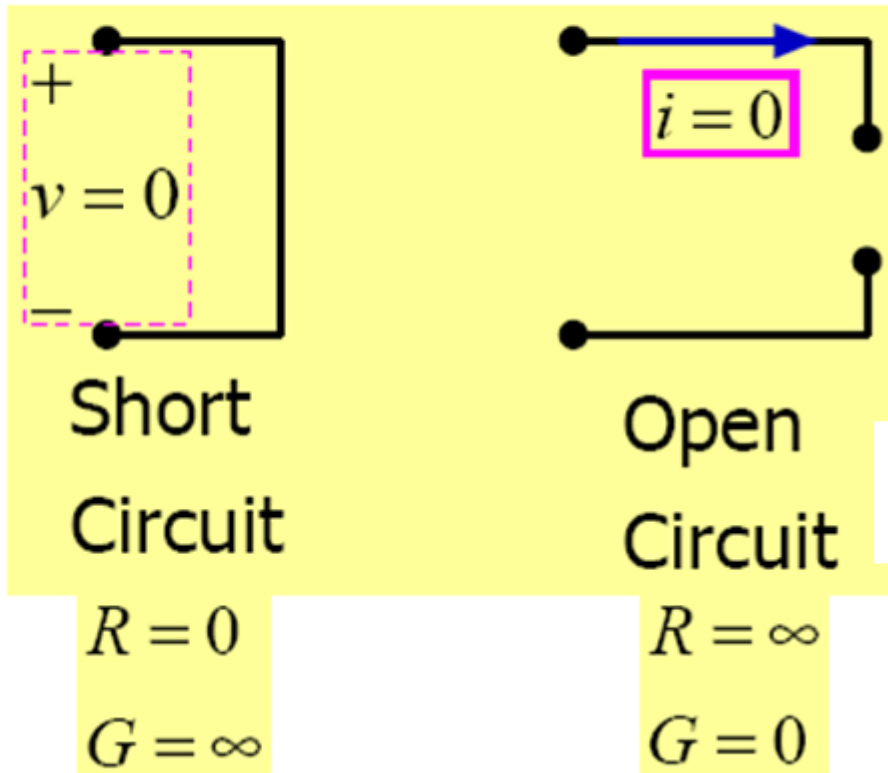

$$R = \frac{v}{i}$$
$$G = \frac{i}{v}$$
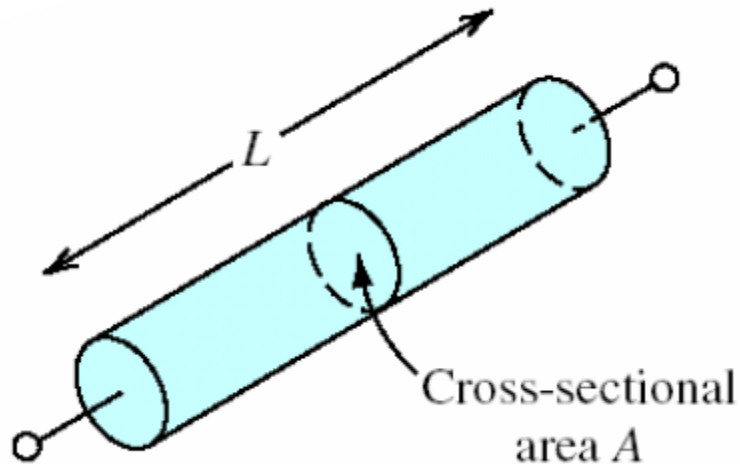
# Resistance Related to Physical Parameters



$$R = \rho \times \frac{L}{A}$$


Resistance is affected by the **dimensions** and **geometry** of the resistor as well as the **particular material** used

$\rho$  is the resistivity of the material in ohm meters [ $\Omega\cdot\text{m}$ ]

- Conductors (Aluminum, Carbon, Copper, Gold)
- Insulators (Glass, Teflon)
- Semiconductors (Silicon)




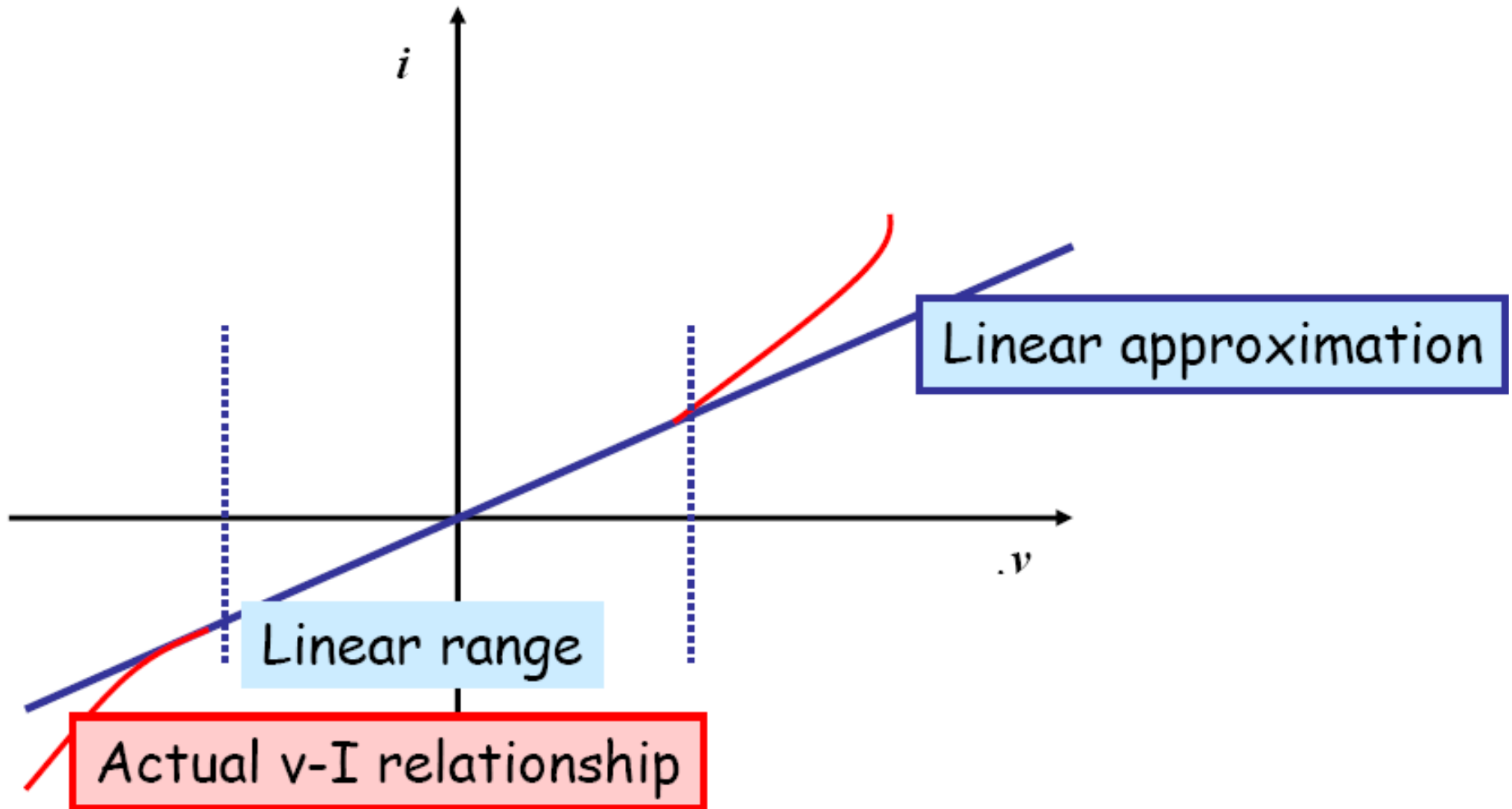Any electrical element which obeys ohms law can be modeled as a resistor




Can we model an electric bulb as a resistor?

# Electrical Bulb

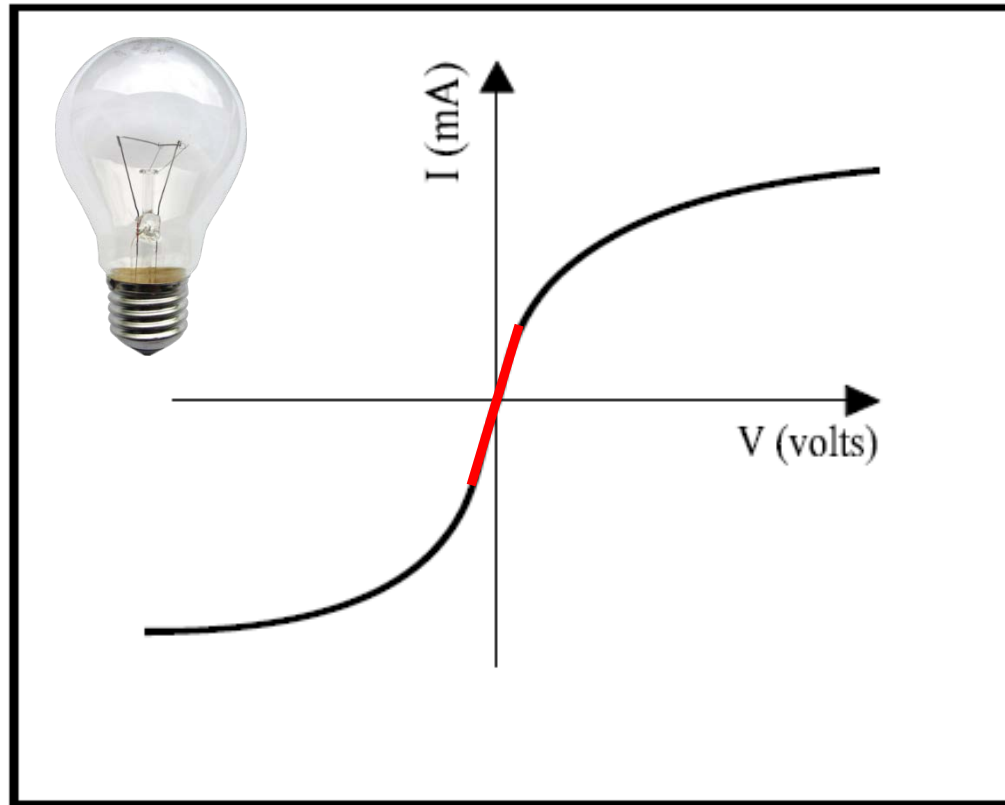


Even though characteristics are non-linear, over a certain range, the bulb can be thought of as a **resistor**

# Power and Energy

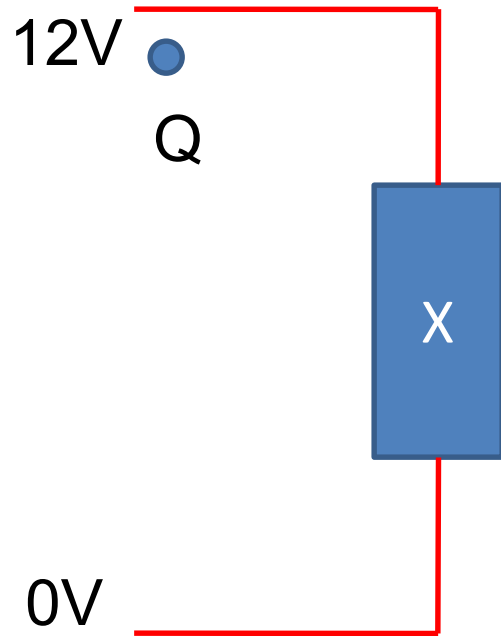

The charge loses energy =  $Q \times 12$  Joules

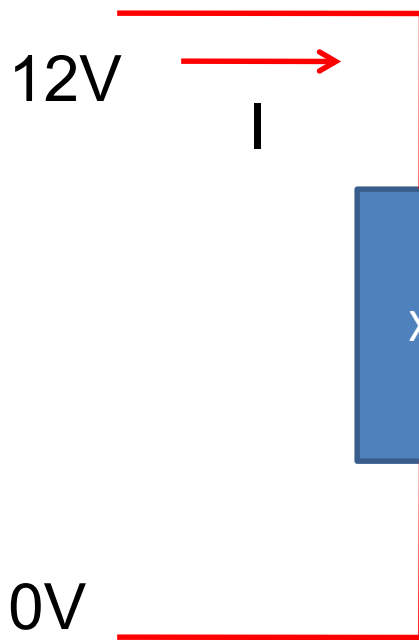This energy is taken from the voltage source and delivered to the circuit element



$$I = \frac{Q}{t}$$

$$Q = I \times t$$

In 1 second, charge equal to  $Q = I$  flows through the element X

Every time a charge  $q$  goes from 12V to 0V it transfers energy  $q \times 12$  J to the element X

Total Energy transferred in 1 second =  $I \times 12$  J

Power = Energy/time

$$P = I \times 12 \text{ Watts}$$

Joules/second = watts

$$P = I \times V$$

A charge of 1 coulomb receives or delivers an energy of 1 joule in moving through a voltage of 1 volt.


$$v = \frac{dw}{dq}$$

$$i = \frac{dq}{dt}$$

$$P(t) = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} = v(t) i(t)$$

$$P(t) = \frac{dw}{dt} \Rightarrow w = \int_{t1}^{t2} p(t) dt$$

# Power

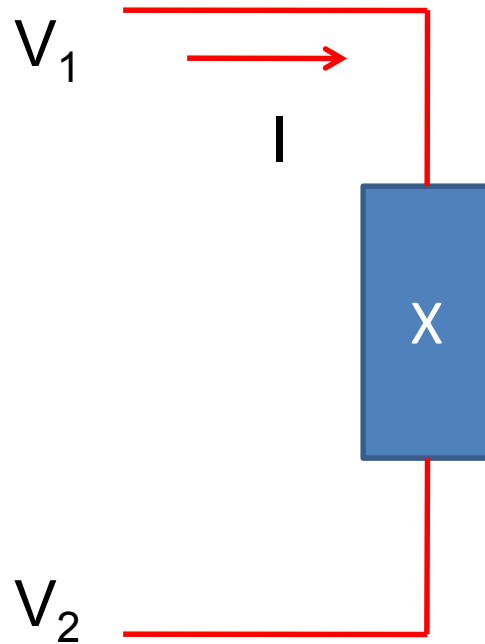


$$P = (V_1 - V_2) \times I$$

If  $V_1 > V_2$  then  $P$  is positive and it means that power is being delivered to the electrical element  $X$


If  $V_1 < V_2$  then  $P$  is negative and it means that power is being extracted from the electrical element  $X$ .

**$X$  is a source of power !**

# Note on direction of current

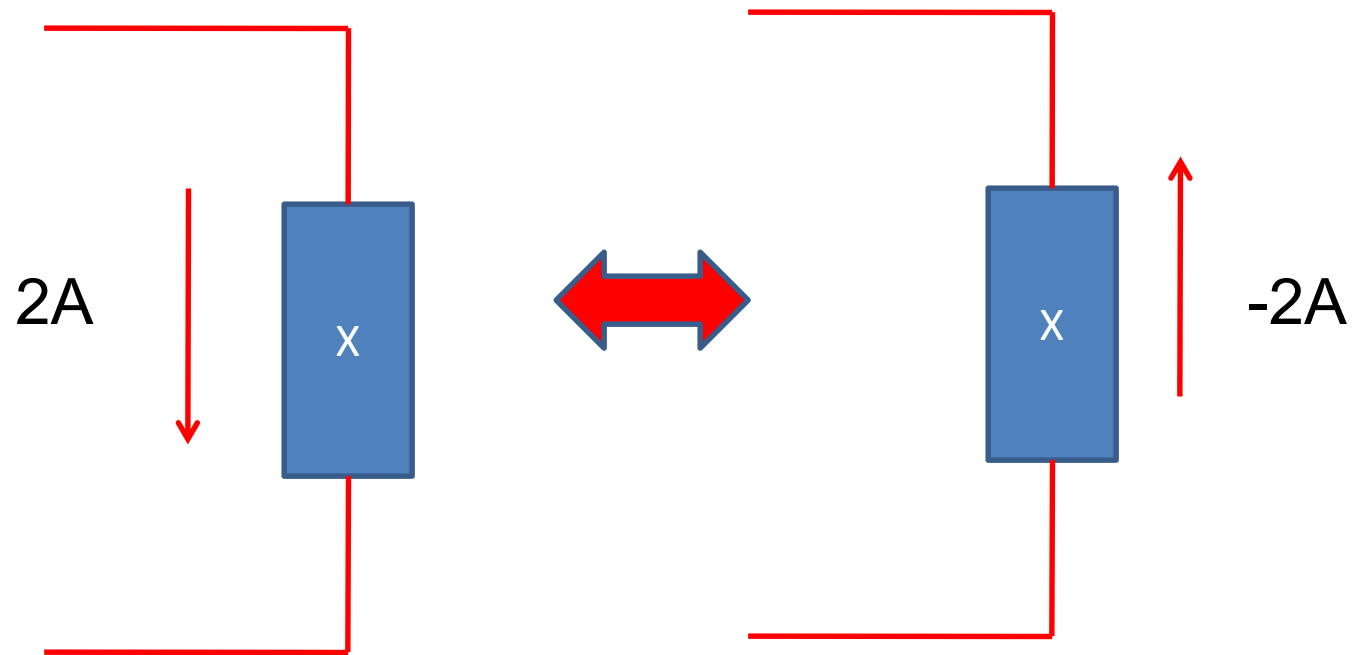


# Examples

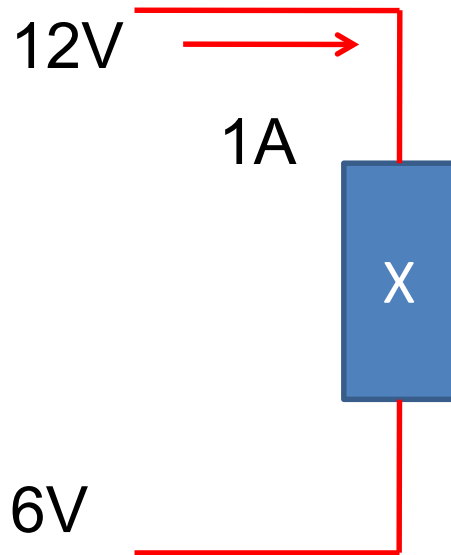

$$P = ?$$
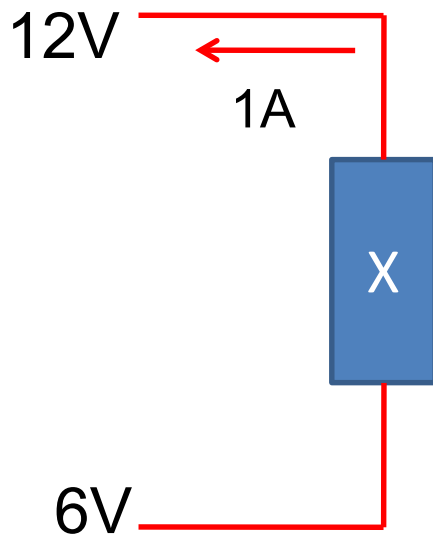
$$\begin{aligned} P &= (V_1 - V_2) \times I \\ &= (12 - 6) \times 1 = 6W \end{aligned}$$




$$P = ?$$

$$\begin{aligned} P &= (V_1 - V_2) \times I \\ &= (12 - 6) \times -1 = -6W \end{aligned}$$

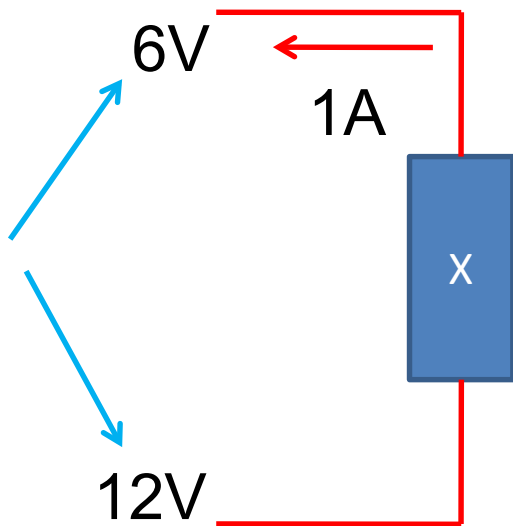Power is supplied by element X instead of dissipation






$P = ?$

$$\begin{aligned} P &= (V_1 - V_2) \times I \\ &= (6 - 12) \times -1 = 6W \end{aligned}$$

power is being delivered to the electrical element X

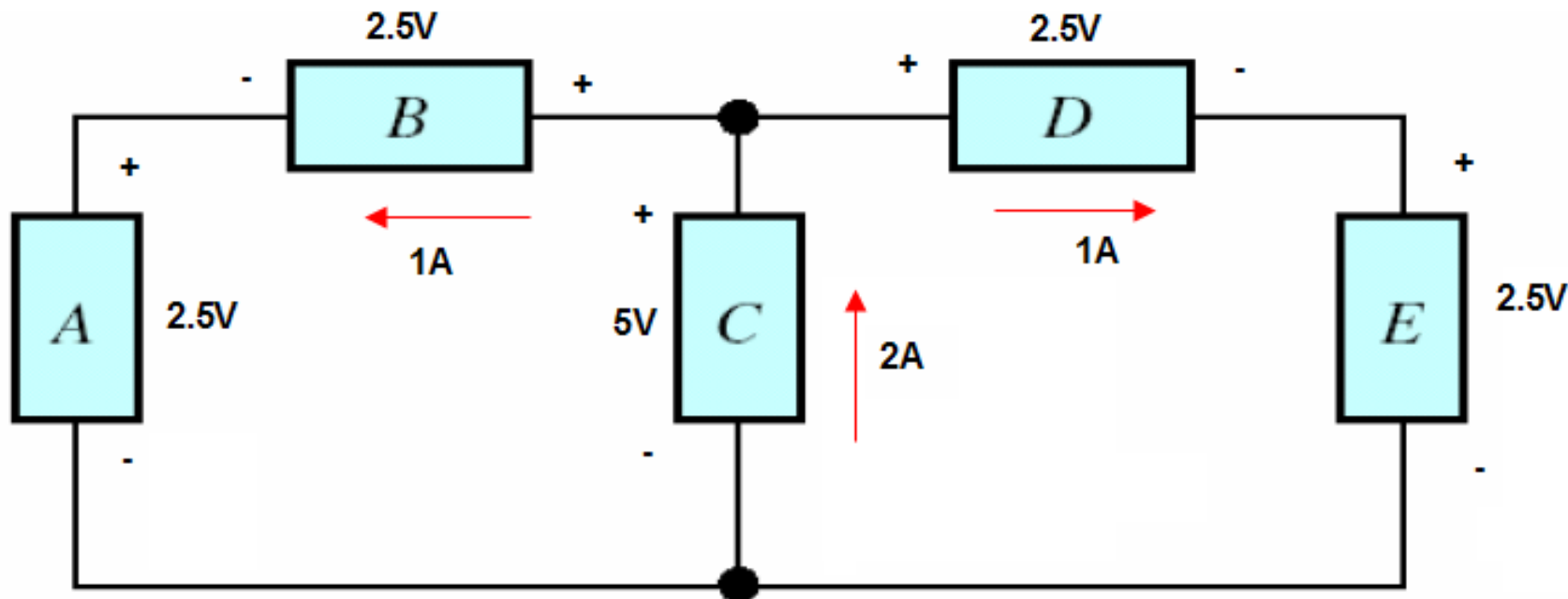
There is only one battery in the circuit. Can you find which element is a battery?



A battery is a source of power, so Power dissipated is negative

Answer is C

# Power dissipated in a Resistor

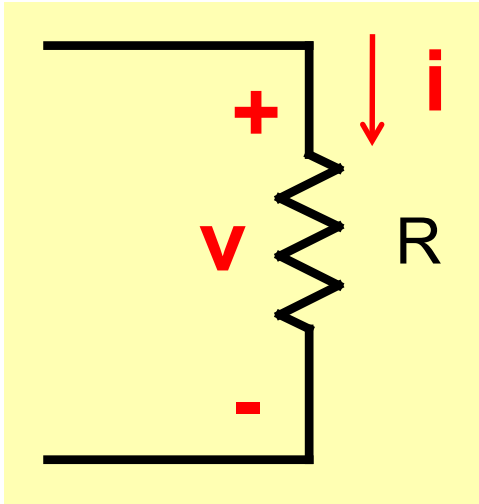

$$v = i \times R$$


$$i = \frac{v}{R}$$

$$P = v \times i$$

$$P = i^2 \times R$$

$$P = \frac{v^2}{R}$$

# Circuit Analysis



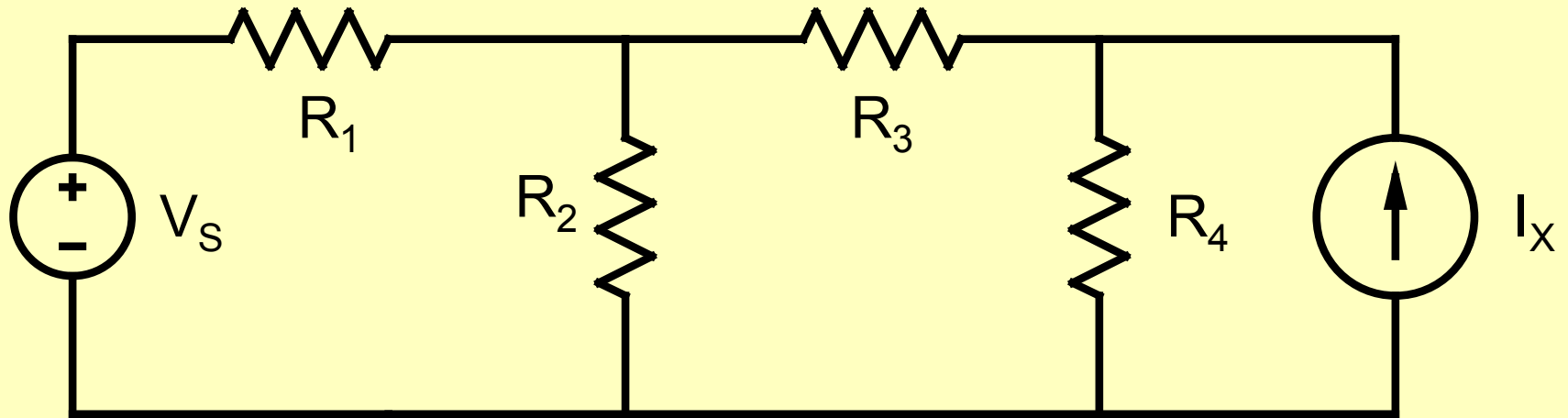


What is current in  $R_2$  ?

Procedure:

Use Kirchhoff's voltage law (KVL) and Kirchhoff's Current law (KCL) to transform the circuit into a set of equations whose solution gives the required voltage or current value


# Engineering Analysis

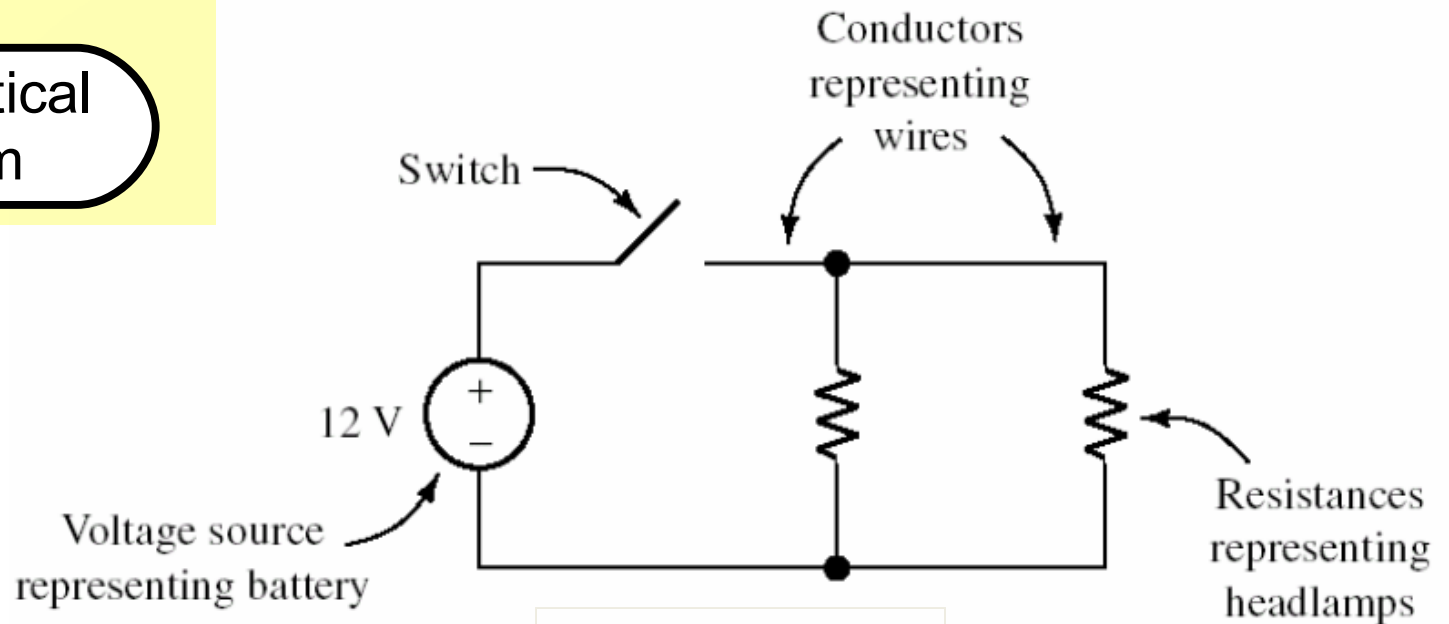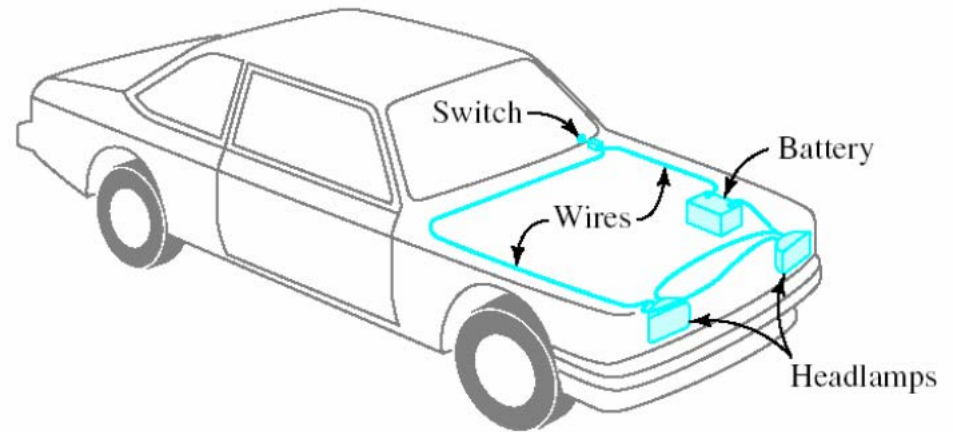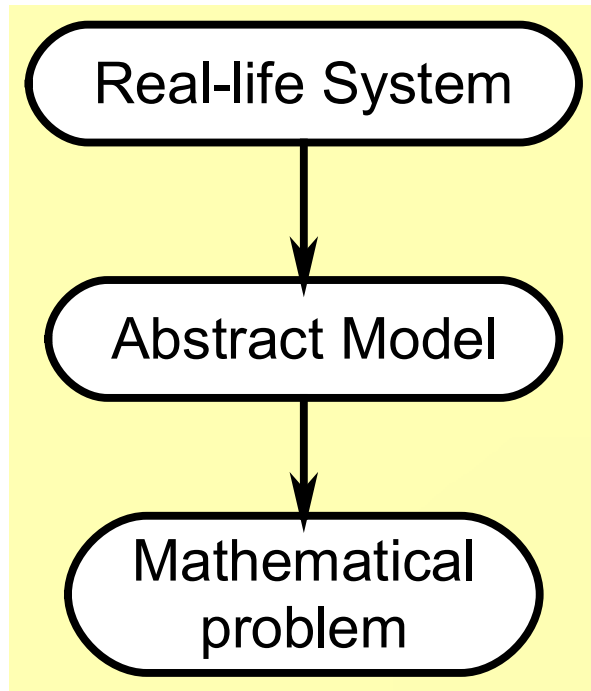


$$P = \frac{v^2}{R_1} + \frac{v^2}{R_2}$$
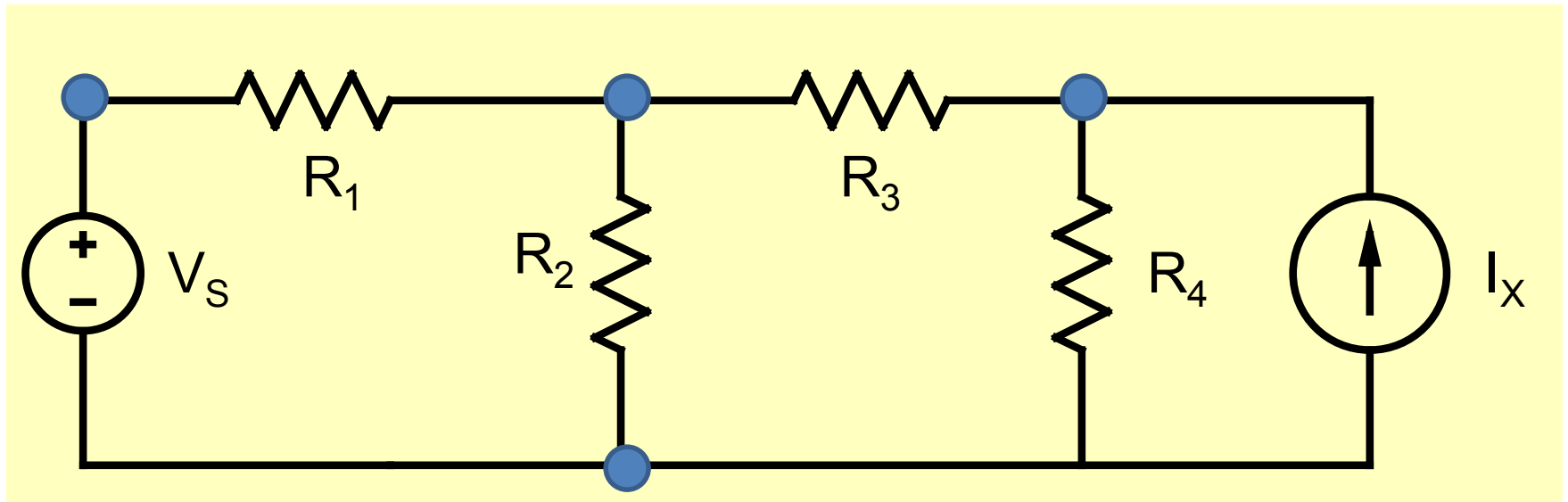
# Nodes and loops

**Node:** A point where 2 or more circuit elements are connected.



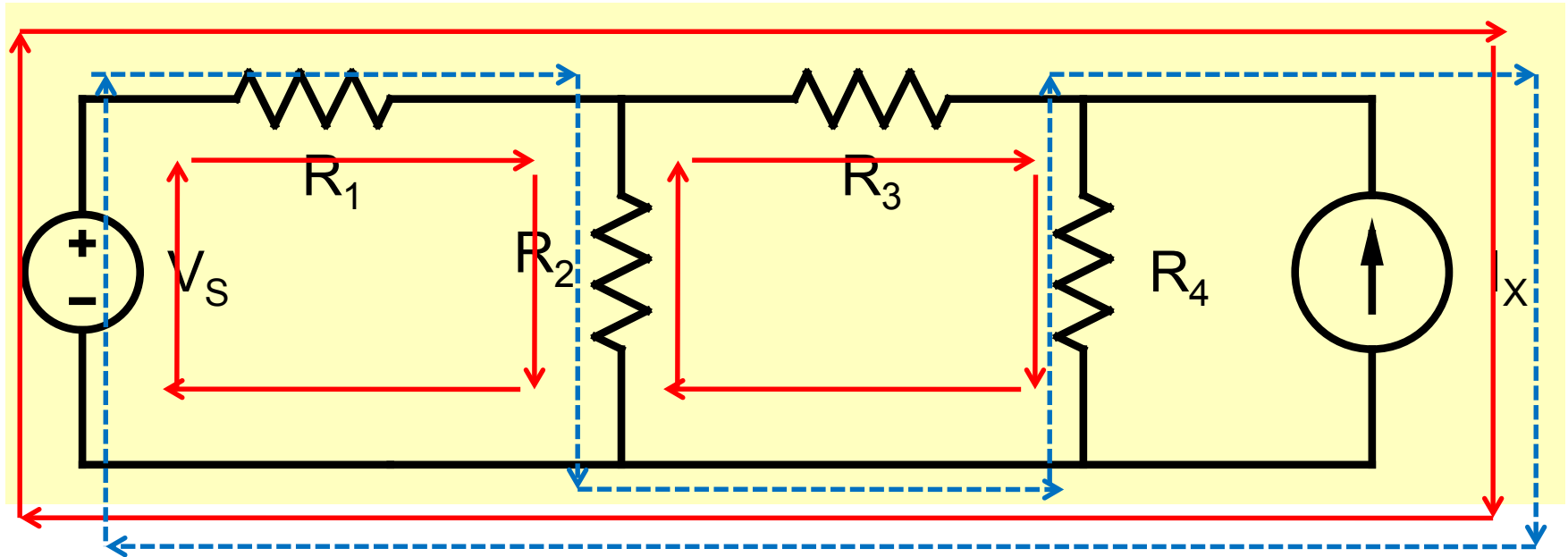
A **loop is formed by tracing a closed path** through circuit elements without passing through any intermediate node more than once



This is not a valid loop !
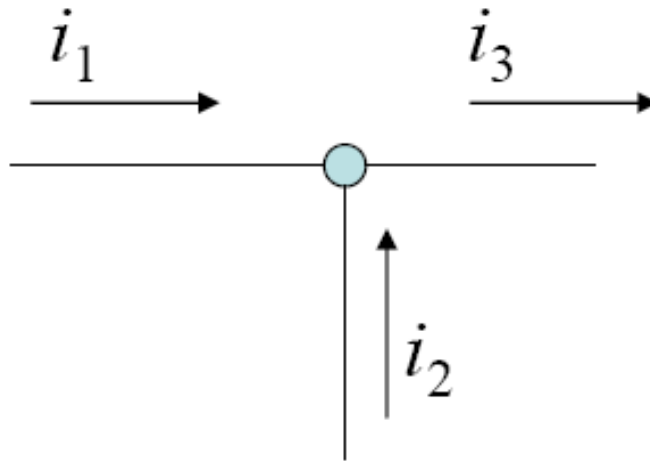
# Kirchhoff's Current Law (KCL)

Sum of currents entering a node is equal to sum of currents leaving a node



$$i_1 + i_2 = i_3$$




# Kirchhoff's Current Law (KCL)


Net current entering a node is zero

$$\sum_{j=1}^N i_j = 0$$

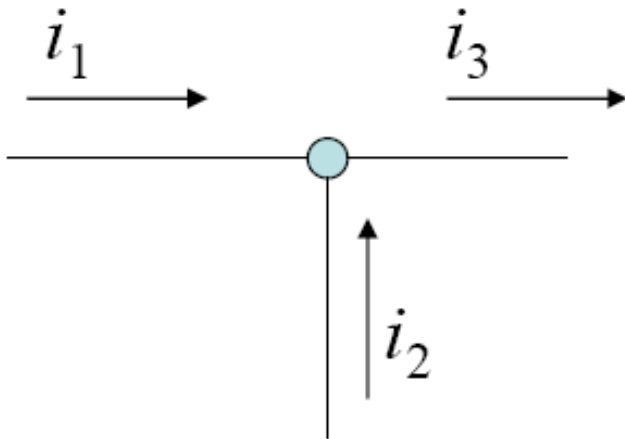
Current entering a node is considered positive and current leaving a node is considered as negative



$$i_1 + i_2 - i_3 = 0$$

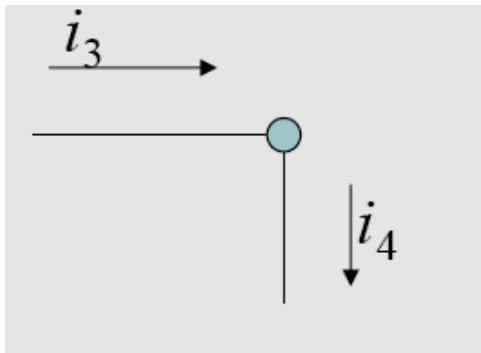


$$i_3 = i_4$$

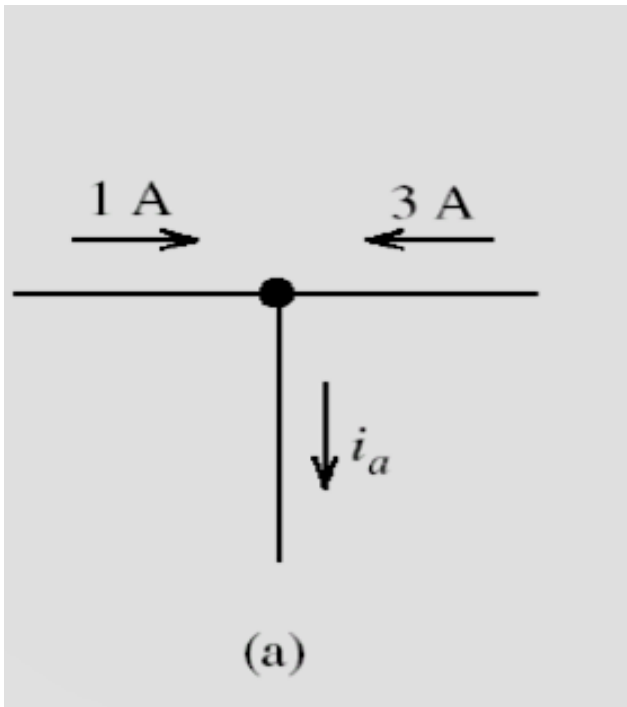


$$1 + 3 - i_a = 0$$

$$i_a = 4A$$

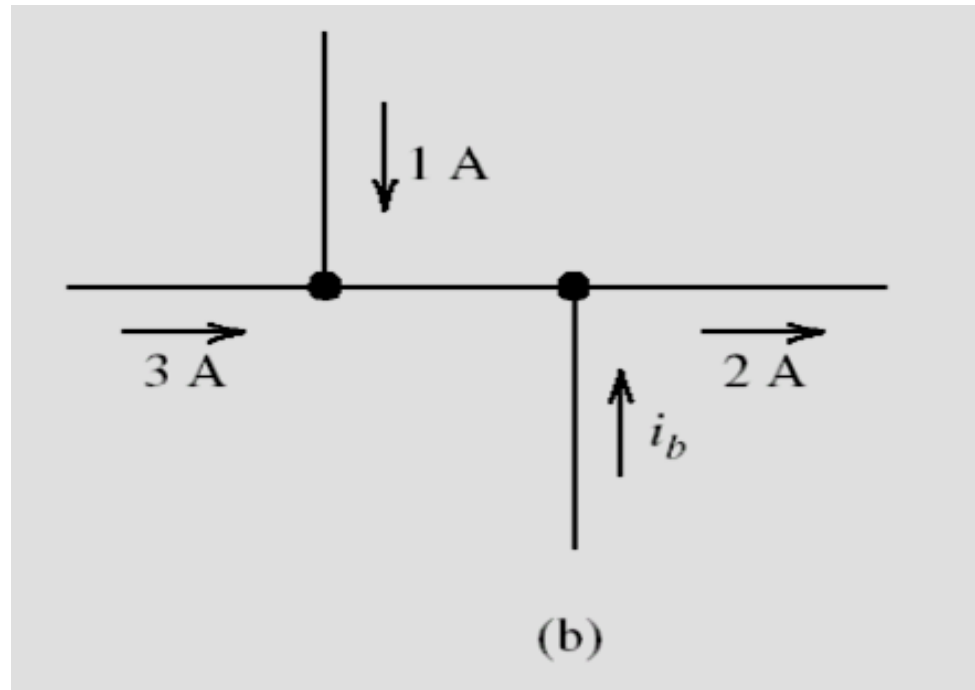

$$1 + 3 + i_b - 2 = 0$$

$$i_b = -2A$$

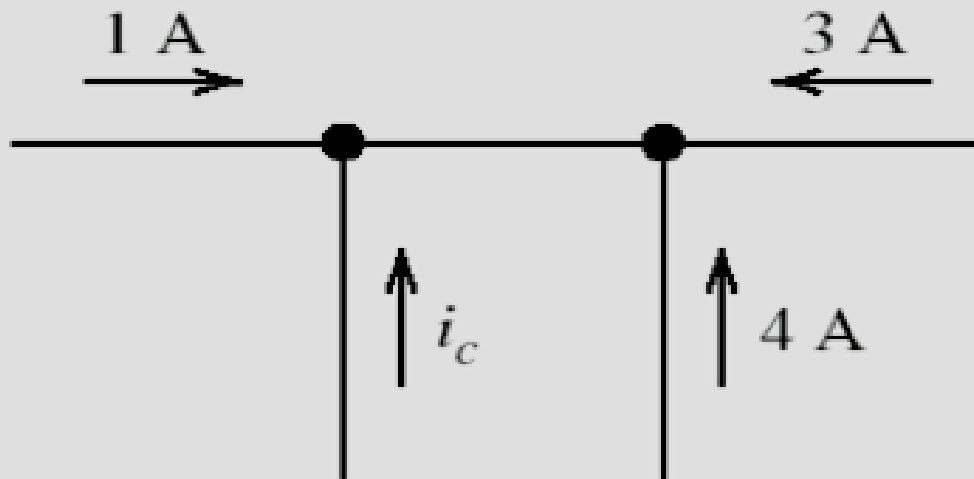


(c)

$$1 + 3 + i_c + 4 = 0$$


$$i_c = -8 A$$

# Example

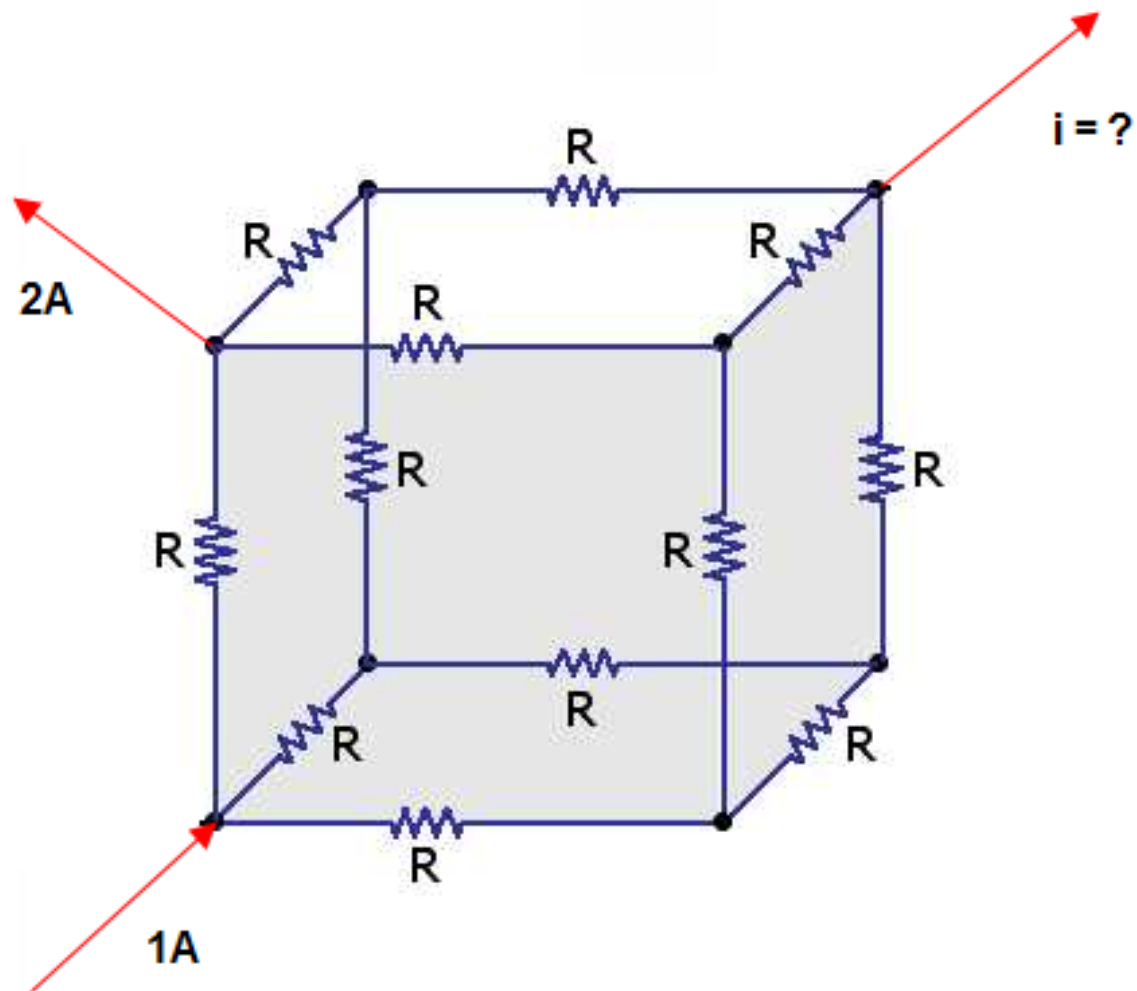
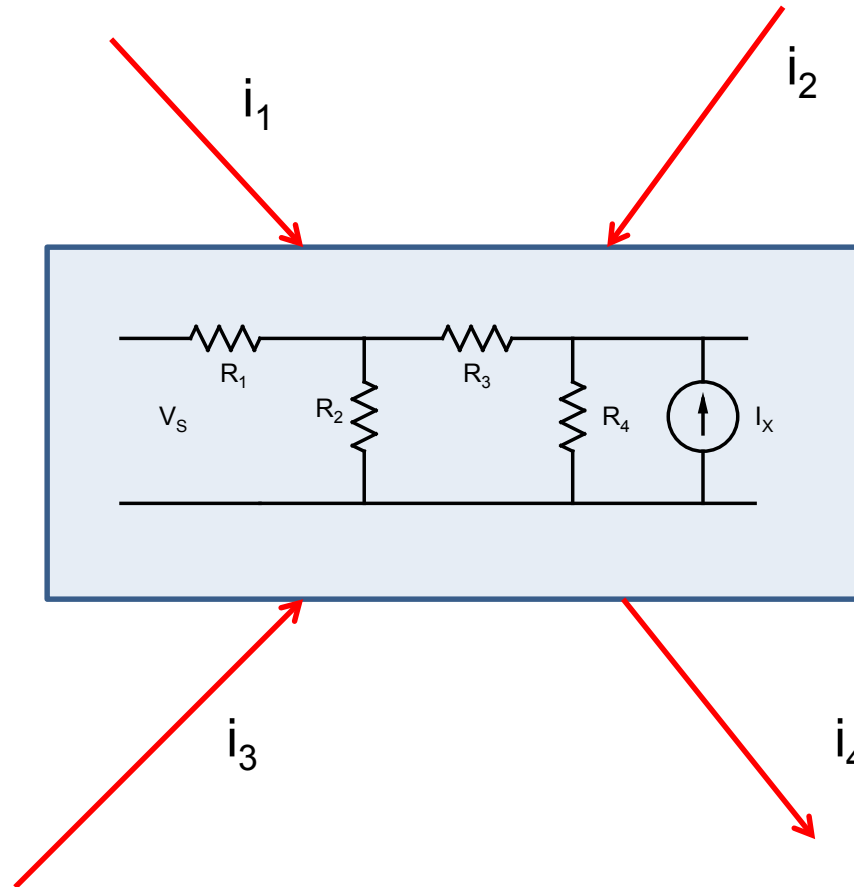
# KCL: More general formulation


The sum of currents entering/leaving a **closed surface** is zero.



$$i_1 + i_2 + i_3 - i_4 = 0$$
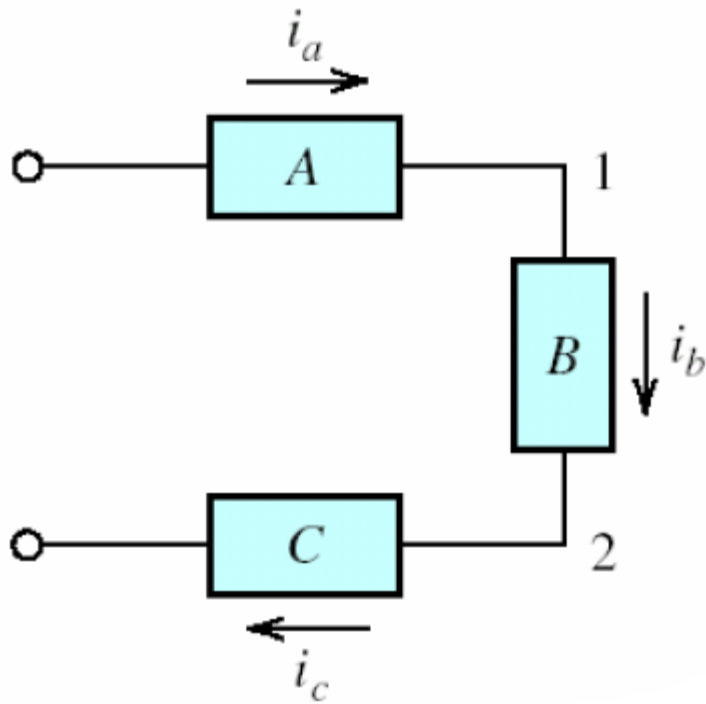
# Series Circuit

Two elements are connected in series if there is no other element connected to the node joining them




A, B and C are in series

The elements have the same current going through them

$$i_a = i_b = i_c$$
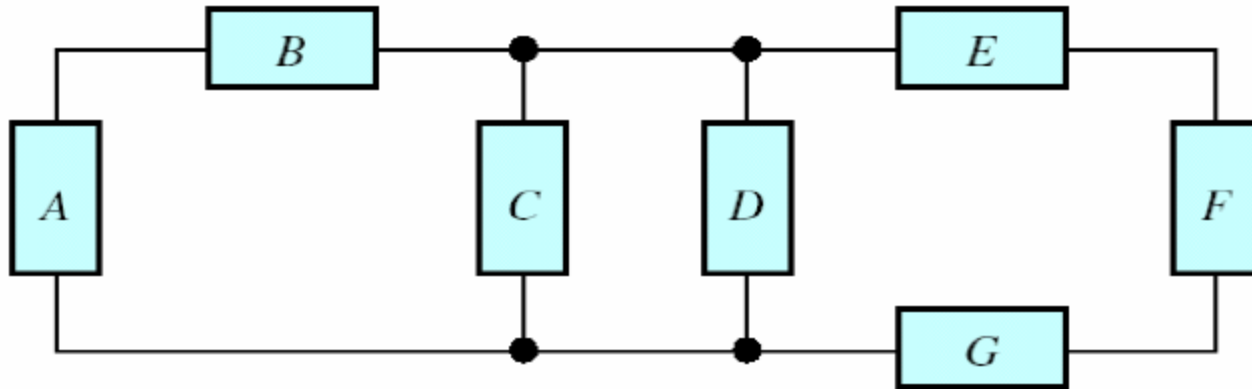
## Example:

Identify the groups of elements connected in series




A and B are in series

E, F and G are in series
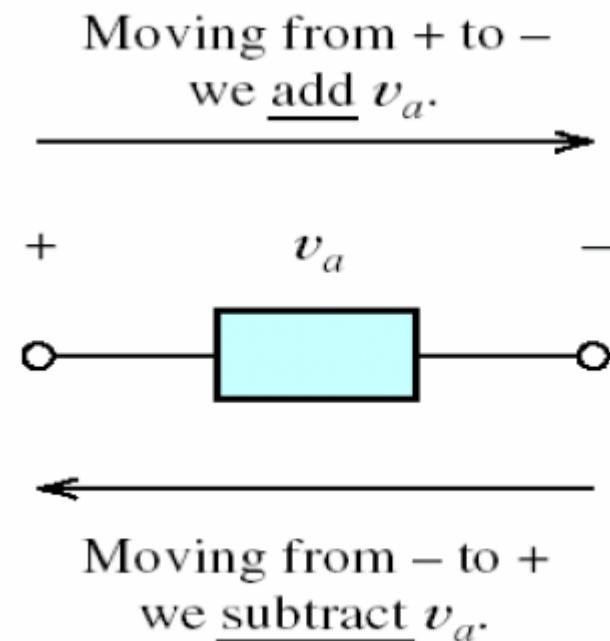
# Kirchhoff's Voltage Law (KVL)


The algebraic sum of the voltages equals zero for any closed path (loop) in an electrical circuit

In applying KVL to a loop, voltages are added or subtracted depending on their reference polarities relative to the direction of travel around the loop.





# Example

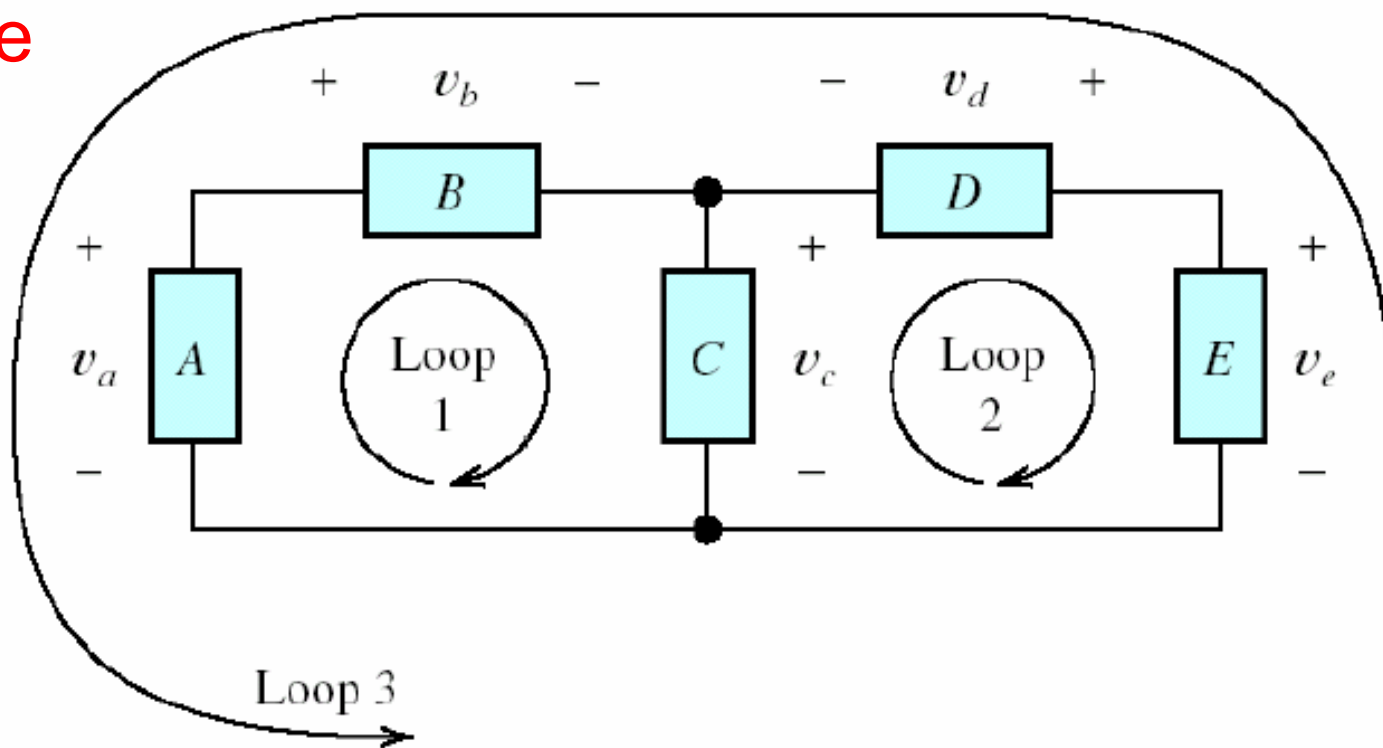


$$\text{Loop 1: } -v_a + v_b + v_c = 0$$

$$\text{Loop 2: } -v_c - v_d + v_e = 0$$

$$\text{Loop 3: } -v_e + v_d - v_b + v_a = 0$$

# KVL and Conservation of Energy

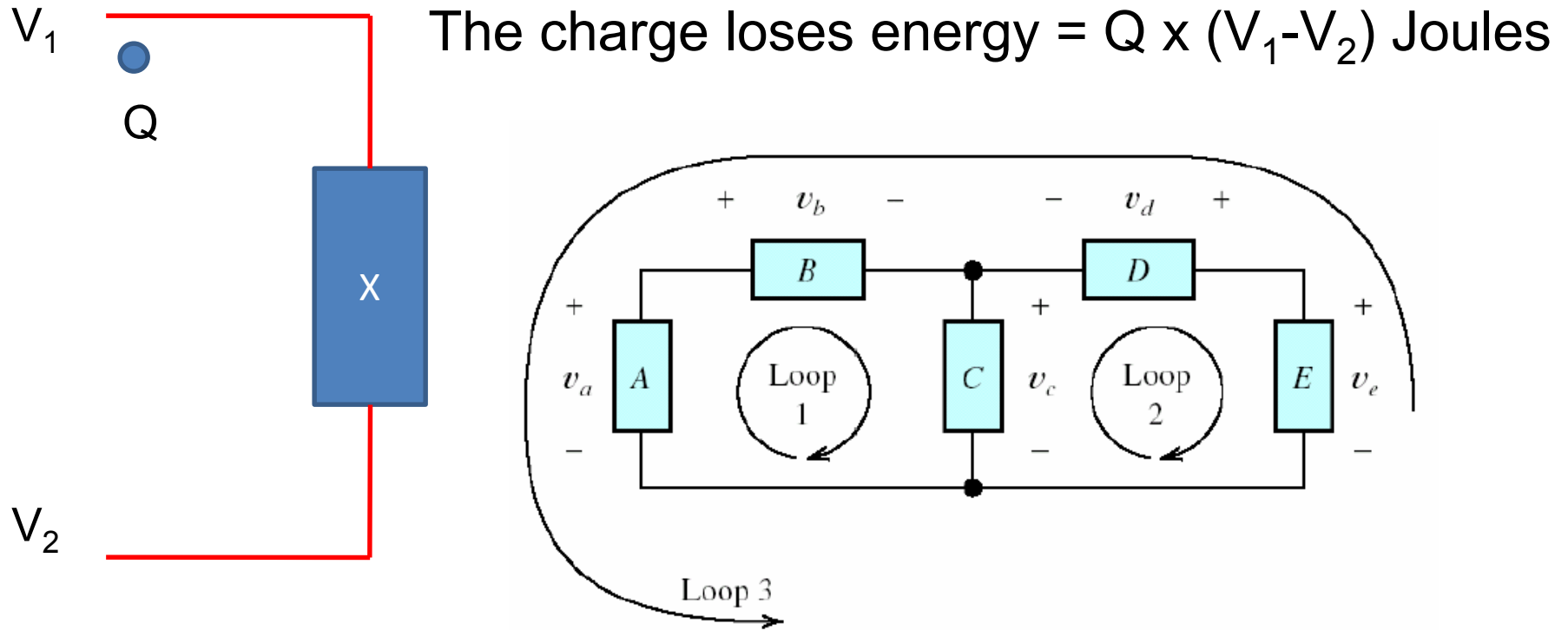

$$\text{Loop 1: } -v_a + v_b + v_c = 0$$


Energy gained

Energy lost

**KVL: law of conservation of Energy**
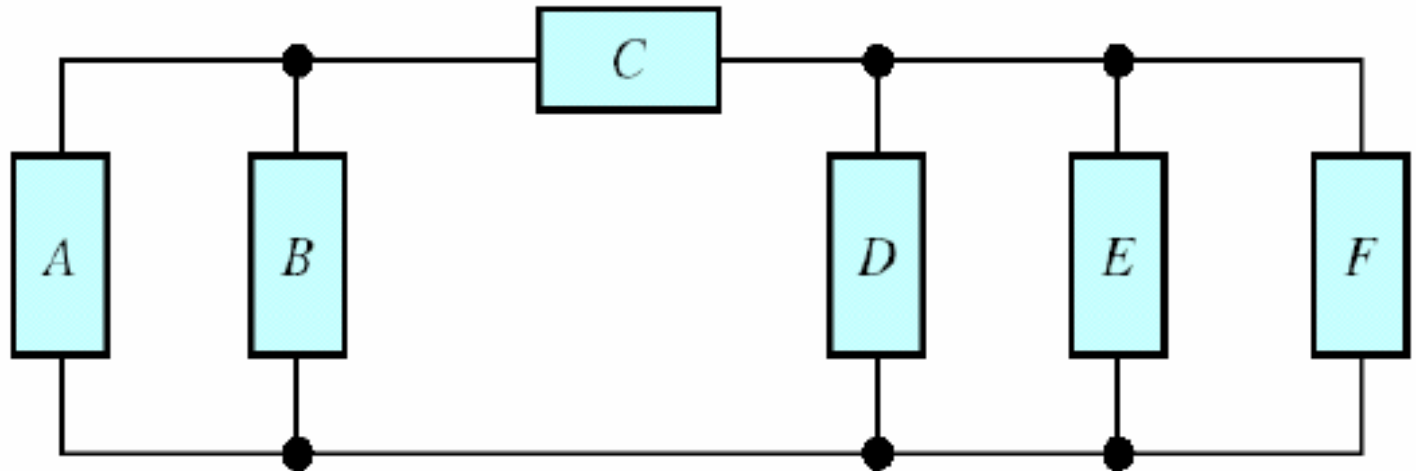
# Parallel Circuits


Two elements are connected in parallel if both ends of one element are connected directly to corresponding ends of the other



*A* and *B* are connected in parallel

*D*, *E* and *F* are connected in parallel

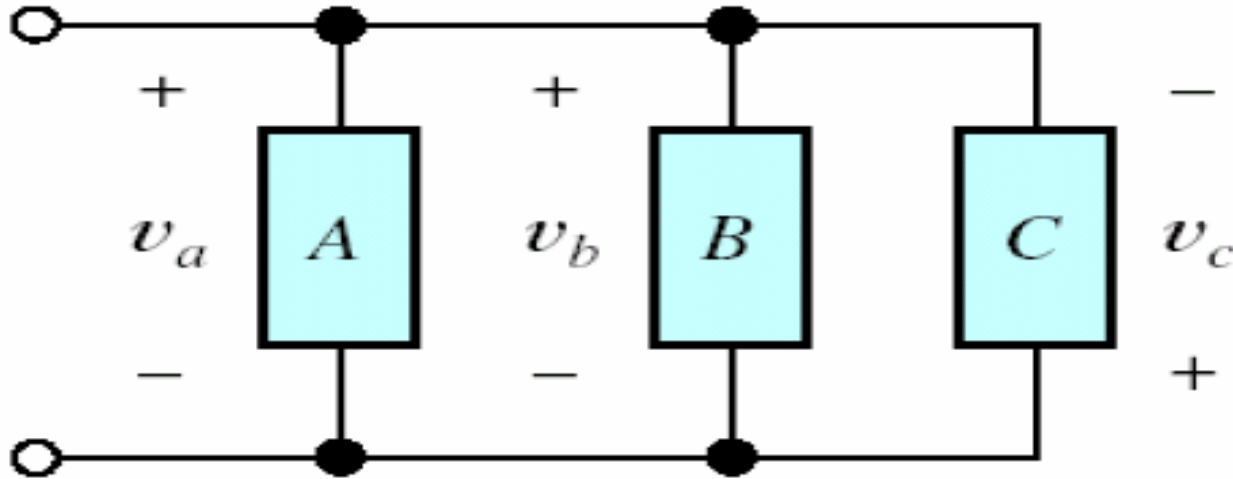
The voltage across parallel elements are equal (both **magnitude and polarity**)



$$v_a = v_b = -v_c$$

## Example

Use KVL to find  $v_c$  and  $v_e$

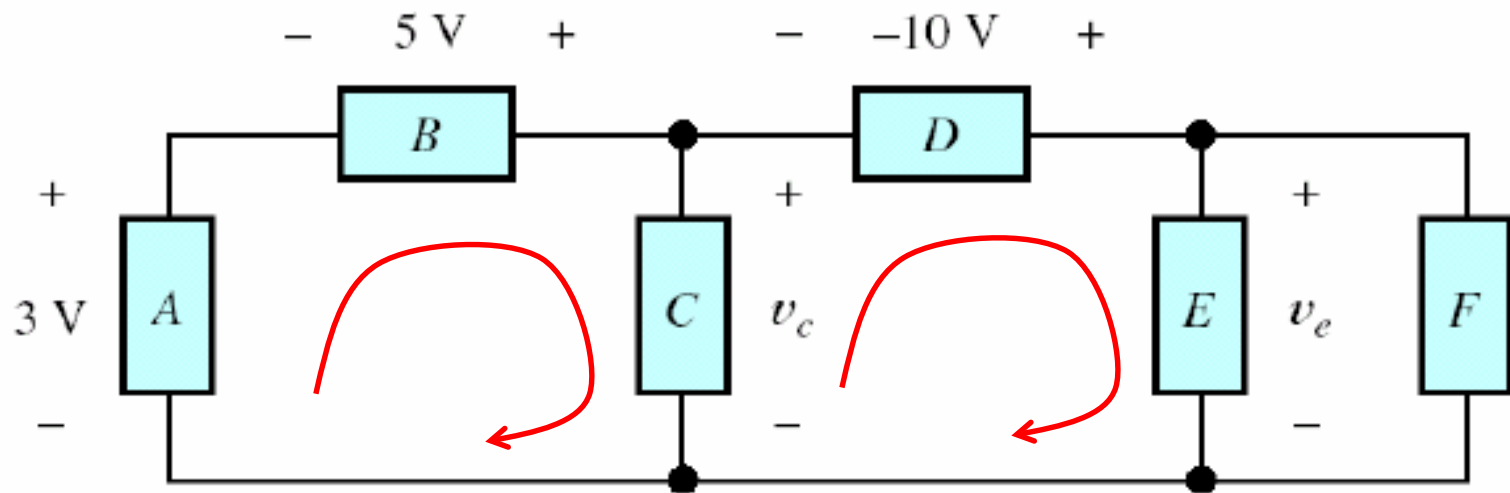


$$-3 - 5 + v_c = 0 \Rightarrow v_c = 8V$$

$$-v_c - (-10) + v_e = 0 \Rightarrow v_e = -2V$$

Use KVL , KCL and Ohm's law to solve the given problem

Find  $V_x$

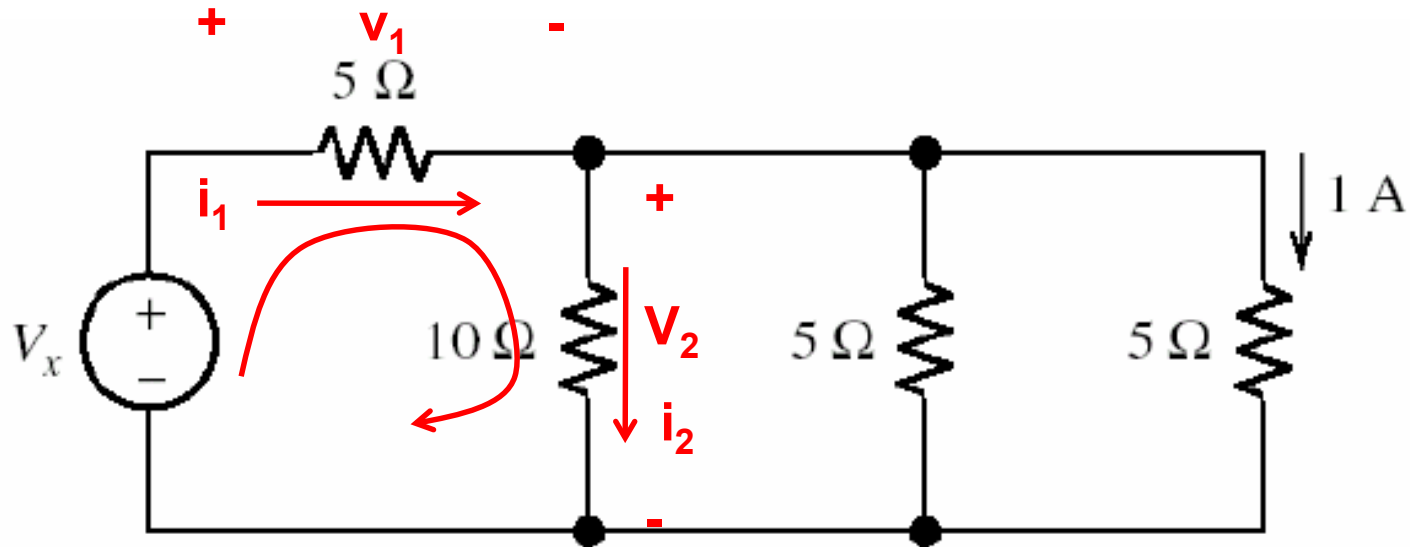


$$-v_x + v_1 + v_2 = 0 \Rightarrow v_x = v_1 + v_2$$

$$v_1 = i_1 \times 5$$

$$v_2 = i_2 \times 10$$

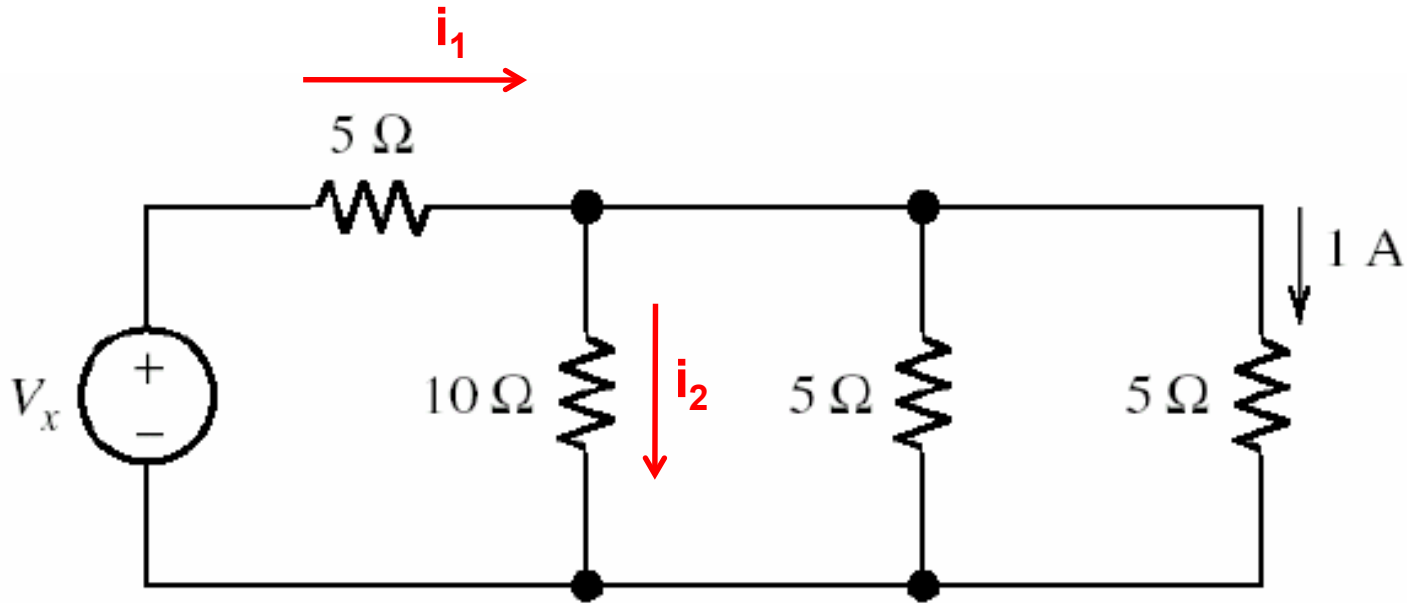**Next Problem:** Find currents  $i_1$  and  $i_2$




$$v_x = v_1 + v_2$$

$$v_1 = i_1 \times 5$$

$$v_2 = i_2 \times 10$$

$$v_x = (i_1 + 2i_2) \times 5$$

Use ohm's law :  $v = I \times R$

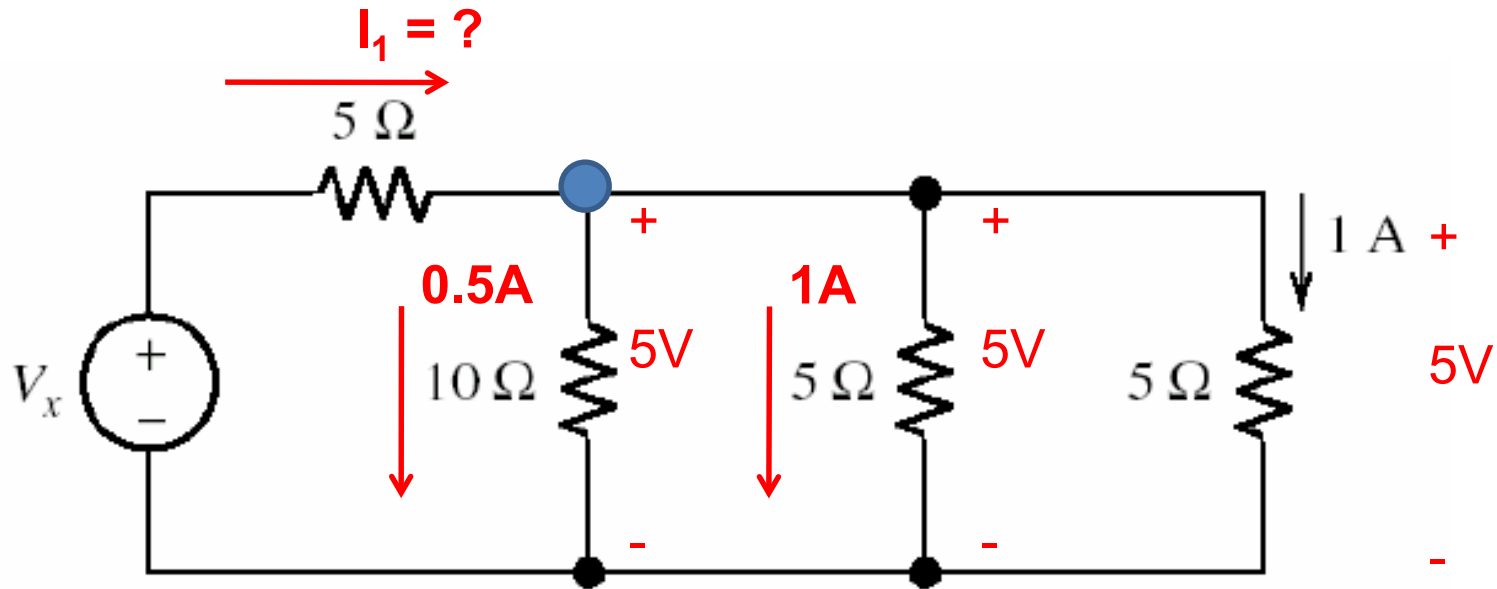

Apply KCL at the indicated node



$$i_1 - 0.5 - 1 - 1 = 0 \Rightarrow i_1 = 2.5 A$$

$$v_1 = i_1 \times 5 = 12.5 V$$


$$v_x = v_1 + v_2 = 12.5 + 5 = 17.5 V$$




# Independent Sources

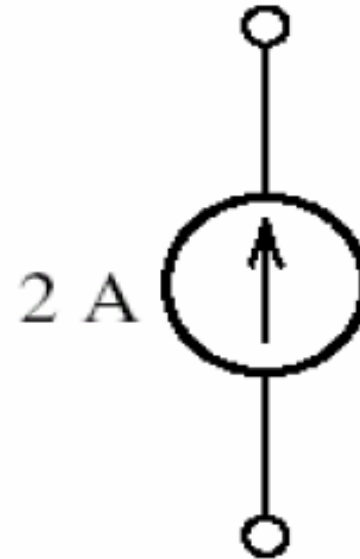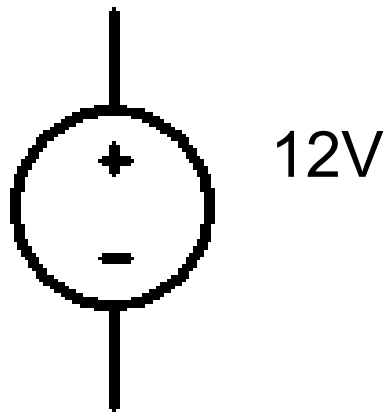

# Dependent (Controlled) Voltage Sources

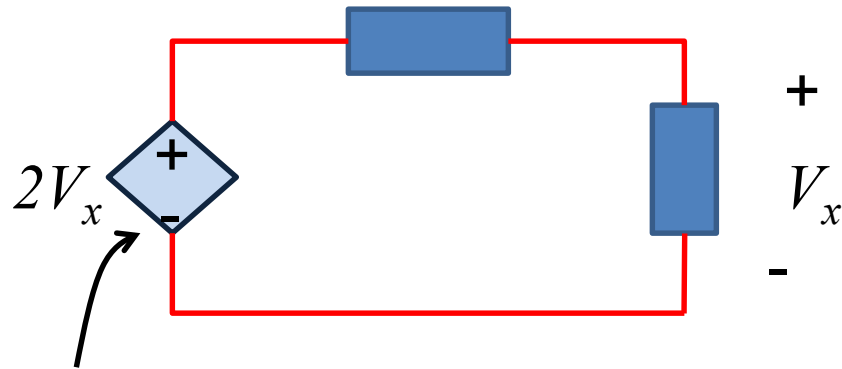

Voltage-controlled  
Voltage source

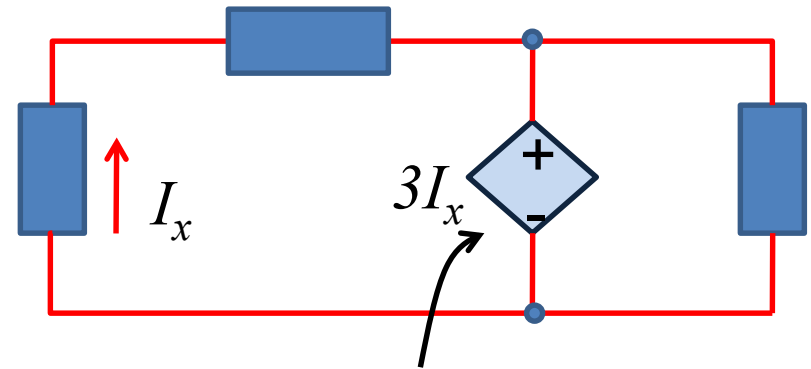


Current-controlled  
Voltage source

❑ Very useful in constructing circuit models for real-world devices such as transistors and amplifiers


❑ For a **voltage controlled source**:  $V = K_1 V_x$ ,  
 $K_1$  is a gain parameter with no units

❑ For a **current controlled source**:  $V = K_2 I_x$ ,  
 $K_2$  is a gain parameter with units [V/A]
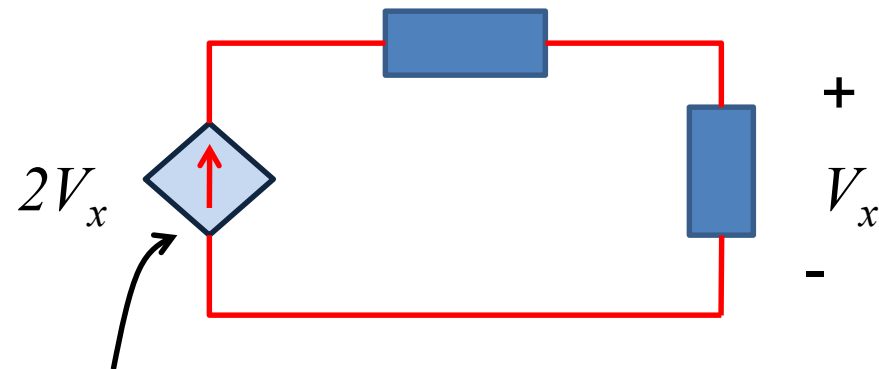
# Dependent (Controlled ) Current Sources



Voltage-controlled  
current source

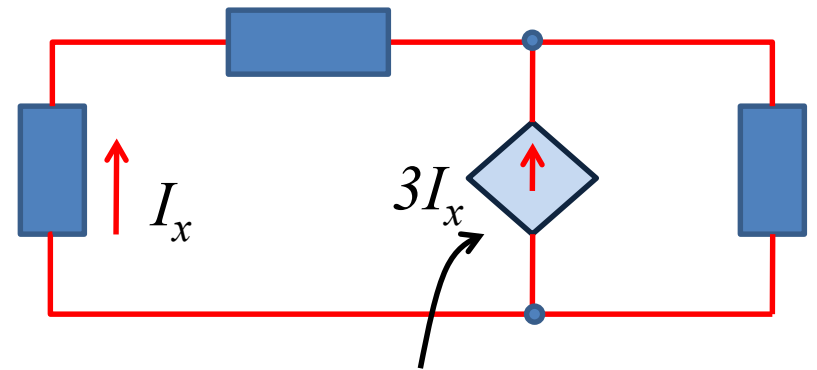

Current-controlled  
current source


❑ Very useful in constructing circuit models for real-world devices such as transistors and amplifiers

❑ For a **voltage controlled source**:  $I = K_3 V_x$ ,  
 $K_3$  is a gain parameter with units [A/V]

❑ For a **current controlled source**:  $I = K_4 I_x$ ,  
 $K_4$  is a gain parameter with no units
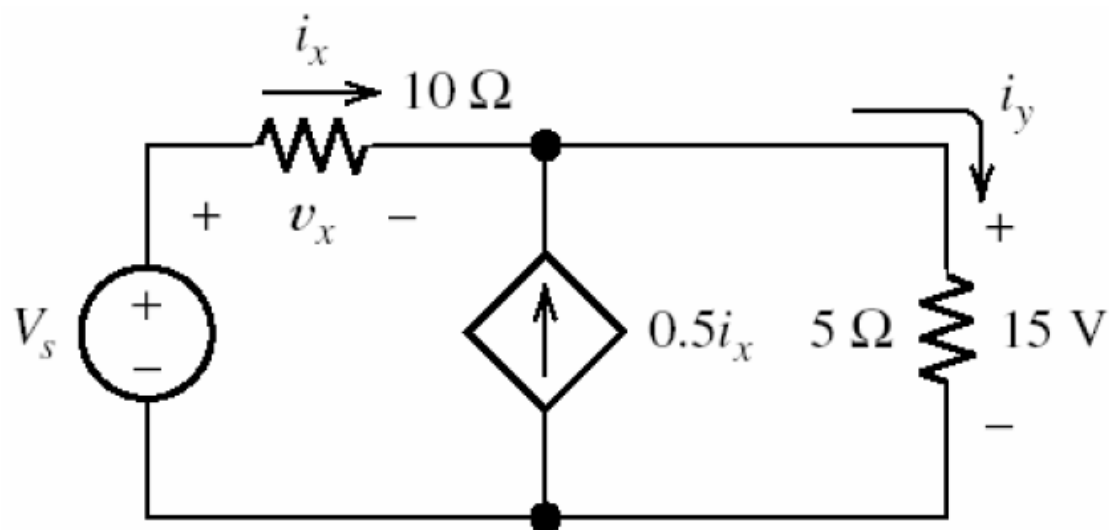
### Example:

Find the source voltage in the following circuit



$$i_y = \frac{15\text{ V}}{5\ \Omega} = 3\text{ A}$$

$$i_x + 0.5i_x = i_y$$

$$i_x = 2\text{ A}$$

$$v_x = 10i_x = 20\text{ V}$$

$$V_s = v_x + 15$$

$$V_s = 35\text{ V}$$


# Summary

**Current:** The time rate of flow of electrical charge  $i(t) = \frac{dq(t)}{dt}$

– The units are amperes (A), which are equivalent to coulombs per second (C/s)

Direction of current flow is opposite to direction of electron flow

**Ohm's law**

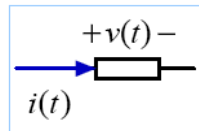


$$v(t) = R \times i(t)$$

$$i(t) = \frac{v(t)}{R} = G \times v(t)$$

$$P = i^2 \times R$$


$$P = \frac{v^2}{R}$$

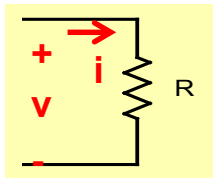

Two elements are connected in series if there is no other element connected to the node joining them. **Same current flows**


Two elements are connected in parallel if both ends of one element are connected directly to corresponding ends of the other.

**Same voltage**

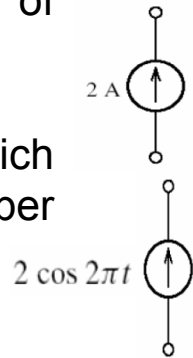


**Voltage difference** is the Source of current flow

Units of Voltage: Volts (V)

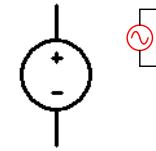

**Power**

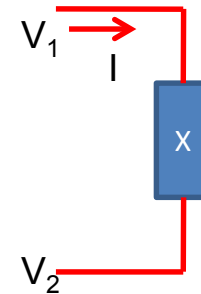


$$P = (V_1 - V_2) \times I$$

$$P(t) = \frac{dw}{dt} \Rightarrow w = \int_{t_1}^{t_2} p(t) dt$$

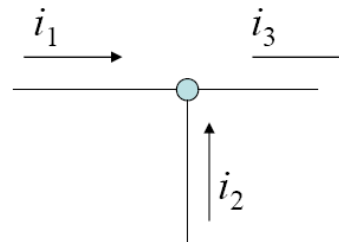**Kirchhoff's Current Law (KCL)**

Sum of currents entering a node is equal to sum of currents leaving a node



$$i_1 + i_2 = i_3$$

**Kirchhoff's Voltage Law (KVL)**

The algebraic sum of the voltages equals zero for any closed path (loop) in an electrical circuit

