


ESc201 : Introduction to Electronics

Sequential Circuit Design -1 Flip Flop / Latch

Dr. Y. S. Chauhan
Dept. of Electrical Engineering
IIT Kanpur


Digital Circuits

Combinational Circuits

 


Output is determined by current values of inputs only.

Sequential Circuits

 

Output is determined in general by current values of inputs and past values of inputs/outputs as well.

NOR SR Latch

 


$Q = 1; \bar{Q} = 0$ Set State

$Q = 0; \bar{Q} = 1$ Reset State



S	R	Q	\bar{Q}	State
1	0	1	0	SET

NOR SR Latch

 


$Q = 1; \bar{Q} = 0$ Set State

$Q = 0; \bar{Q} = 1$ Re set State

  


S	R	Q	\bar{Q}	State
1	0	1	0	SET
0	1	0	1	RESET

HOLD State


 


S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	1	0	1	RESET
0	0	Q	\overline{Q}	HOLD
1	1	0	0	INVALID

 





Both the outputs are well defined and 0.
The first problem is that we do not get complementary output.

  A more serious problem occurs when we switch the latch to the hold state by changing RS from $11 \rightarrow 00$. Suppose the inputs do not change simultaneously and we get the situation $11 \rightarrow 01^* \rightarrow 00$






$Q = 1$

 

   

$Q = 1$

 
 
 
Suppose the inputs change as $RS = 11 \rightarrow 10^* \rightarrow 00$



$Q = 0$

So although output is well defined when we apply $RS = 11$, it becomes unpredictable once we switch the latch to hold state by applying $RS = 00$. That is why $RS = 11$ is not used as an input combination.

 
 
 
The error can occur also due to unequal gate delays.



$Q = 1$


Suppose gate-1 is faster

   On the other hand suppose that gate-2 is faster.




Again the output is unpredictable in general $Q = 0$

NAND Latch

 


S	R	Q	\overline{Q}	State
0	1	1	0	SET
1	0	0	1	RESET
1	1	Q	\overline{Q}	HOLD
0	0	1	1	INVALID

RS NAND Latch with Enable

 


Hold State

 


Enable	S	R	Q	\overline{Q}	State
0	x	x	Q	\overline{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\overline{Q}	Hold
1	1	1	0	0	Invalid

D latch

 


Enable	S	R	Q	\overline{Q}	State
0	x	x	Q	\overline{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\overline{Q}	Hold
1	1	1	0	0	Invalid

 


If $EN = 1$ then $Q = D$ otherwise the latch is in Hold state



Problem with Latch

 

 Circuits are designed with the idea there would be single change in output or memory state in single clock cycle.





Edge Triggered Latch or Flip-flop


 
 


Positive edge triggered flipflop

  Negative Edge Triggered Latch or Flip-flop




Master-Slave D Flip-flop

 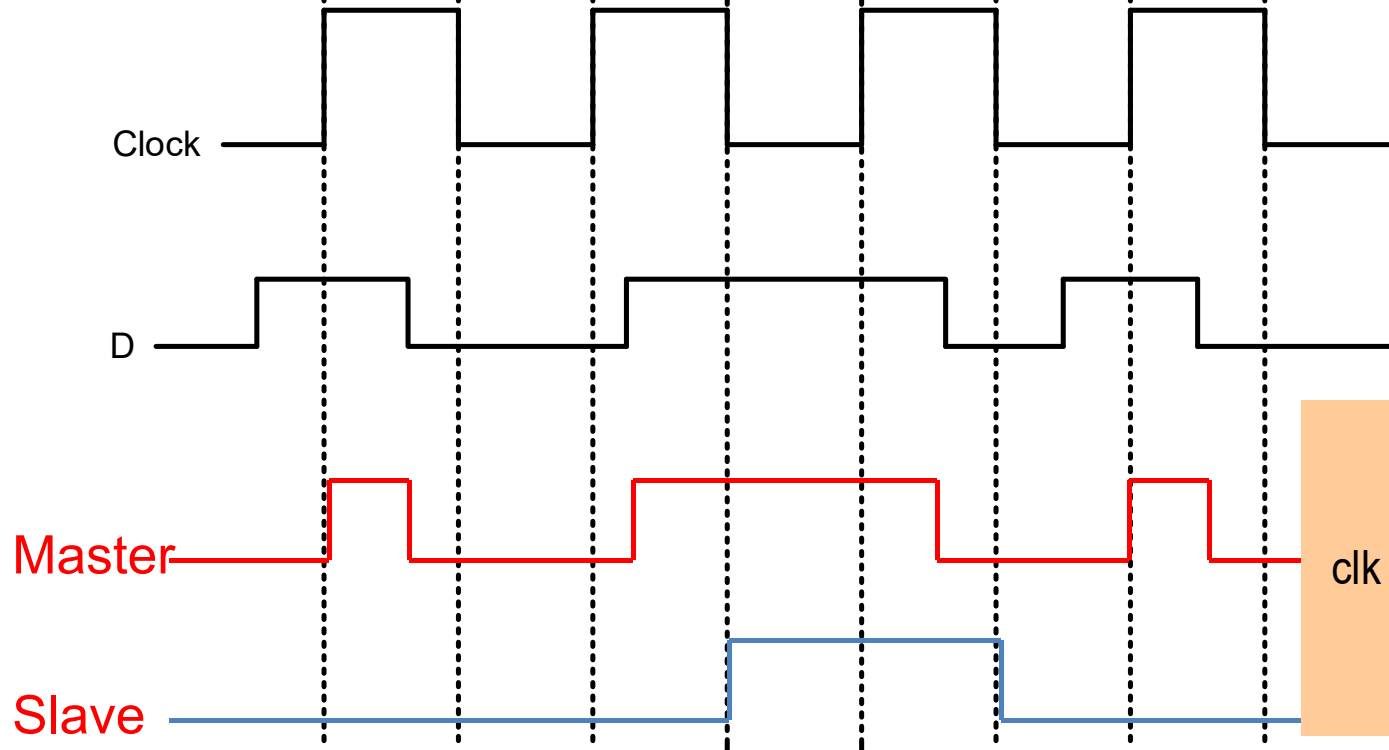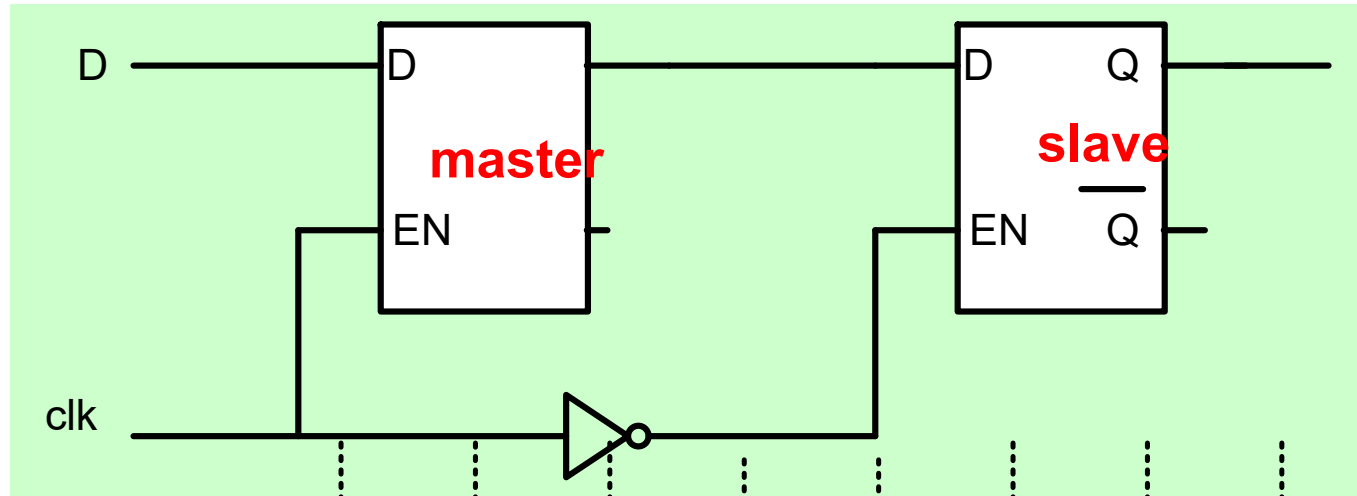


How do convert this into a positive edge triggered D flip-flop?


Positive edge triggered D Flip-flop

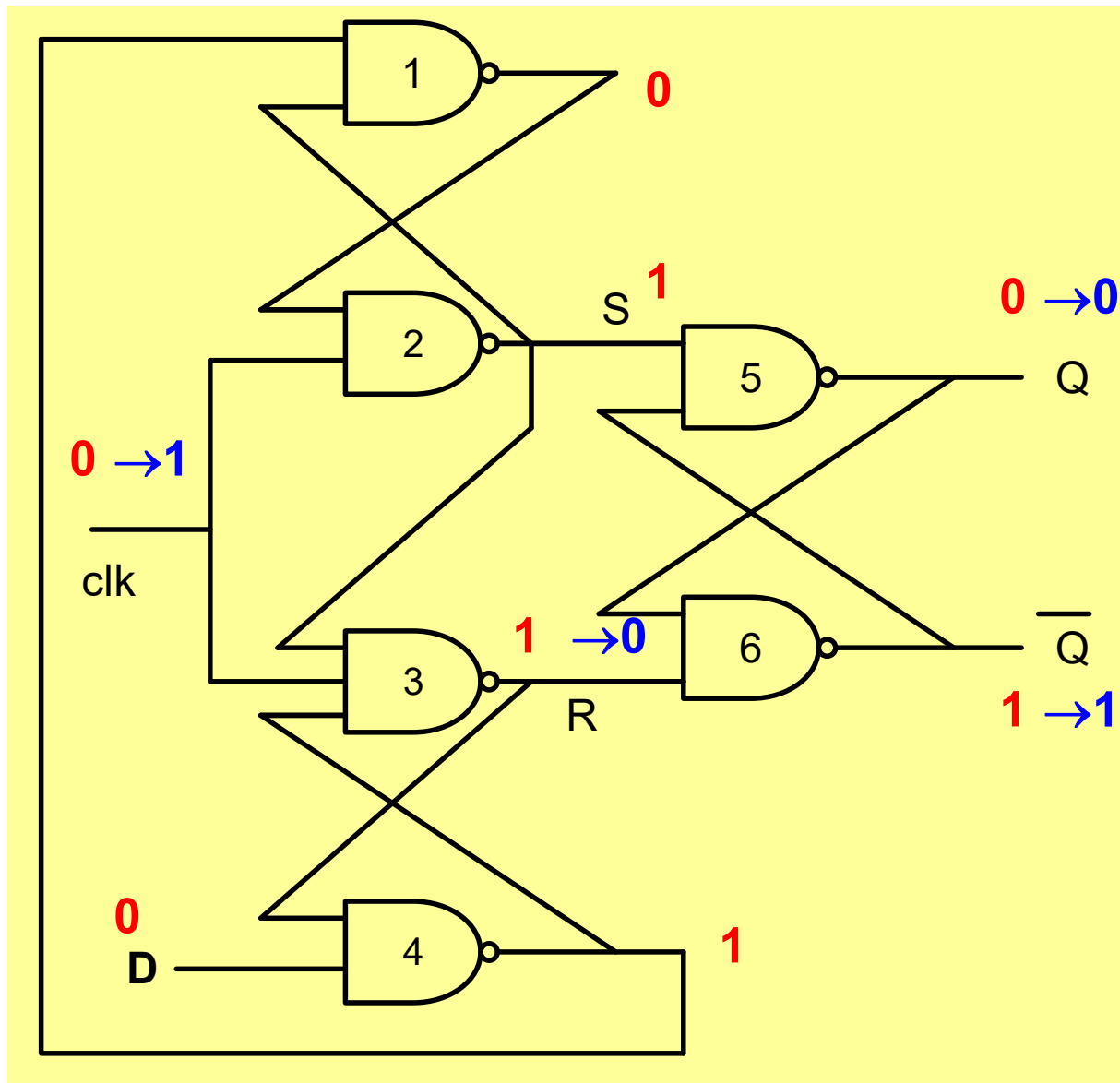

Positive edge triggered D Flip-flop

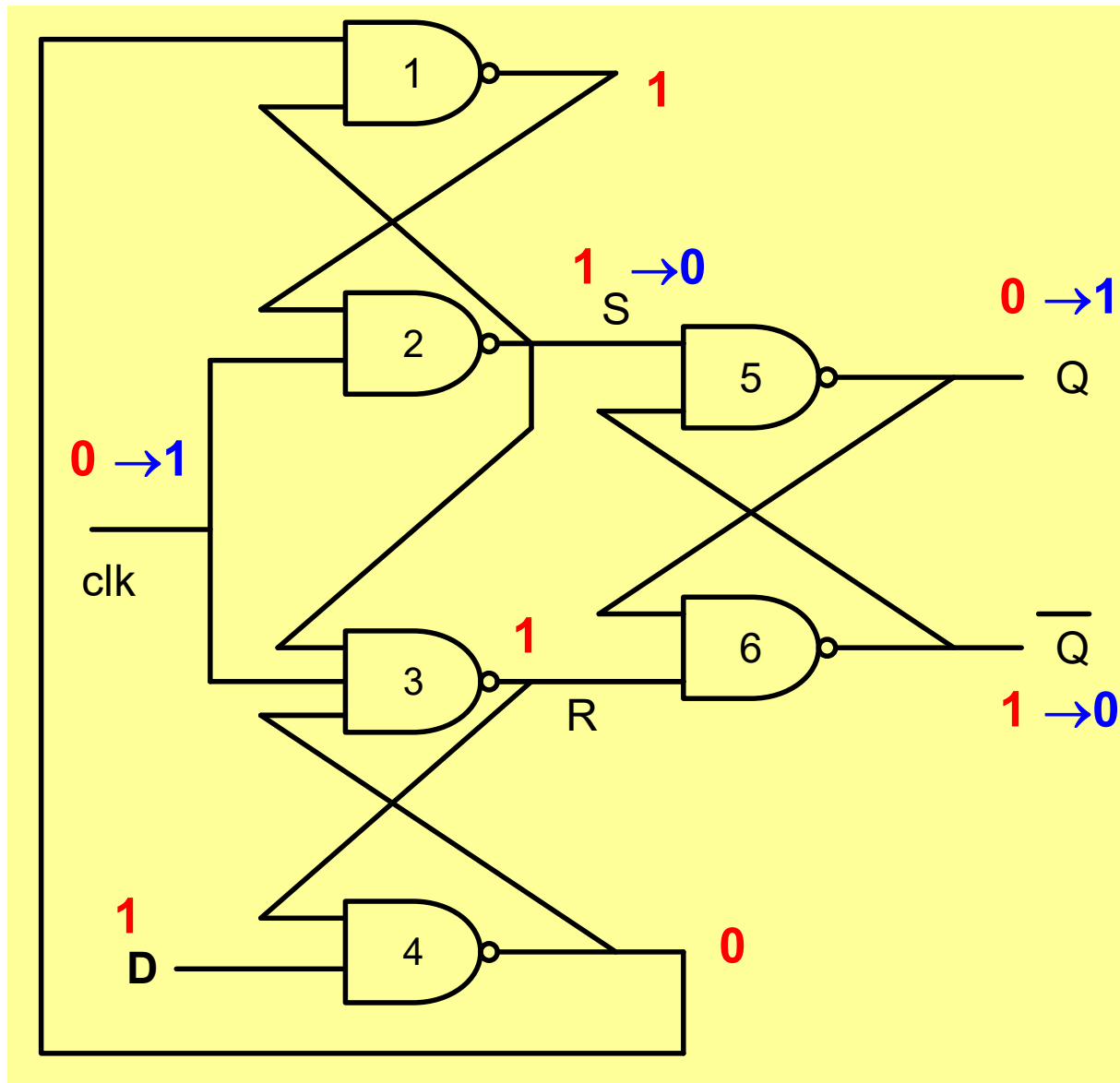

Positive edge triggered D Flip-flop

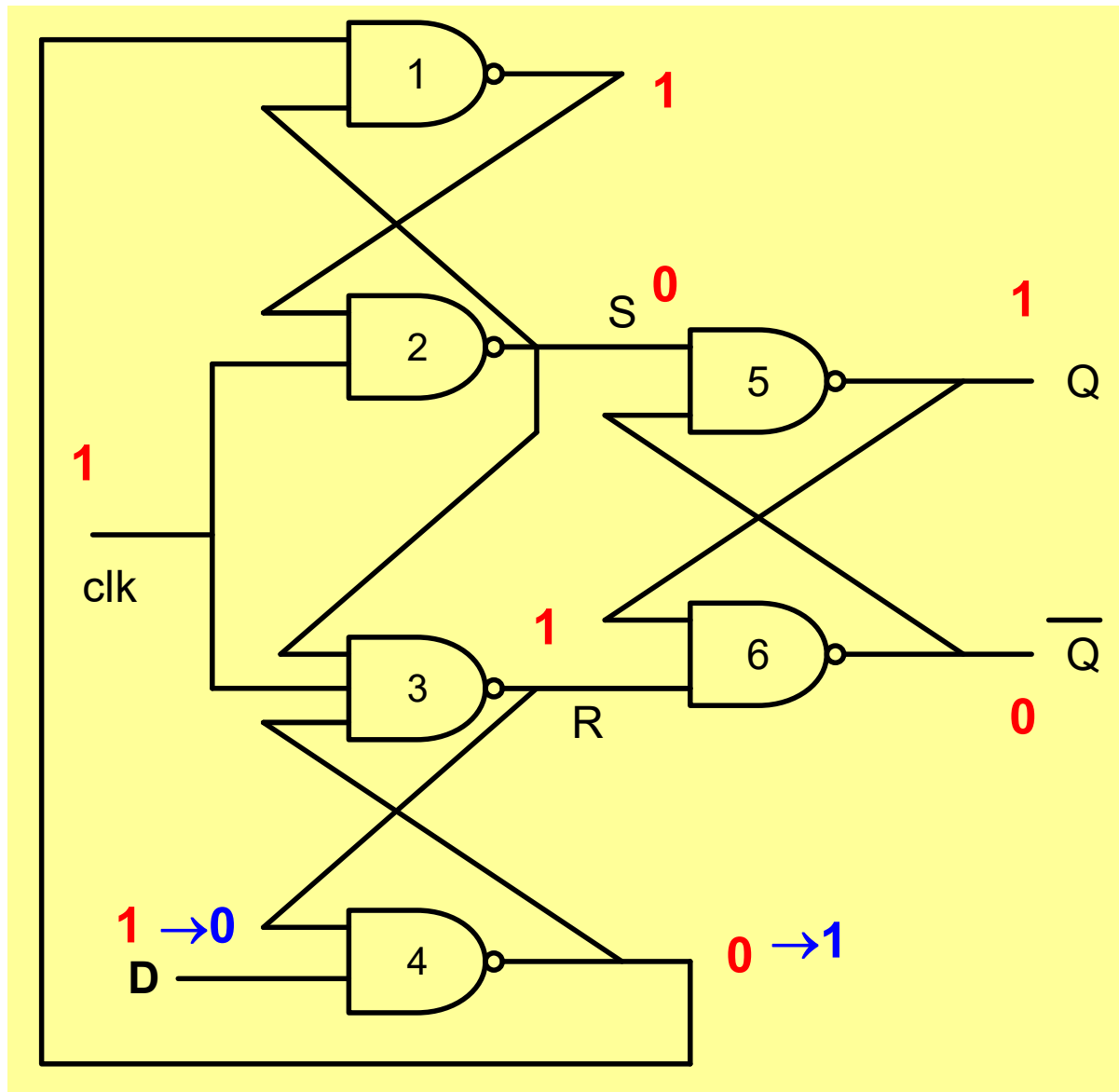

A change in input has no effect if it occurs after the clock edge