

# **ESc201 : Introduction to Electronics**



## **DC Power Supply**



**Dr. Y. S. Chauhan**  
**Dept. of Electrical Engineering**  
**IIT Kanpur**
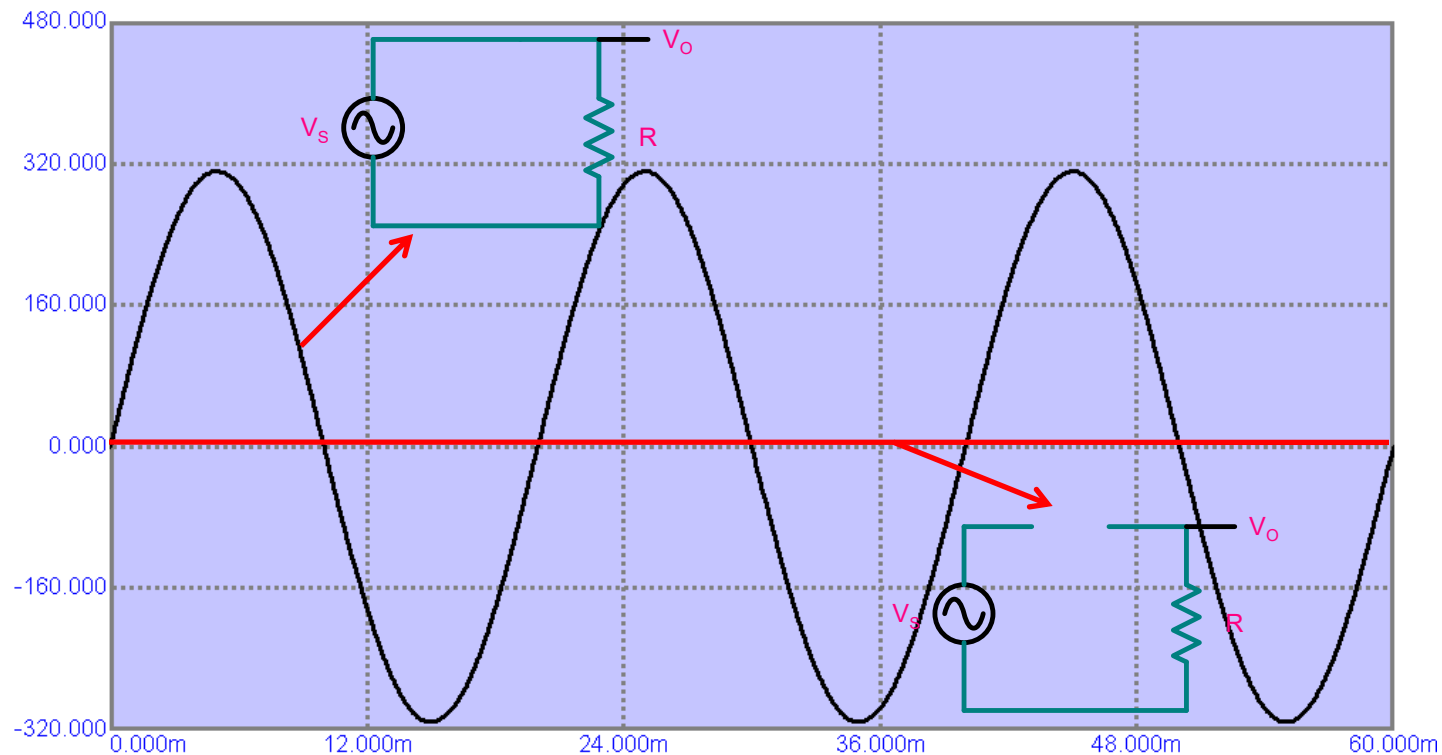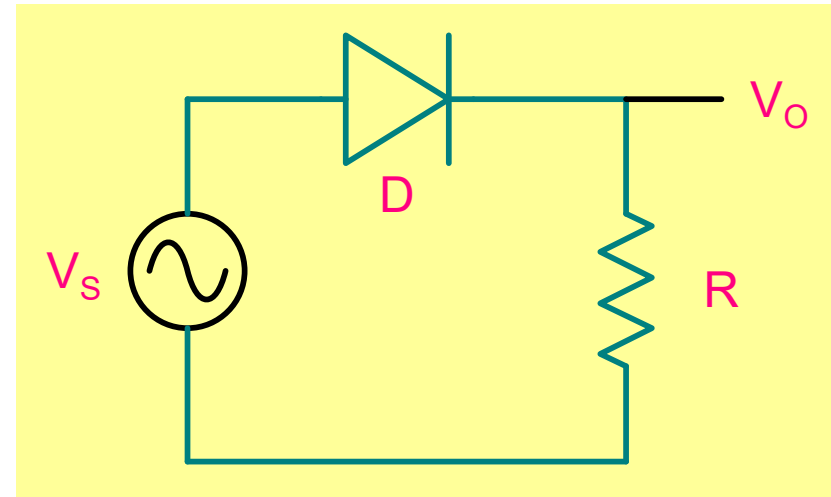
# Half wave Rectifier circuit



$220V_{rms}$

$$220V \times \sqrt{2} \\ = 311.127V \text{ peak value}$$



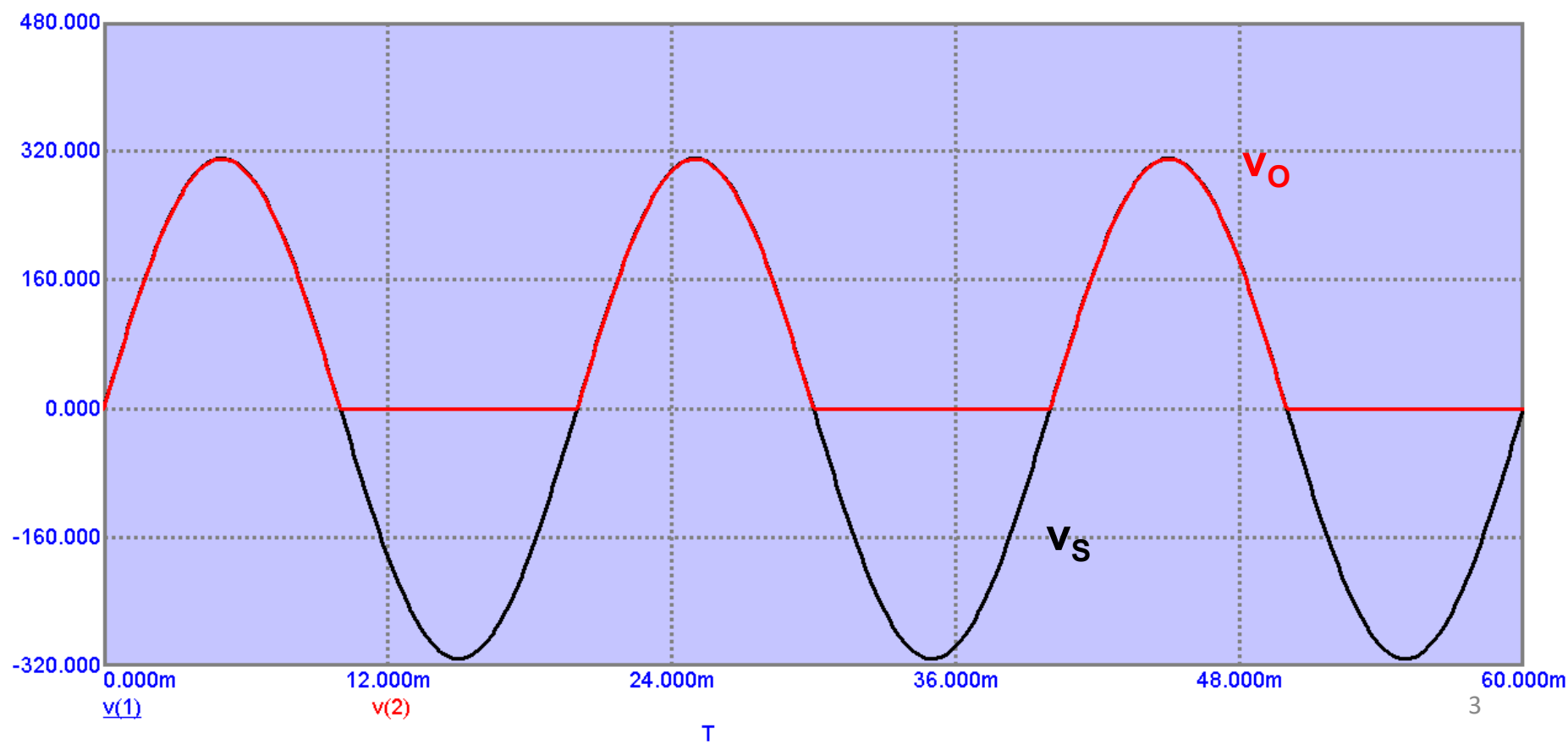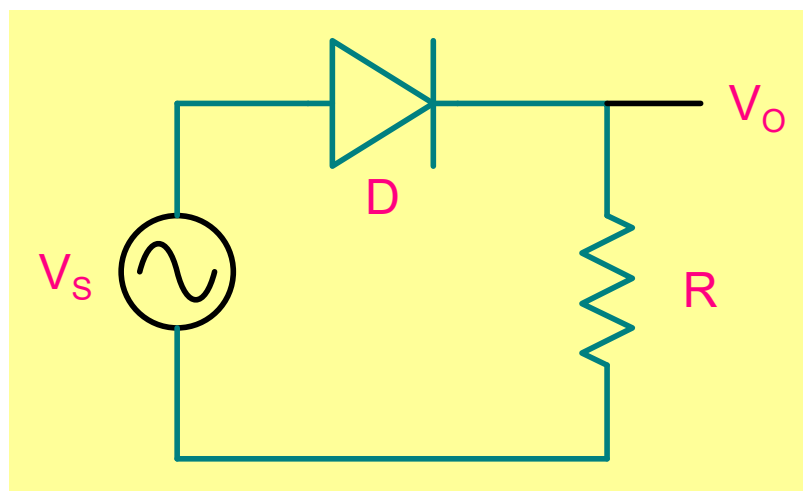



# Transformer

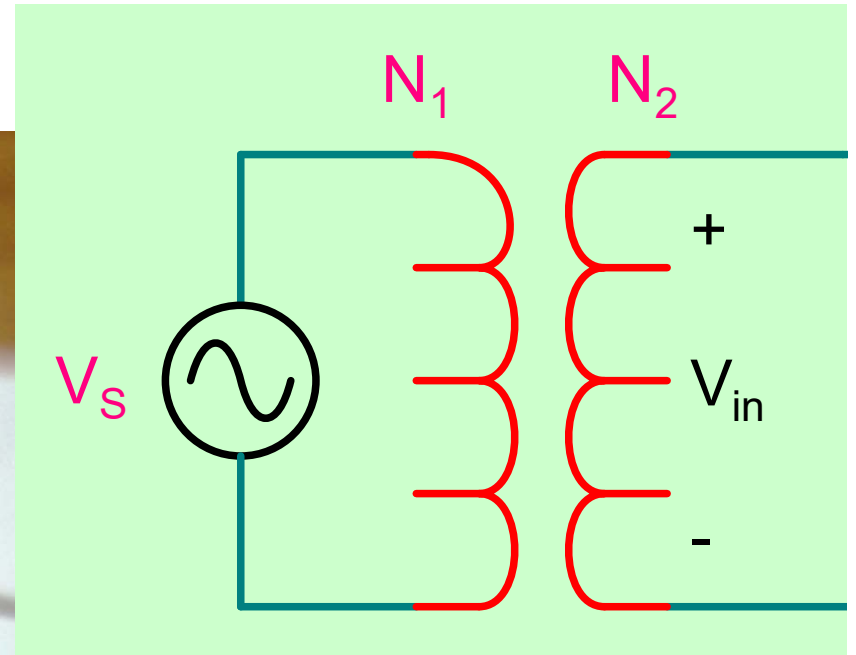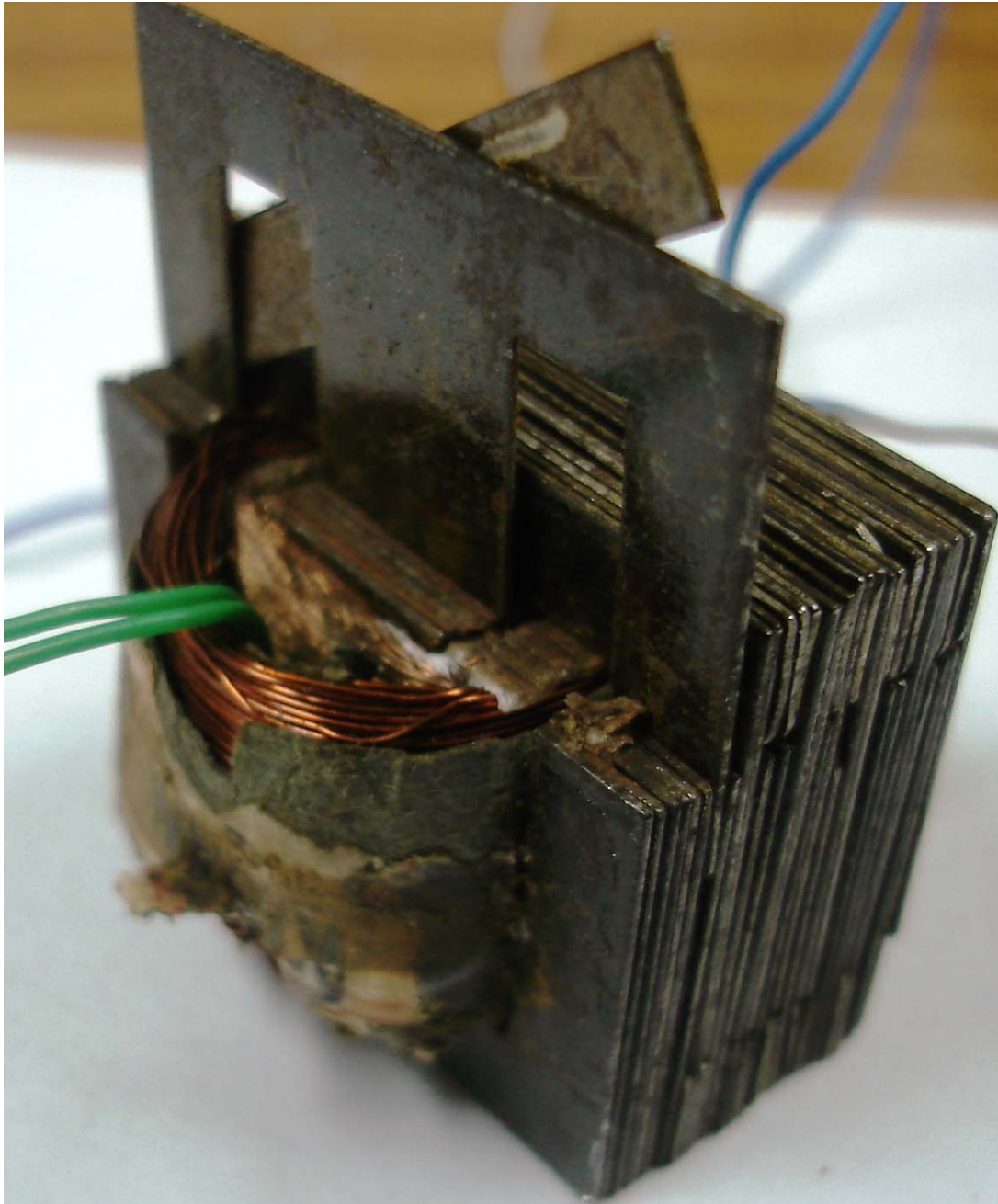

$$\frac{V_s}{V_{IN}} = \frac{N_1}{N_2}$$

# Half Wave Rectifier

$$\frac{V_S}{V_{IN}} = \frac{N_1}{N_2}$$

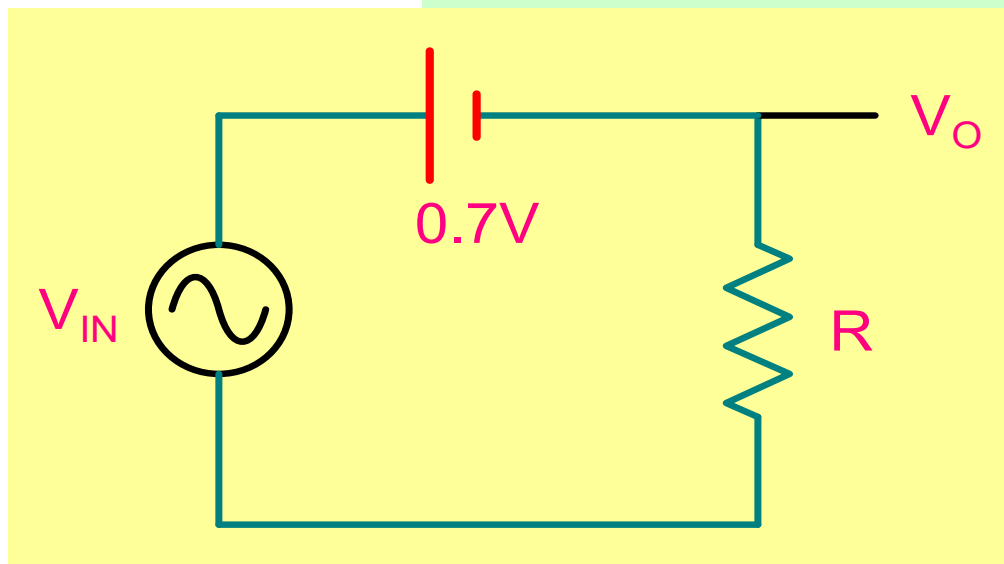
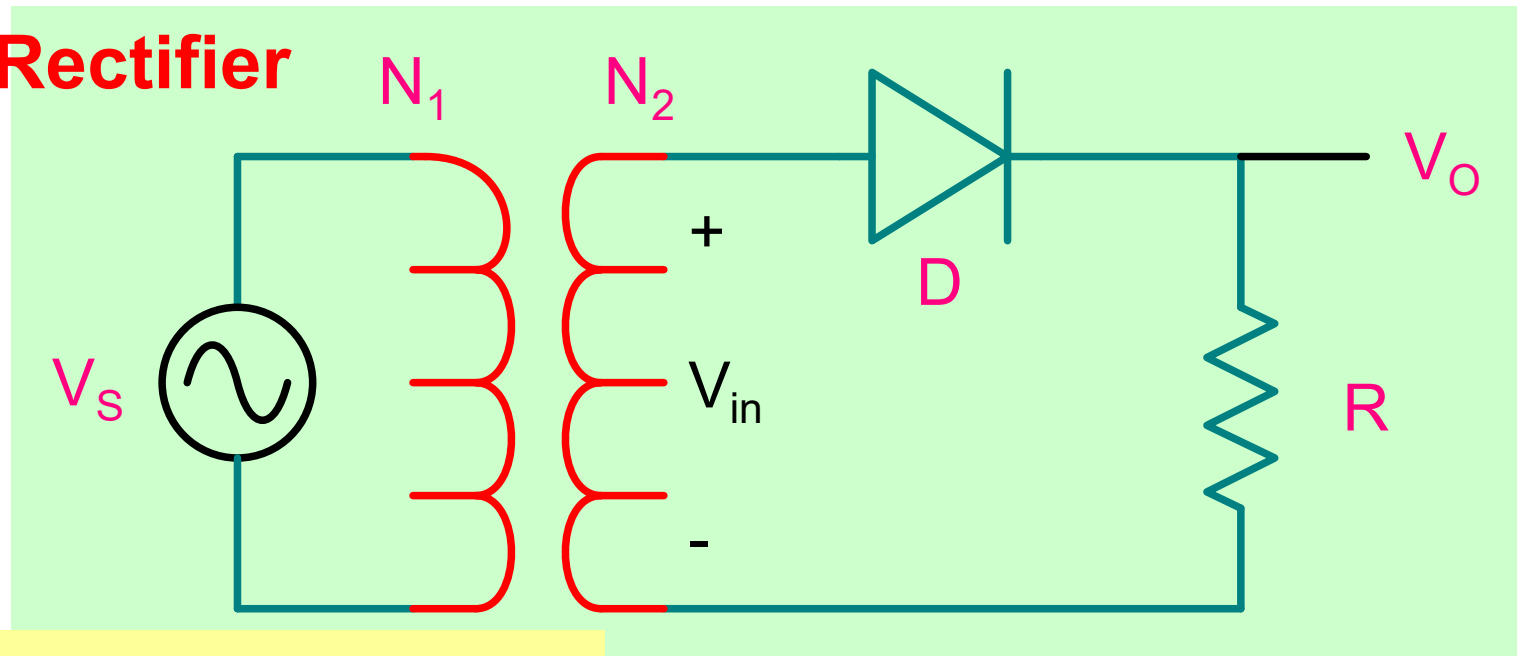


$$V_S = 220V \times \sqrt{2} \\ = 311.127V \text{ peak value}$$

For  $V_O$  to be 12V, the input  $V_{IN}$  should be ~12.7V




$$\frac{N_1}{N_2} = \frac{311}{12.7} = 24.5$$




$$V_o = V_{IN} - 0.7$$

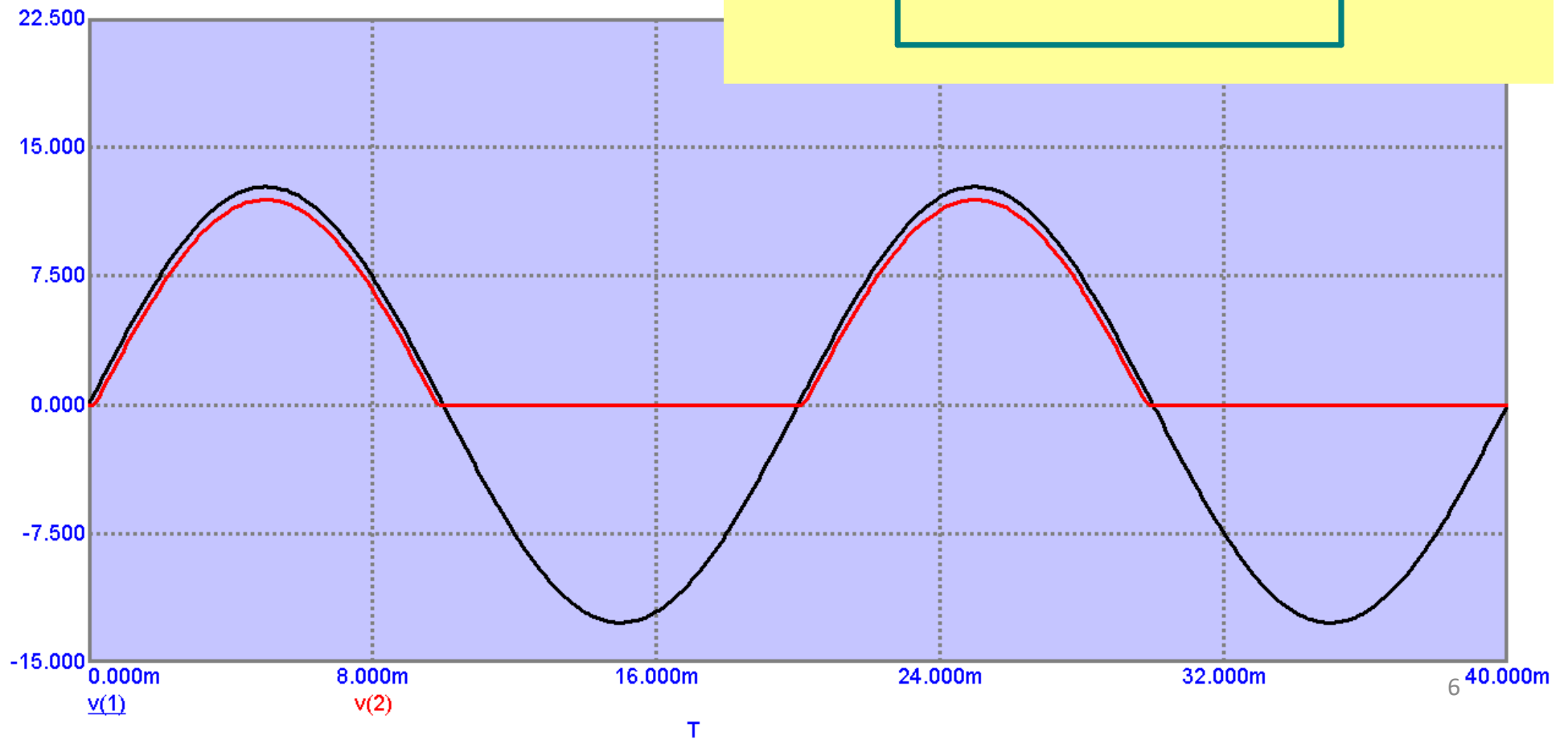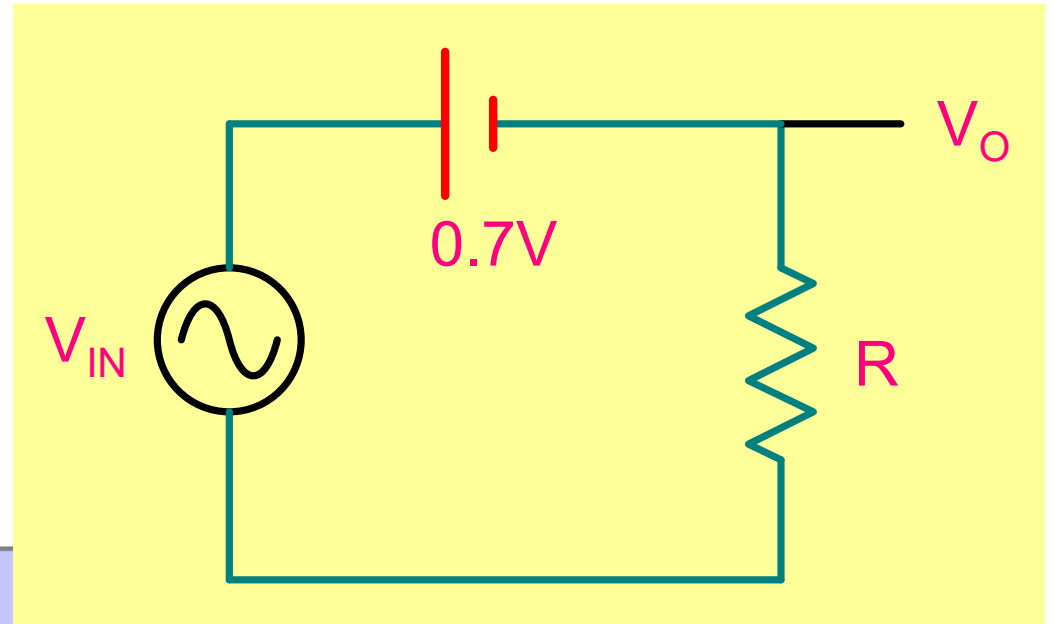


## Zoomed view

$$V_0 = V_{IN} - 0.7$$

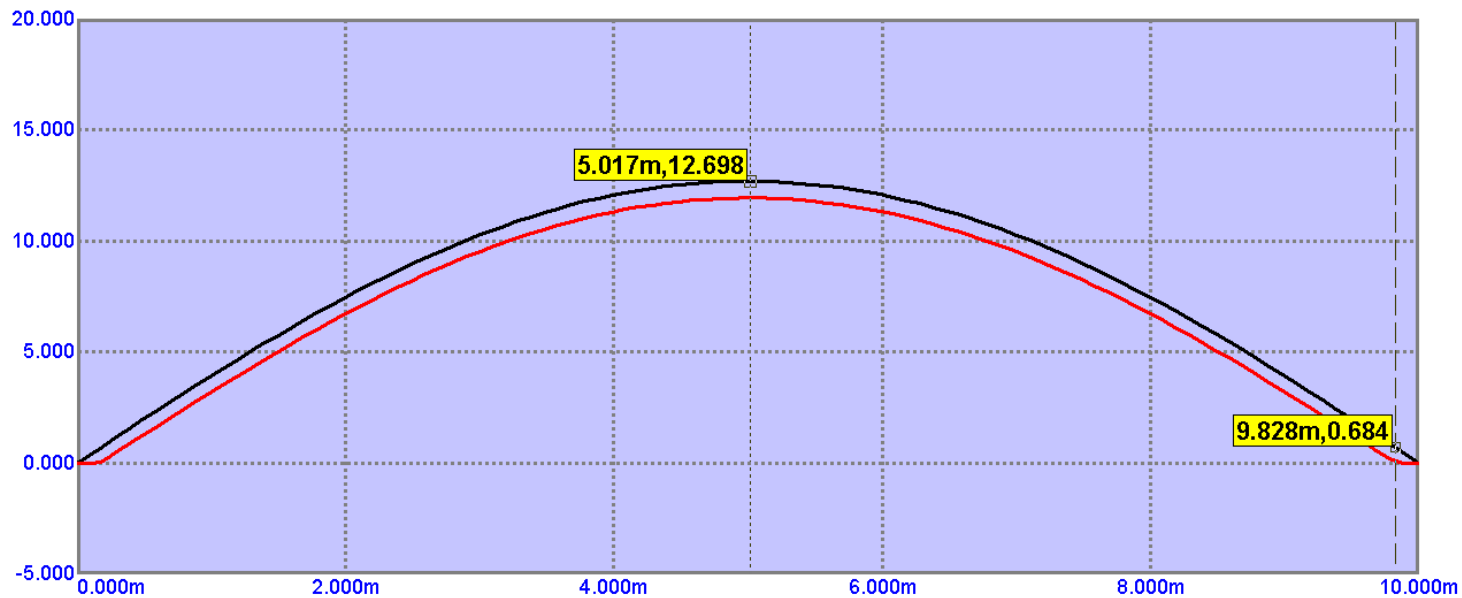
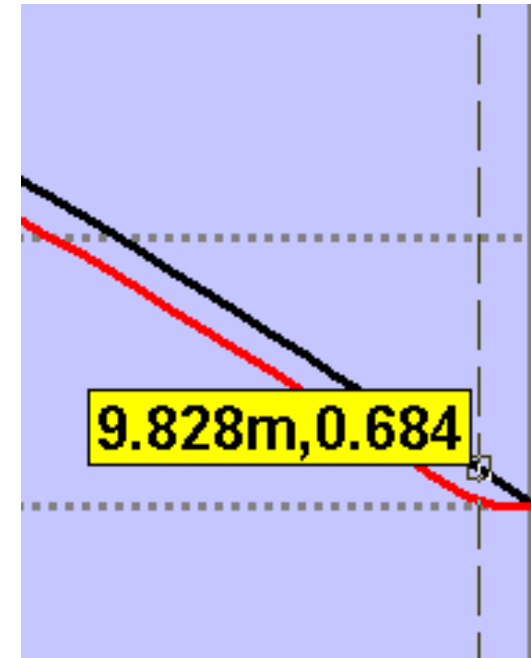
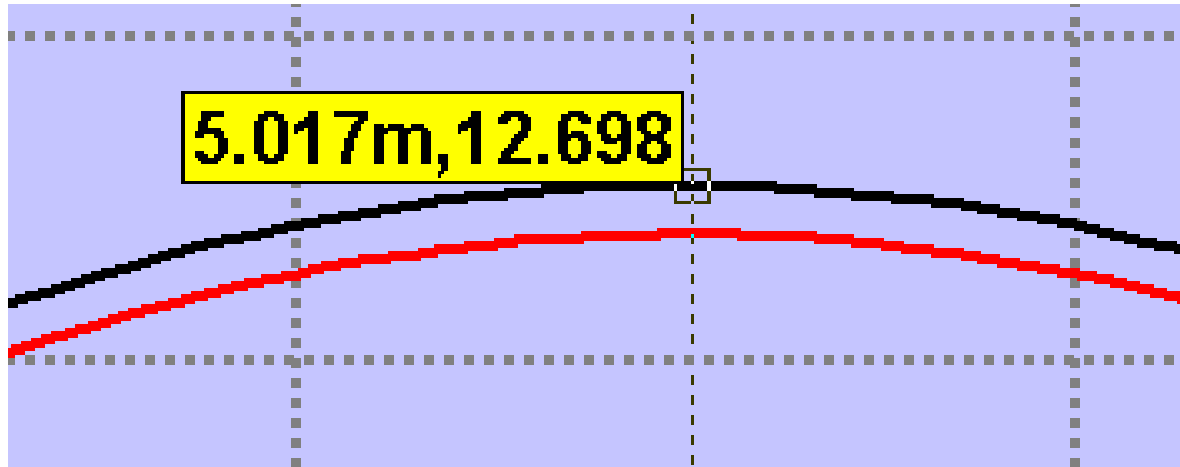


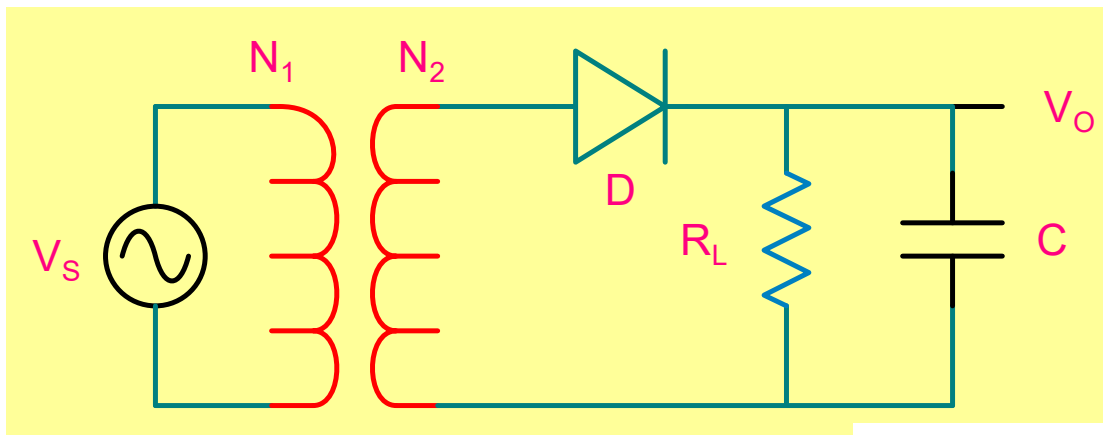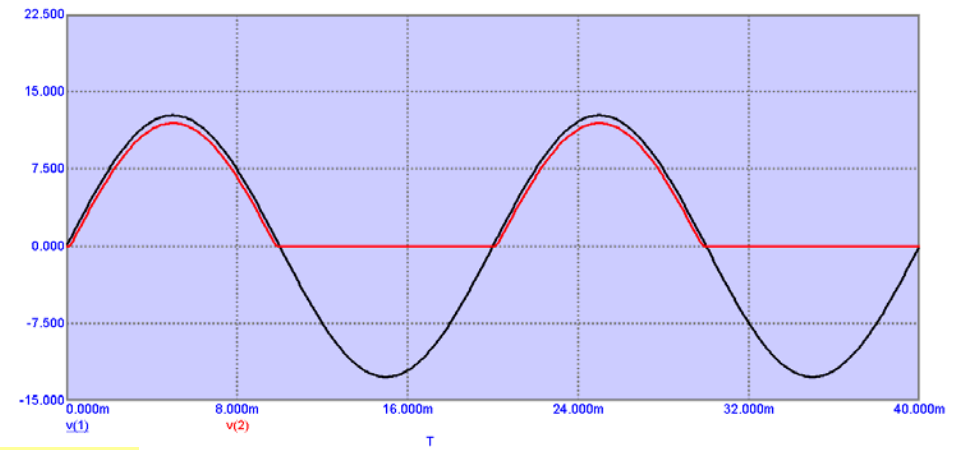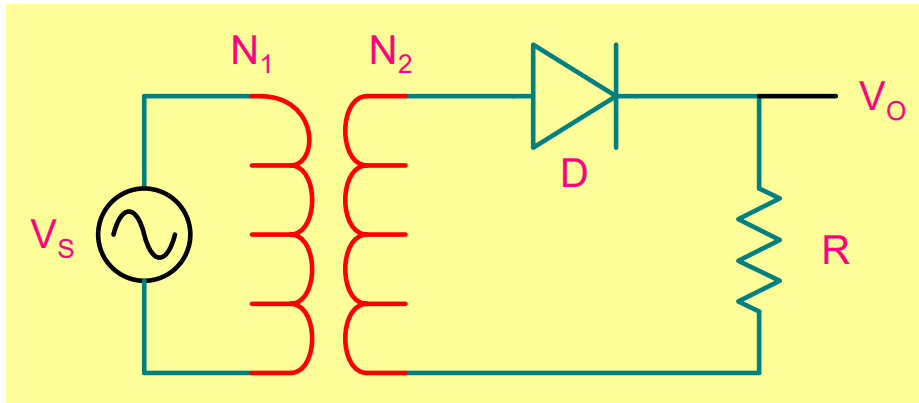

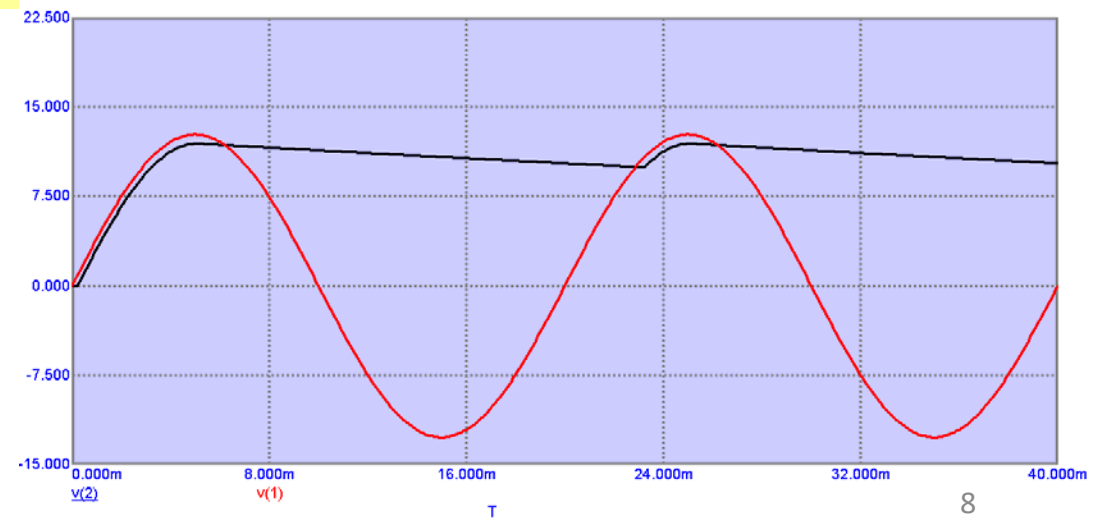Want to hold that voltage during negative half cycle






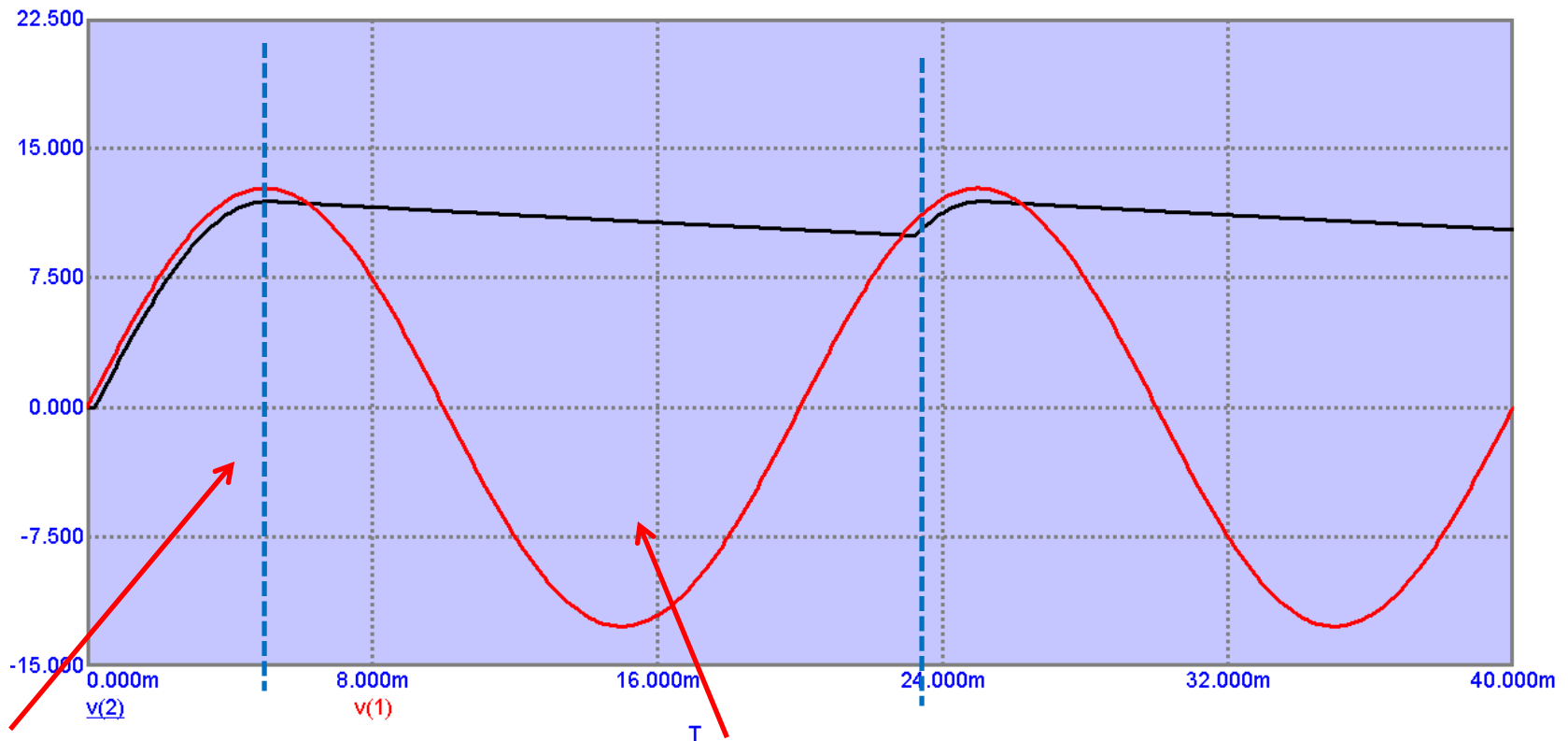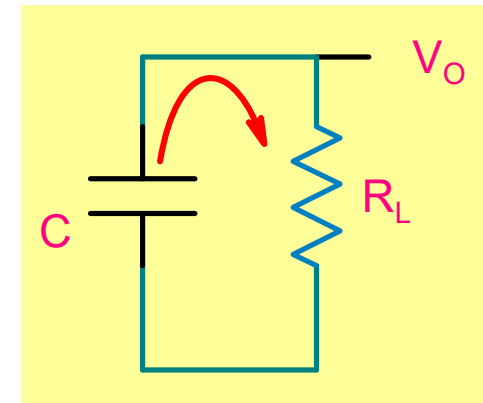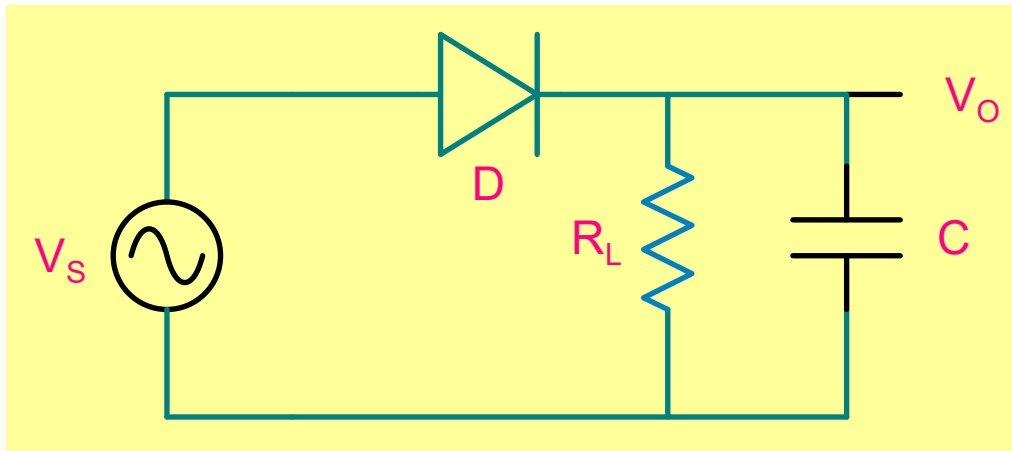

Diode is forward biased

Diode is reverse biased




# Output has a ripple

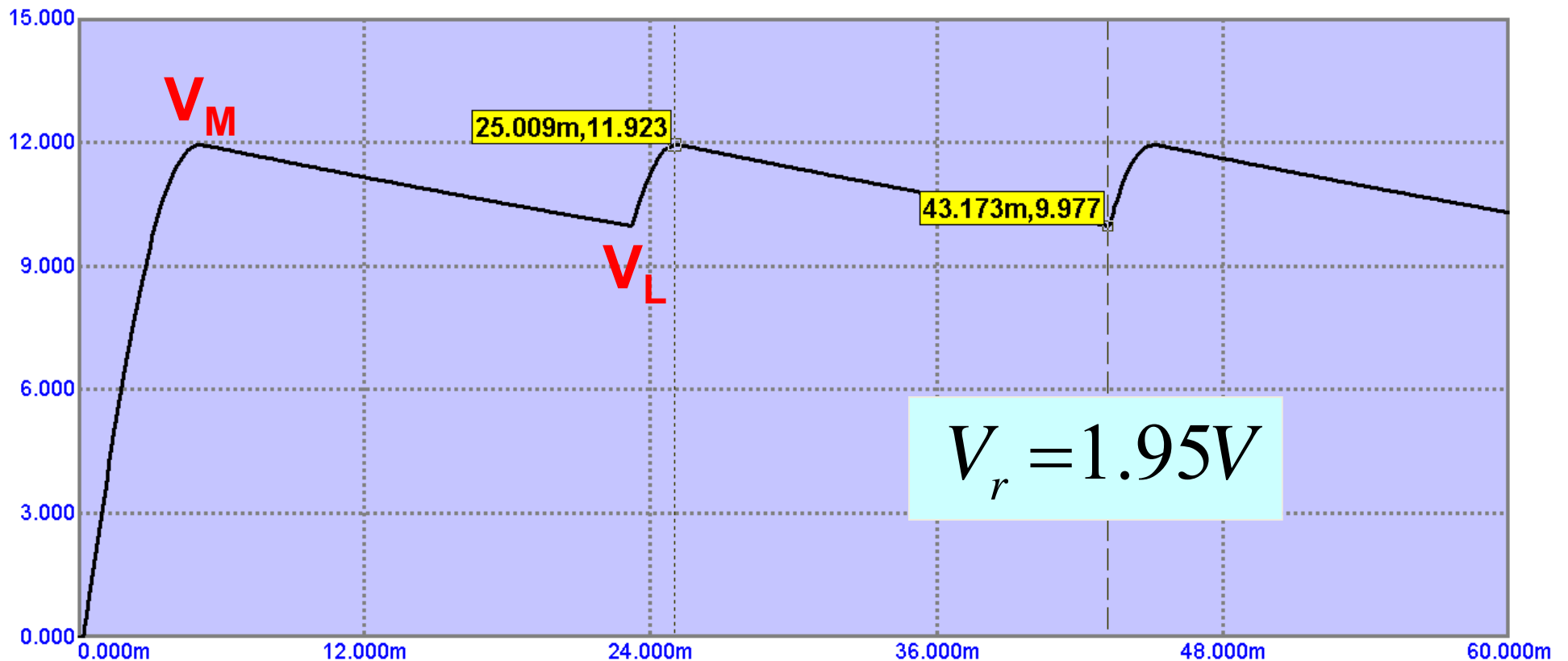

Ripple Voltage :  $V_r = V_M - V_L$


Average Output Voltage :  $V_o(avg) \cong V_M - \frac{V_R}{2}$

# What does ripple voltage depend on?

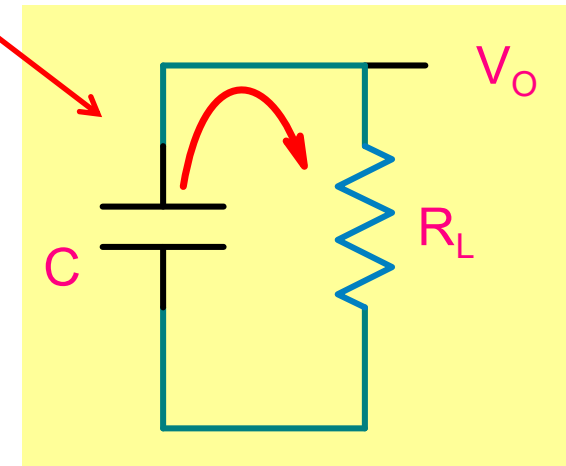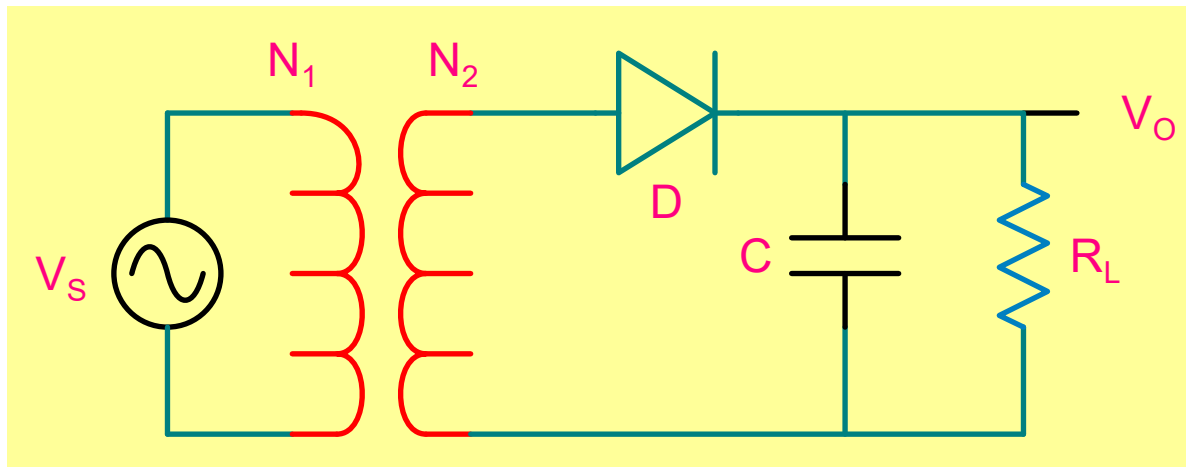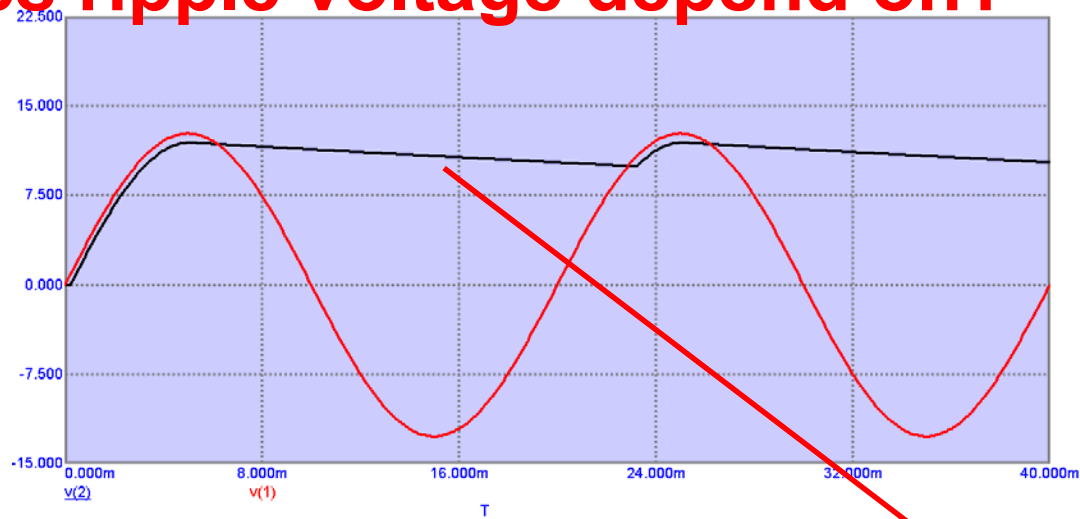

$$C \frac{dV_o}{dt} + \frac{V_o}{R_L} = 0 \Rightarrow \frac{dV_o}{dt} = -\frac{V_o}{R_L C}$$
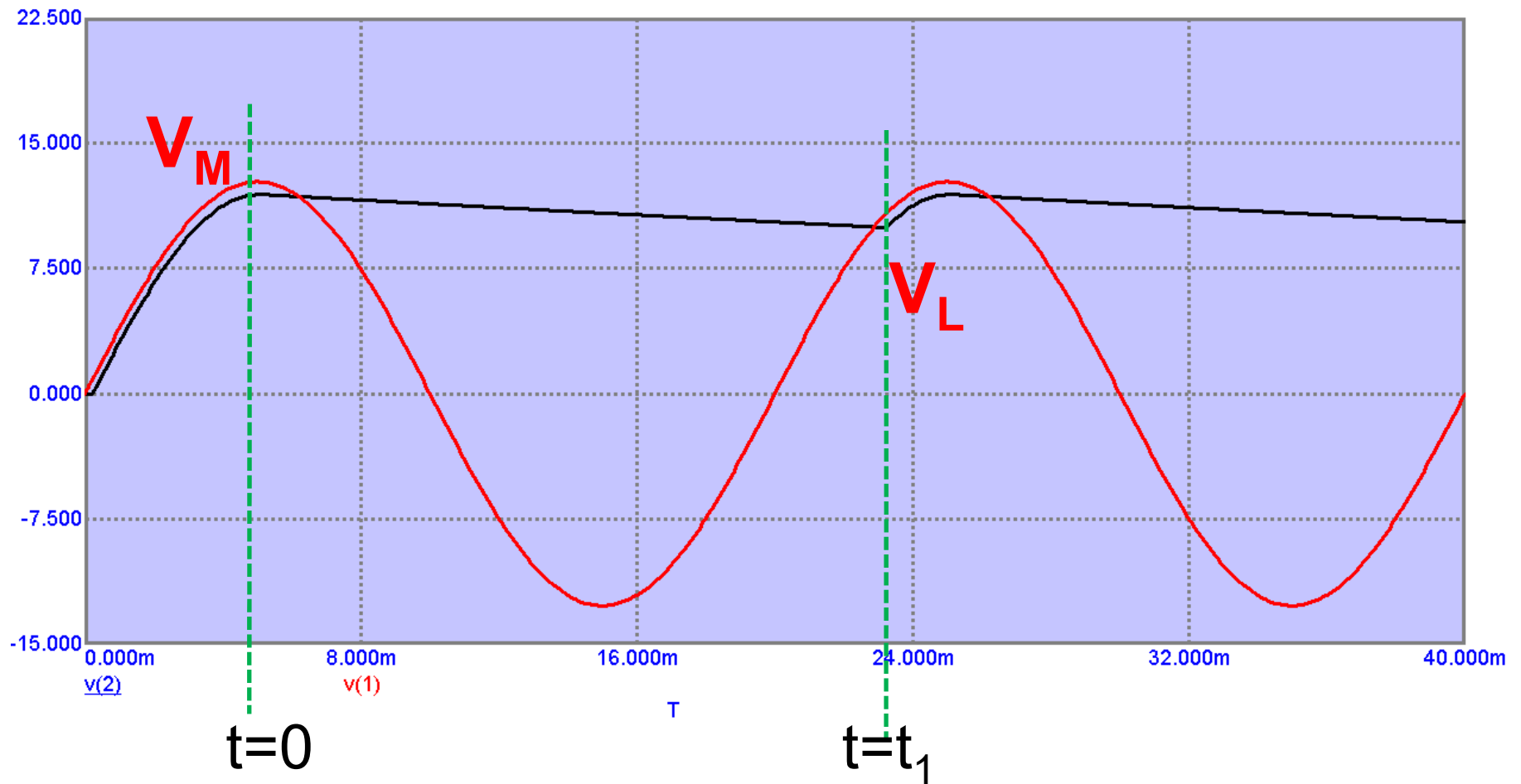
$$V_o(t) = V_M \times e^{-\frac{t}{R_L C}}$$




$$V_L = V_M \times e^{-\frac{t_1}{R_L C}}$$

$$V_r = V_M - V_L = V_M \times (1 - e^{-\frac{t_1}{R_L C}})$$

Assuming that  $t_1 \ll R_L C$
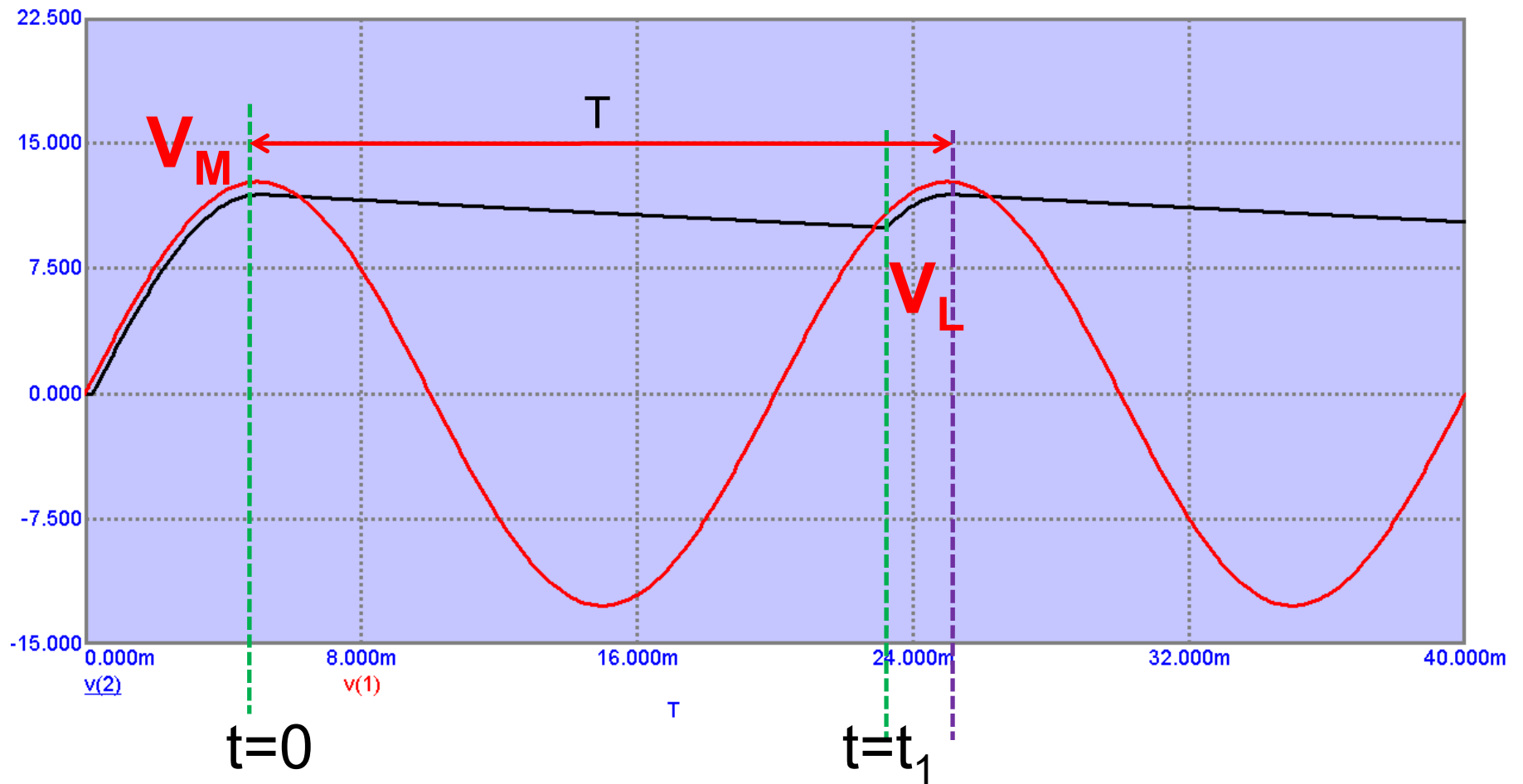
$$V_r \cong V_M \times \left\{ 1 - \left( 1 - \frac{t_1}{R_L C} \right) \right\} = \frac{V_M t_1}{R_L C}$$





$$t_1 \cong T$$

$$V_r = \frac{V_M t_1}{R_L C} \cong \frac{V_M T}{R_L C}$$

$$V_r \cong \frac{V_M}{f R_L C}$$



# Example

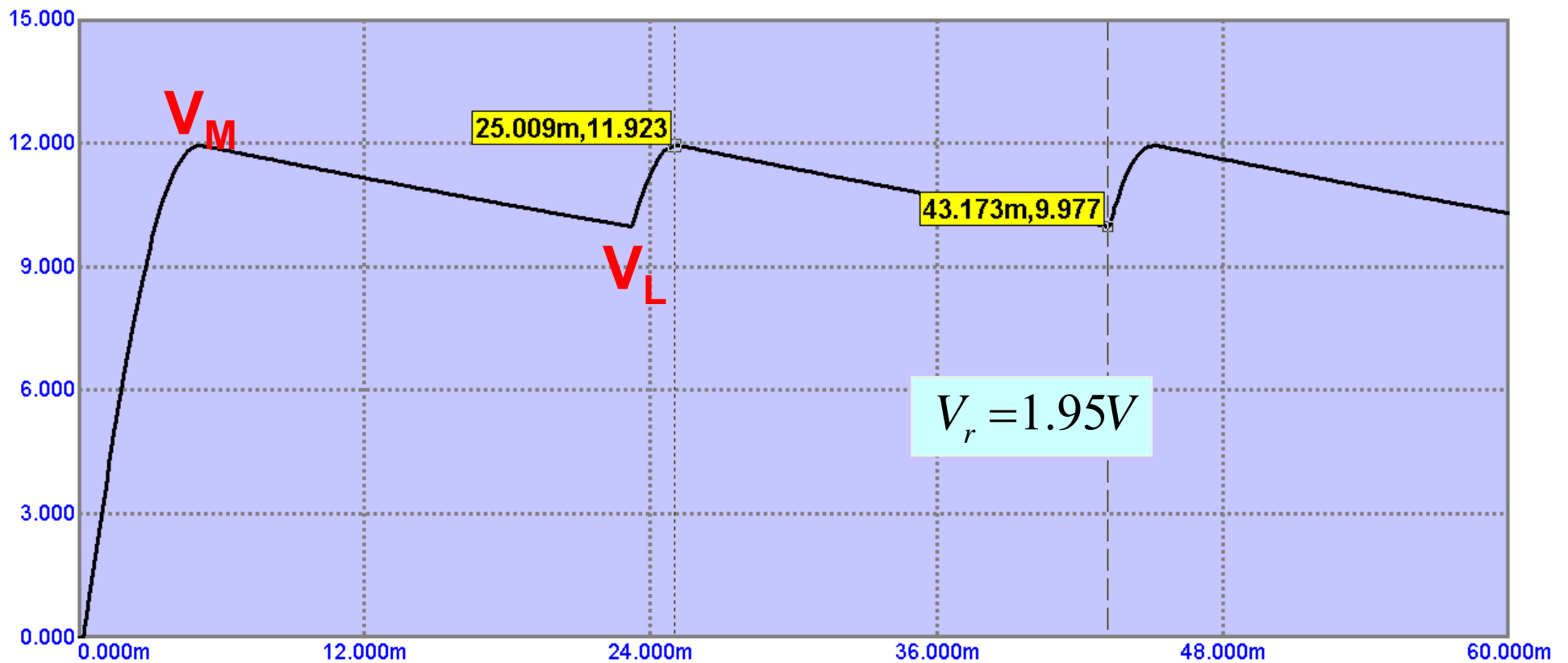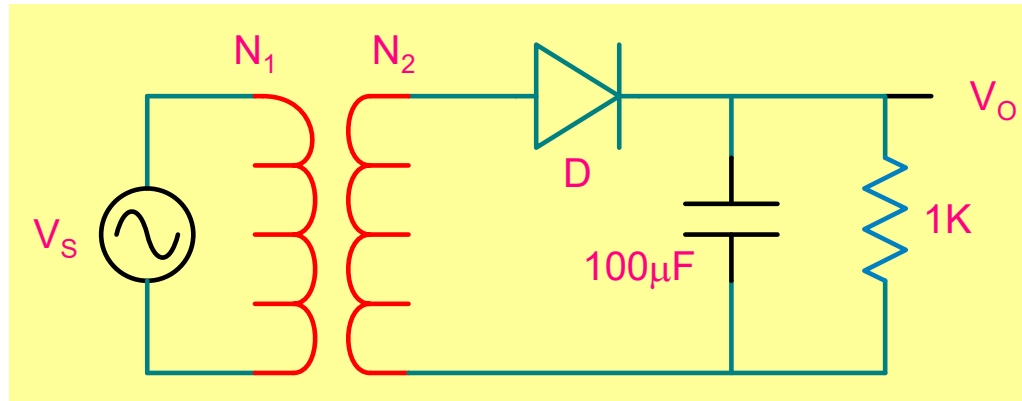

$$V_r \cong \frac{V_M}{fR_L C} = \frac{11.923}{50 \times 10^3 \times 100 \times 10^{-6}} = 2.385V$$

$$\frac{R_L C}{T} = 5$$

# Example

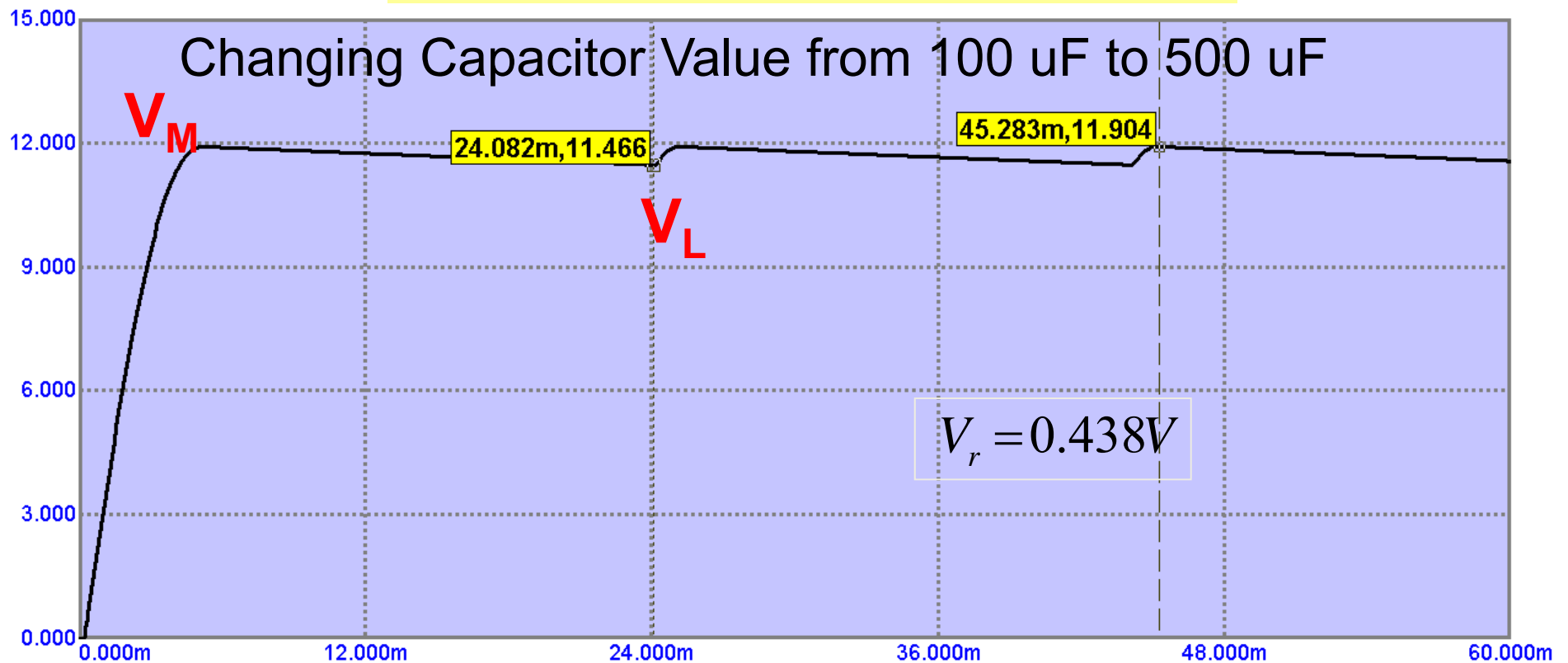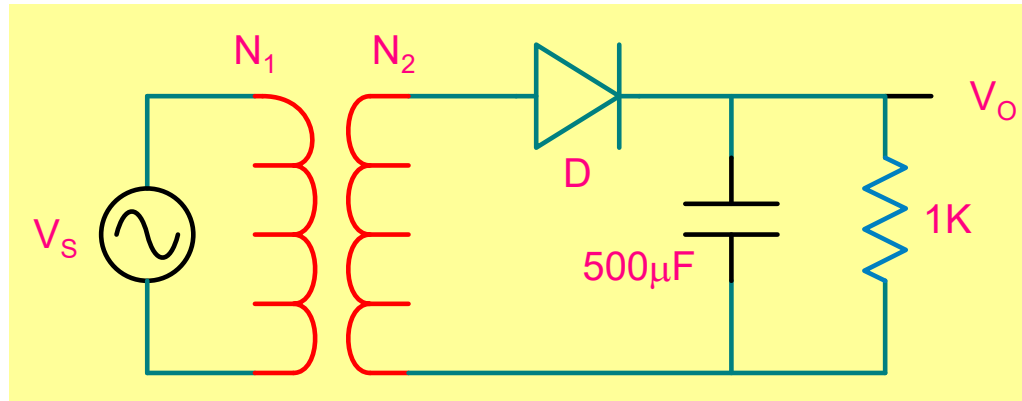


$$V_r \cong \frac{V_M}{fR_L C} = \frac{11.904}{50 \times 10^3 \times 500 \times 10^{-6}} = 0.476V$$

$$\frac{R_L C}{T} = 25$$
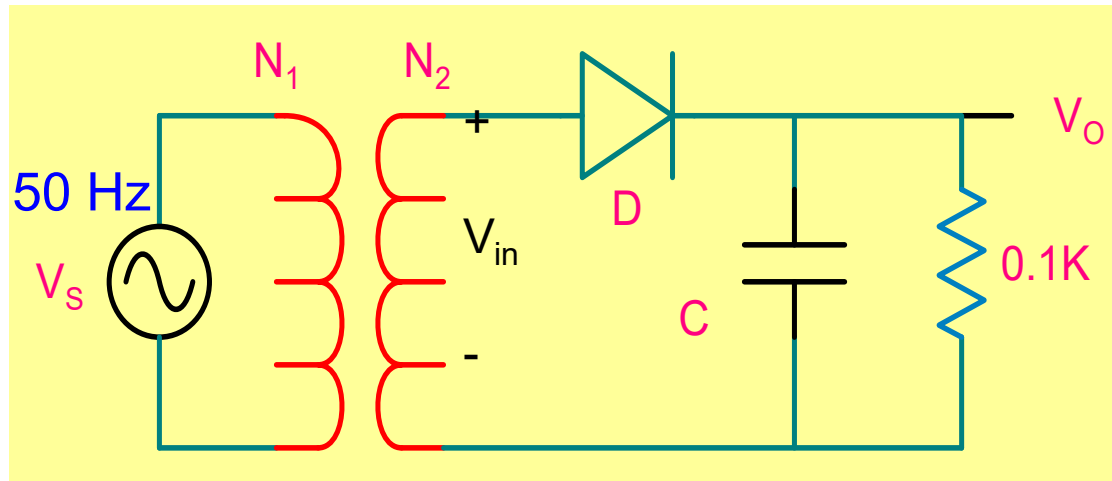
## Design Example

Design a power supply that will supply 6V to a load of  $100\Omega$  with ripple voltage less than 0.1V.



For  $V_o$  to be 6V, the input  $V_{in}$  should be  $\sim 6.7V$


$$\frac{N_1}{N_2} = \frac{311.127}{6.7} = 46.4$$

$$V_r \cong \frac{V_M}{fR_L C} = 0.1 \Rightarrow C = 12mF$$


How do we choose a diode for this application?



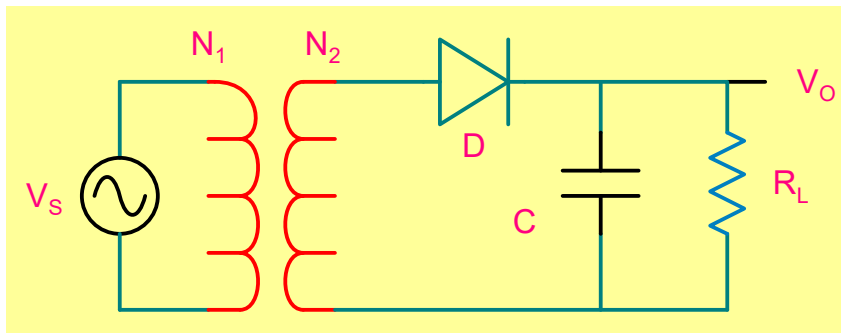
How do we choose a diode for this application?



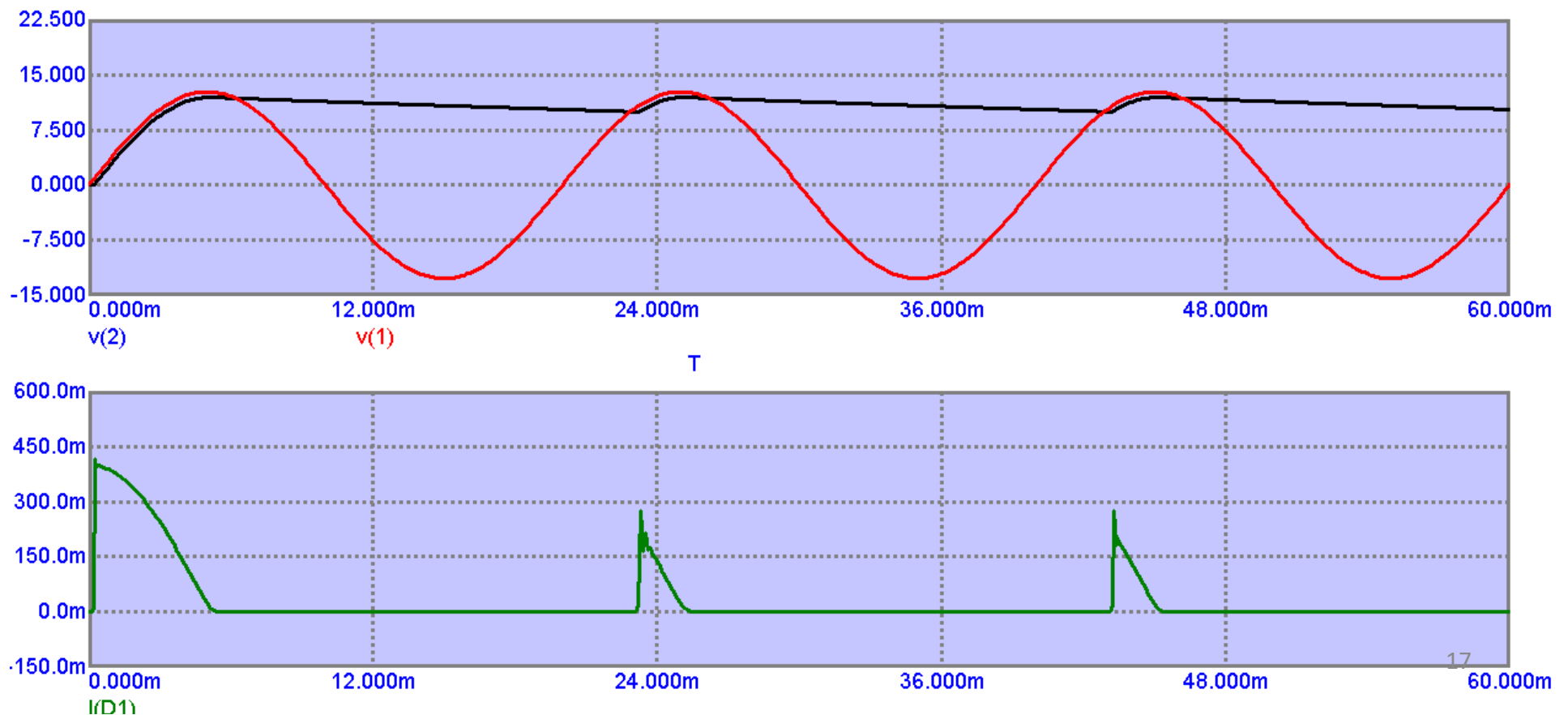
Peak diode current, average diode current and peak inverse voltage



## Diode forward bias current

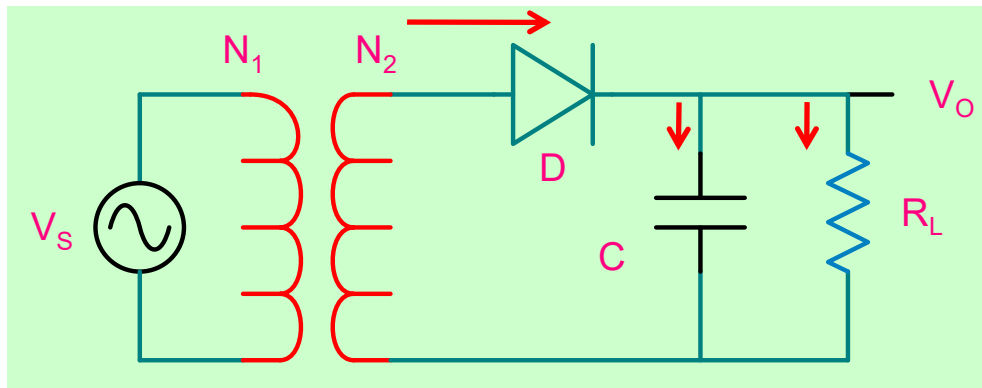

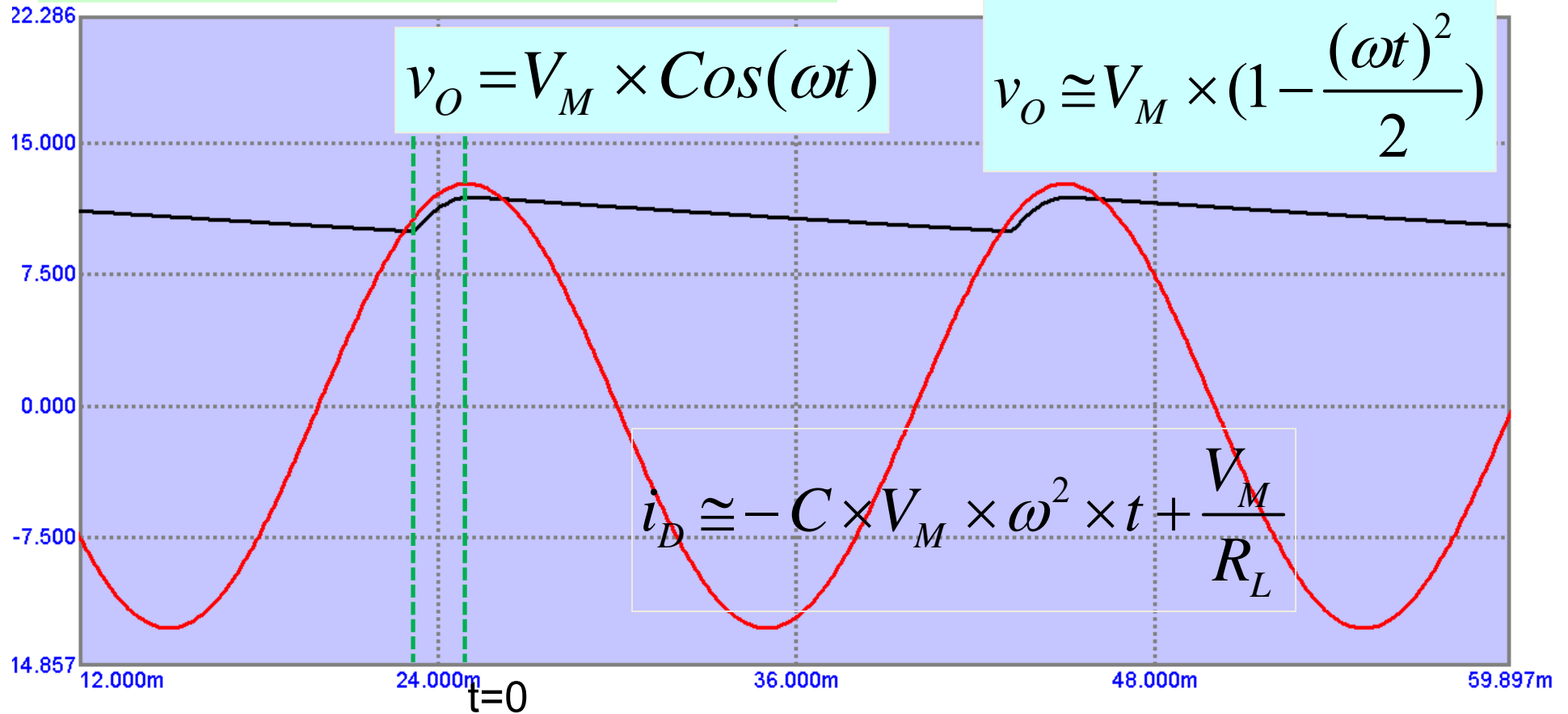
$$i_D = C \times \frac{dv_o}{dt} + \frac{v_o}{R_L}$$



$$v_O \cong V_M \times \left(1 - \frac{(\omega t)^2}{2}\right)$$
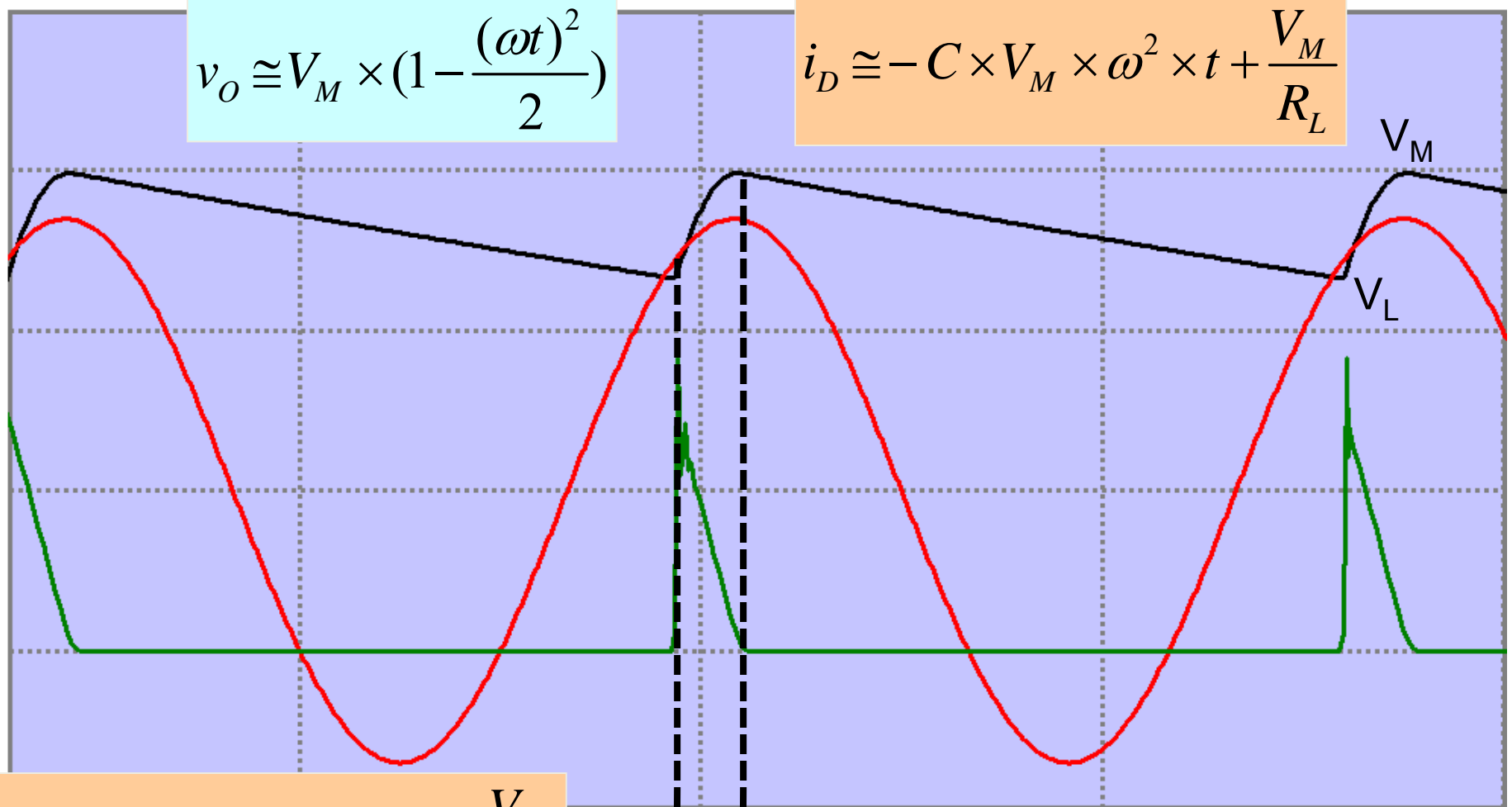
$$i_D \cong -C \times V_M \times \omega^2 \times t + \frac{V_M}{R_L}$$



$$i_{D\max} \cong C \times V_M \times \omega^2 \times \Delta t + \frac{V_M}{R_L} \quad t = -\Delta t \quad t = 0$$

$$V_L \cong V_M \times \left(1 - \frac{(\omega \Delta t)^2}{2}\right) \Rightarrow \Delta t = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_M}}$$

$$i_{D\max} \cong \omega C \times \sqrt{2V_r V_M} + \frac{V_M}{R_L}$$

## Peak Diode Current

$$i_{D\max} \cong \omega C \times \sqrt{2V_r V_M} + \frac{V_M}{R_L}$$


$$V_r \cong \frac{V_M}{fR_L C}$$

$$\Delta t = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_M}}$$

$$i_{D\max} = \frac{V_M}{R_L} \left[ 1 + 2\pi \sqrt{\frac{2V_M}{V_r}} \right]$$
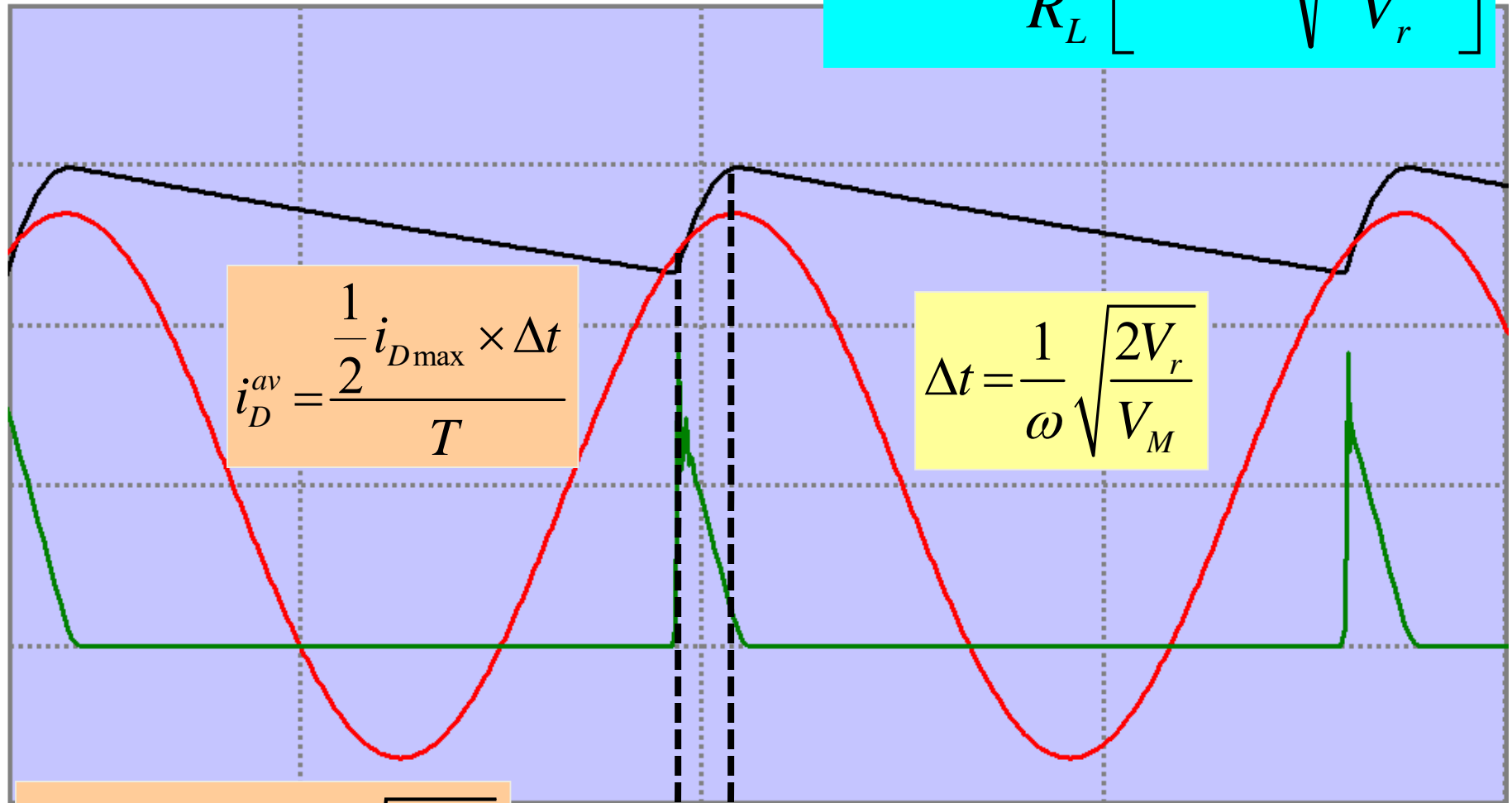
# Average Diode Currents

$$i_{D\max} = \frac{V_M}{R_L} \left[ 1 + 2\pi \sqrt{\frac{2V_M}{V_r}} \right]$$



$$i_D^{av} = \frac{\frac{1}{2} i_{D\max} \times \Delta t}{T}$$


$$\Delta t = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_M}}$$

$$i_D^{av} = \frac{i_{D\max}}{4\pi} \times \sqrt{\frac{2V_r}{V_M}}$$

$t = -\Delta t$   $t = 0$

$$i_D^{av} = \frac{V_M}{R_L} + \frac{\sqrt{2V_r V_M}}{4\pi R_L} \approx \frac{V_M}{R_L}$$



# Peak and Average Diode Currents

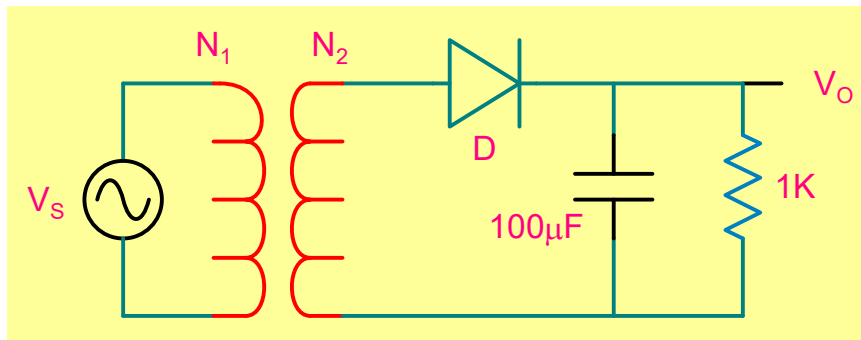

$$V_r = 1.95\text{V}$$

$$i_D^{av} \cong \frac{V_M}{R_L} = 12\text{mA}$$


$$i_{D\max} \cong 250\text{mA}$$

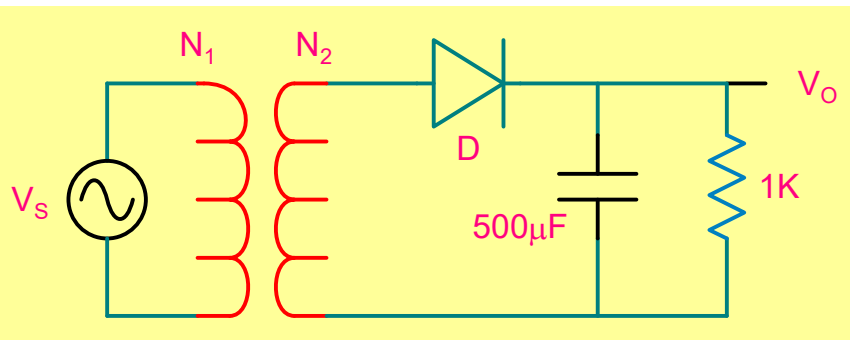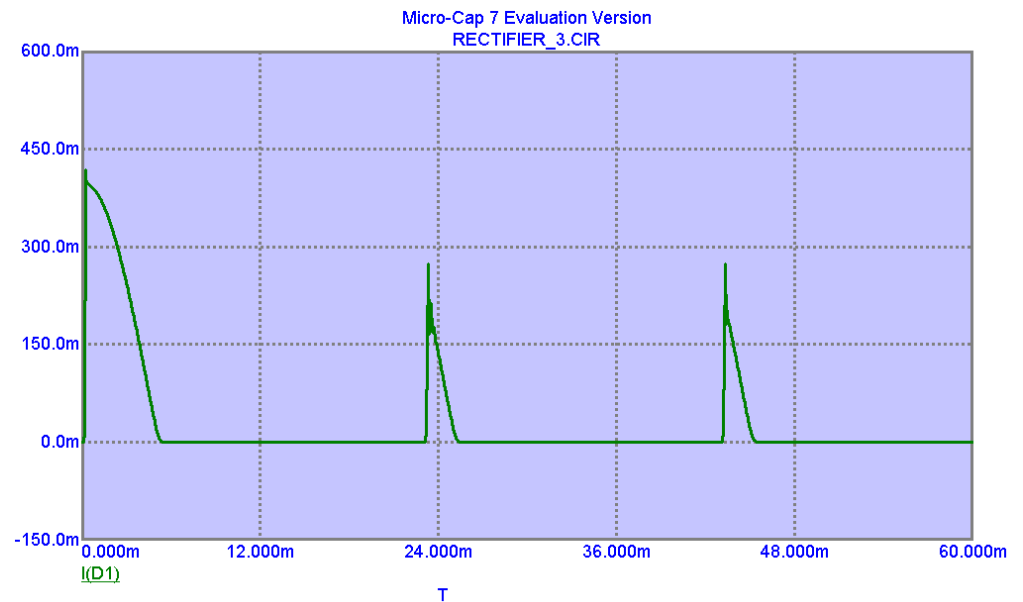

$$V_r = 0.438\text{V}$$

$$i_D^{av} \cong \frac{V_M}{R_L} = 12\text{mA}$$

$$i_{D\max} \cong 545\text{mA}$$

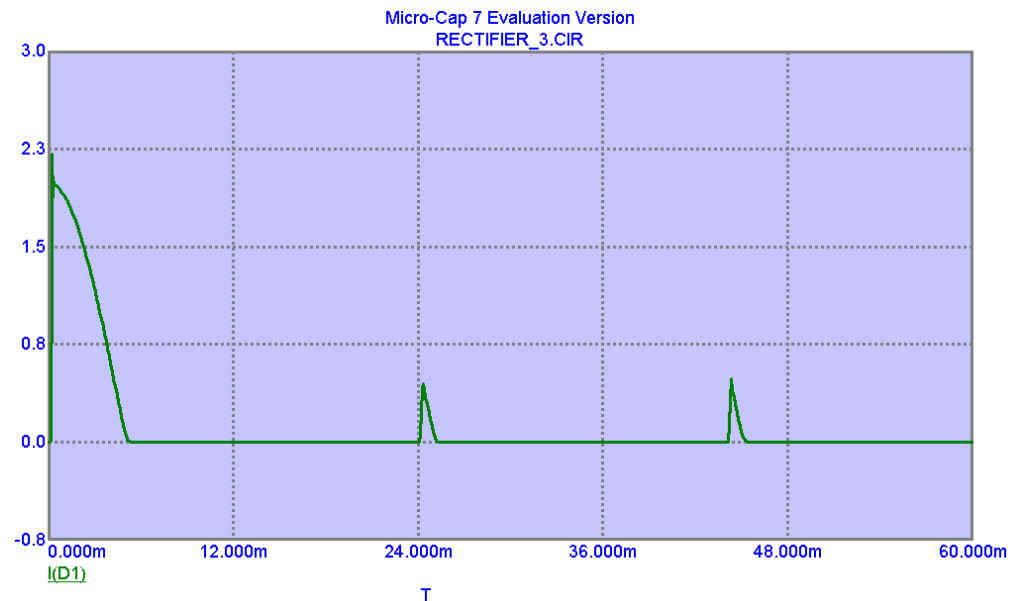

**Peak diode current increases as ripple reduces<sup>22</sup>**