


ESc201 : Introduction to Electronics





Frequency Domain Response

Dr. Y. S. Chauhan
Dept. of Electrical Engineering
IIT Kanpur





Time domain vs. Frequency domain analysis

Signal

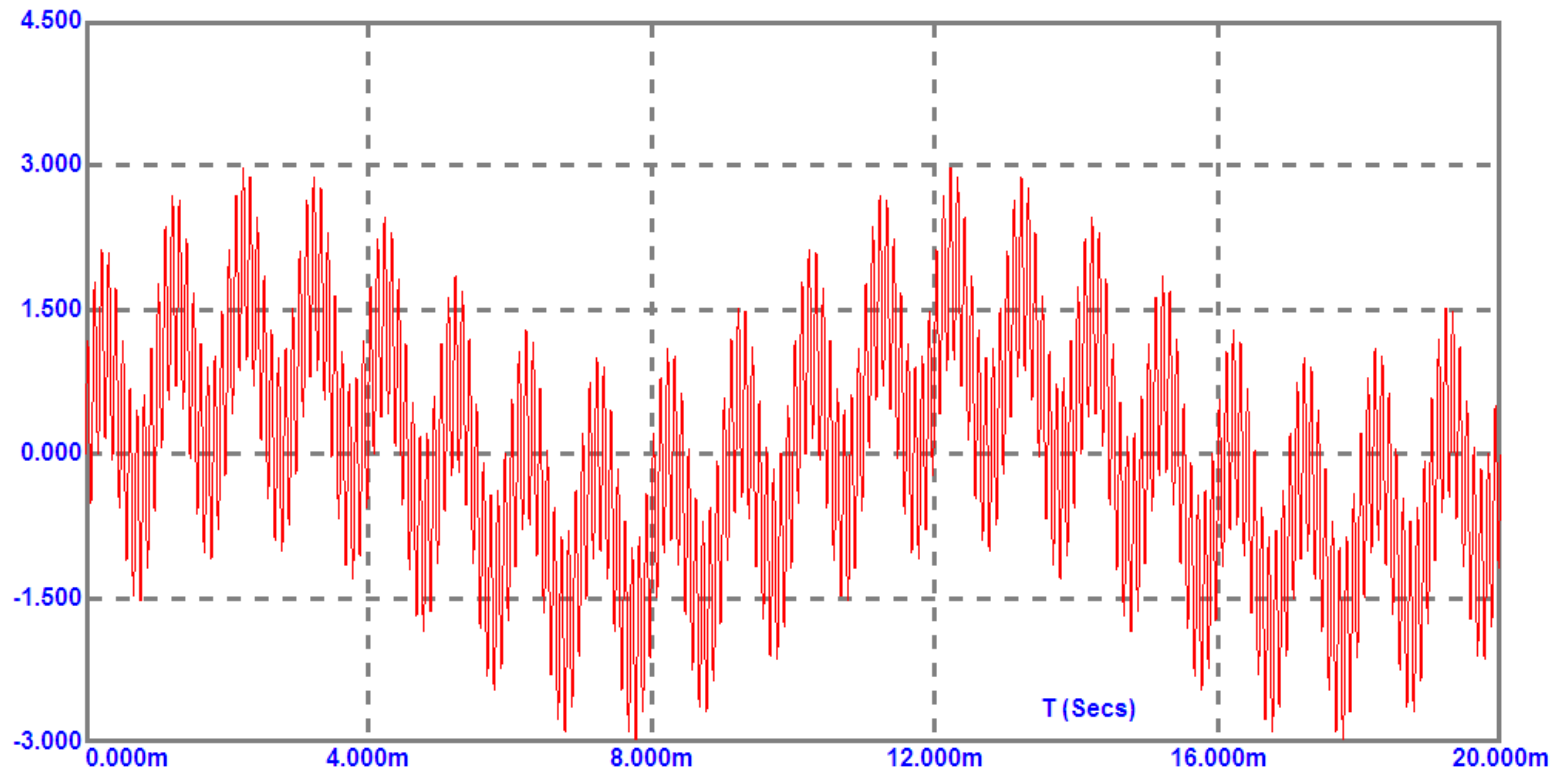

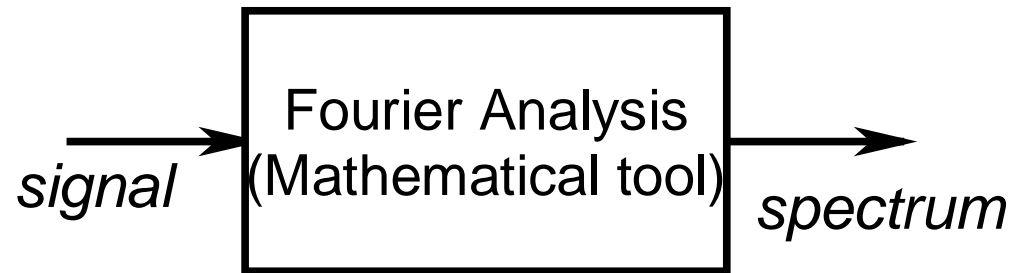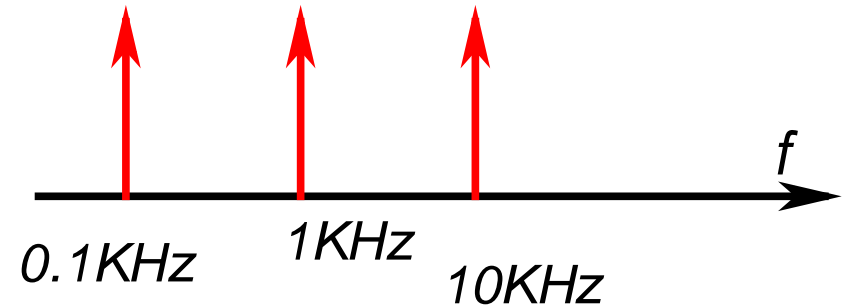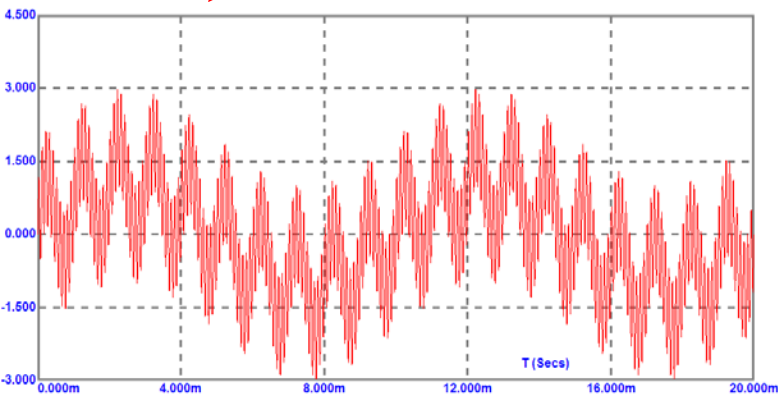
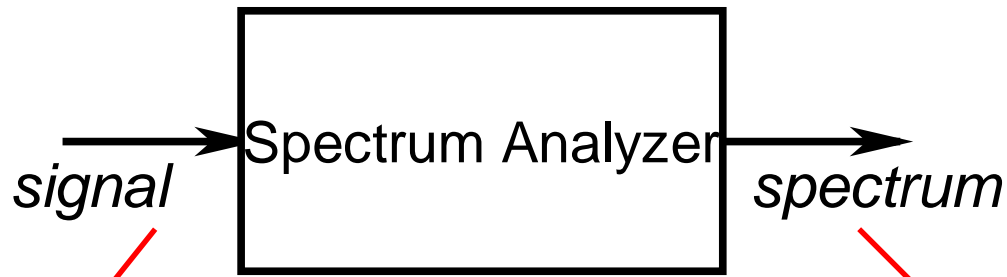


Speech signal

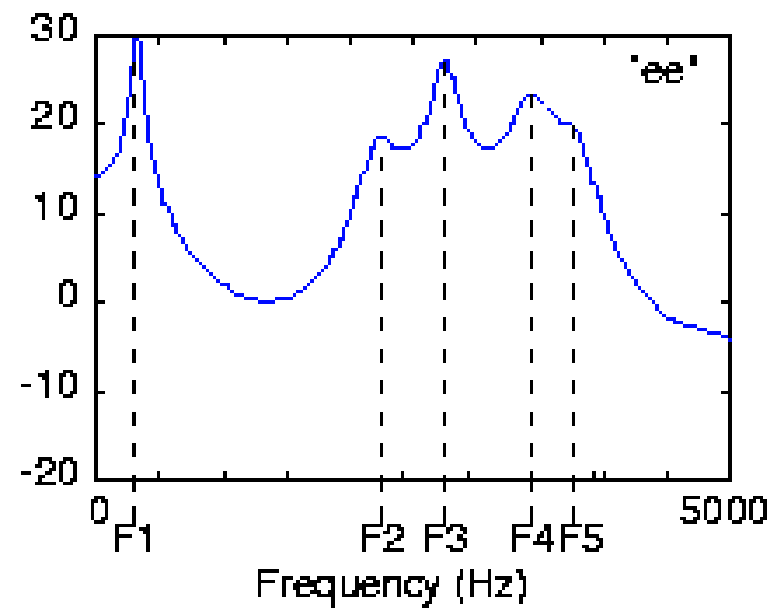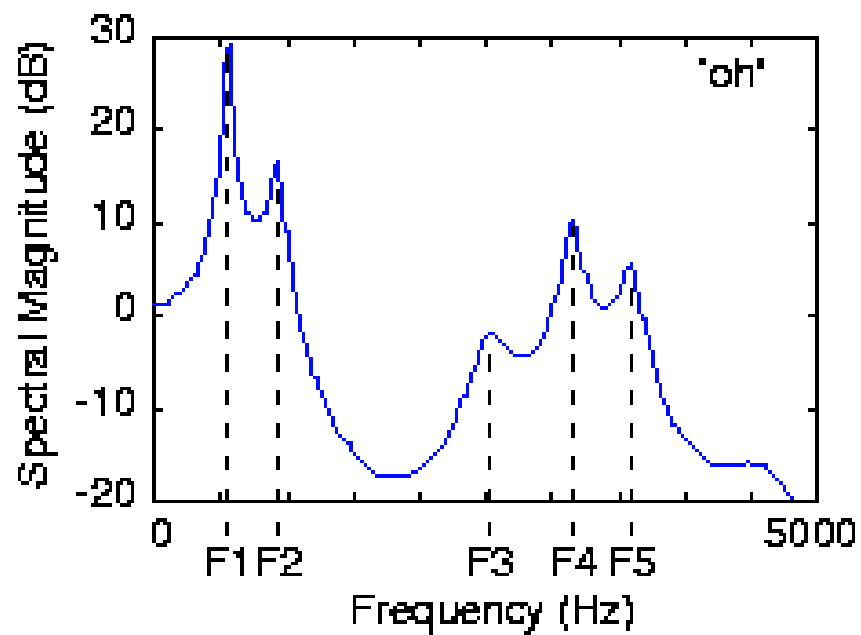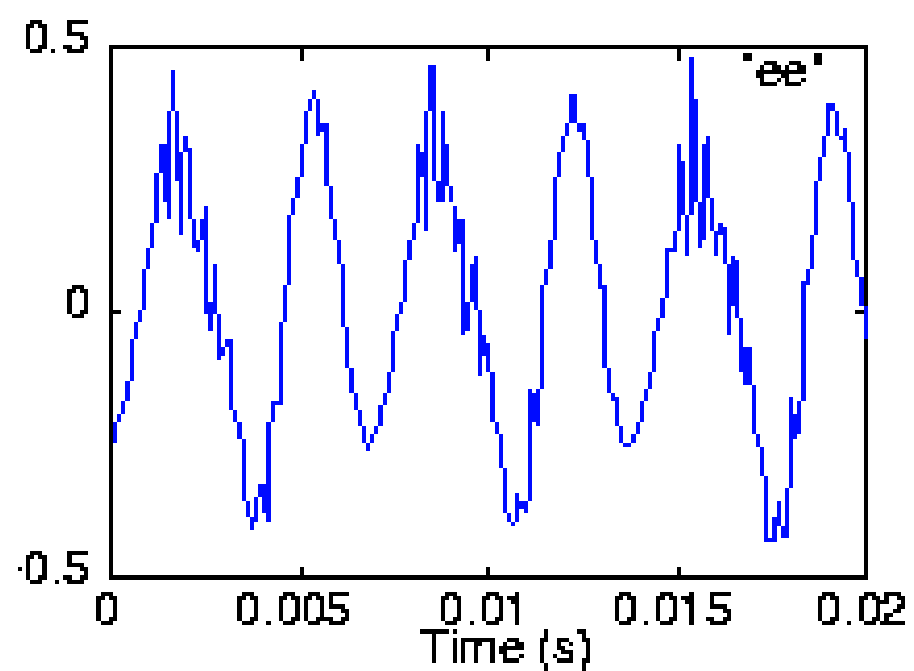
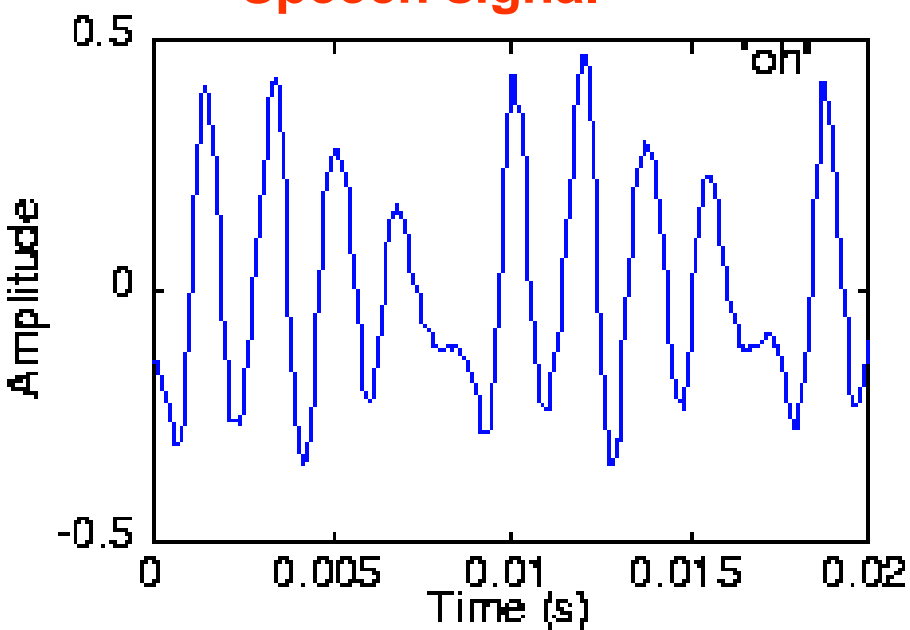


System

What does this circuit do ?

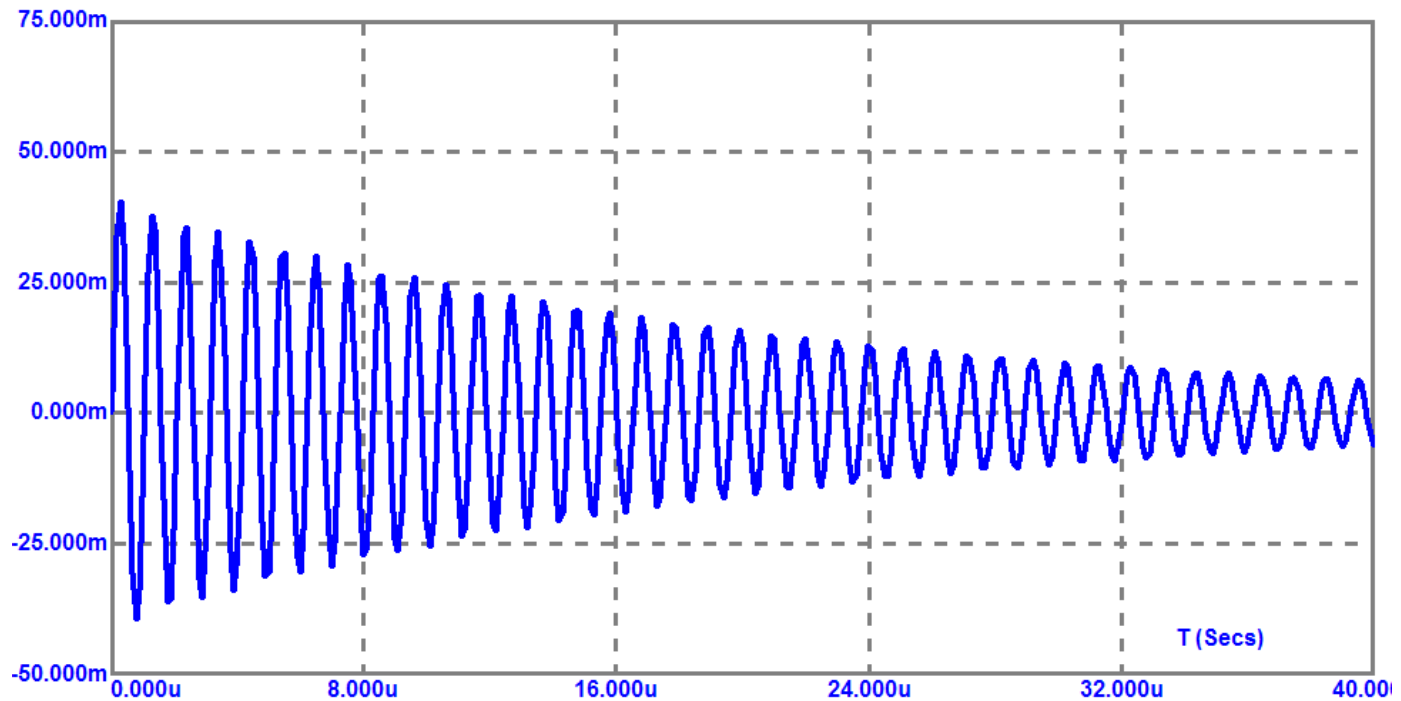
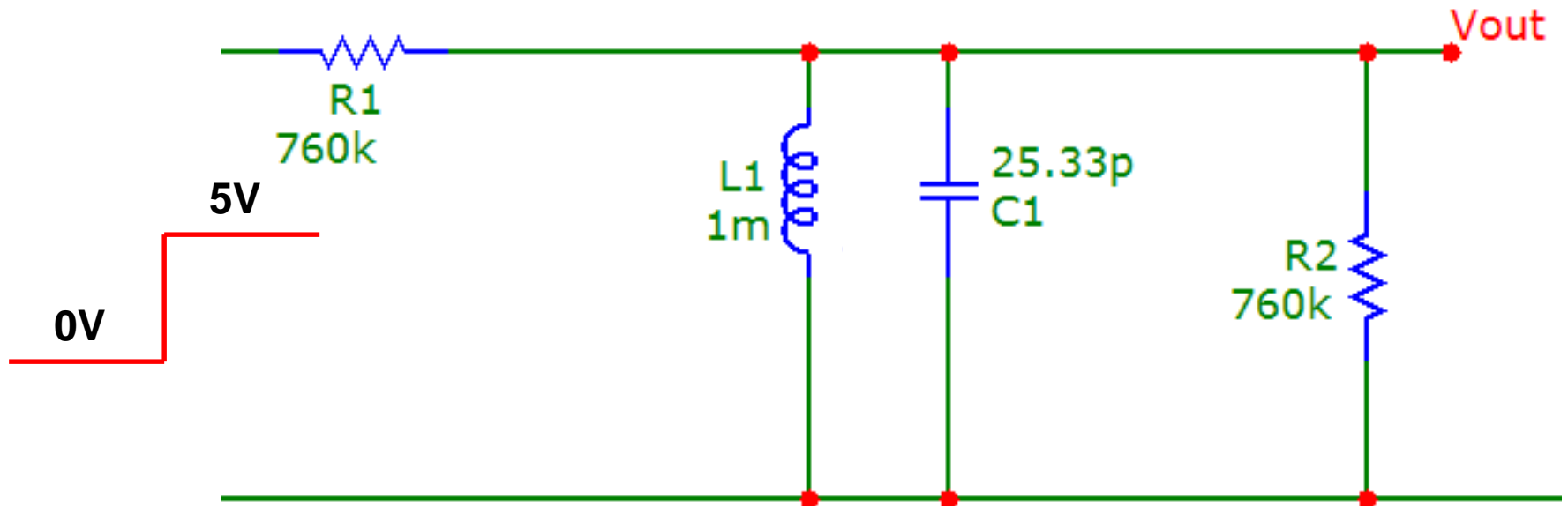


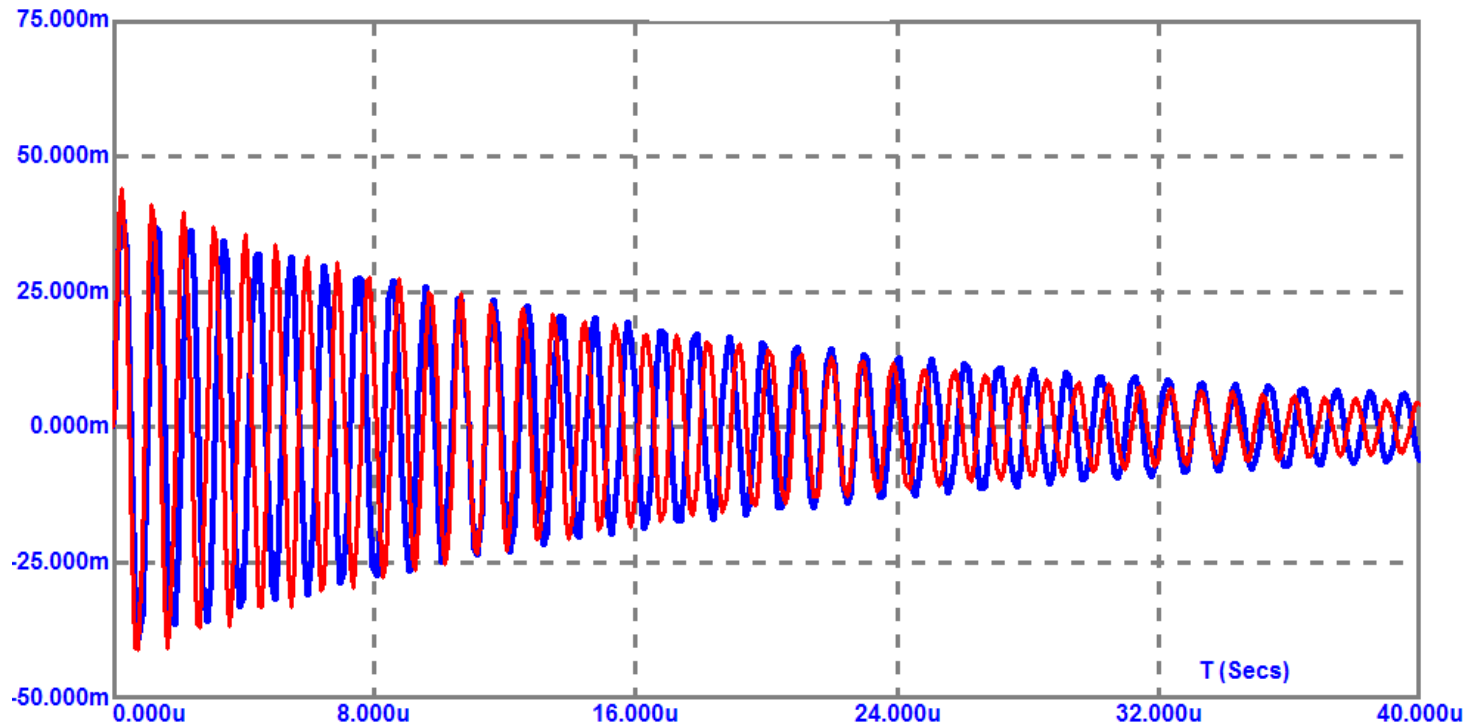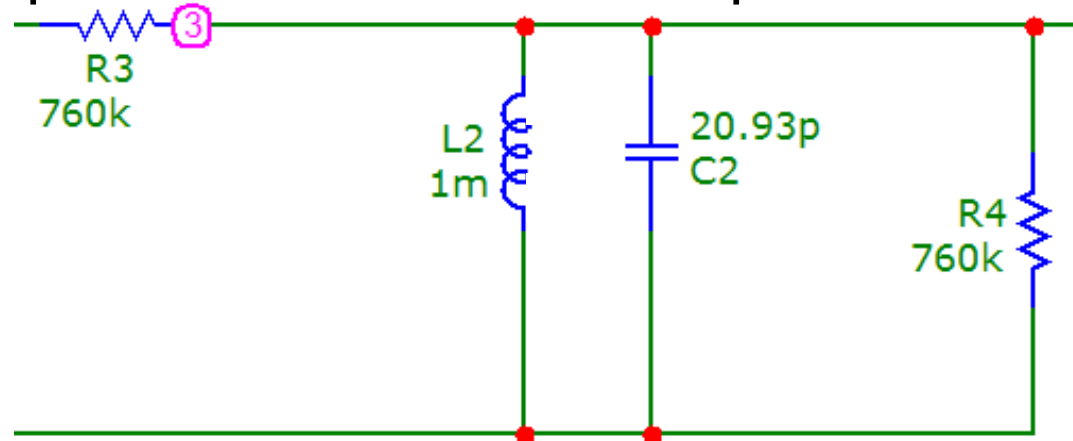Suppose the capacitor is reduced to $\sim 21\text{pF}$.





It is hard to find out what impact the change in capacitor has on circuit behavior


Frequency domain analysis

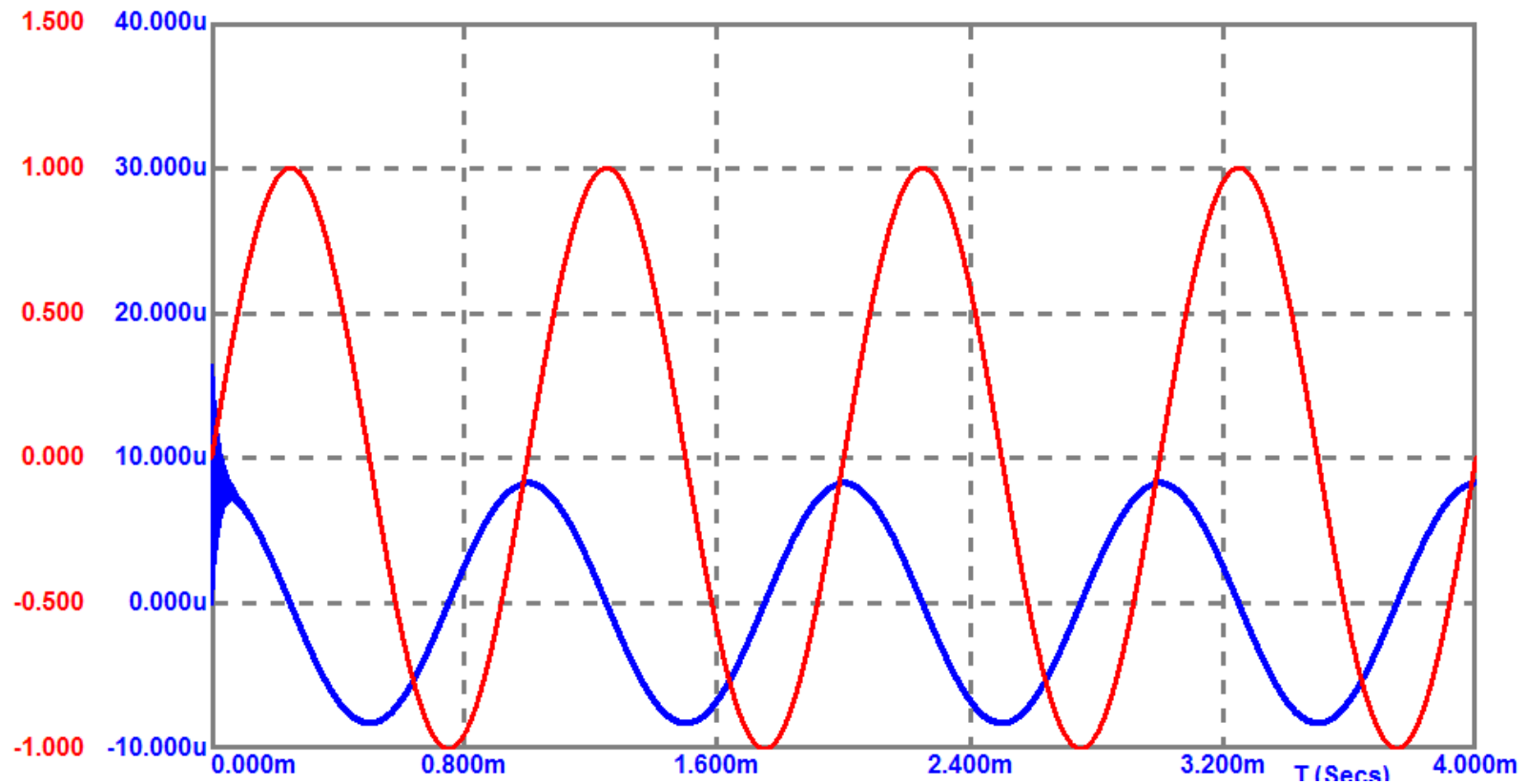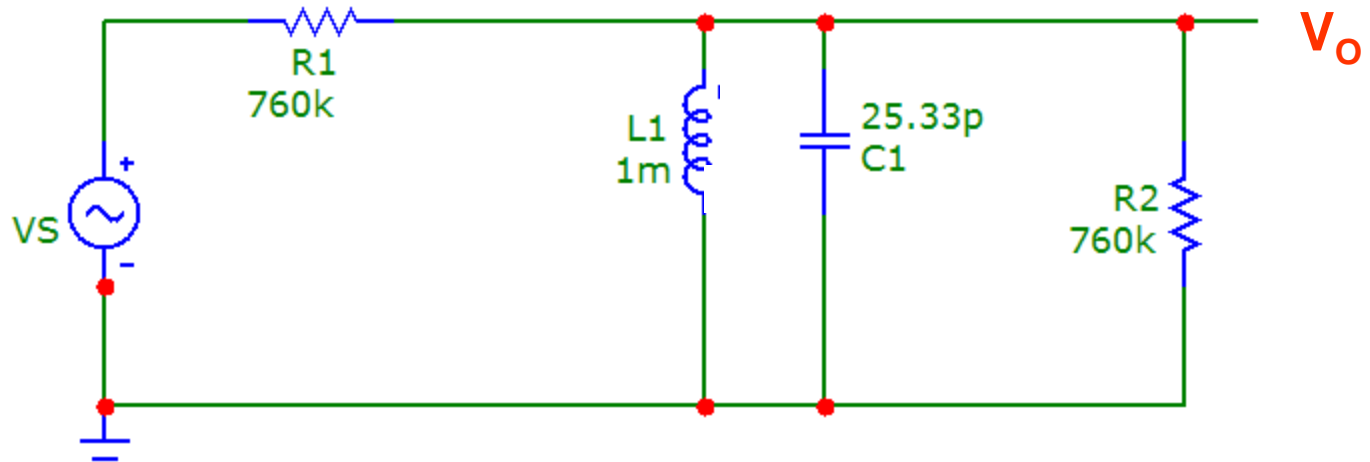

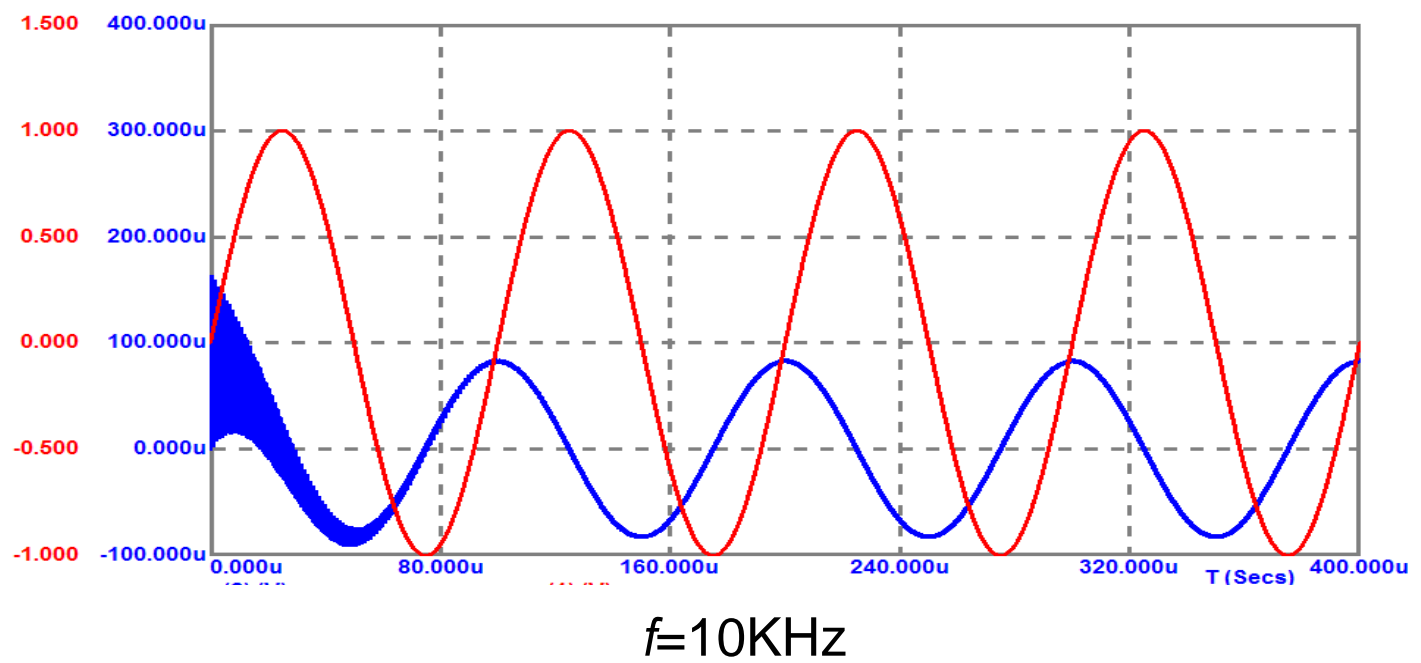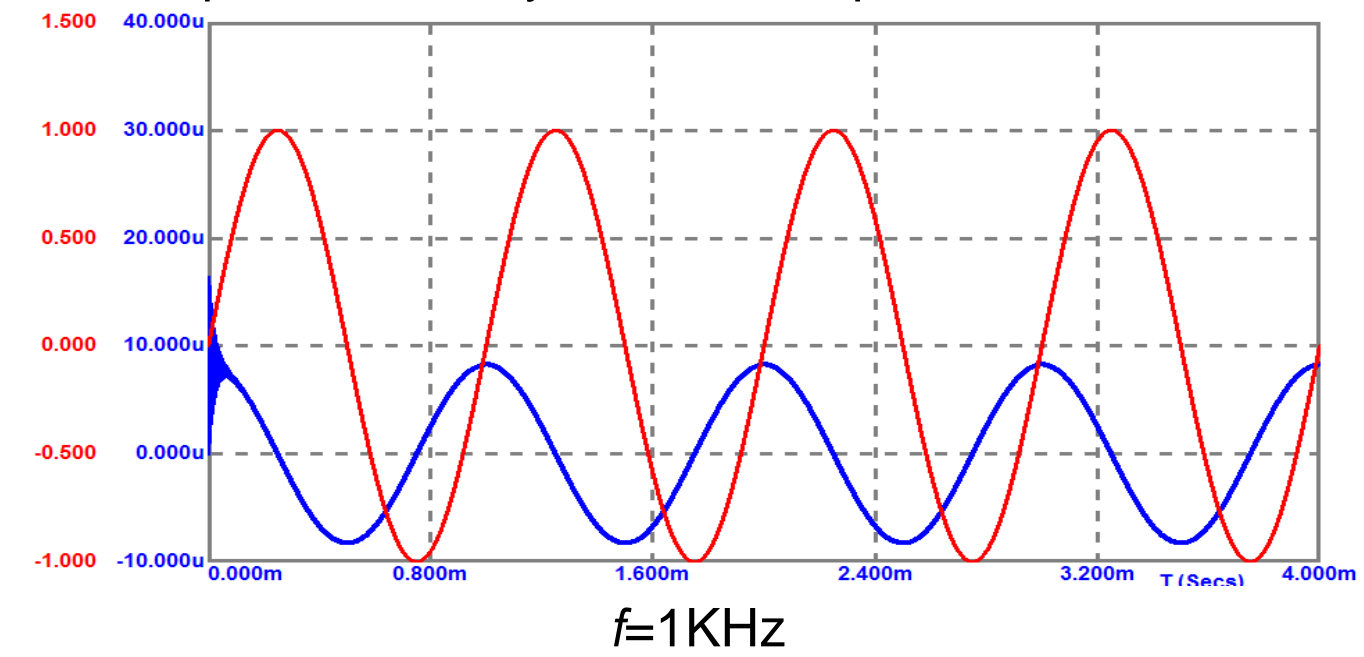
Measure response at many different frequencies for a constant input amplitude



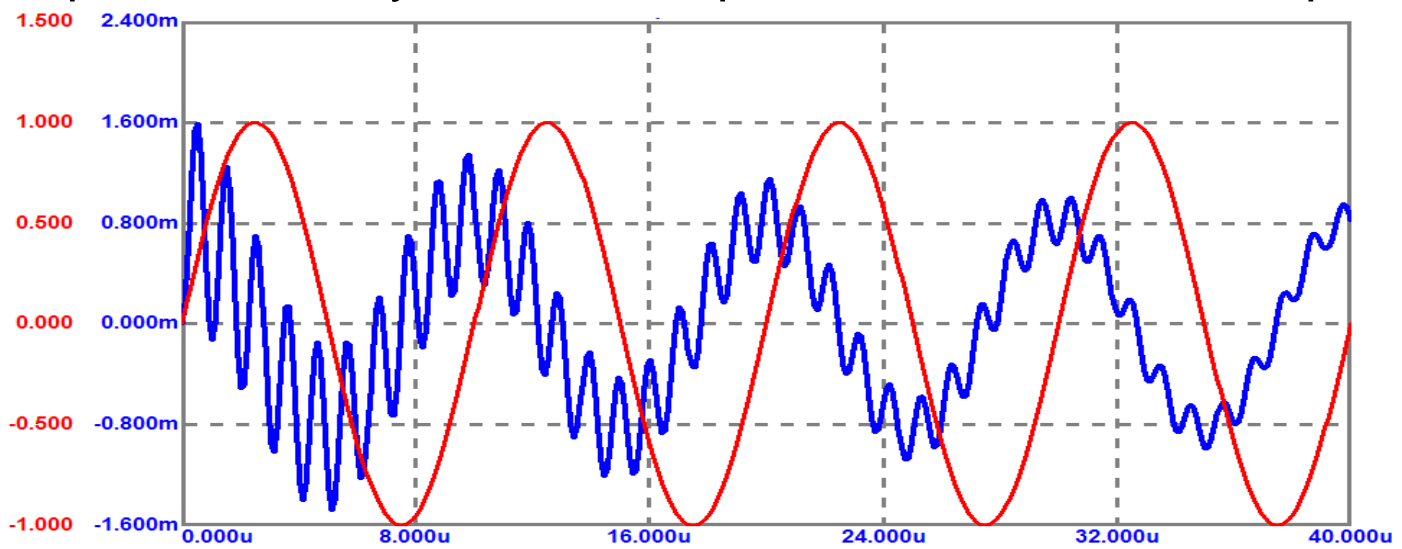Measure response at many different frequencies for a constant input amplitude




$f=100\text{KHz}$

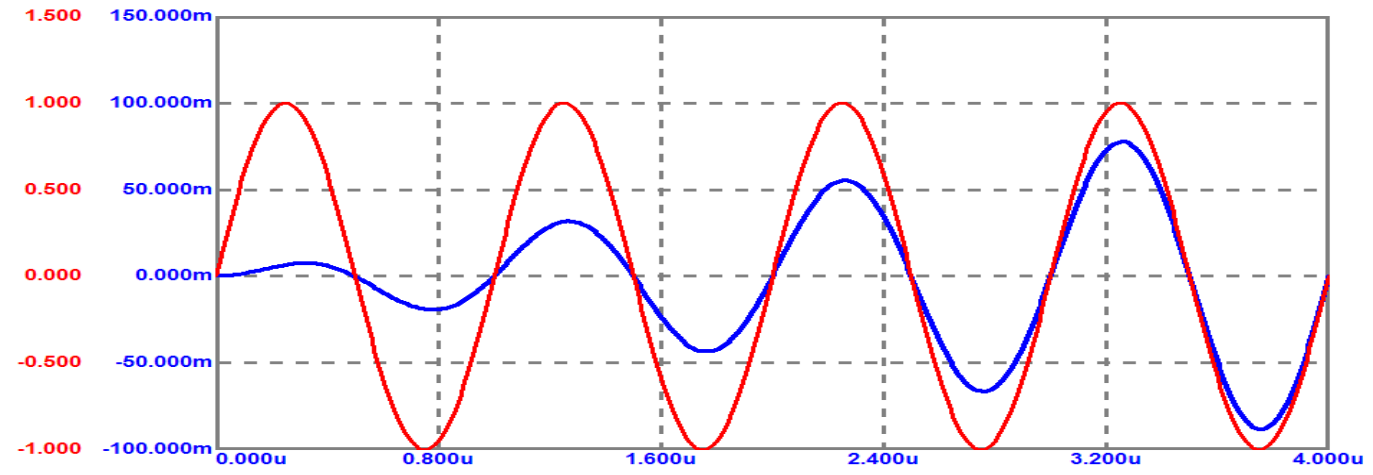

$f=1000\text{KHz}$


Plot the amplitude and phase as a function of frequency

Amplitude as a function of frequency


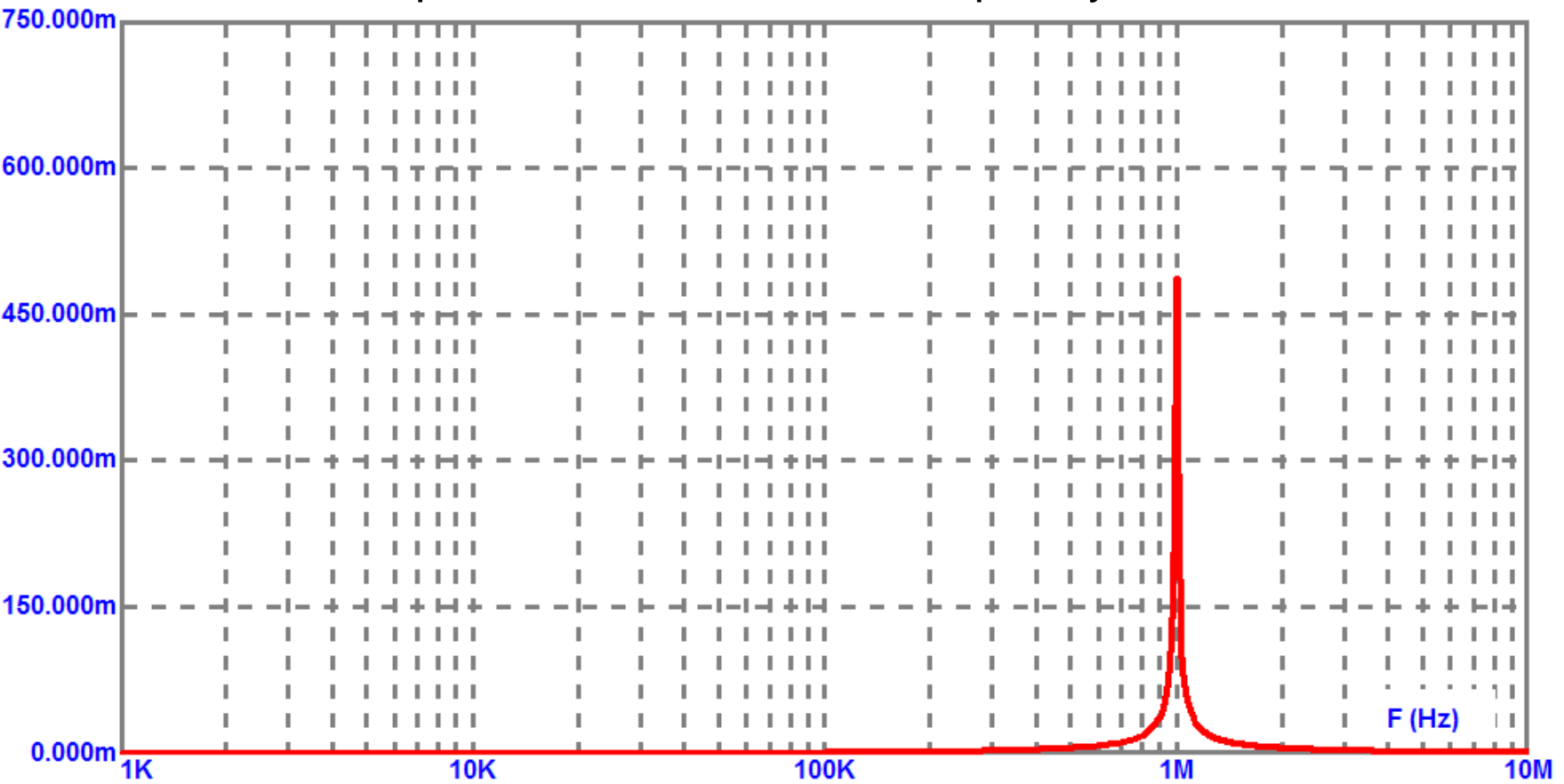


One can clearly see the frequency selective (often called a filter) nature of the circuit

Phase as a function of frequency

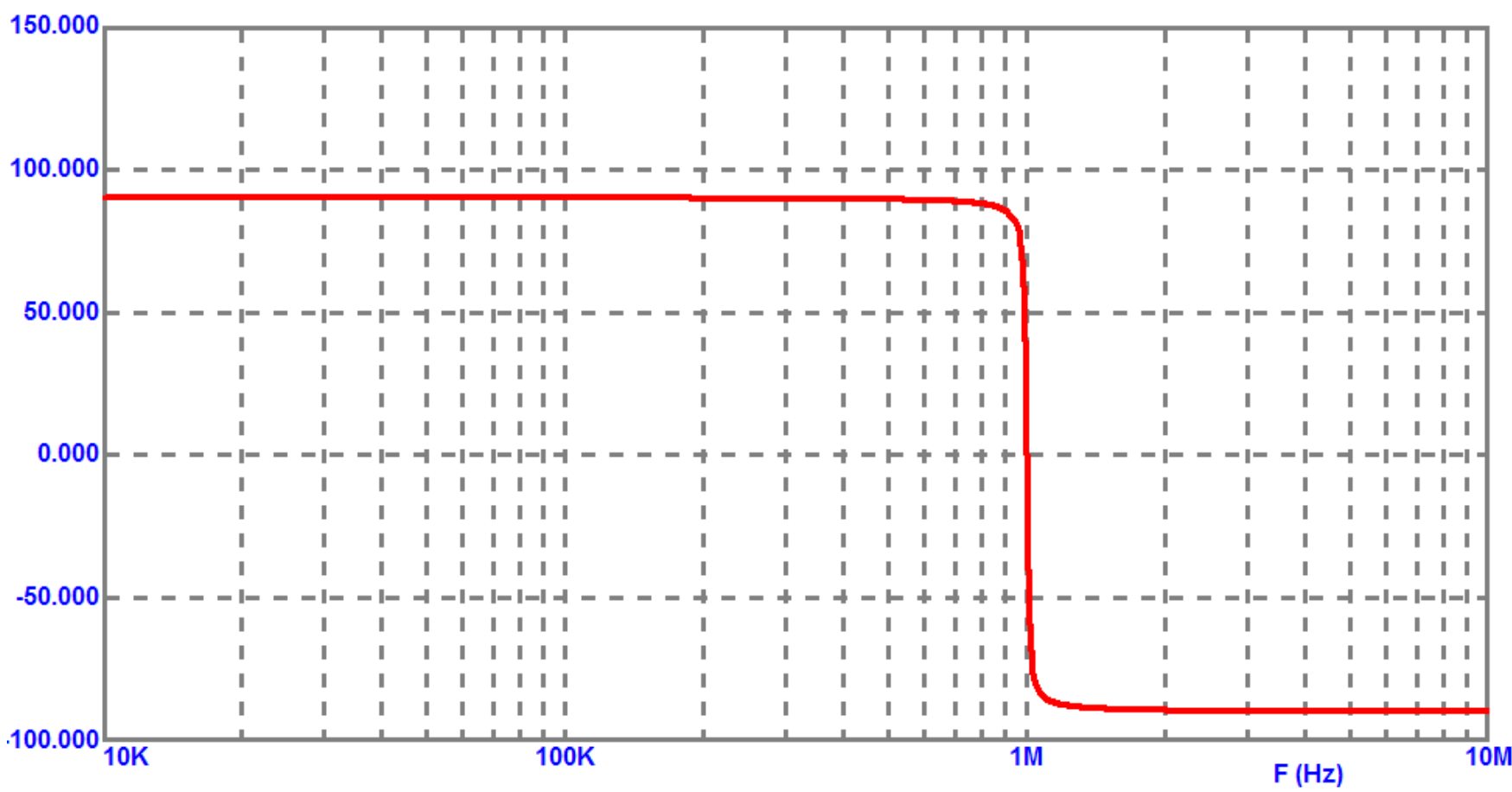

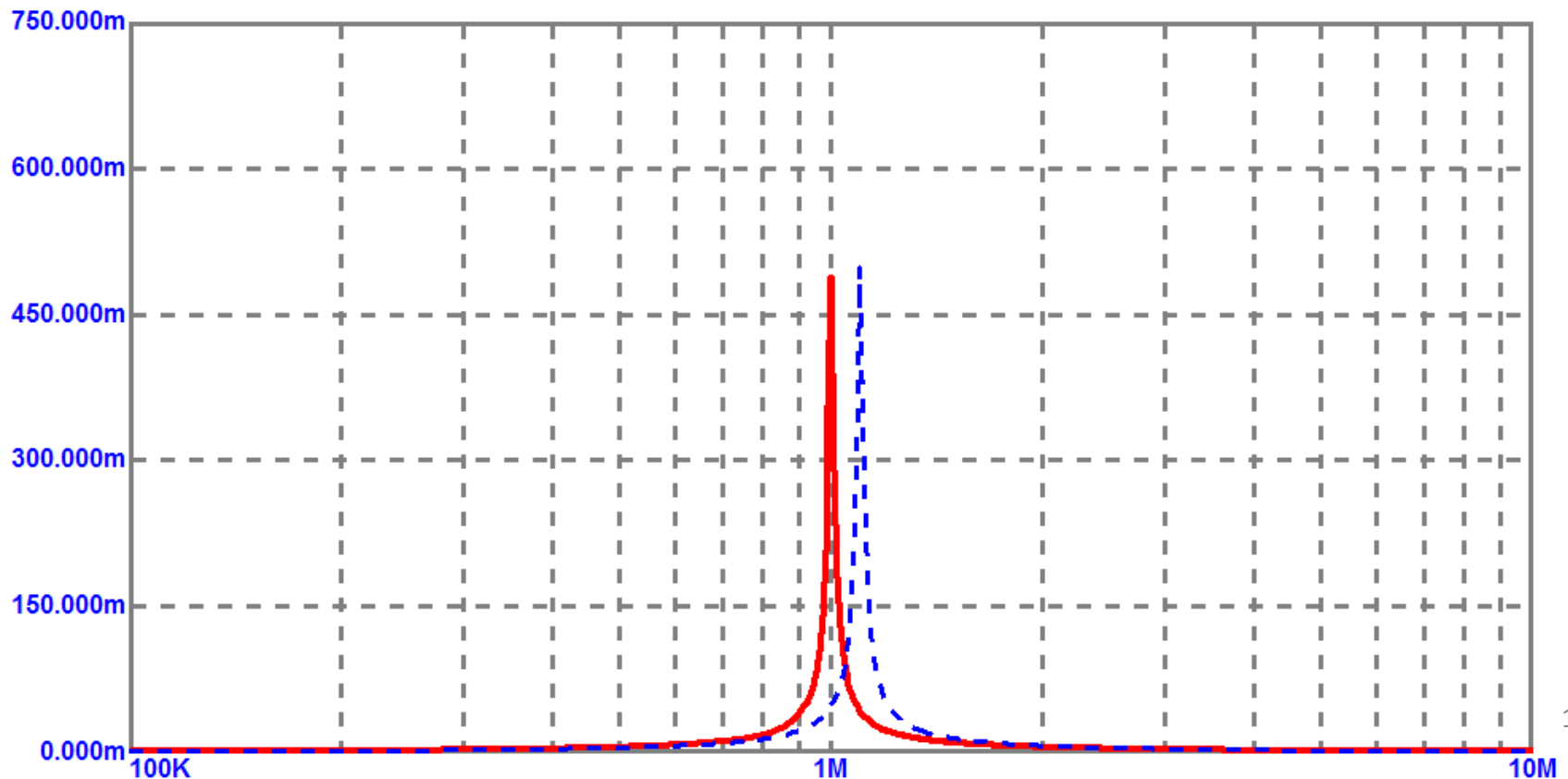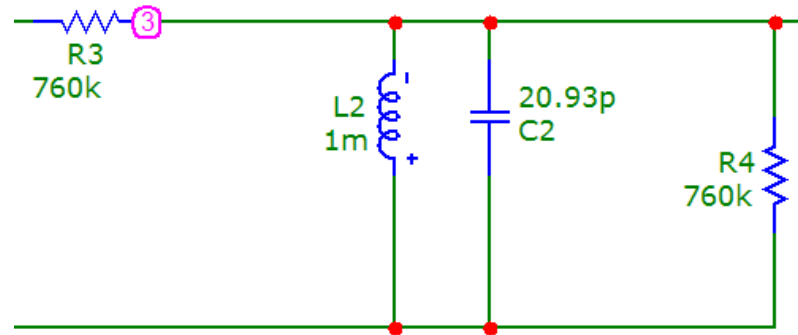
Suppose the capacitor is reduced to $\sim 21\text{pF}$.



Analysis of signals and systems in frequency domain often provides useful insight into their behavior.

Frequency domain analysis

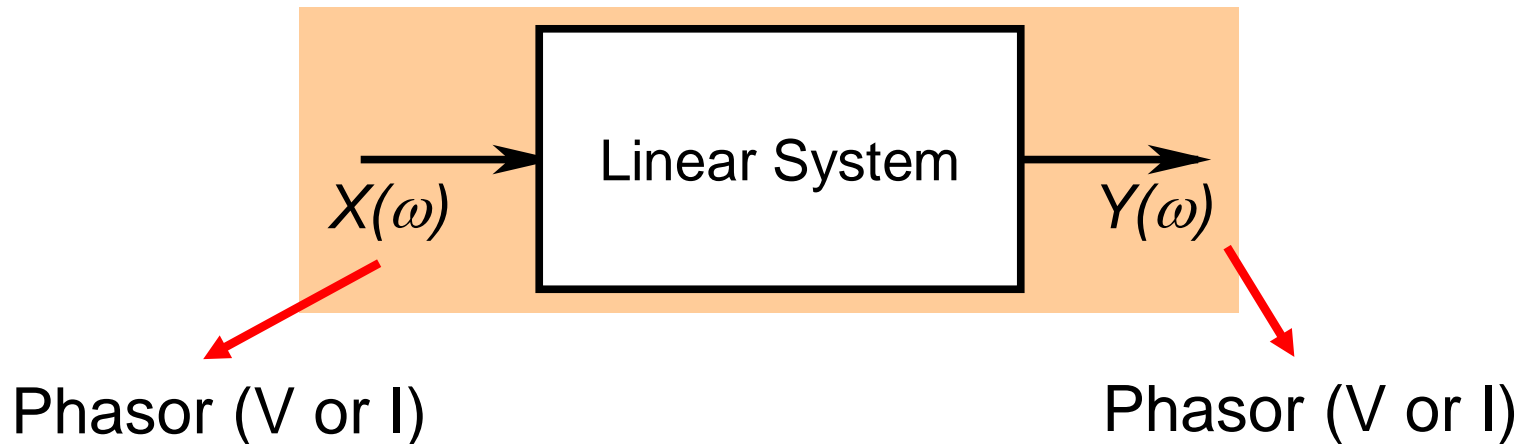Transfer function is a useful tool for finding the frequency response of a system



$$\text{Transfer Function: } H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

Transfer function has a magnitude and a phase

$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$



$$\mathbf{H}(\omega) = \text{Voltage gain} = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Current gain} = \frac{\mathbf{I}_o(\omega)}{\mathbf{I}_i(\omega)}$$


$$\mathbf{H}(\omega) = \text{Transfer Impedance} = \frac{\mathbf{V}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Transfer Admittance} = \frac{\mathbf{I}_o(\omega)}{\mathbf{V}_i(\omega)}$$

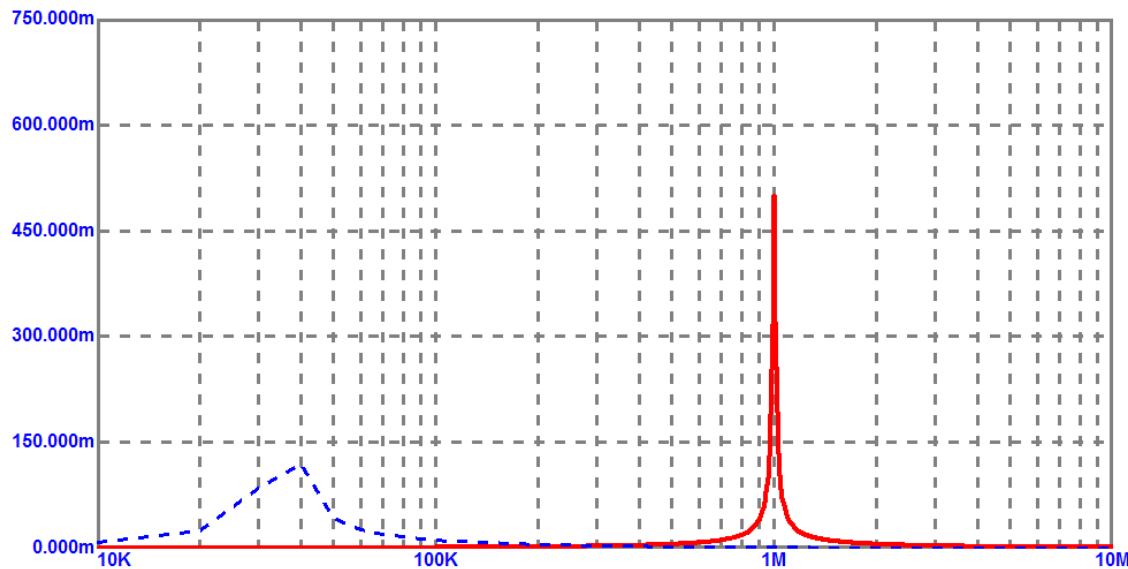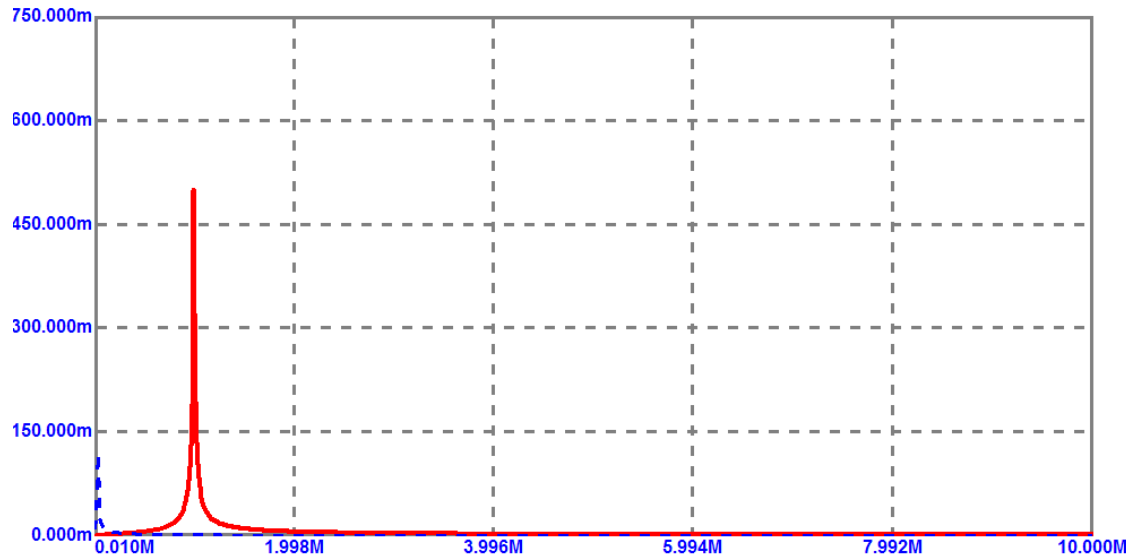Because of the wide dynamic range of frequency, plotting frequency on log axis is often more revealing !




Logarithmic frequency scale

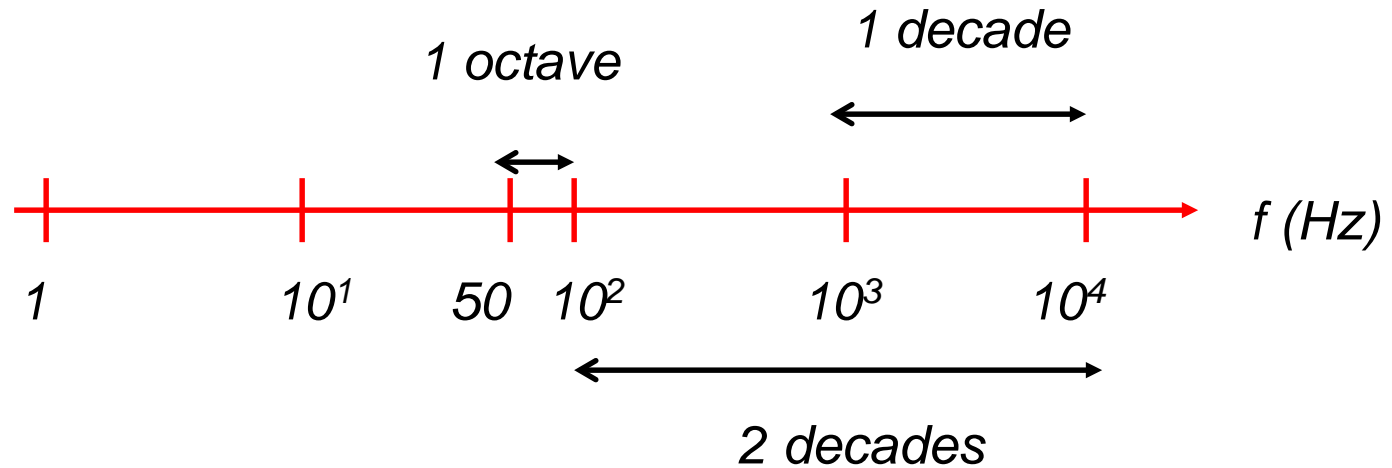

$$\text{No. of decades} = \log_{10}\left(\frac{f_2}{f_1}\right)$$

$$\text{No. of octaves} = \log_2\left(\frac{f_2}{f_1}\right) = \frac{\log_{10}\left(\frac{f_2}{f_1}\right)}{\log_{10}(2)}$$

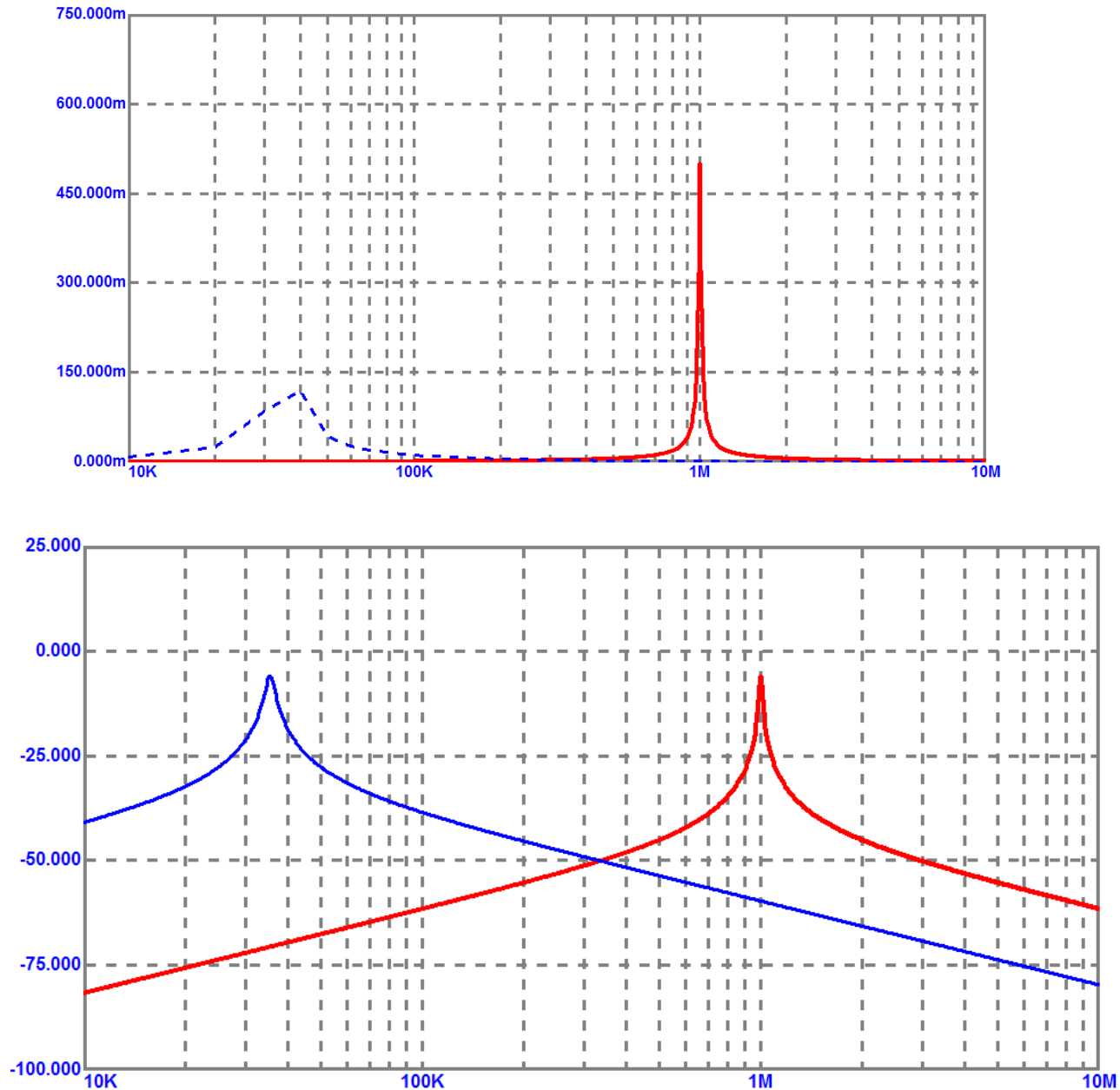Decibel scale often reveals more information about behavior



The magnitude of transfer function is often specified in **decibels**

$$G_{dB} = 10 \log_{10} \left(\frac{P_2}{P_1} \right)$$

Because power is proportional to V^2 or I^2 , voltage gain and current gain in decibels is specified as

$$G_{dB} = 20 \log_{10} \left(\frac{V_2}{V_1} \right)$$


$$G_{dB} = 20 \log_{10} \left(\frac{I_2}{I_1} \right)$$

Decibel scale is more convenient for our perception of hearing

Decibel Scale


$ H $	$20\text{Log}_{10}(H)$
1000	60
100	40
10	20
2	6
$\sqrt{2}$	3
1	0
$1/\sqrt{2}$	-3
0.5	-6
0.1	-20
0.01	-40

dB Scale

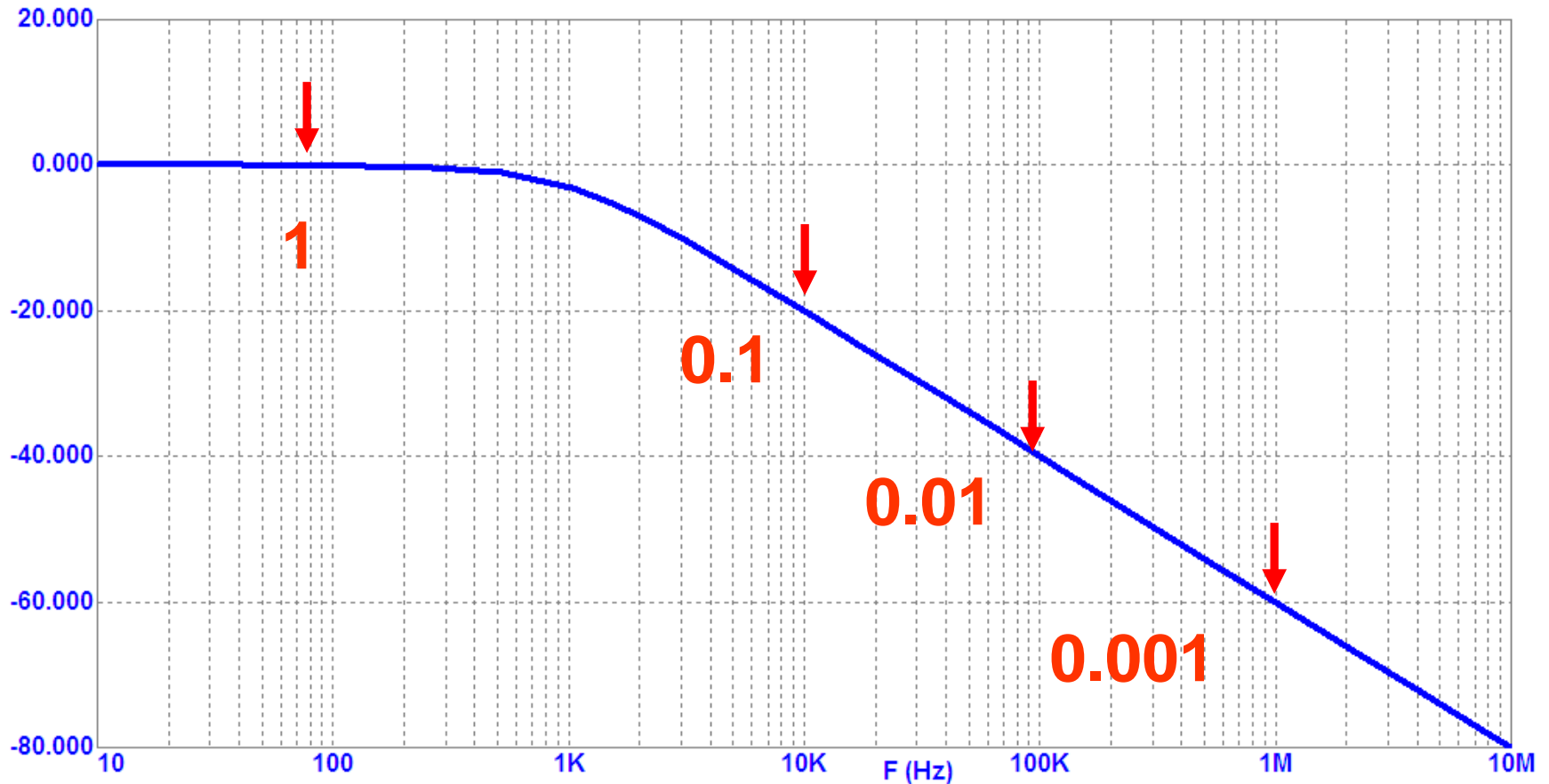


A plot of the decibel magnitude of transfer function versus frequency using a logarithmic scale for frequency is called a **Bode plot**

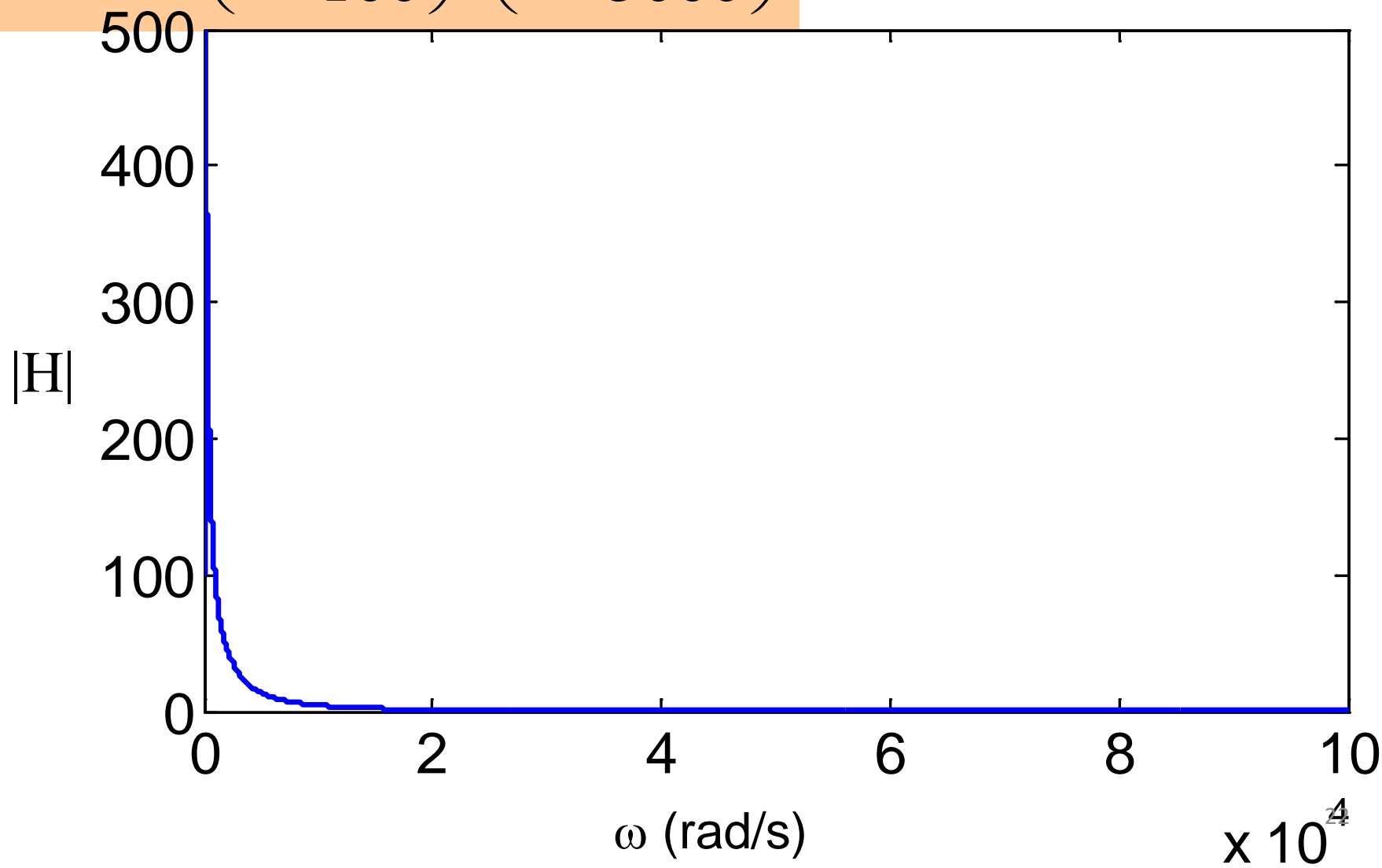
$$H(j\omega) = \frac{10j\omega}{\left(1 + \frac{j\omega}{100}\right)^2 \left(1 + \frac{j\omega}{5000}\right)}$$



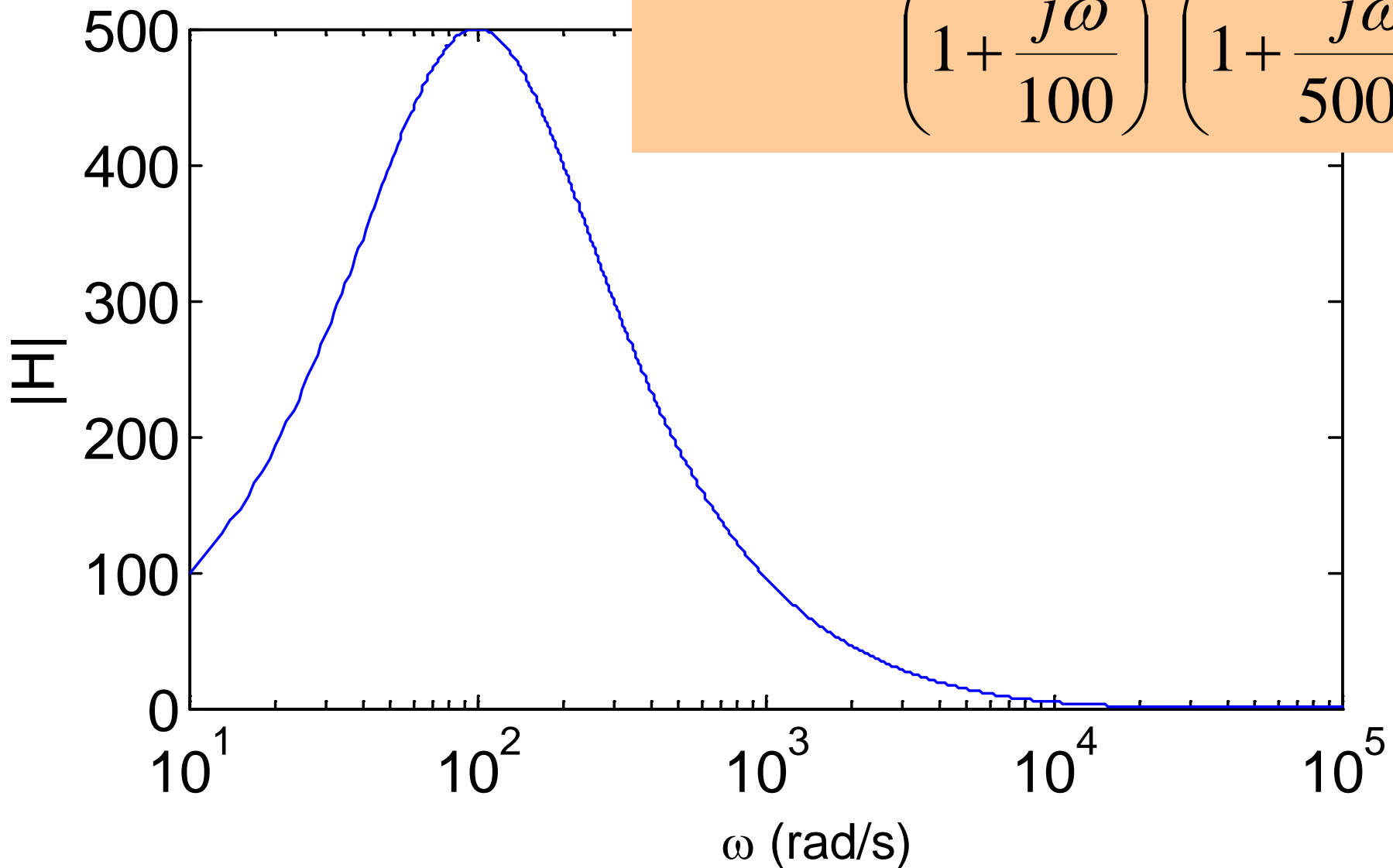
$$H(j\omega) = \frac{10j\omega}{\left(1 + \frac{j\omega}{100}\right)^2 \left(1 + \frac{j\omega}{5000}\right)}$$


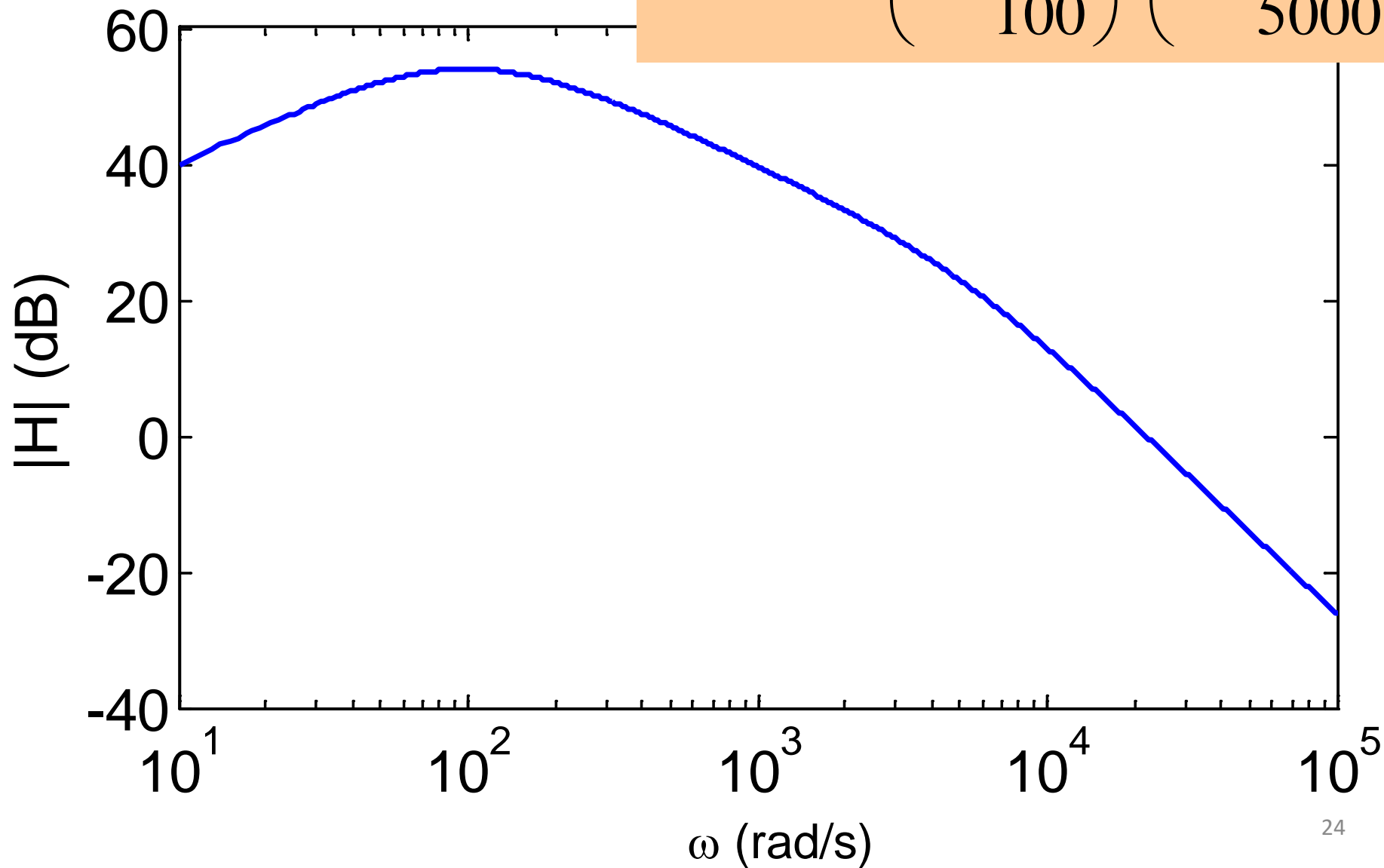
$$H(j\omega) = \frac{10j\omega}{\left(1 + \frac{j\omega}{100}\right)^2 \left(1 + \frac{j\omega}{5000}\right)}$$



How to determine the transfer function?

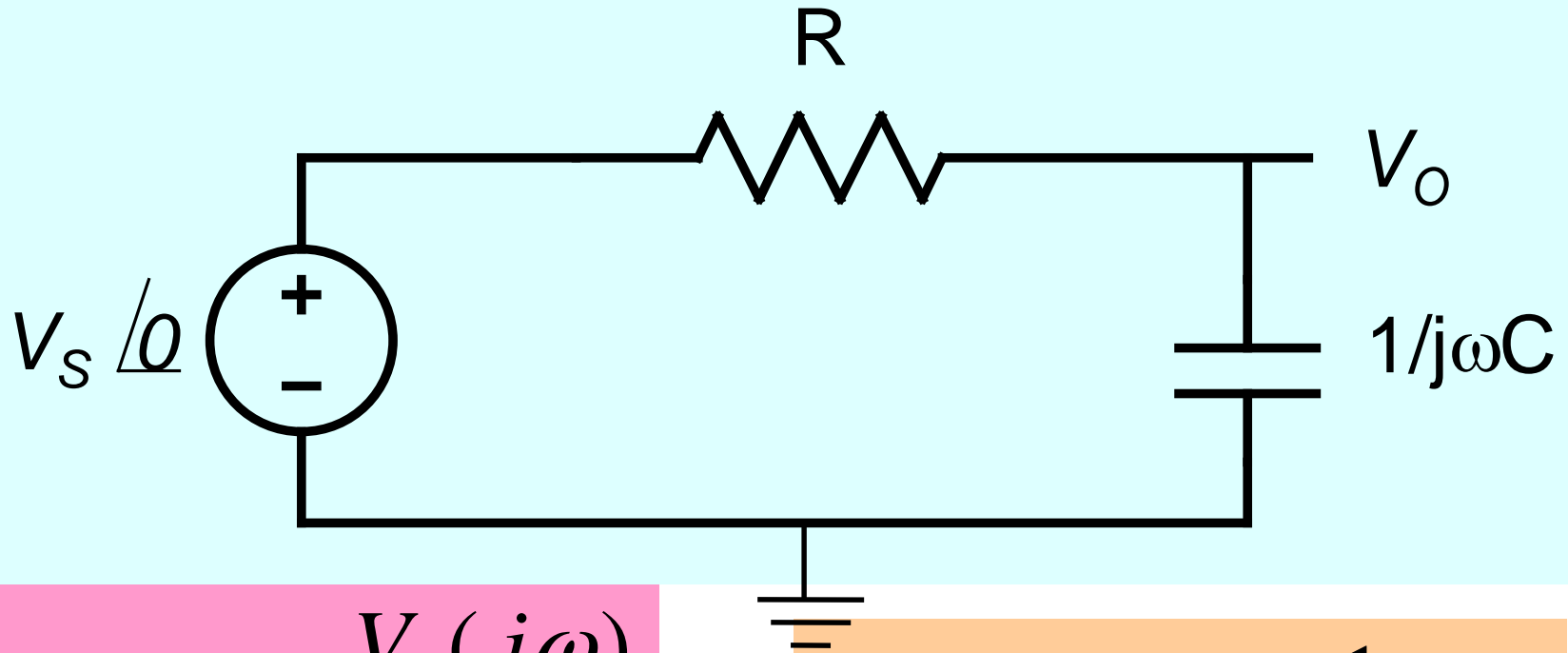

$$H(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)}$$

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\phi(\omega) = -\tan^{-1}(\omega CR)$$

Plot Magnitude

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$H_{dB} = -20 \log_{10} \sqrt{1 + (\omega RC)^2}$$

$$\omega_{3dB} = \frac{1}{RC}$$

$$H_{dB} = -20 \log_{10} \sqrt{1 + \left(\frac{\omega}{\omega_{3dB}} \right)^2}$$

$$\omega \ll \omega_{3dB}$$

$$H_{dB} \approx -20 \log_{10}(1) = 0$$

$$\omega \gg \omega_{3dB}$$

$$H_{dB} \approx -20 \log_{10} \left(\frac{\omega}{\omega_{3dB}} \right)$$

$$\omega \gg \omega_{3dB}$$

$$H_{dB} \approx -20 \log_{10} \left(\frac{\omega}{\omega_{3dB}} \right)$$


ω	H_{dB}
ω_{3dB}	0
$10 \omega_{3dB}$	-20
$100 \omega_{3dB}$	-40

-20 dB per decade

$$\log_{10} 10 = 1$$

3dB point

$$\omega_{3dB} = \frac{1}{RC}$$

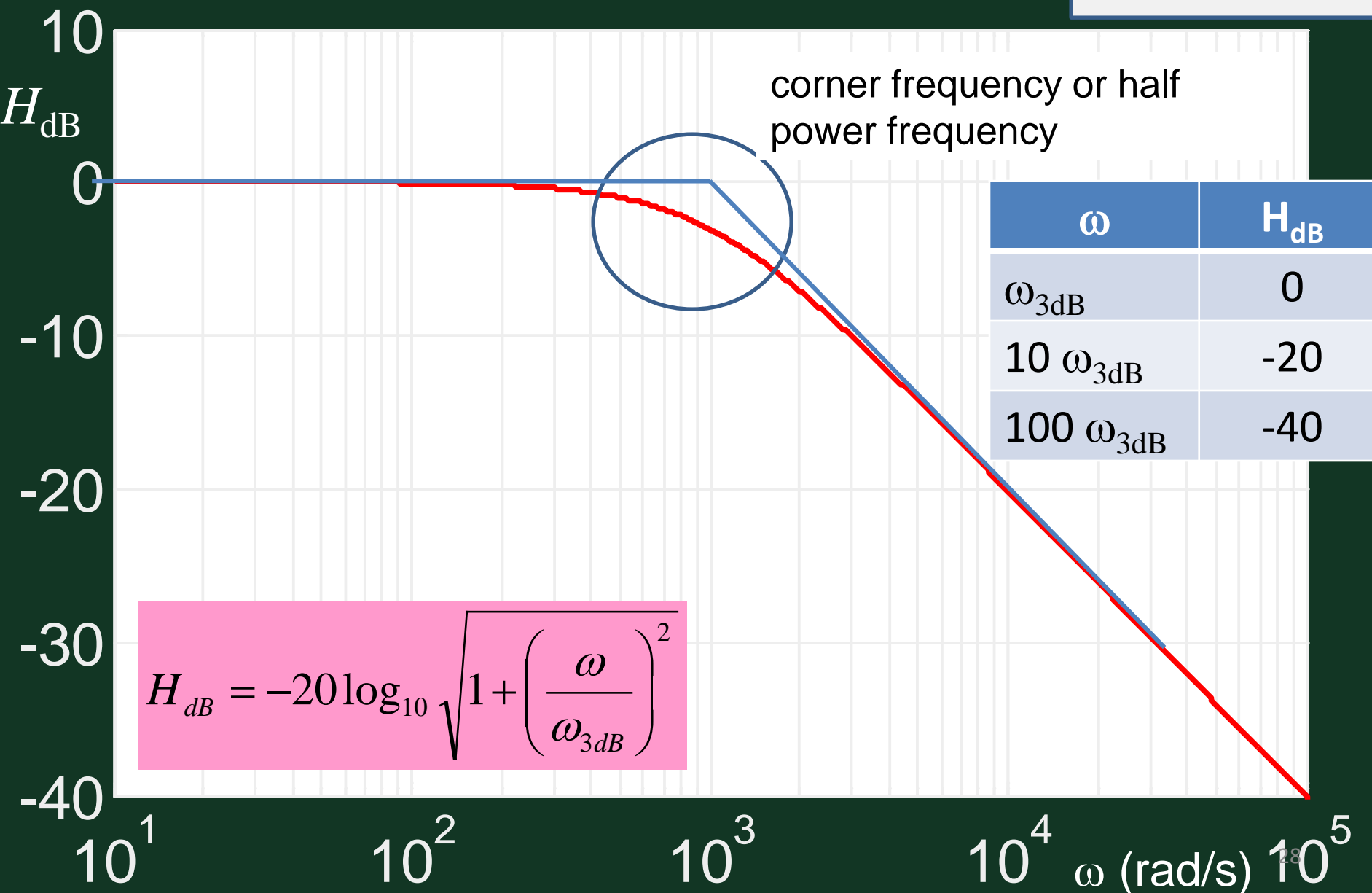

Example


$$H(j\omega) = \frac{10}{1 + j\omega 10^{-3}}$$




$$\omega_{3dB} = 10^3$$

$$H_{dB} = 20 - 20 \log_{10} \sqrt{1 + \left(\frac{\omega}{10^3} \right)^2}$$

$$\omega \ll 10^3 : 0dB$$

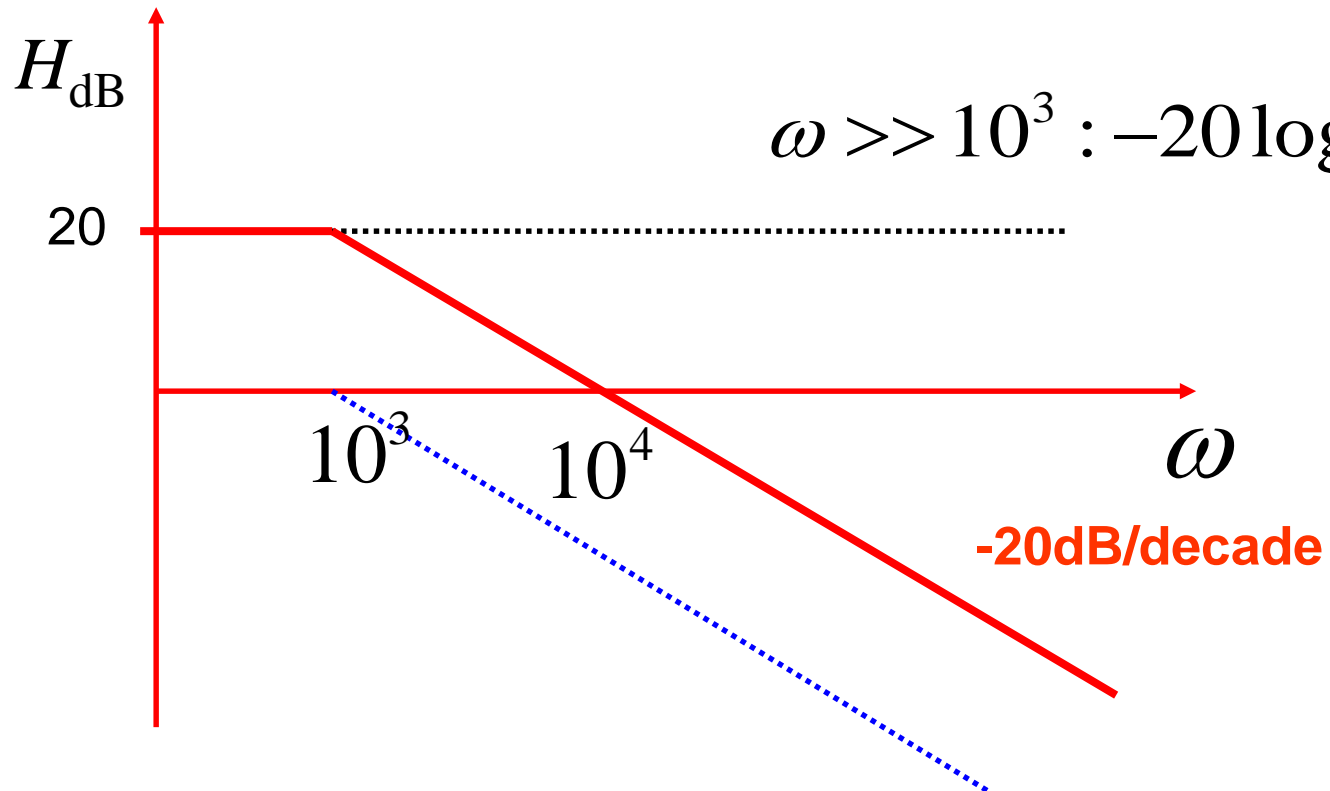
$$\omega \gg 10^3 : -20 \log_{10} \frac{\omega}{10^3}$$



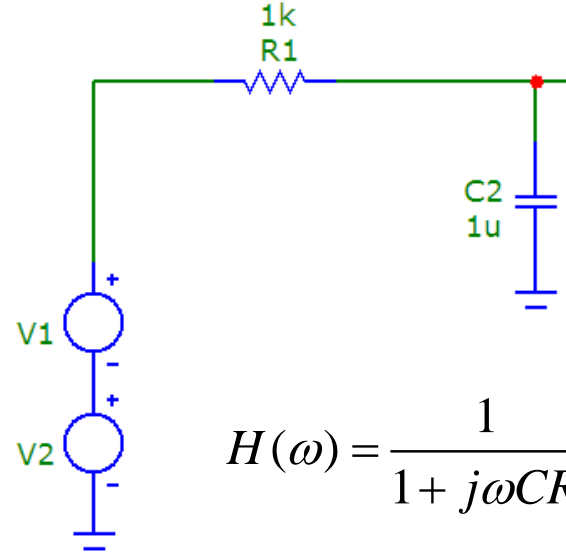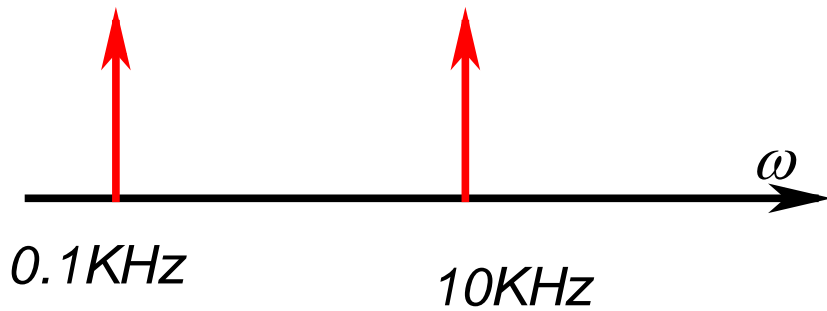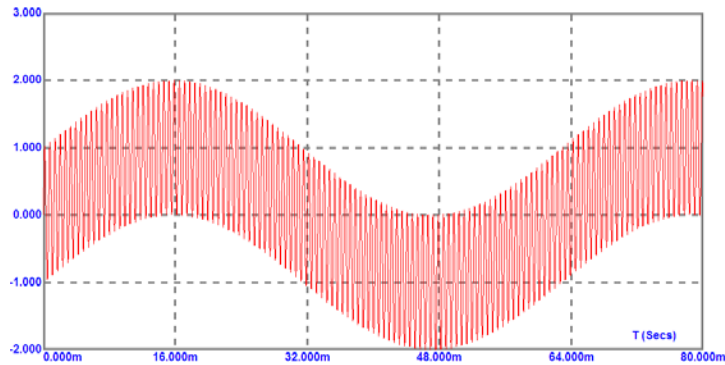






$$H(\omega) = \frac{1}{1 + j\omega CR}$$



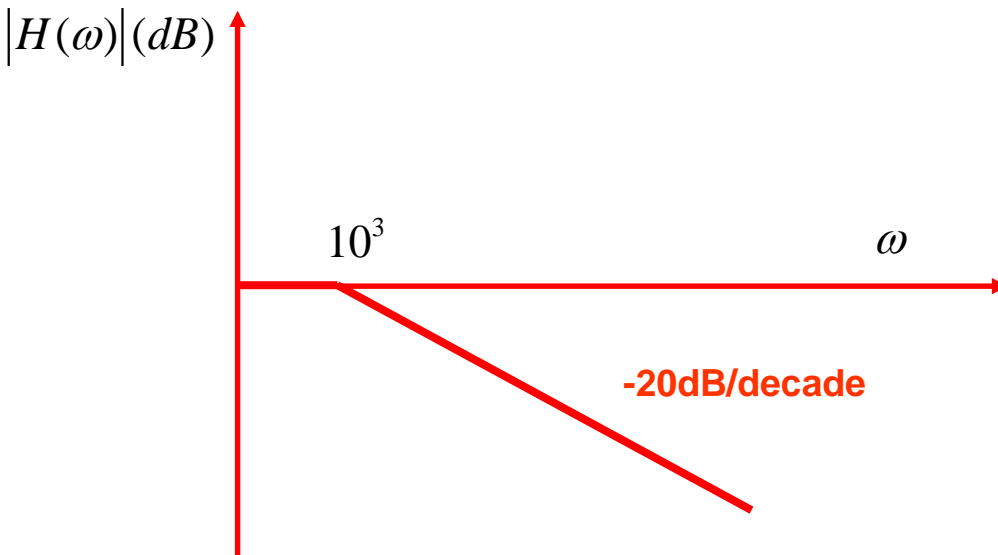
$$H(\omega) = \frac{1}{1 + j\omega 10^{-3}} = \frac{1}{1 + j\frac{\omega}{10^3}}$$



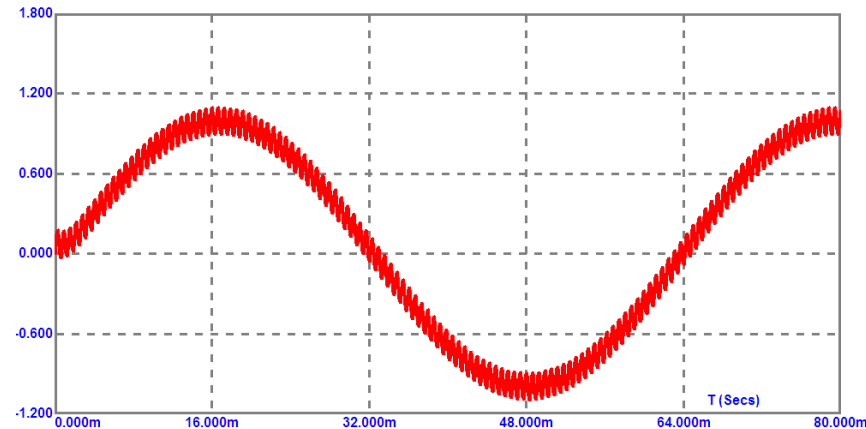
$$V_o(t) = 1\sin(100t) + 0.1\sin(10^4 t)$$



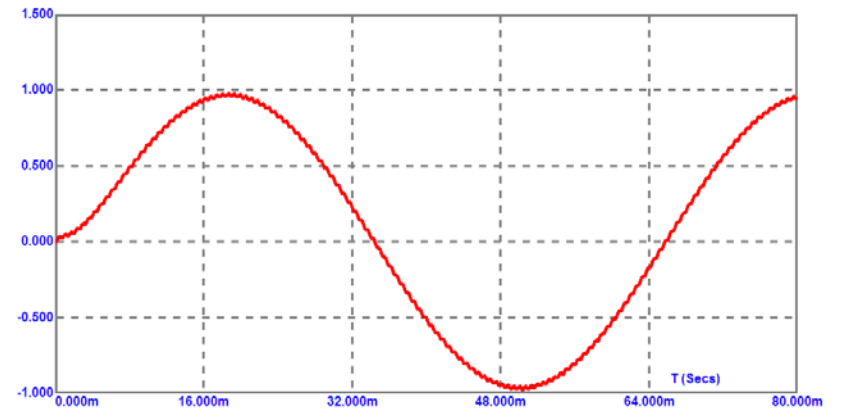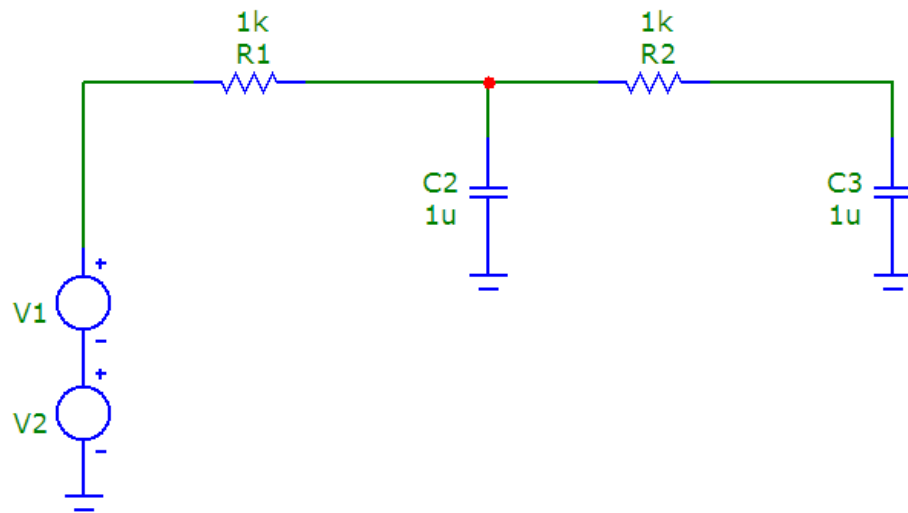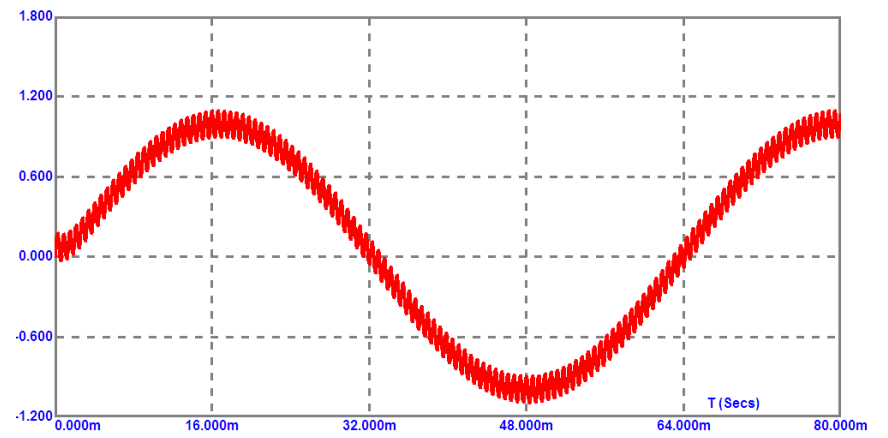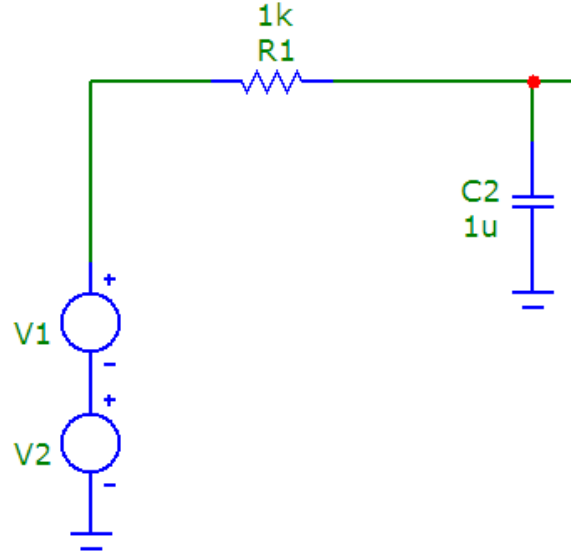

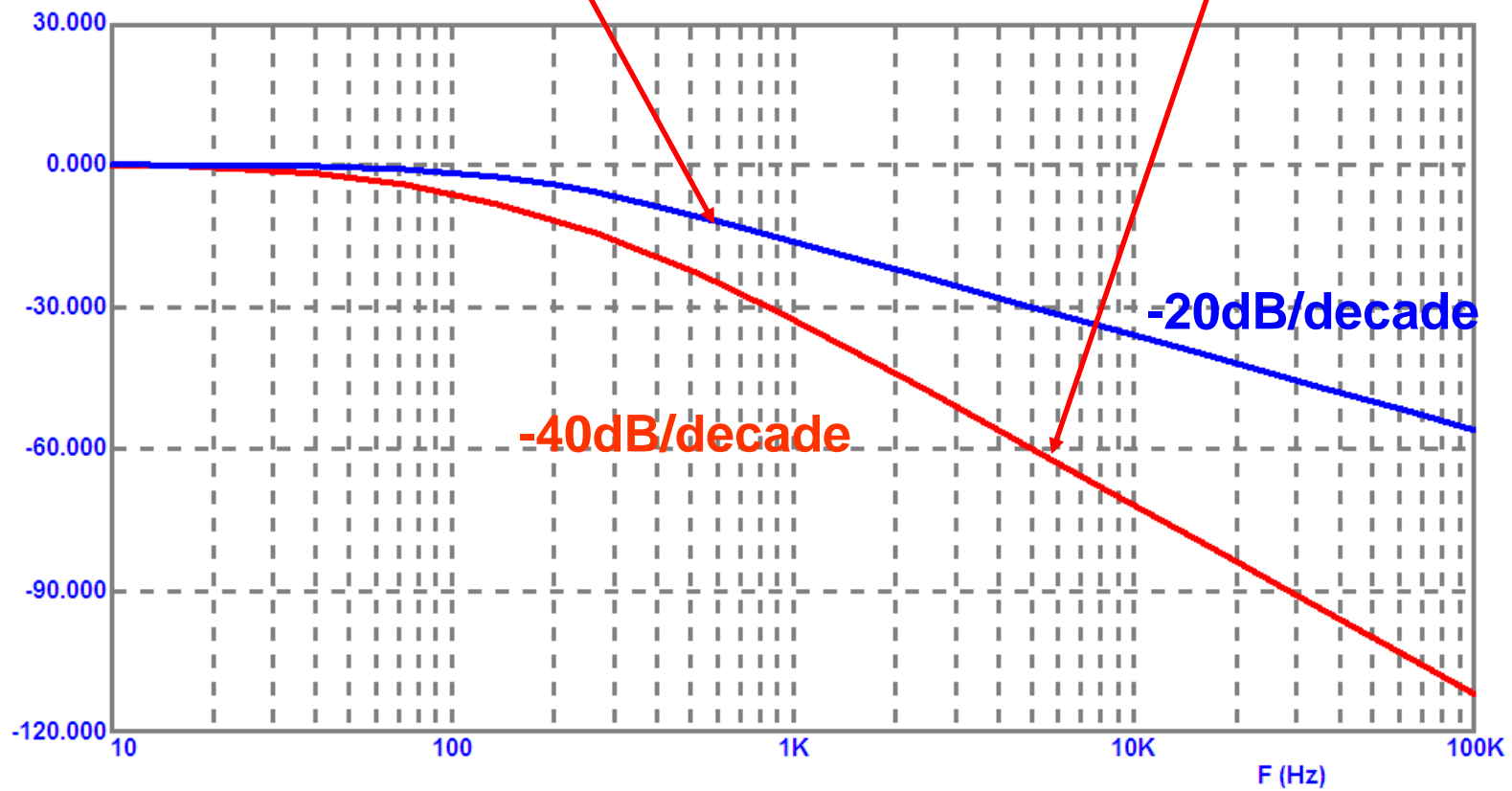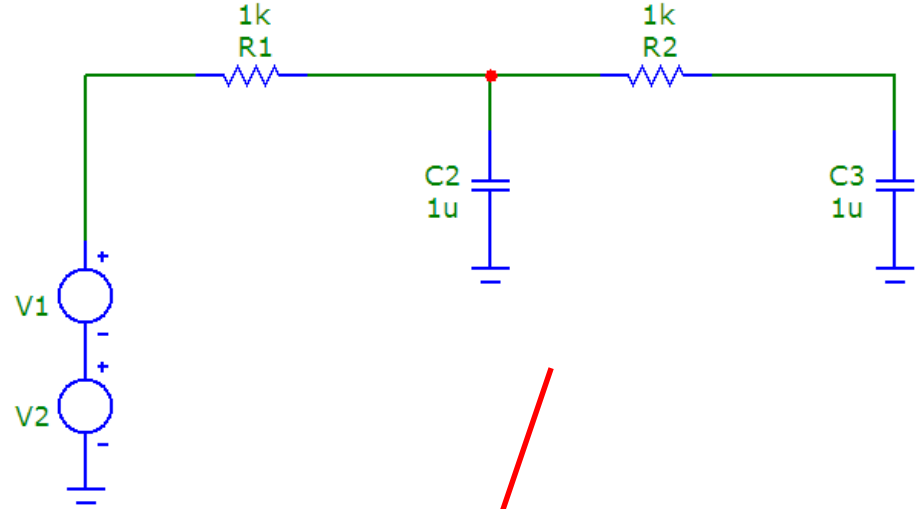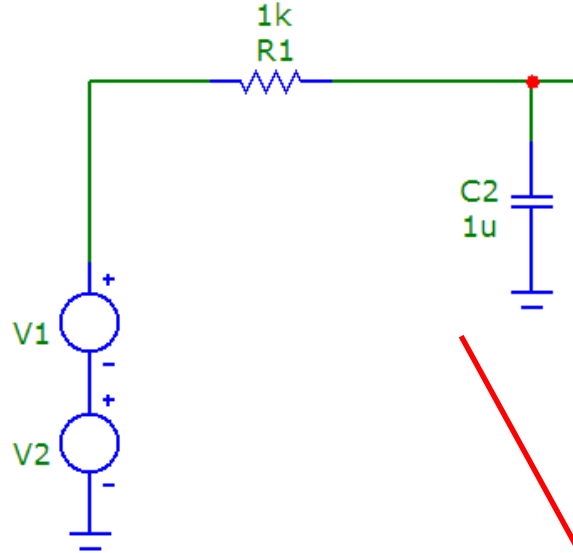

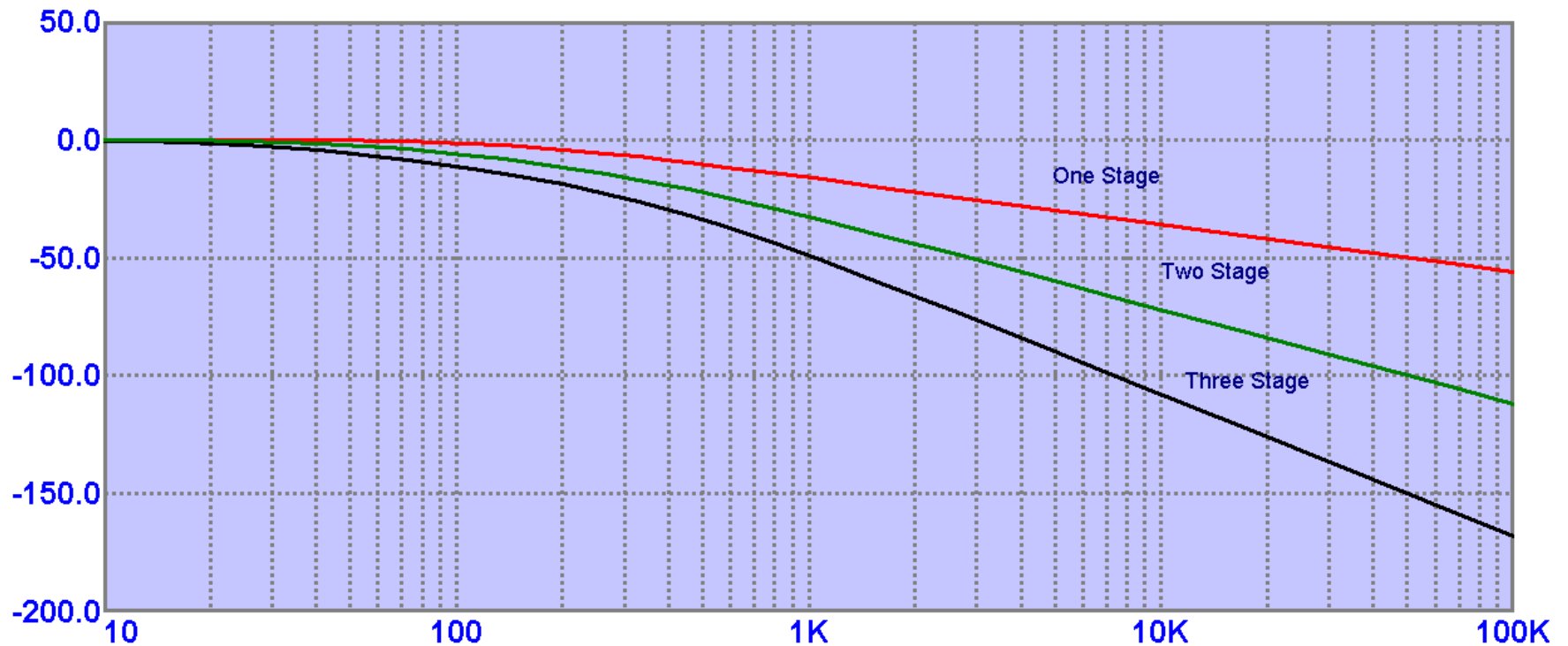
Adding more RC stages, makes the characteristics sharper



Sketching of Transfer function: Bode Magnitude Plot

$$H(\omega) = \frac{10}{1 + j\frac{\omega}{10^3}} \times \frac{1}{1 + j\frac{\omega}{10^4}}$$

$$20\text{Log}_{10}(|H(\omega)|) = 20 - 20\text{Log}_{10}\sqrt{(1 + (\frac{\omega}{10^3})^2)} - 20\text{Log}_{10}\sqrt{(1 + (\frac{\omega}{10^4})^2)}$$

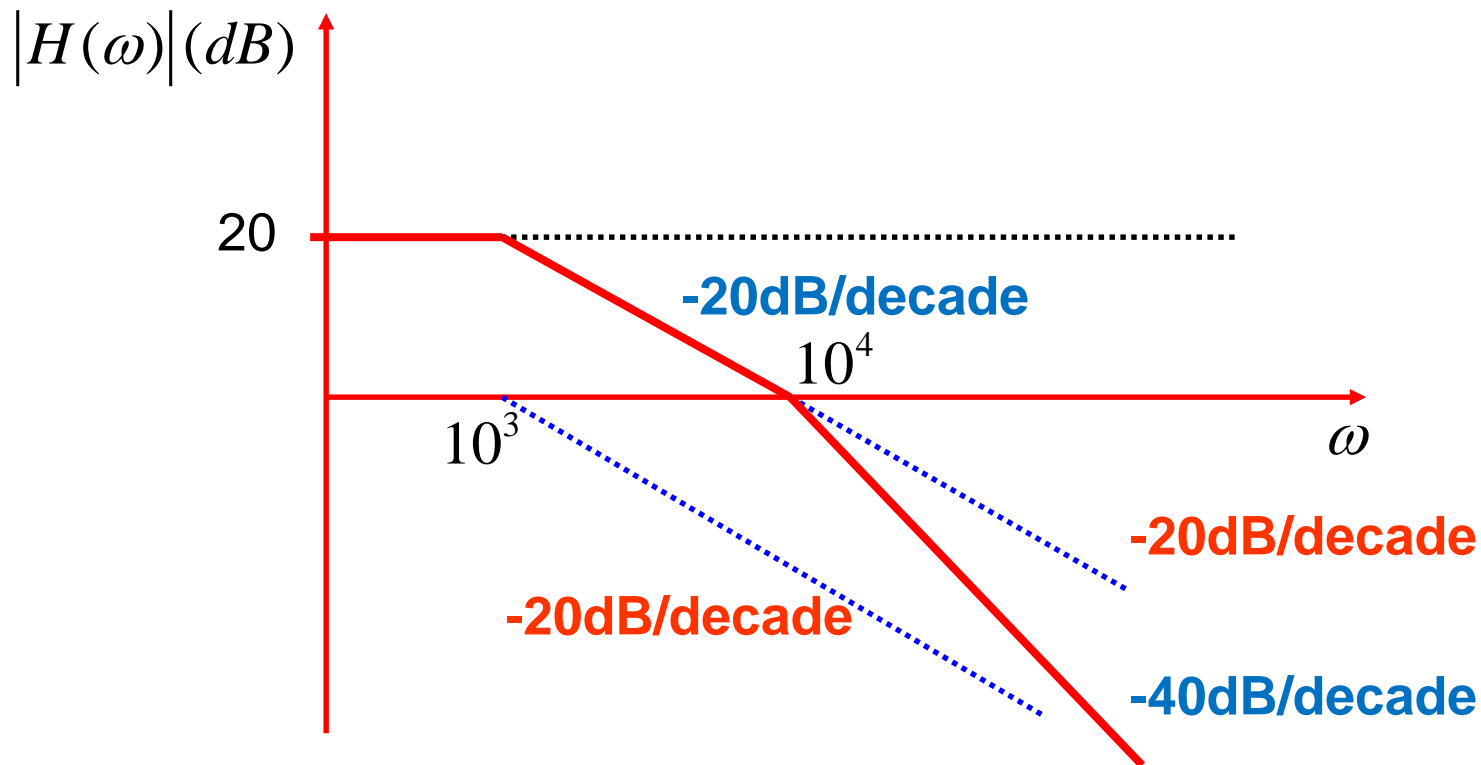


Sketching of Transfer function

Bode Magnitude Plot

$$H(\omega) = \frac{10}{1 + j\frac{\omega}{10^3}} \times \frac{1}{1 + j\frac{\omega}{10^4}} \times \frac{1}{1 + j\frac{\omega}{10^5}}$$


$$20\text{Log}_{10}(|H(\omega)|) = 20 - 20\text{Log}_{10}\sqrt{(1 + (\frac{\omega}{10^3})^2)} - 20\text{Log}_{10}\sqrt{(1 + (\frac{\omega}{10^4})^2)} - 20\text{Log}_{10}\sqrt{(1 + (\frac{\omega}{10^5})^2)}$$

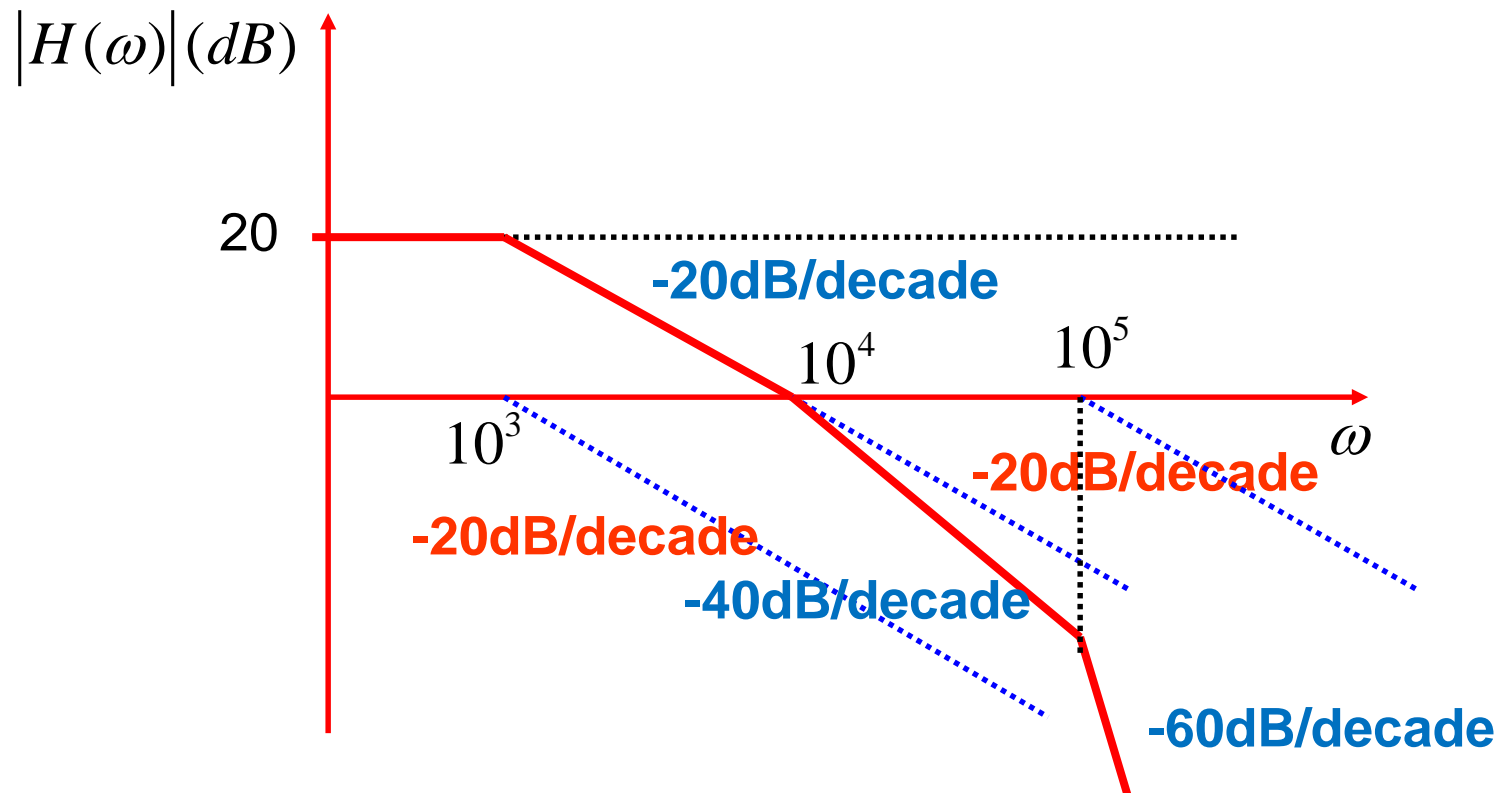


Bode Magnitude Plot

$$H(\omega) = (j\omega)^N$$

$$20\text{Log}_{10}(|H(\omega)|) = 20N \times \text{Log}_{10}(\omega)$$

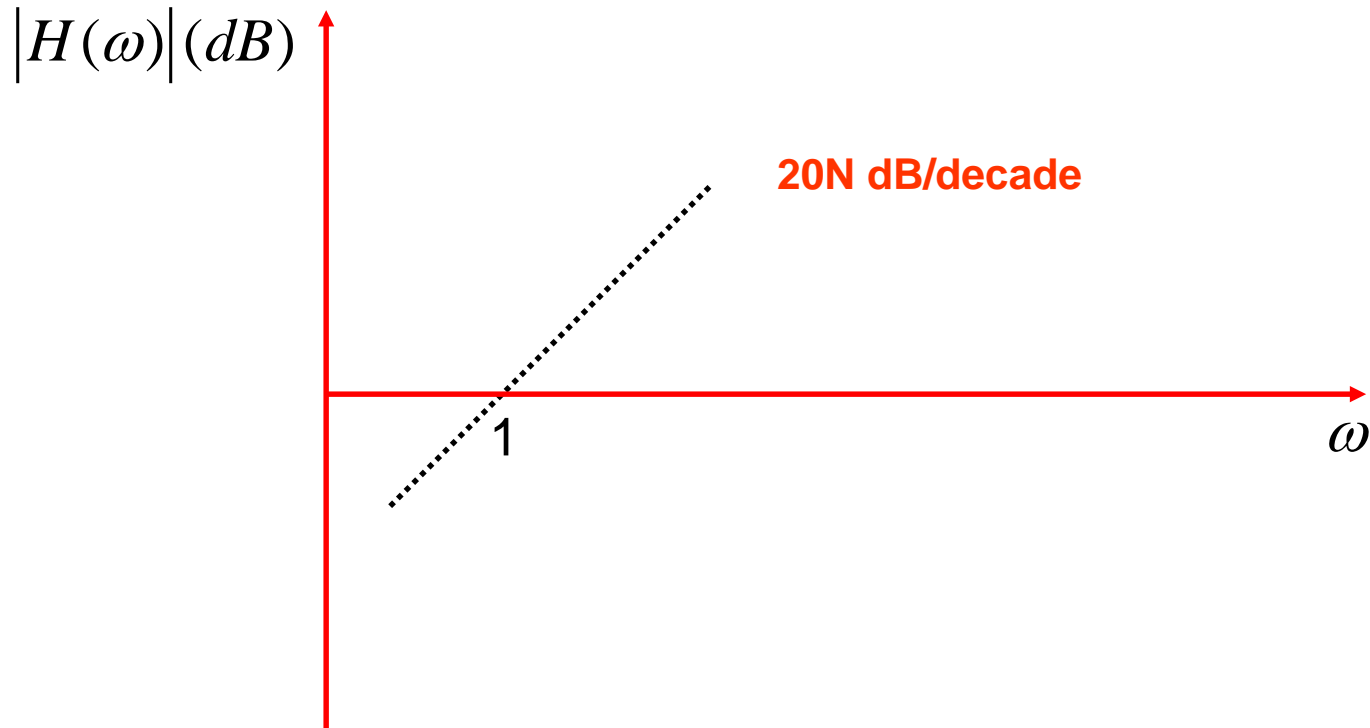

Determine transfer function?

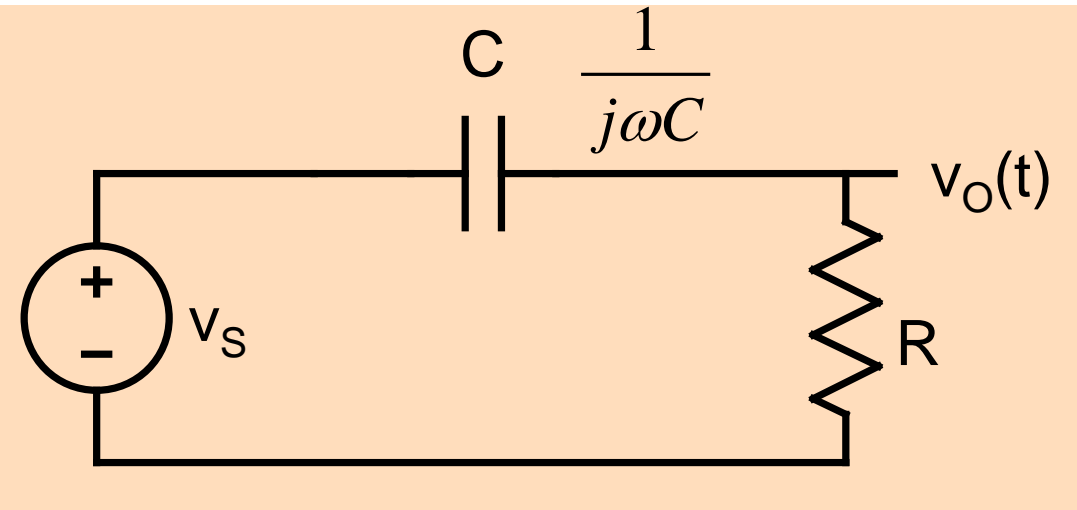

$$H(\omega) = \frac{V_O(\omega)}{V_S(\omega)}$$

$$H(\omega) = \frac{j\omega CR}{1 + j\omega CR}$$


$$H(\omega) = \frac{j(\omega / \omega_{3dB})}{1 + j(\omega / \omega_{3dB})}$$

$$\omega_{3dB} = \frac{1}{RC} \quad ; \quad f_{3dB} = \frac{1}{2\pi RC}$$


$$20\text{Log}_{10}(|H(\omega)|) = 20\log_{10}\left(\frac{\omega}{\omega_{3dB}}\right) - 20\log_{10}\sqrt{\left(1 + \left(\frac{\omega}{\omega_{3dB}}\right)^2\right)}$$

Bode Magnitude Plot


$$20\text{Log}_{10}(|H(\omega)|) = 20\log_{10}\left(\frac{\omega}{\omega_{3dB}}\right) - 20\log_{10}\sqrt{\left(1 + \left(\frac{\omega}{\omega_{3dB}}\right)^2\right)}$$

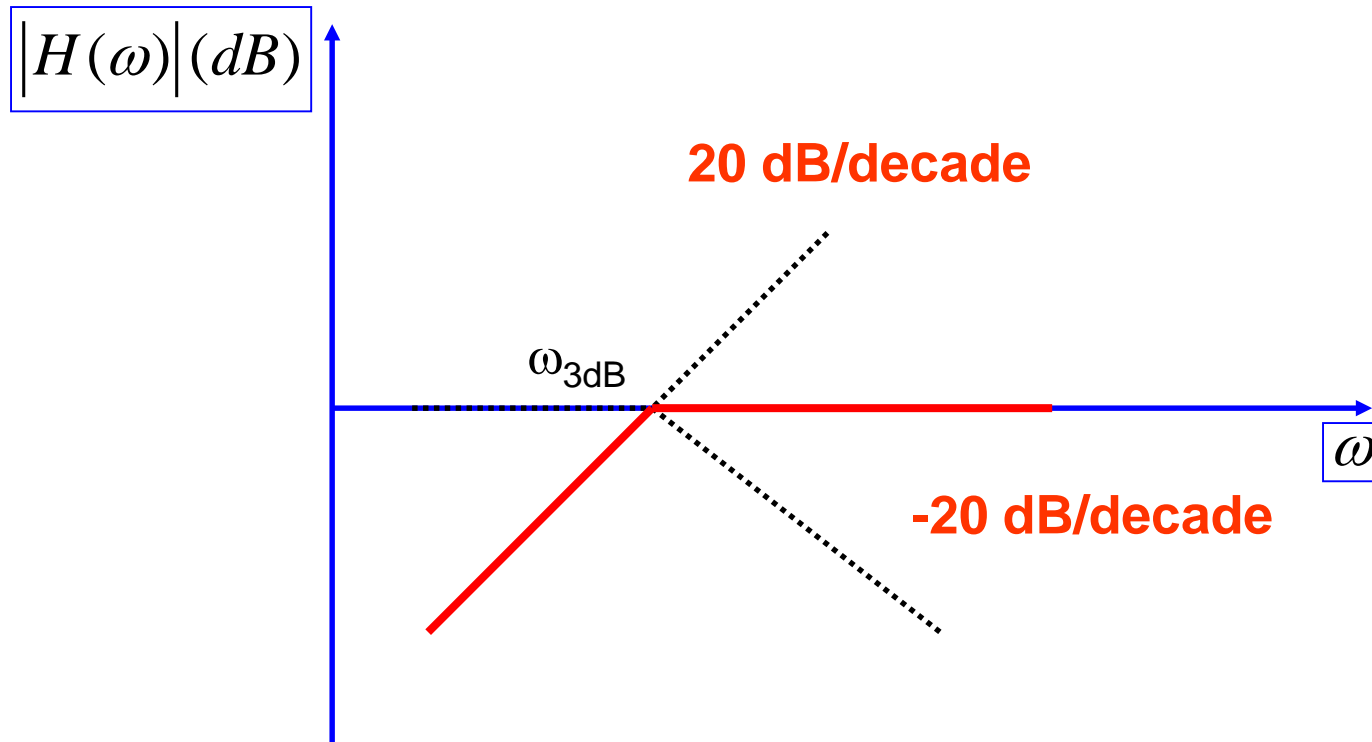

High Pass Filter

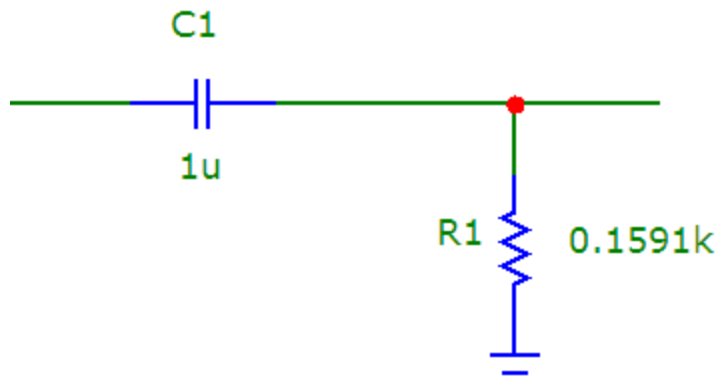

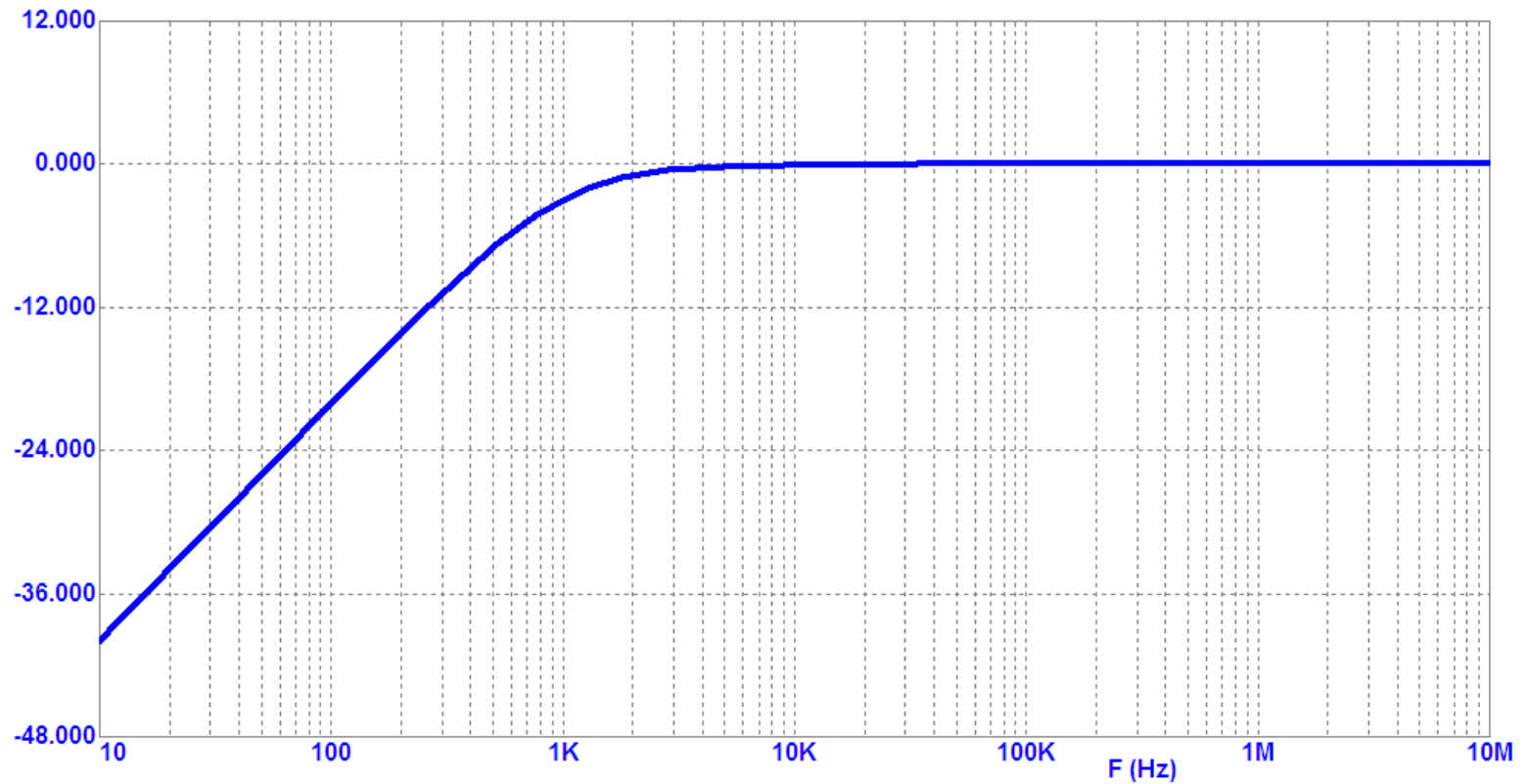
$$f_{3dB} = \frac{1}{2\pi RC} = 10^3 \text{ Hz}$$



High Pass Filter

Bode Plot segments

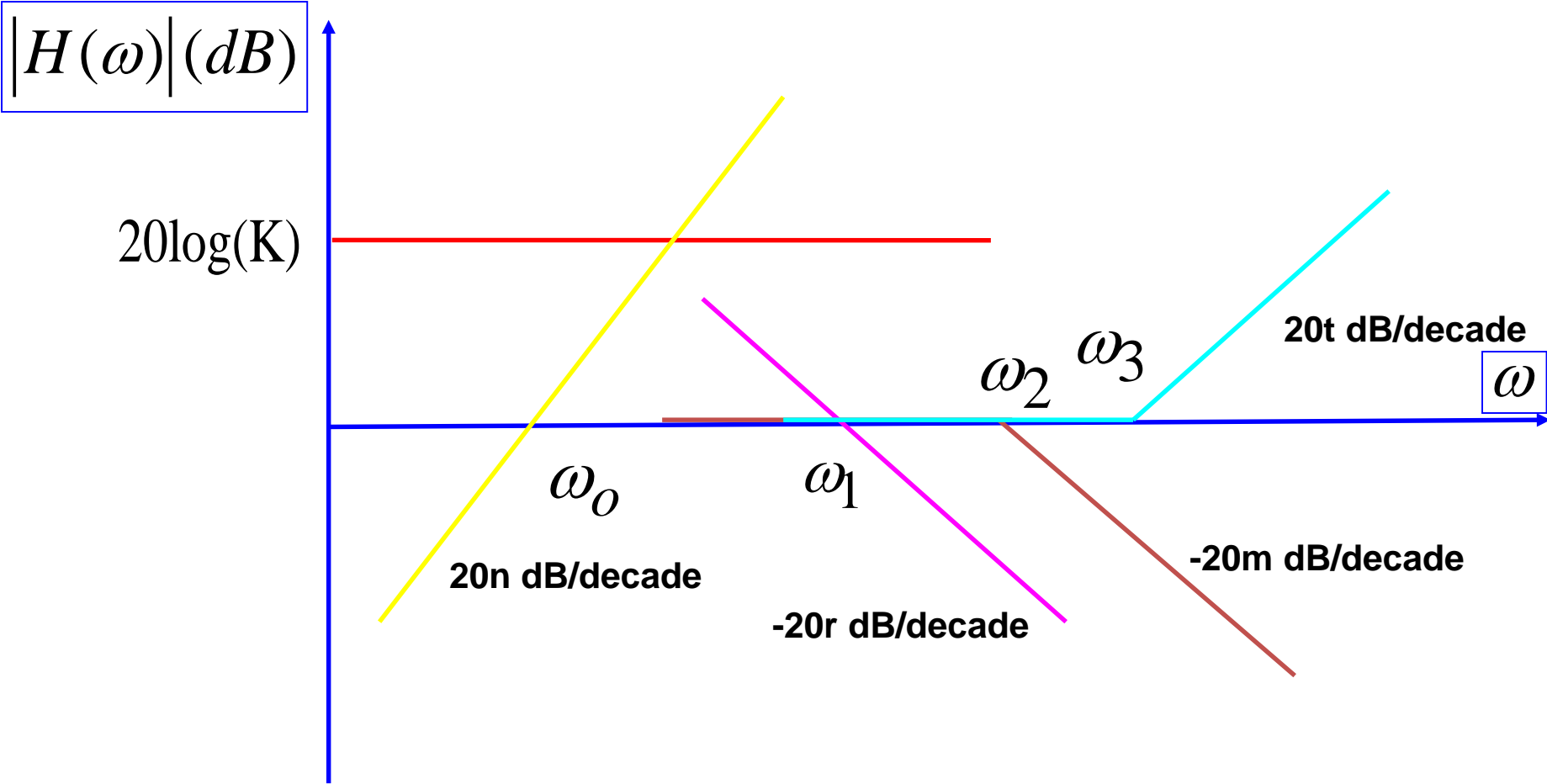
$$H(\omega) = K \times j(\omega / \omega_o)^n \times \frac{1}{j(\omega / \omega_1)^r} \times \frac{1}{\{1 + j(\omega / \omega_2)\}^m} \times \{1 + j(\omega / \omega_3)\}^t$$






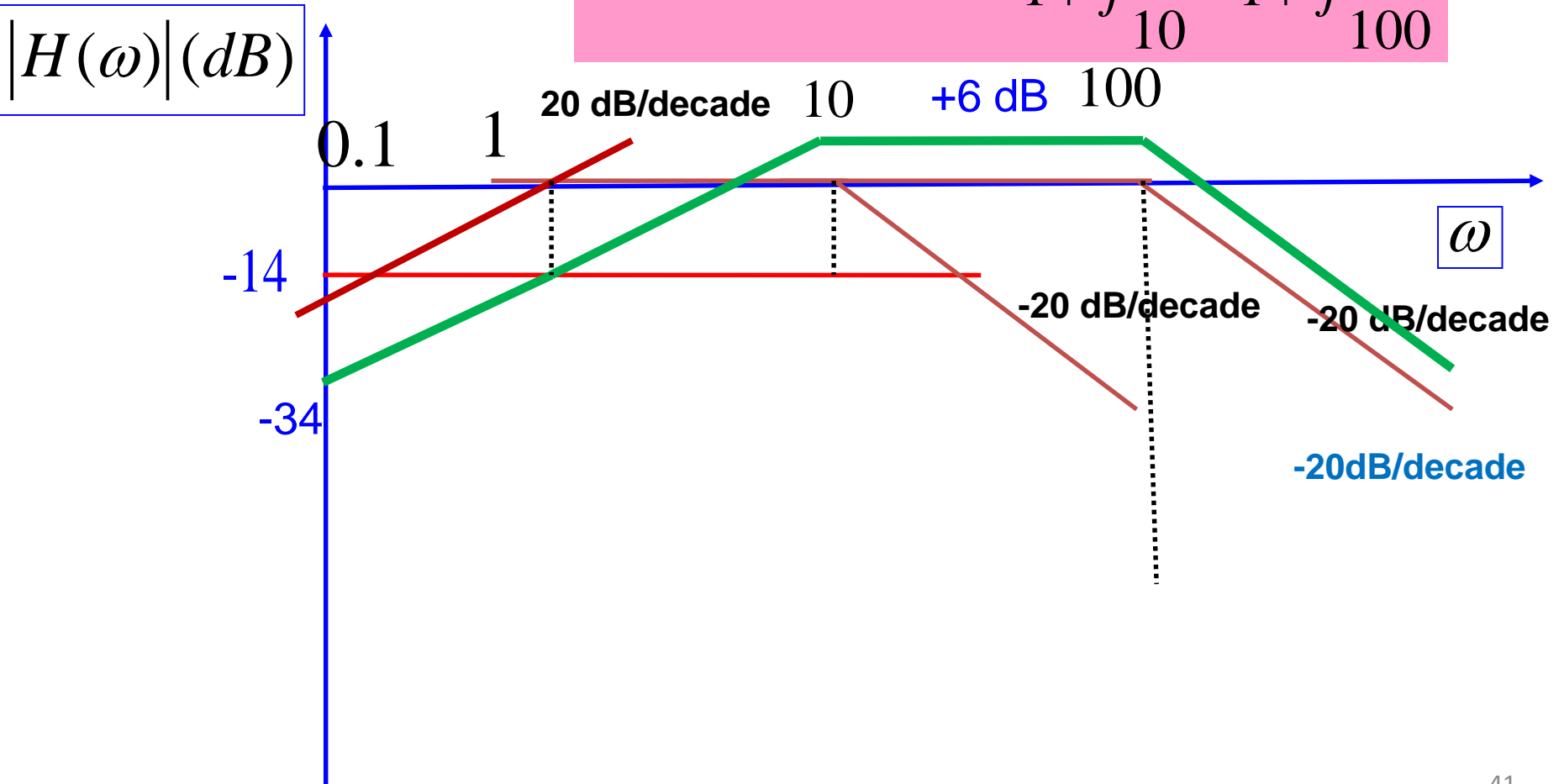
Example:





$$H(\omega) = 200 \times j\omega \times \frac{1}{10 + j\omega} \times \frac{1}{100 + j\omega}$$

$$H(\omega) = 0.2 \times j\omega \times \frac{1}{1 + j\frac{\omega}{10}} \times \frac{1}{1 + j\frac{\omega}{100}}$$




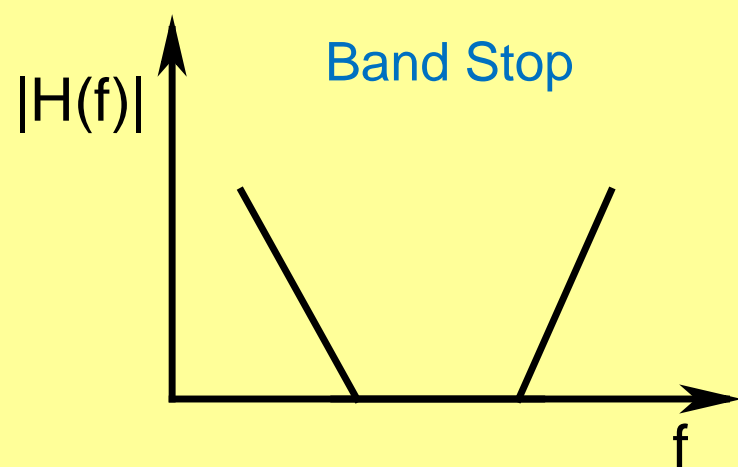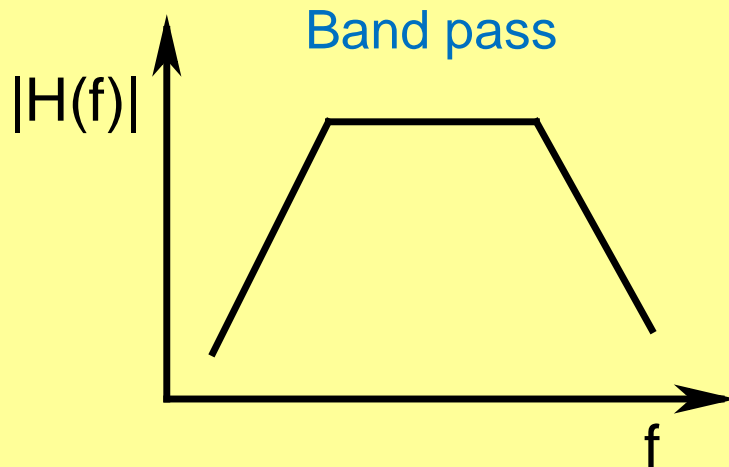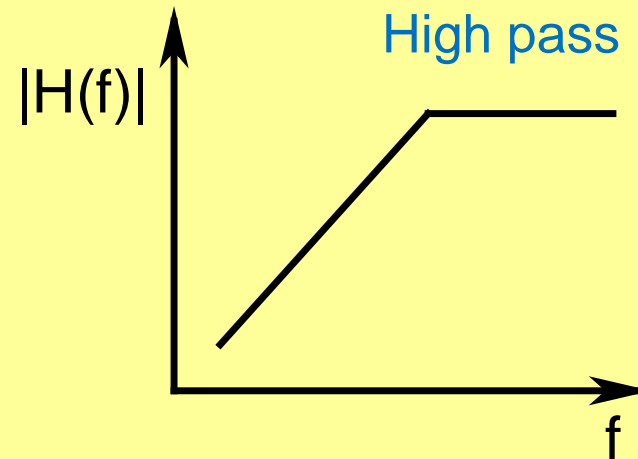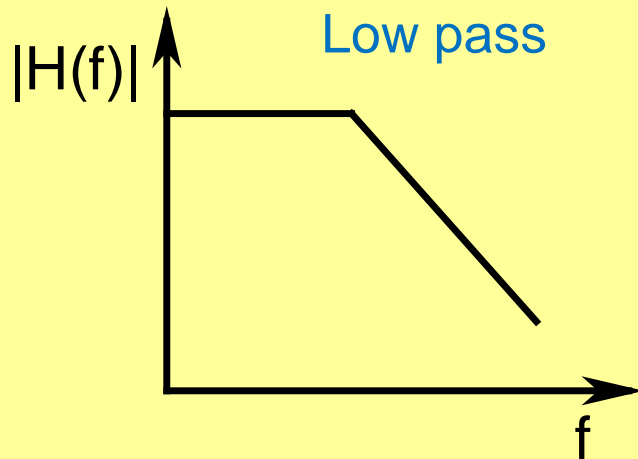Filter -pass a band of frequency and reject the remaining




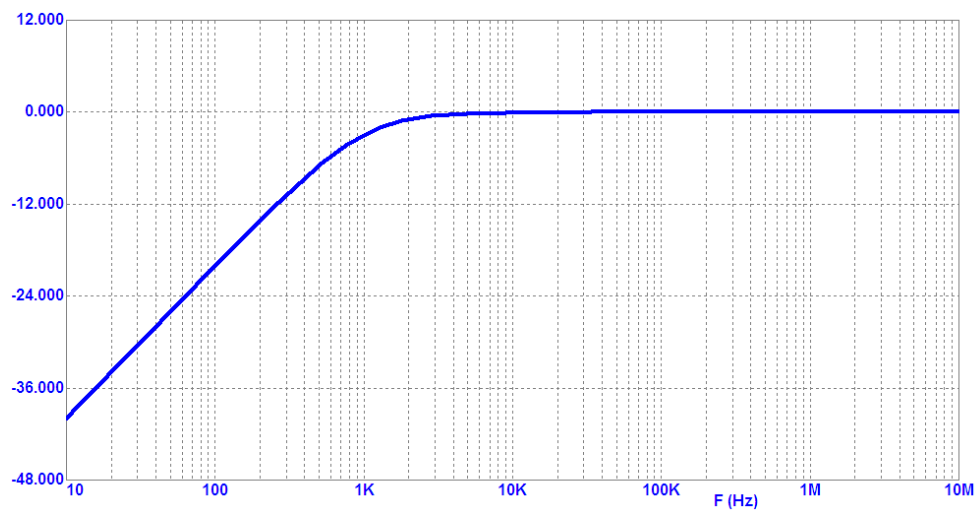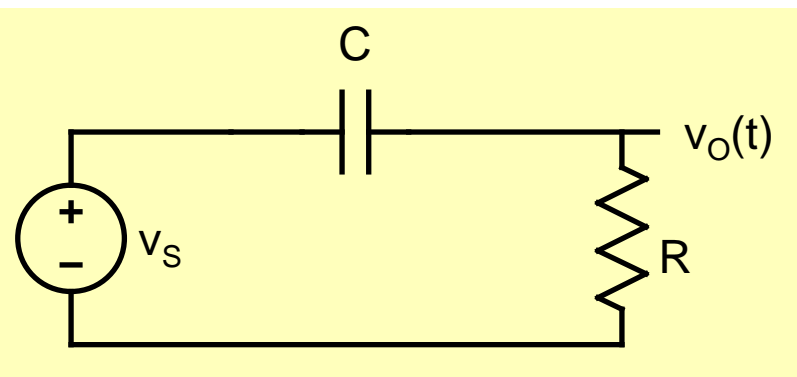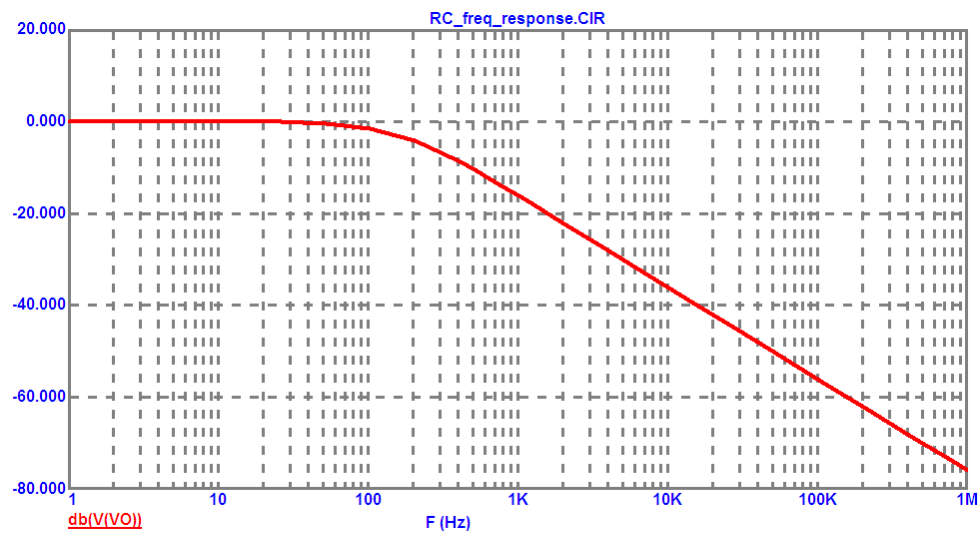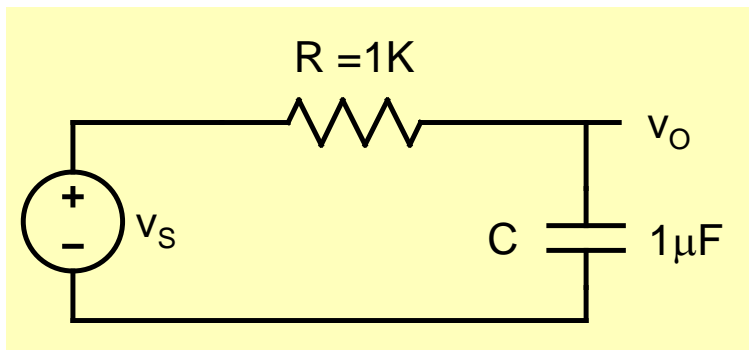

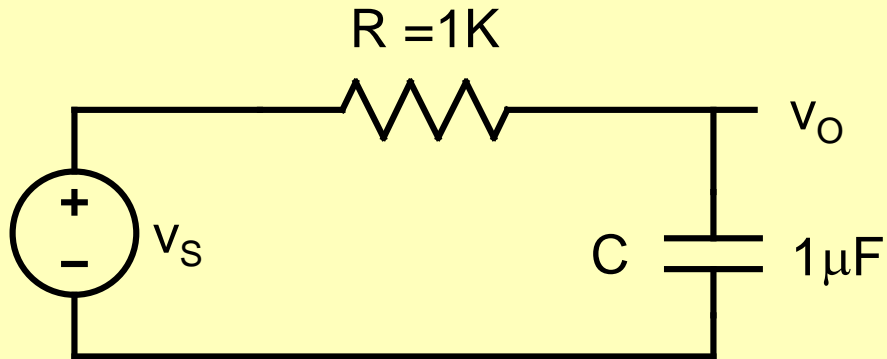
3dB Frequency of single capacitor filters


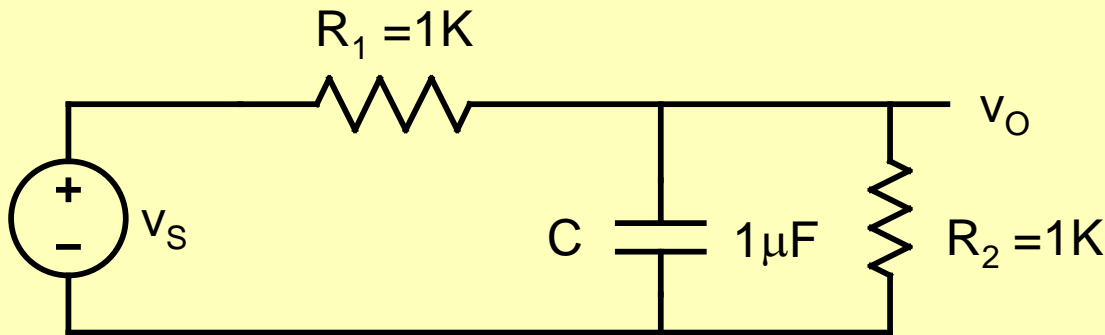
$$\omega_{3dB} = \frac{1}{RC} = 10^3 \text{ rad/s}$$



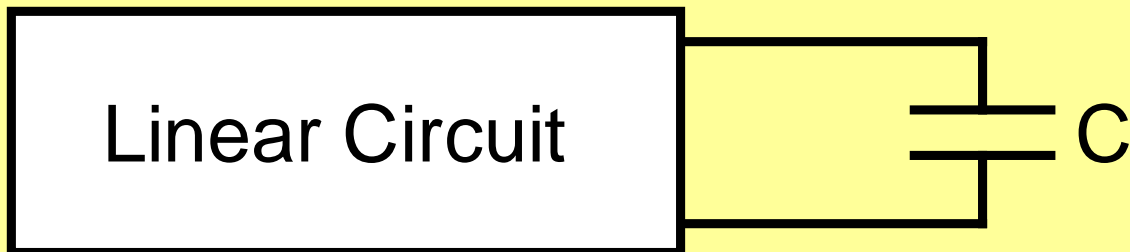
$$\omega_{3dB} = \frac{1}{R_1 \parallel R_2 C}$$




$$\omega_{3dB} = \frac{1}{\tau} = \frac{1}{R_{eq} C}$$

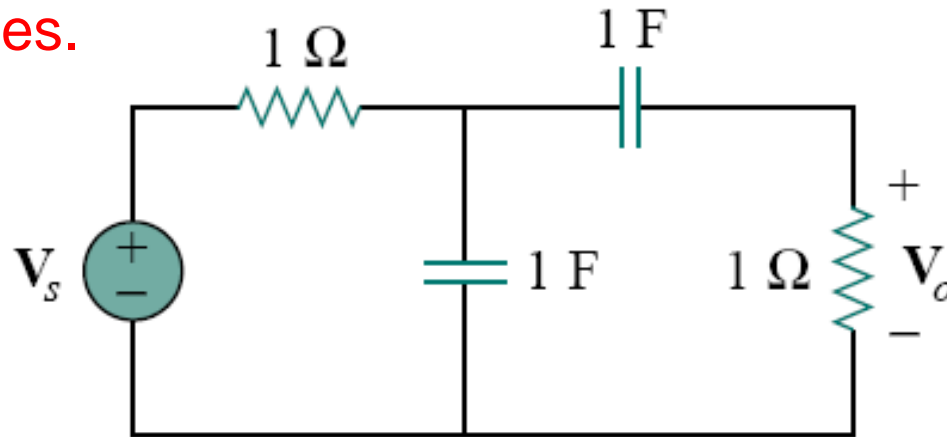One can often tell the type of filter by looking at **behavior at very low and very high frequencies** and keeping in mind that **capacitor offers very high impedance at low frequencies** and **very low impedance at high frequencies**.




Low f

High f

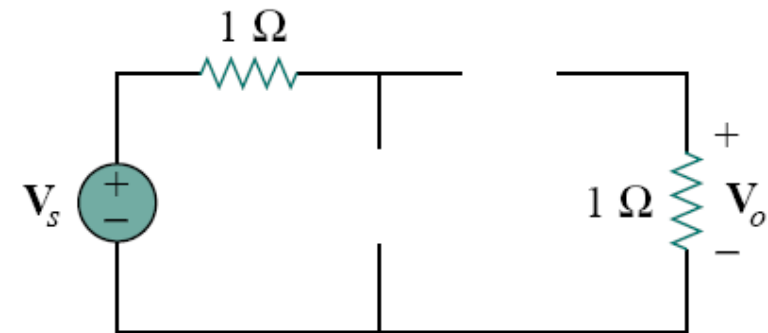



$V_o \sim 0$

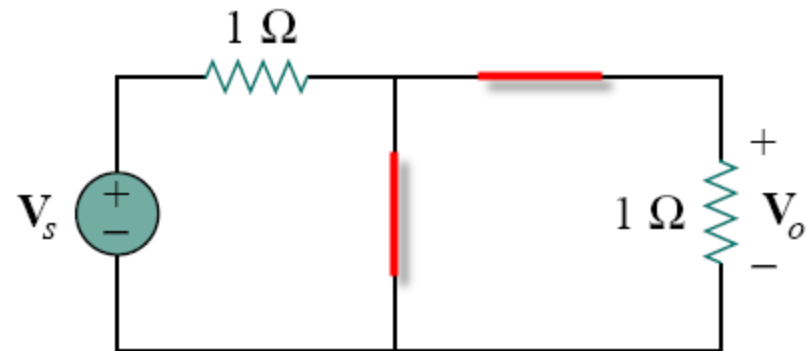

$V_o \sim 0$

Bandpass filter

Bandpass Filter

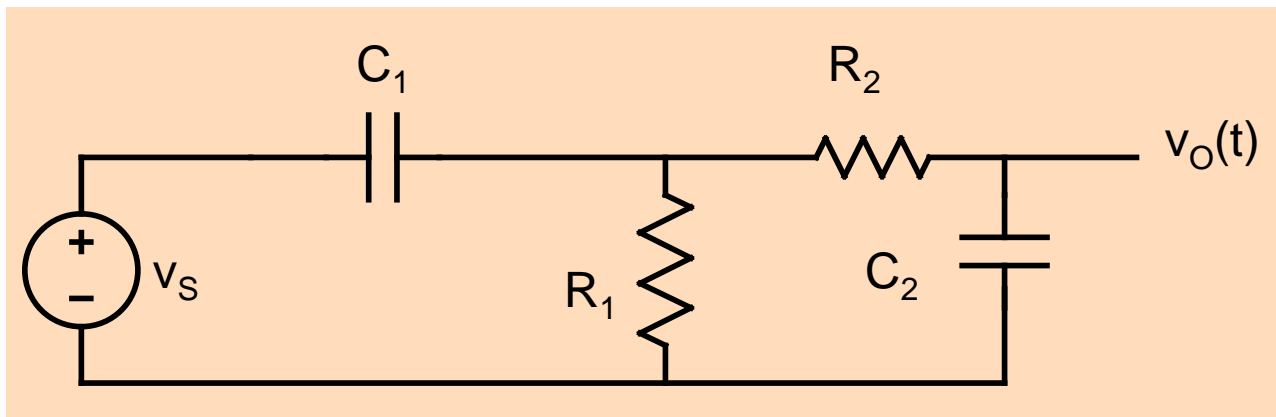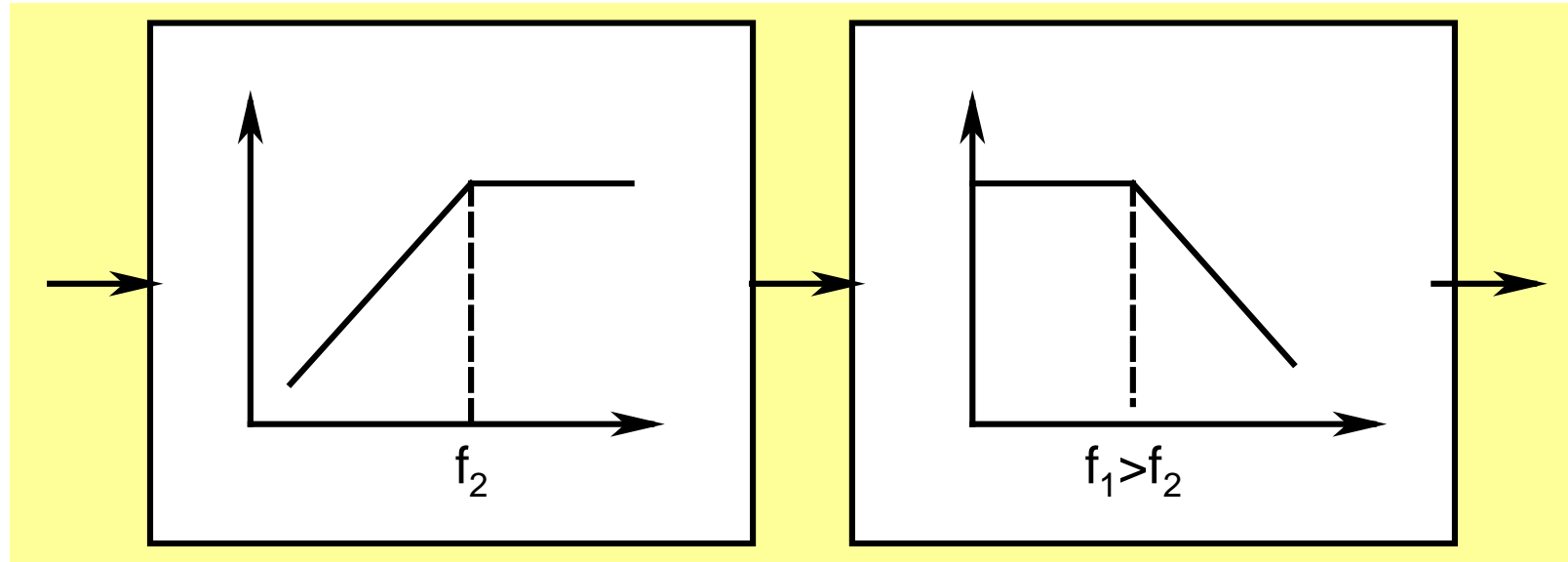

$$f_2 \cong \frac{1}{2\pi R_1 C_1} ; f_1 \cong \frac{1}{2\pi R_2 C_2}$$

Example: Band Pass filter

